

Solutions to Quiz-2 Paper (Group-A)

IEC103

Q1) For the oscillator circuit shown in Fig. Q1, find the frequency of oscillation and condition on ratio $\frac{R_2}{R_1}$ for oscillation


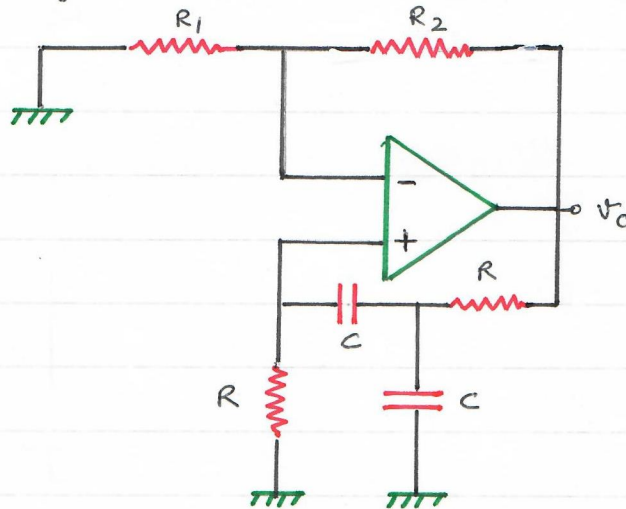


Fig. Q1

Sol.

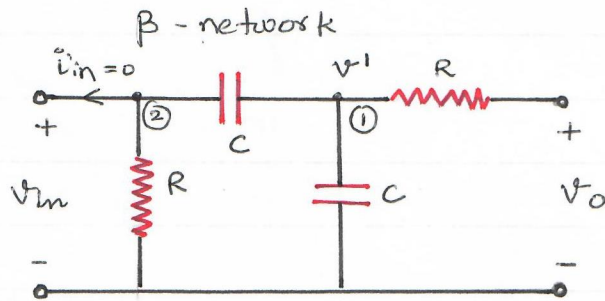

$$v_o = A v_m$$

$$= \left(1 + \frac{R_2}{R_1}\right) v_m \quad \dots (I)$$

Applying KCL at node (1)

$$\frac{v_1 - v_o}{R} + \frac{v_1}{(1/sc)} + \frac{v_1 - v_{in}}{(1/sc)} = 0 \quad \dots (A)$$

Applying KCL at node (2) (ie., i/p node)

$$\frac{v_{in}}{R} + \frac{v_{in} - v_1}{(1/sc)} = 0 \quad \dots (B)$$

$$\Rightarrow v_{in} \left(\frac{1}{R} + sc \right) = sc v_1$$

$$\text{Let } \frac{1}{R} = a$$

$$\therefore v_{in} (a + sc) = sc v_1$$

$$\Rightarrow v_1 = \frac{(a + sc) v_{in}}{sc} \quad \dots (C)$$

Eq. n (A)

$$\frac{V^1 - V_0}{R} + \frac{V^1}{(1/sC)} + \frac{V^1 - V_{in}}{C/sC} = 0$$

$$\Rightarrow V^1 (1 + sC + sC) - 1 V_0 - sC V_{in} = 0$$

$$\Rightarrow V^1 (1 + 2sC) - 1 V_0 - sC V_{in} = 0$$

$$1 = \frac{1}{R}$$

subst. V^1 in eqn. (2) in the above equation

$$(1 + 2sC) \frac{(1 + sC)}{sC} V_{in} - 1 A V_{in} - sC V_{in} = 0$$

$$\Rightarrow (1 + 2sC)(1 + sC) - A sC - (sC)^2 = 0$$

$$\Rightarrow (1^2 + 3sC + 2s^2 C^2) - (A sC) - C^2 s^2 = 0$$

$$\Rightarrow (2C^2 - C^2)s^2 + (3sC - A sC) + 1^2 = 0$$

$$\Rightarrow C^2 s^2 + (3 - A)sC + 1^2 = 0$$

put $s = j\omega$

$$\Rightarrow -C^2 \omega^2 + j(3 - A)sC + 1^2 = 0$$

$$\Rightarrow (1^2 - C^2)\omega^2 + j(3 - A)sC = 0$$

Equating real & imaginary parts of LHS & RHS

$$(1^2 - C^2)\omega^2 = 0$$

$$(3 - A)sC = 0$$

$$\Rightarrow \frac{(1 - R^2 C^2)\omega^2}{R^2} = 0$$

$$(3 - A)sC = 0$$

$$\Rightarrow R^2 C^2 \omega^2 = 1$$

$$\Rightarrow A = 3 = 1 + \frac{R_2}{R_1}$$

$$\Rightarrow \boxed{\omega_0 = \frac{1}{RC}}$$

$$\Rightarrow \boxed{\frac{R_2}{R_1} = 2}$$

Q2 Determine the output waveform (V_{out}) of the diode circuit shown in Fig. Q2 below. Use simplified model of the diode. Both the diodes are silicon diodes.


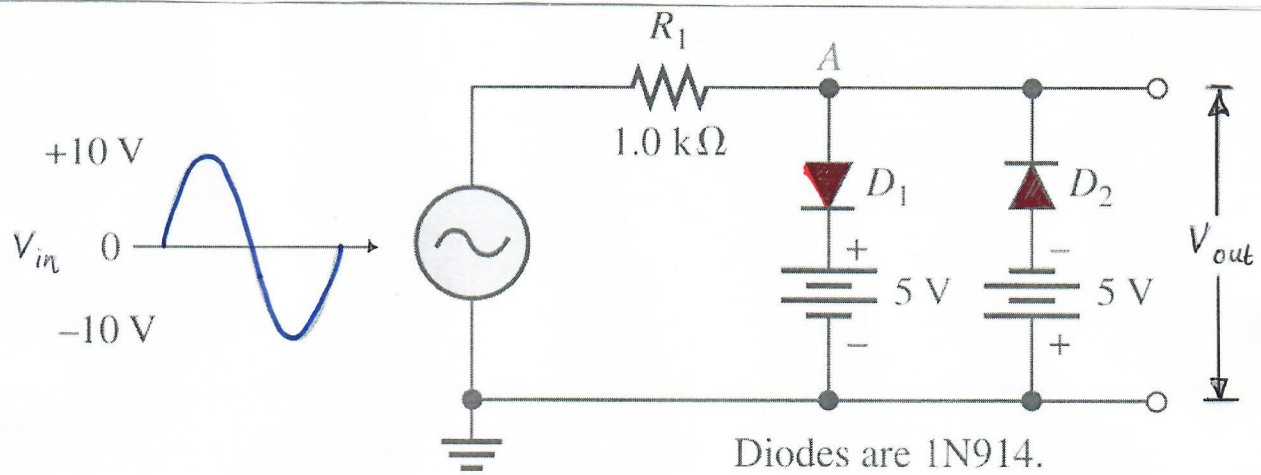



Fig. Q2

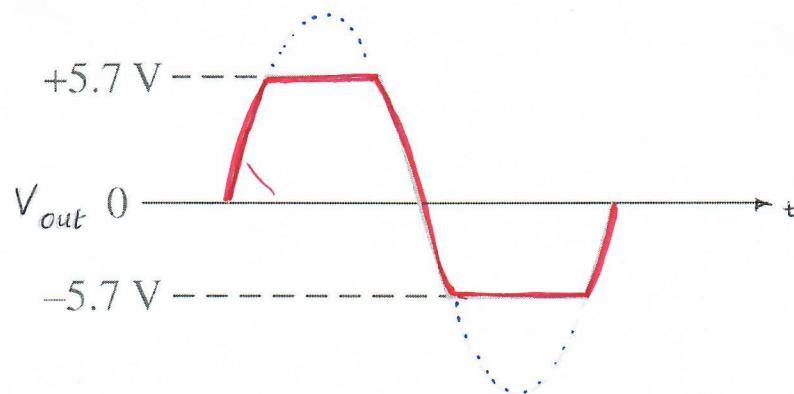Sol. When the voltage at point A reaches $+5.7\text{V}$, diode D_1 conducts and limits the waveform to $+5.7\text{V}$. Diode D_2 does not conduct until the voltage reaches -5.7V . Therefore, positive voltages above $+5.7\text{V}$ and negative voltage below -5.7 are clipped off. The resulting output waveform is shown below.



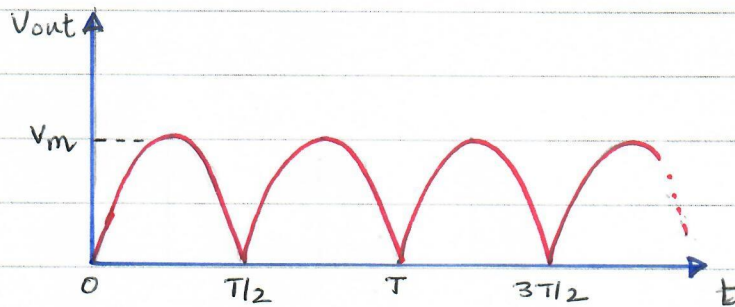Q3) Derive the expression and the value of rectifier efficiency of a full wave rectifier.

Sol. The output of a full wave rectifier is as shown below.



T is the time period of the input supply.

$$\text{Rectifier efficiency} = \frac{\text{DC power output}}{\text{AC power output}}$$

Let load resistance be R_L .

For the output waveform

$$V_{DC} = \frac{2V_m}{\pi} ; V_{(RMS)} = \frac{V_m}{\sqrt{2}}$$

$$\text{DC power output} = (V_{DC})^2 / R_L = P_{DC}$$

$$\text{AC power output} = (V_{(RMS)})^2 / R_L = P_{AC}$$

$$\text{Rectifier efficiency} = \frac{P_{DC}}{P_{AC}} = \left(\frac{V_{DC}}{V_{AC}} \right)^2 = \frac{(2V_m/\pi)^2}{(V_m/\sqrt{2})^2}$$

$$= \frac{4/\pi^2}{1/2} = \frac{8}{\pi^2} = 0.81$$

$$= 81\%$$