

Basic Electronic Circuits (IEC-103)

Lecture-08

Nonlinear Applications of Operational Amplifiers

Non-Linear Op-Amp Applications


□ Applications using saturation

- Comparators**
- Comparator with hysteresis (Schmitt trigger)**
- Square wave and triangular wave generators**


□ Applications using active feedback components

- Log, antilog, squaring etc. amplifiers**
- Precision rectifier**

Comparators

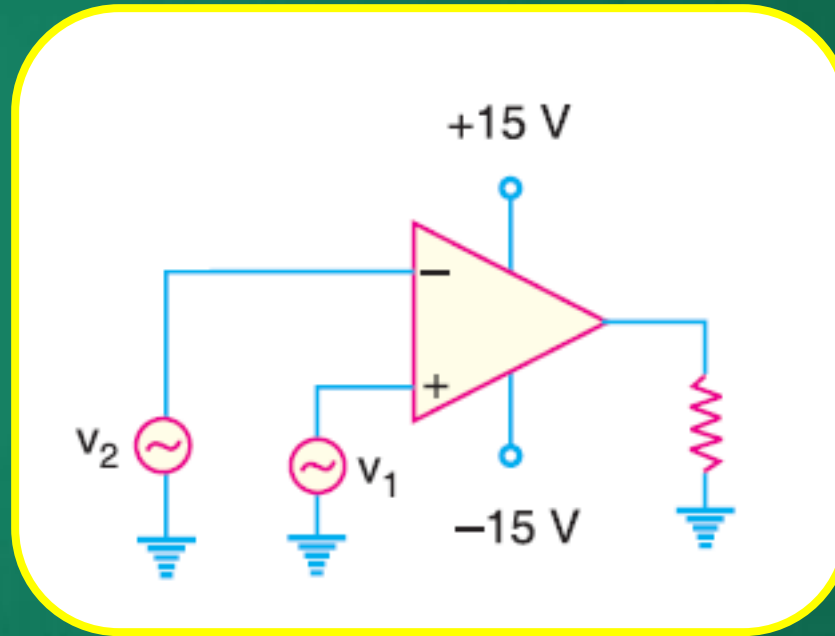


Comparators

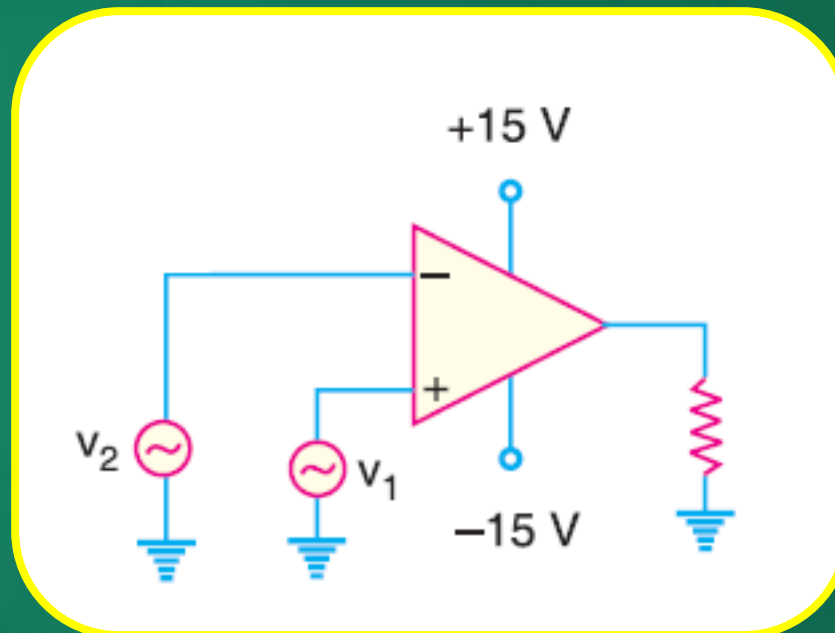

- ❑ **A comparator is an op-amp circuit without negative feedback and takes the advantage of very high open-loop gain.**

Comparators

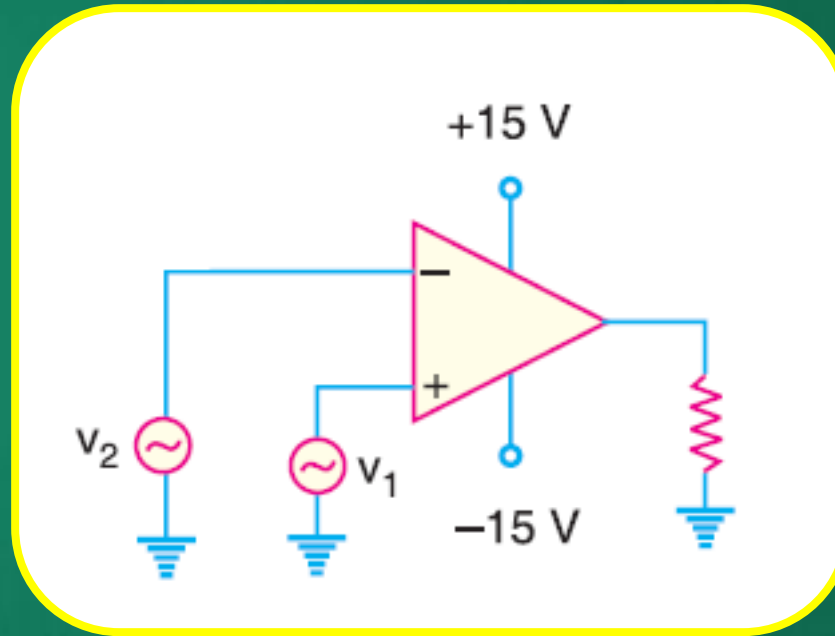


- ❑ A comparator is an op-amp circuit without negative feedback and takes the advantage of very high open-loop gain.
- ❑ It is operated in a non-linear mode.

Comparators



$$+V_{sat} = +V_{supply} - 2 = 15 - 2 = +13 \text{ V}$$

$$-V_{sat} = -V_{supply} + 2 = -15 + 2 = -13 \text{ V}$$


Comparator (Square Wave Generator)

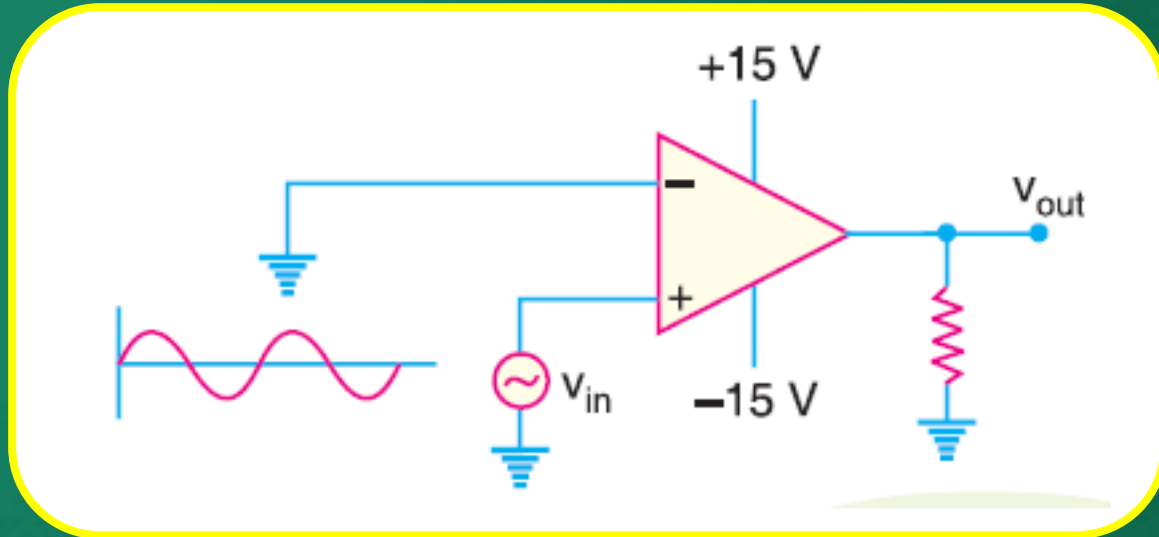



Comparator (Square Wave Generator)

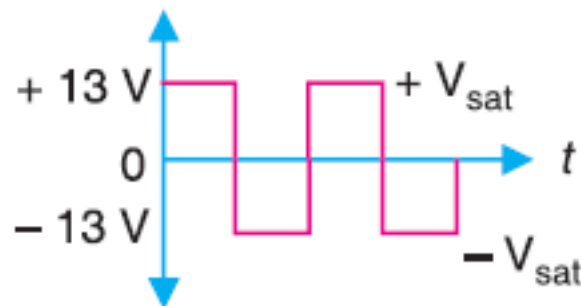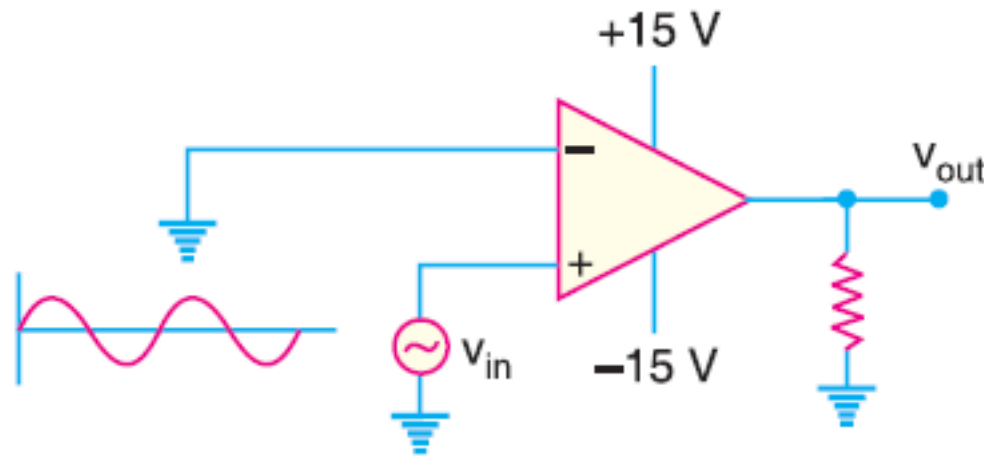


Comparator (Zero Crossing Detector)

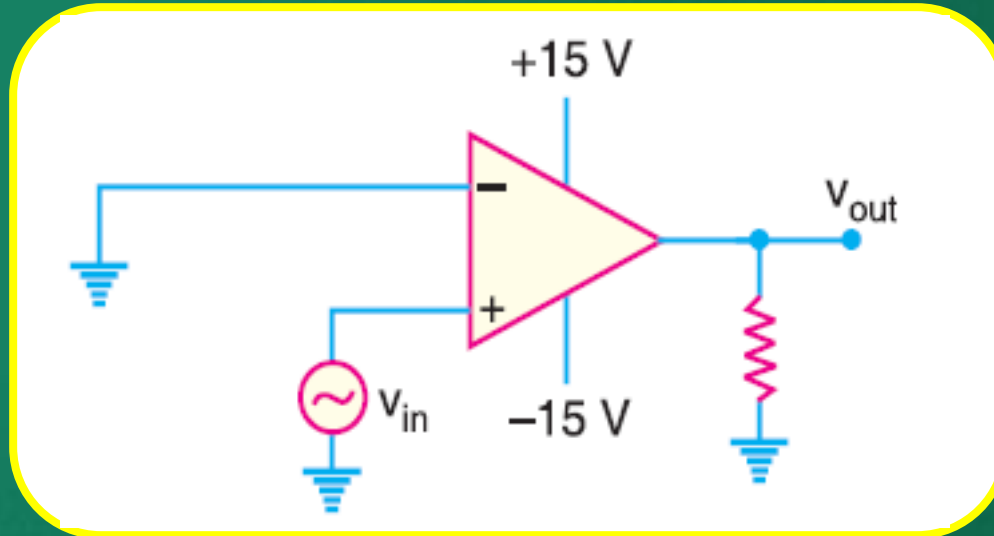

Comparator (Zero Crossing Detector)

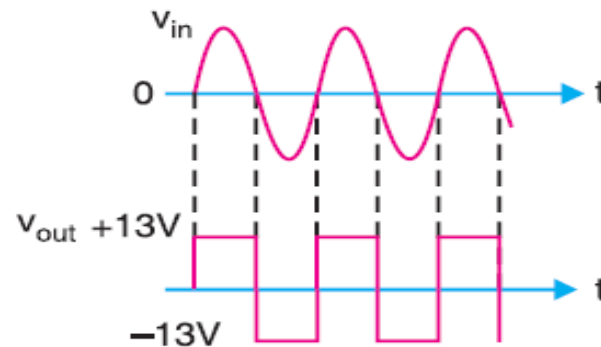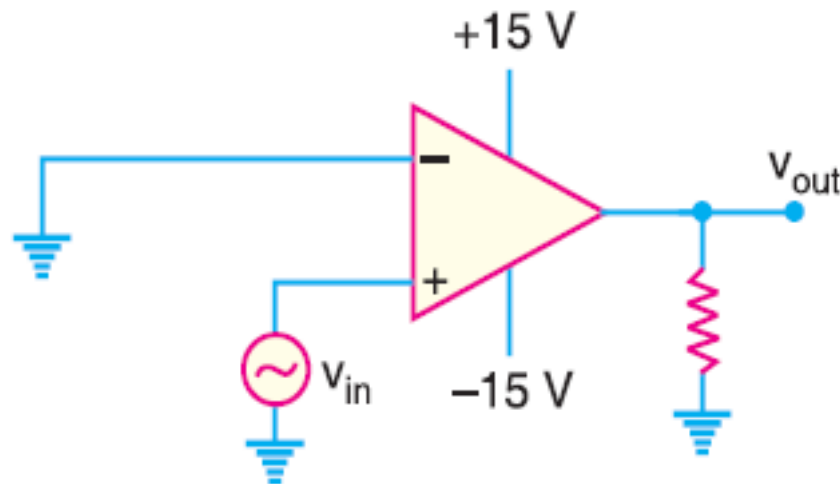


Comparator (Level Detector)

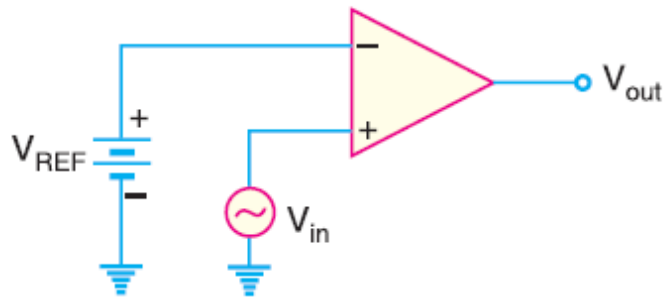


(i) Battery reference

Comparator (Level Detector)

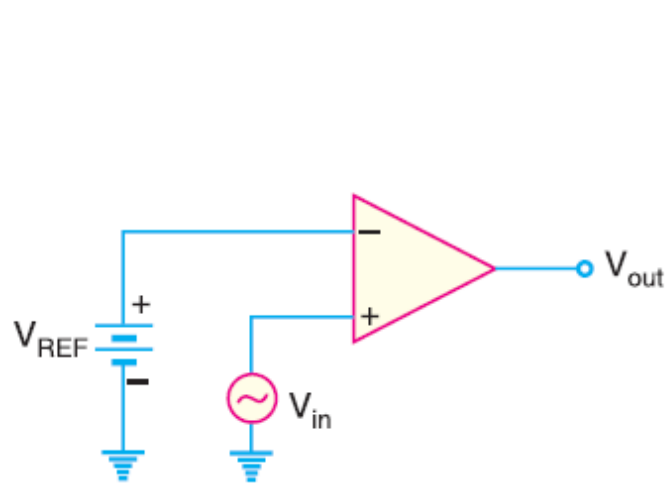


(i) Battery reference

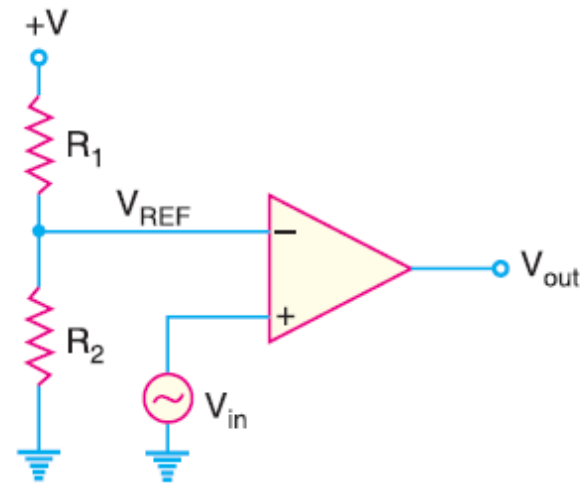

(ii) Voltage-divider reference

Comparator (Level Detector)

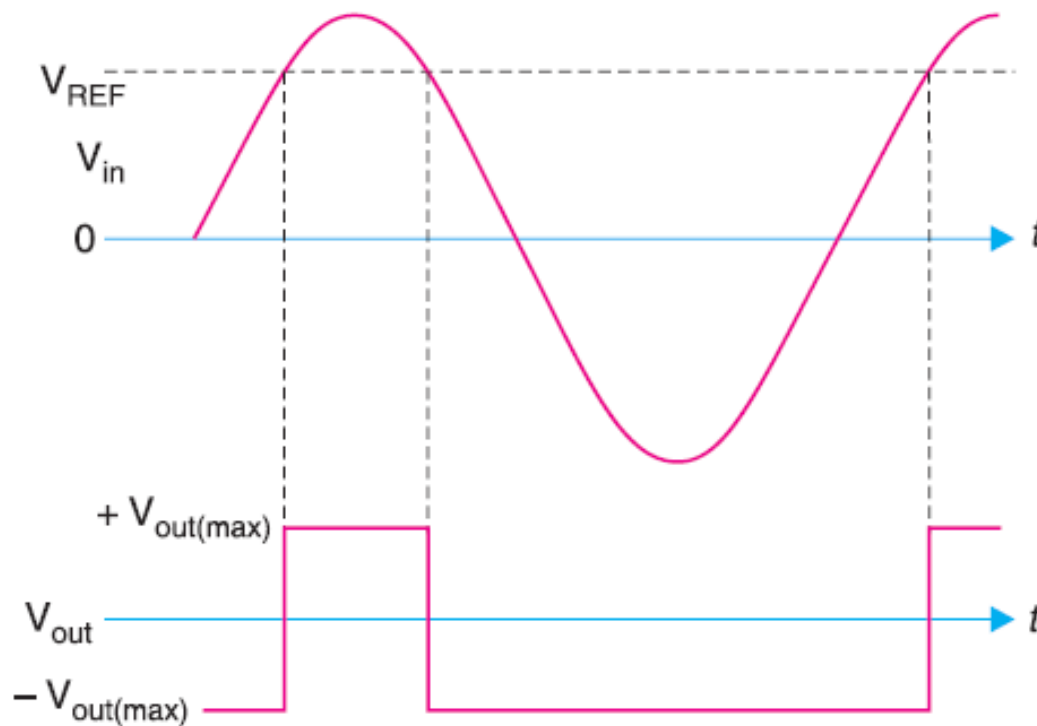

Hysteresis

Hysteresis


- A comparator with hysteresis has a safety margin.

Hysteresis

- ❑ A comparator with hysteresis has a **safety margin**.
- ❑ One of two thresholds is used depending on the **current output state**.


Hysteresis

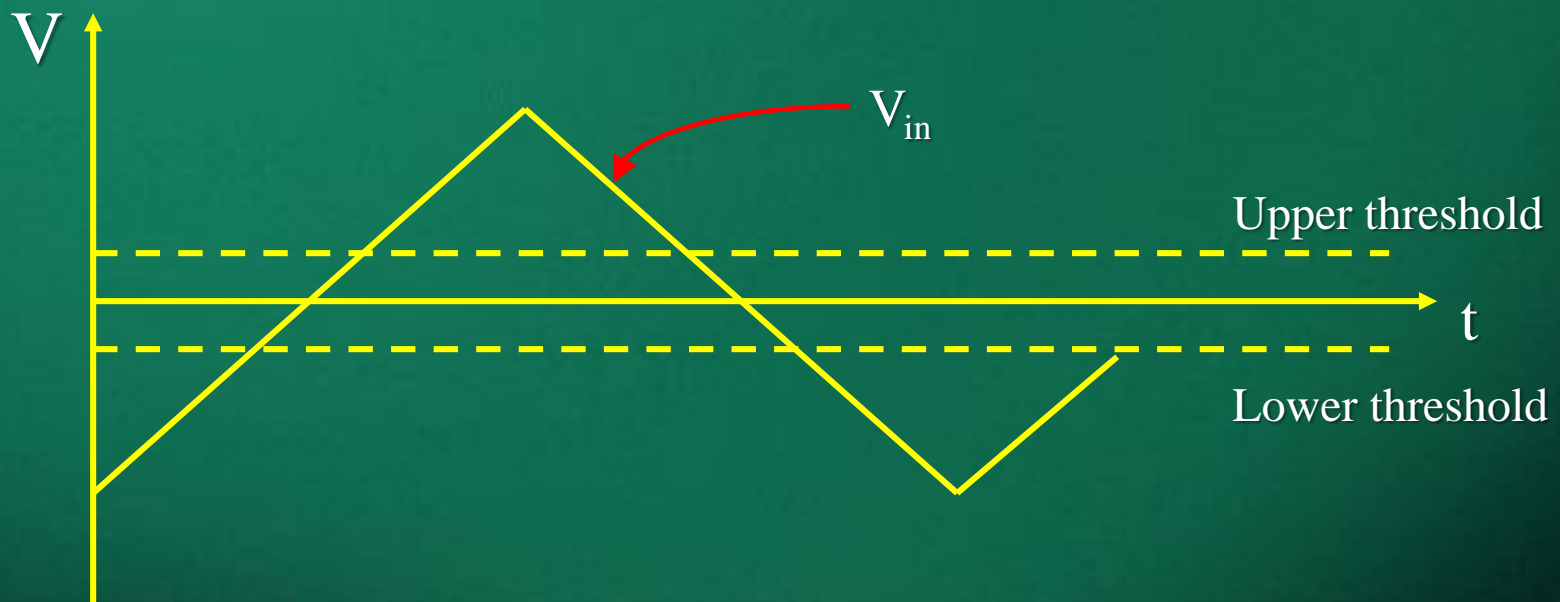- A comparator with hysteresis has a **safety margin**.
- One of two thresholds is used depending on the **current output state**.




Hysteresis

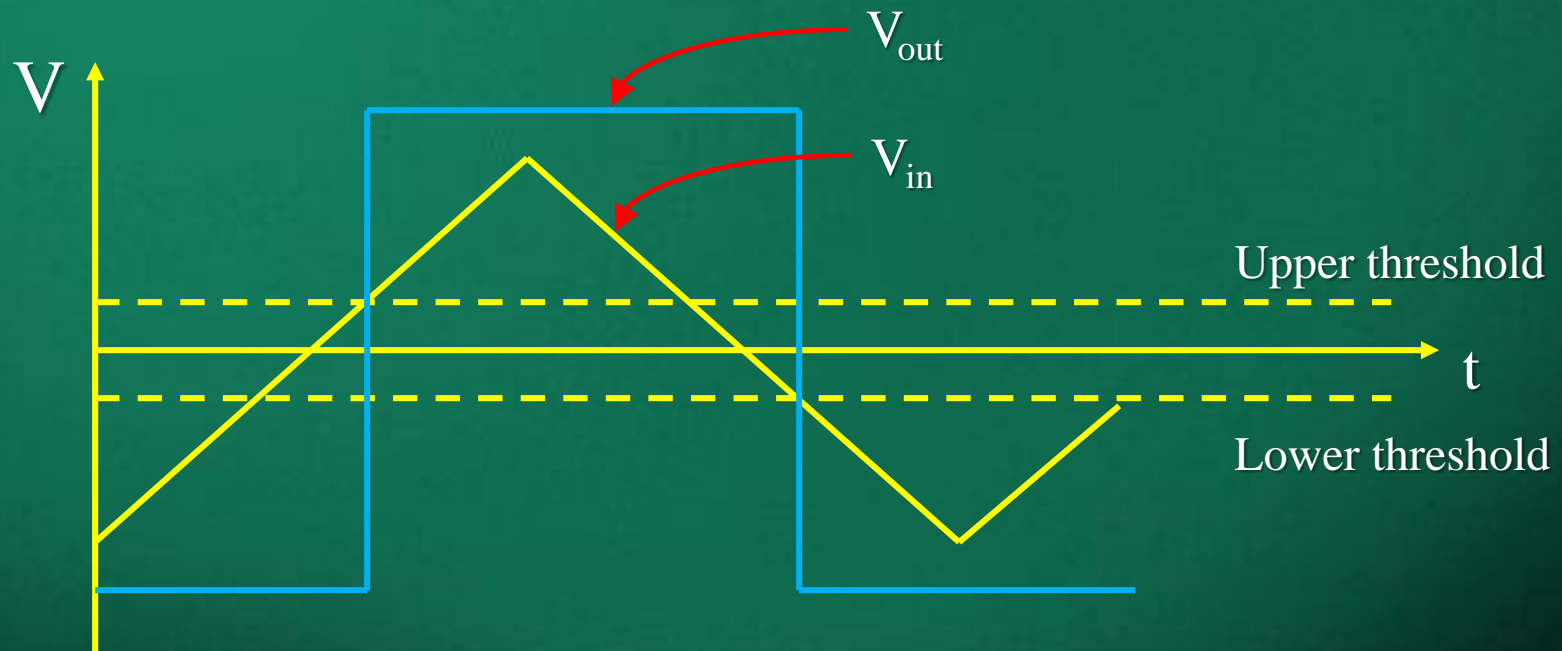- A comparator with hysteresis has a **safety margin**.
- One of two thresholds is used depending on the **current output state**.



Hysteresis

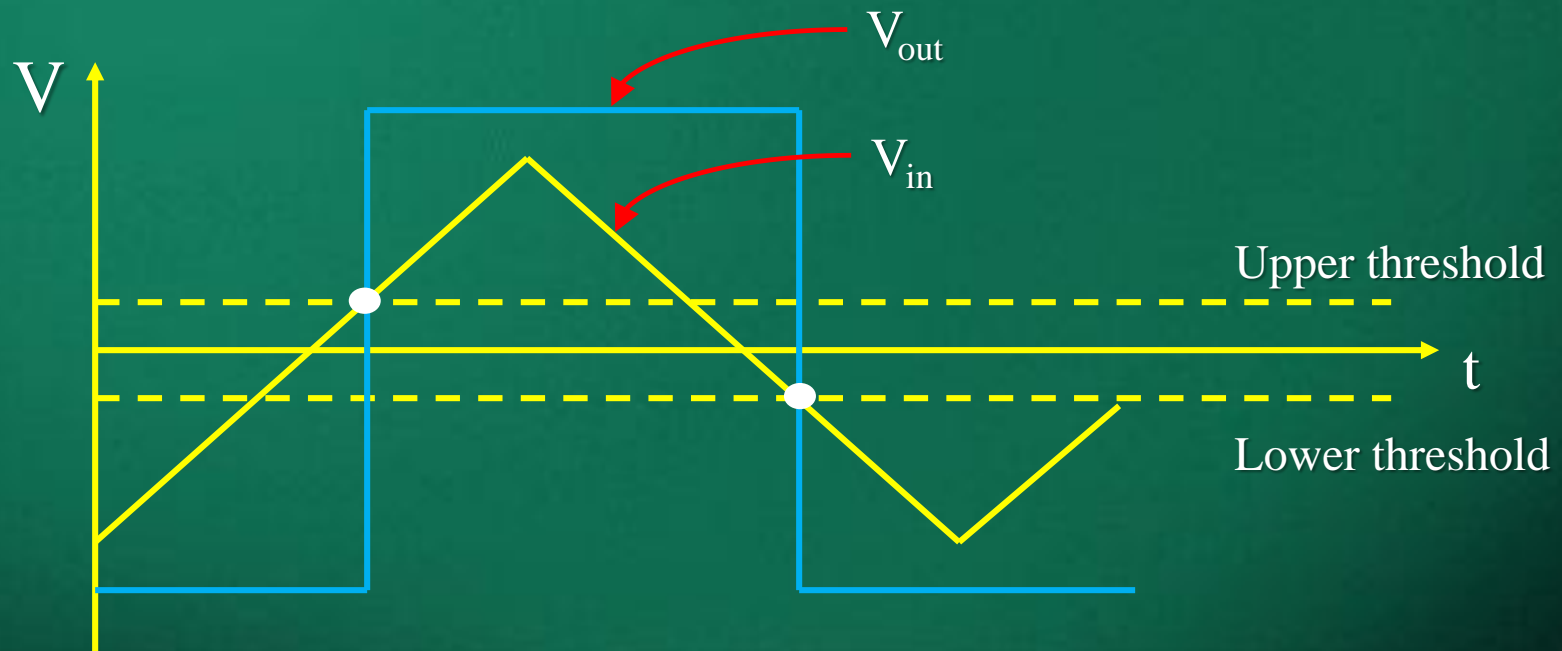- A comparator with hysteresis has a **safety margin**.
- One of two thresholds is used depending on the **current output state**.



Hysteresis

- ❑ **The output level depends on the direction you are coming from.**

Hysteresis

- ☐ **The output level depends on the direction you are coming from.**
- ☐ **There is window around the threshold level where nothing happens.**


Hysteresis

- ☐ **The output level depends on the direction you are coming from.**
- ☐ **There is window around the threshold level where nothing happens.**
- ☐ **The advantage is immunity against small noise spikes.**

Hysteresis

- ☐ **The output level depends on the direction you are coming from.**
- ☐ **There is window around the threshold level where nothing happens.**
- ☐ **The advantage is immunity against small noise spikes.**
- ☐ **It takes at minimum the hysteresis range to make it switch.**

Rejecting Interference

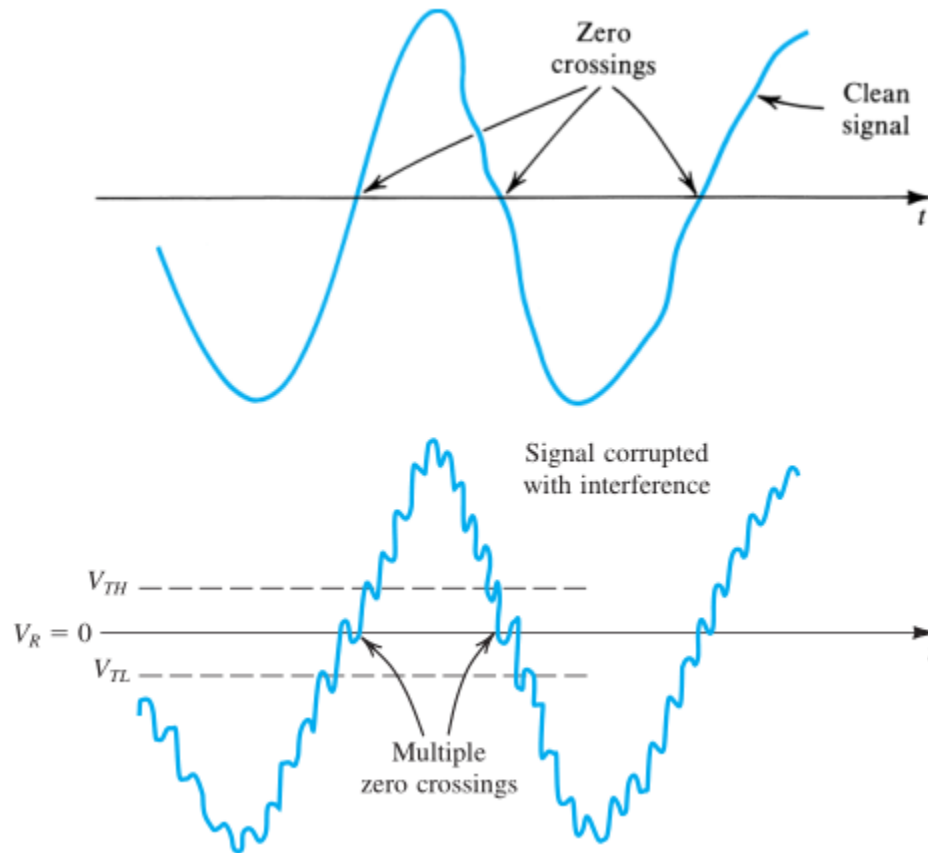

Schmitt Trigger

Schmitt Trigger


- **The Schmitt trigger is an op-amp comparator circuit featuring hysteresis.**

Schmitt Trigger


- ☐ **The Schmitt trigger is an op-amp comparator circuit featuring hysteresis.**
- ☐ **The inverting variety is the most commonly used.**

Schmitt Trigger

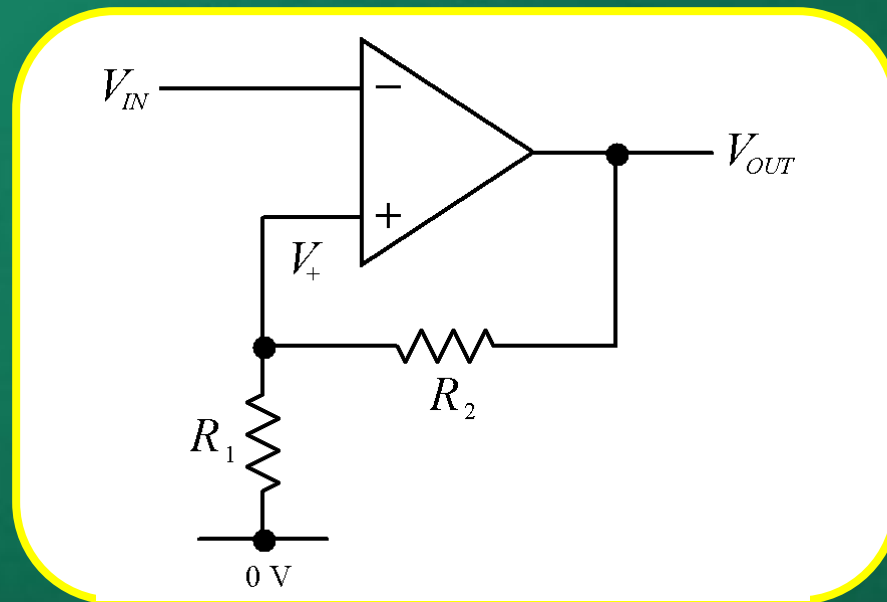- ❑ The Schmitt trigger is an op-amp comparator circuit featuring hysteresis.
- ❑ The inverting variety is the most commonly used.




Schmitt Trigger Analysis

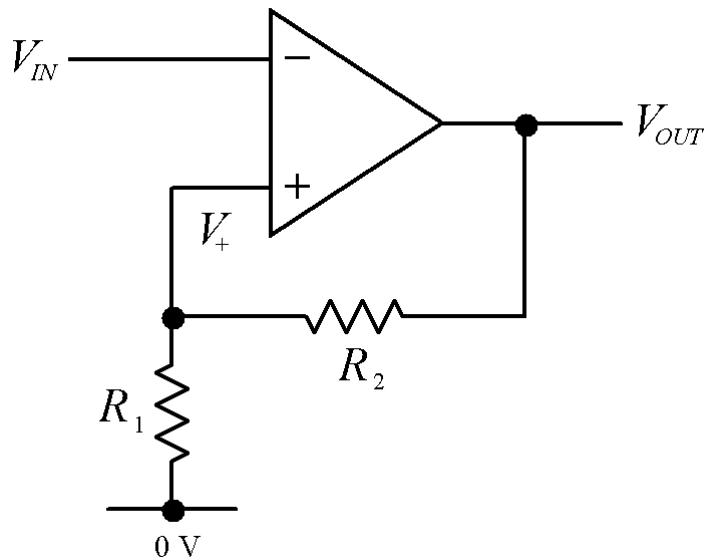


Schmitt Trigger Analysis

Switching occurs when:

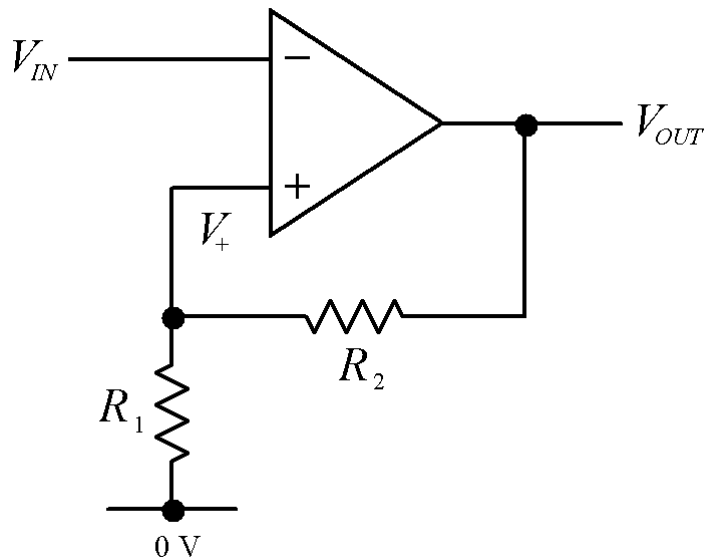

Schmitt Trigger Analysis


Switching occurs when:

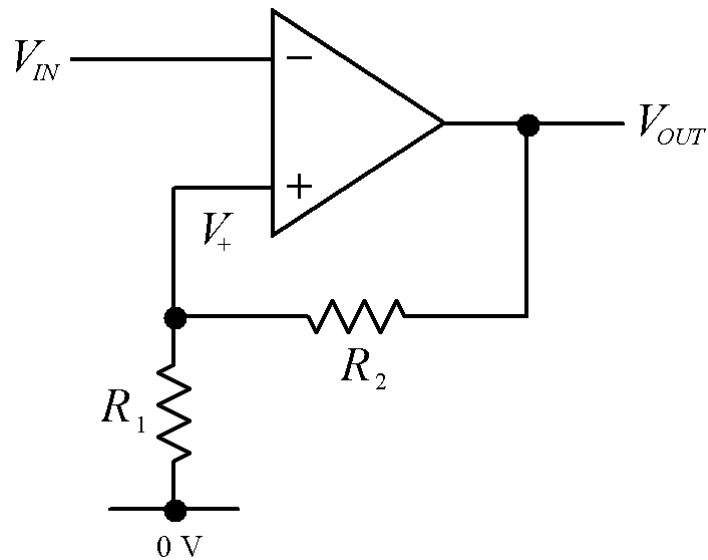

$$V_{IN} = V_- = V_+ = V_{OUT} \frac{R_1}{R_1 + R_2}$$

Schmitt Trigger Analysis

Switching occurs when:

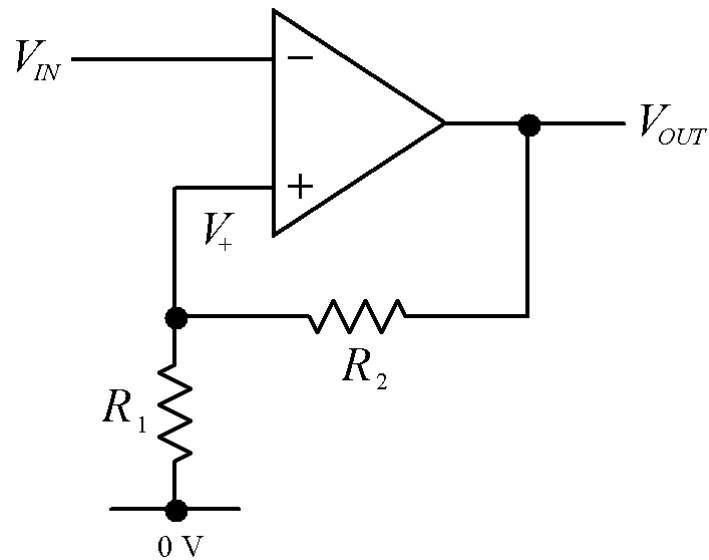

$$V_{IN} = V_- = V_+ = V_{OUT} \frac{R_1}{R_1 + R_2}$$

But,


$$V_{OUT} = \pm V_{SAT}$$

$$\therefore V_{THRESH} = \pm V_{SAT} \frac{R_1}{R_1 + R_2}$$

Input-Output Relationship




Input-Output Relationship

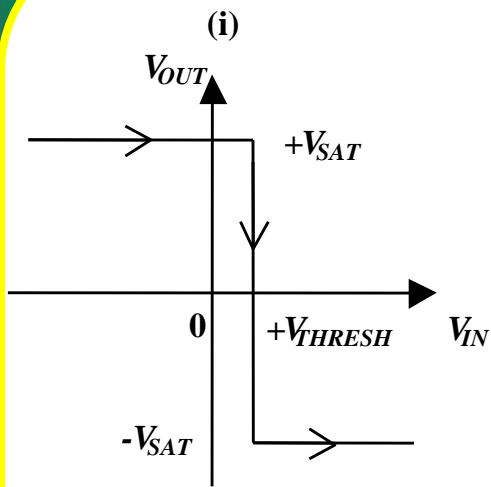


V_{IN} increasing

Input-Output Relationship

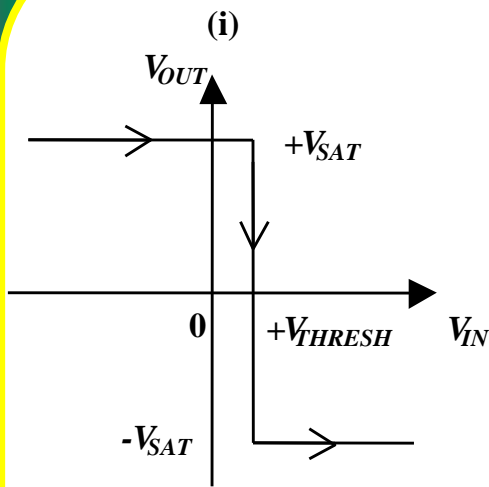


V_{IN} increasing

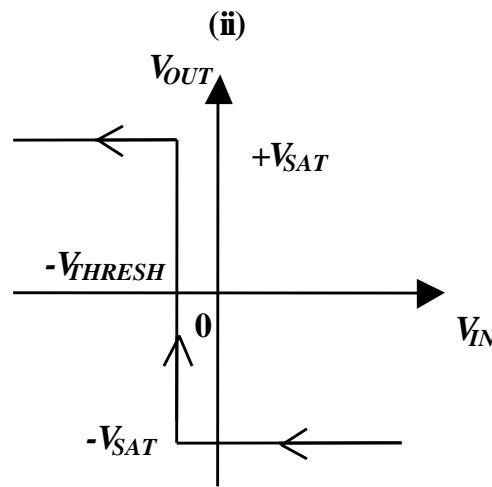


V_{IN} decreasing


Input-Output Relationship

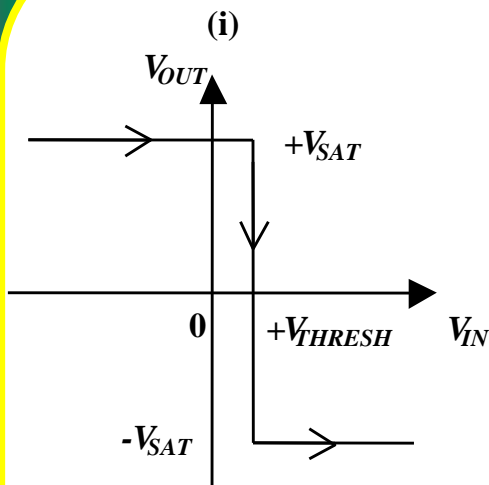

V_{IN} increasing

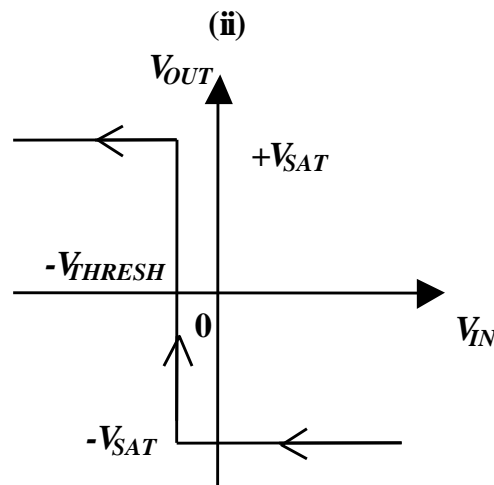

V_{IN} decreasing

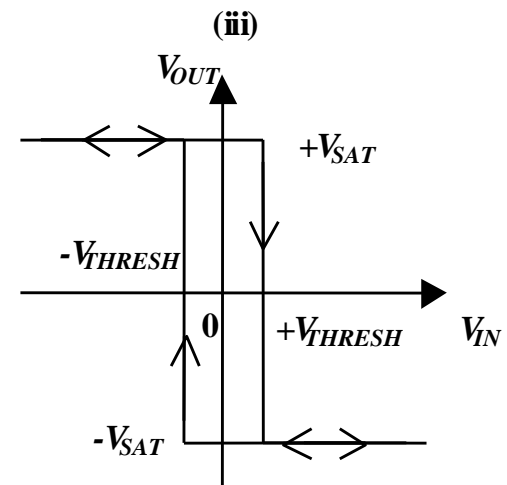

(i) & (ii) combined

Square Wave Generator

Square Wave Generator

- ❑ Square waves are generally used in digital switching circuits.


Square Wave Generator

- ❑ Square waves are generally used in digital switching circuits.
- ❑ Square wave can be generated using op-amp in positive feedback configuration without the need of an external input.


Square Wave Generator

- ☐ Square waves are generally used in digital switching circuits.
- ☐ Square wave can be generated using op-amp in positive feedback configuration without the need of an external input.
- ☐ The circuits generating a square wave can be called as relaxation oscillator or astable multi vibrator.


Square Wave Generator

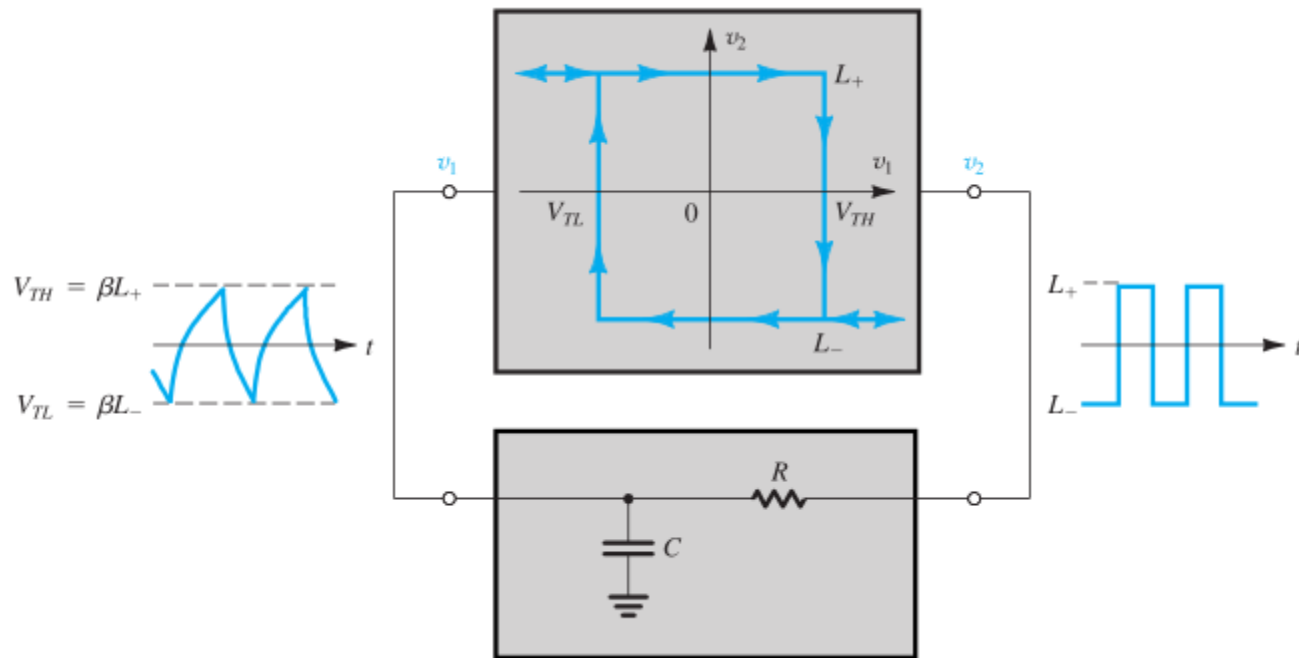

Square Wave Generator

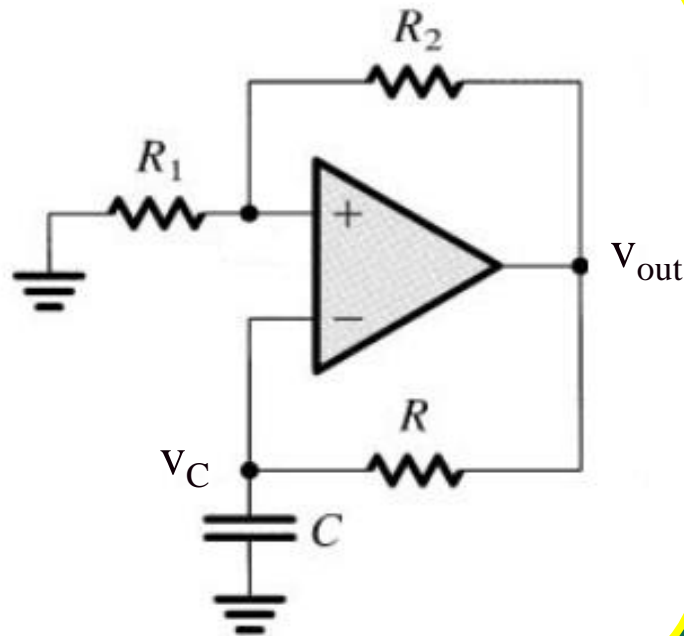


Square Wave Generator

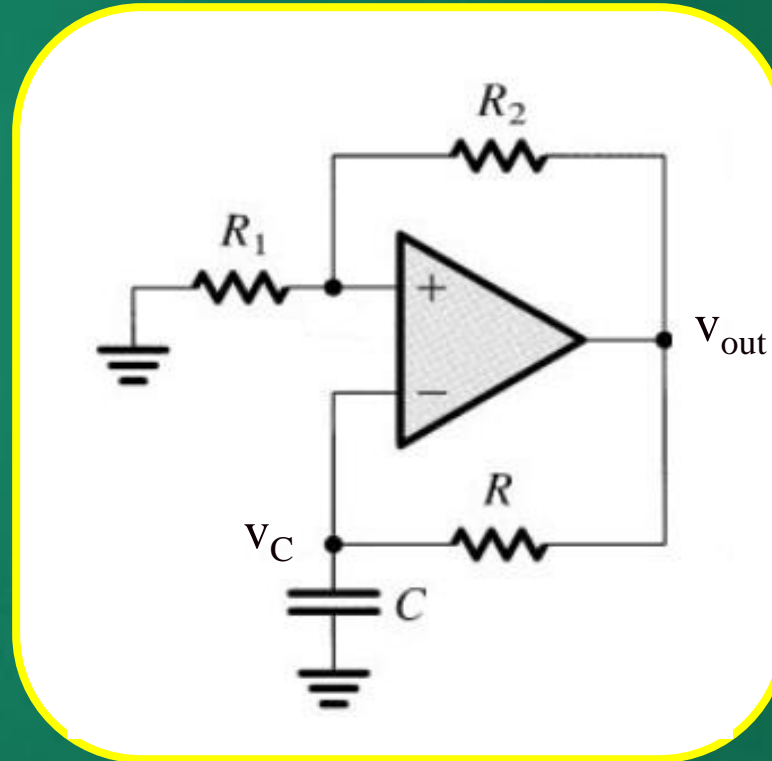


The circuit's frequency of oscillation will depend on the charging and discharging of capacitor C through feedback resistor R .


Hysteresis Loop

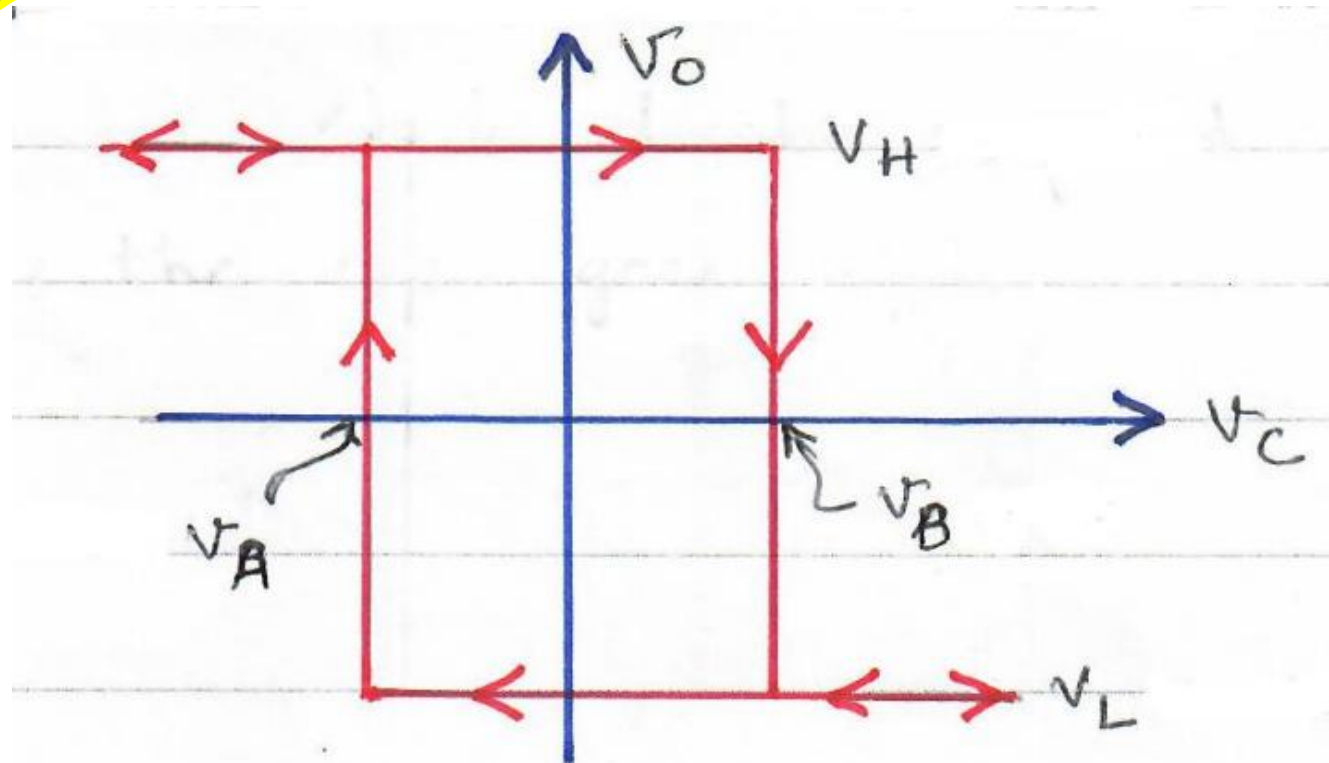


Capacitor Voltage

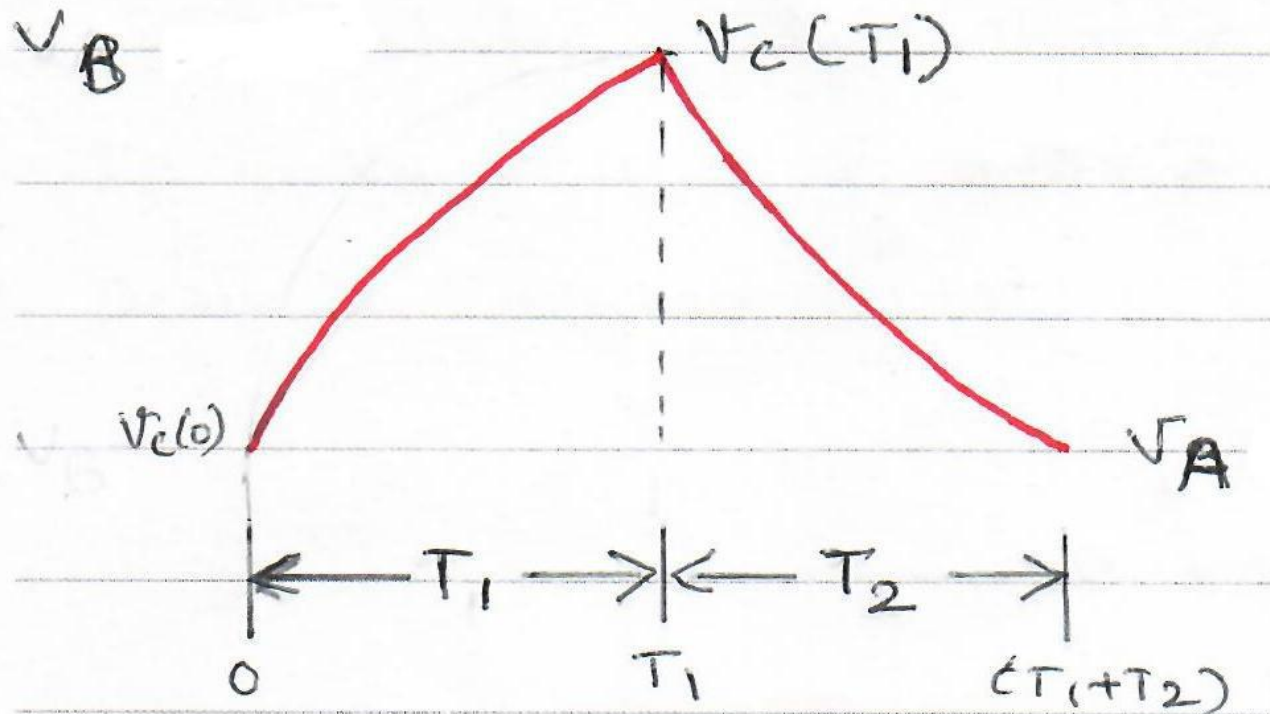

Output Voltage

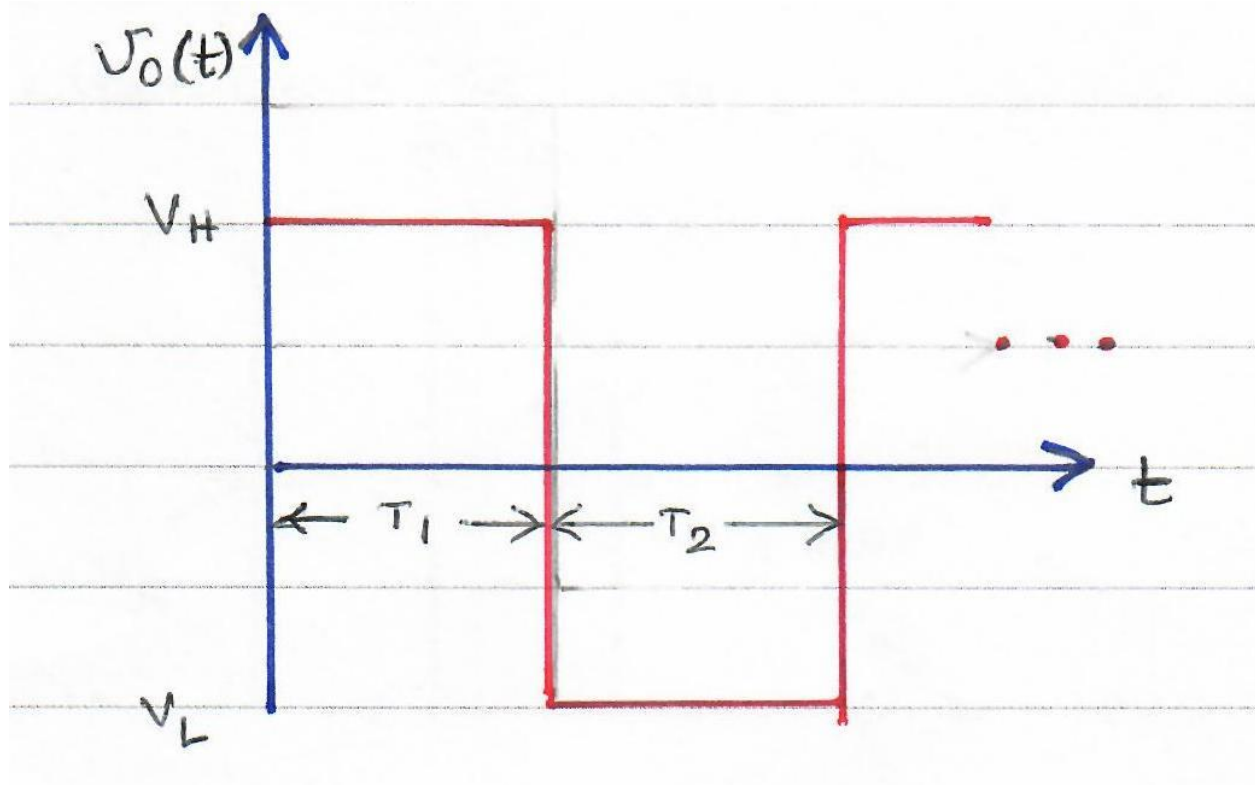


Analysis

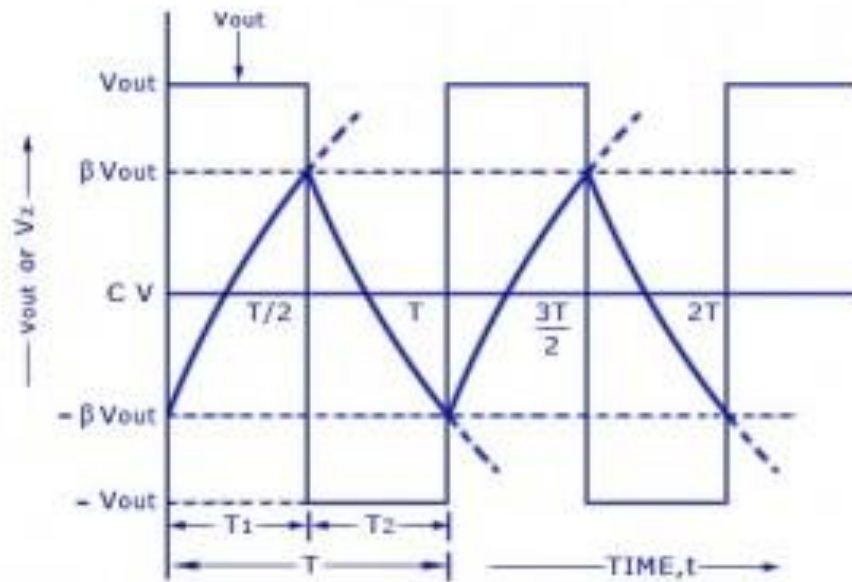

Output and Capacitor Voltage Waveforms

Analysis

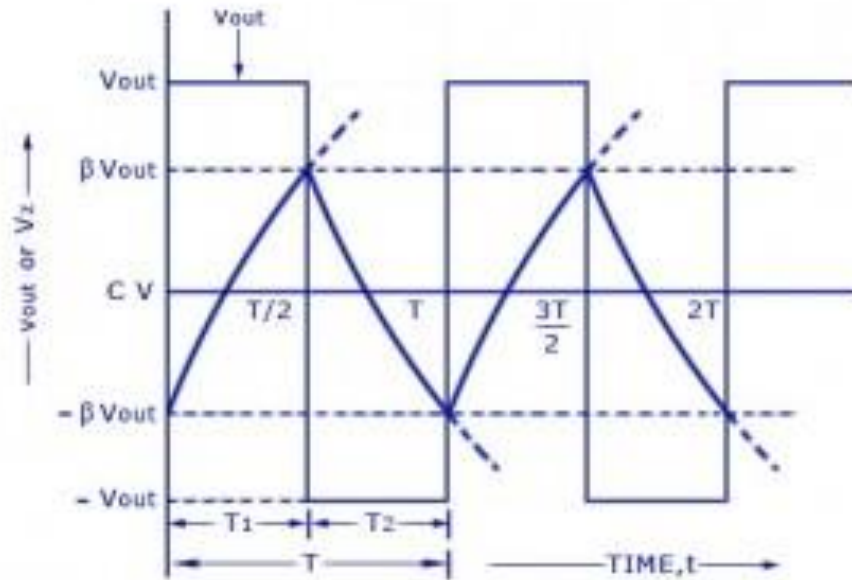

Output and Capacitor Voltage Waveforms

$$T_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right) \text{ where } \beta = \frac{R_1}{R_1 + R_2}$$

Analysis

$$T_2 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right) \text{ where } \beta = \frac{R_1}{R_1 + R_2}$$

Analysis

$$T_2 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right) \text{ where } \beta = \frac{R_1}{R_1 + R_2}$$

$$\therefore T_1 = T_2$$

Analysis

$$T_2 = RC \ln\left(\frac{1+\beta}{1-\beta}\right) \text{ where } \beta = \frac{R_1}{R_1 + R_2}$$

$$\therefore T_1 = T_2$$

$$T = T_1 + T_2 = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

Analysis

$$T_2 = RC \ln\left(\frac{1+\beta}{1-\beta}\right) \text{ where } \beta = \frac{R_1}{R_1 + R_2}$$

$$\therefore T_1 = T_2$$

$$T = T_1 + T_2 = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

If $R_1 = R_2 = R$ then $\beta = 0.5$

Analysis

$$T_2 = RC \ln\left(\frac{1+\beta}{1-\beta}\right) \text{ where } \beta = \frac{R_1}{R_1 + R_2}$$

$$\therefore T_1 = T_2$$

$$T = T_1 + T_2 = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

If $R_1 = R_2 = R$ then $\beta = 0.5$

$$\Rightarrow T = 2RC \ln\left(\frac{1+0.5}{1-0.5}\right) = 2RC \ln(3) = 2.197RC$$


Triangular Wave Generator

Triangular Wave Generator




Generating triangular wave from a square wave

Integrator Circuit

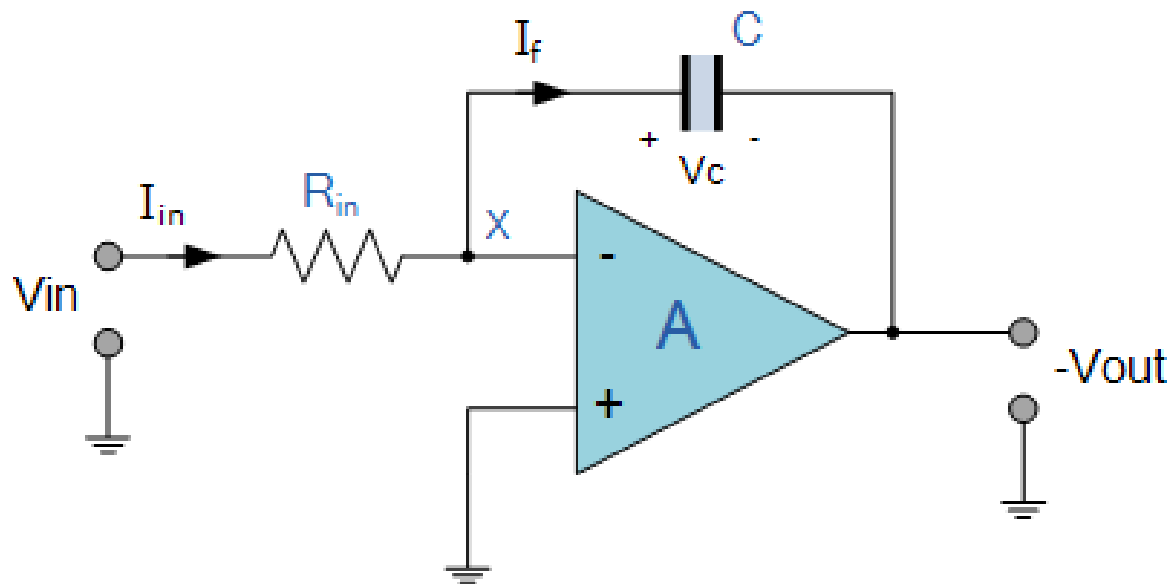


Integrator Circuit

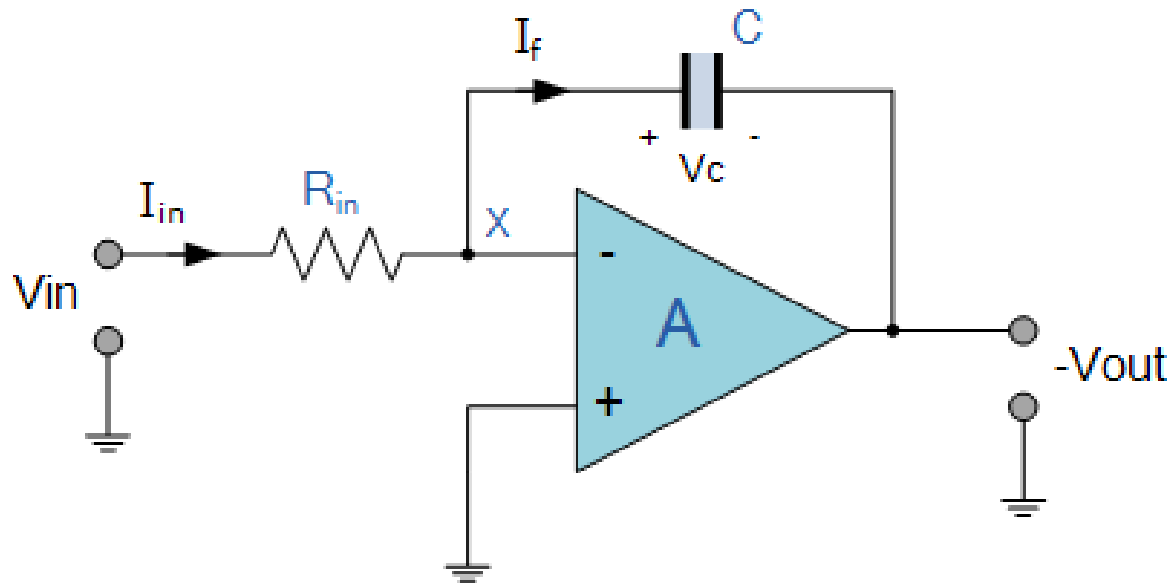

$$V_{out}(t) = -\frac{1}{R_{in}C} \int_0^t V_{in}(t) dt$$


Integrator Circuit

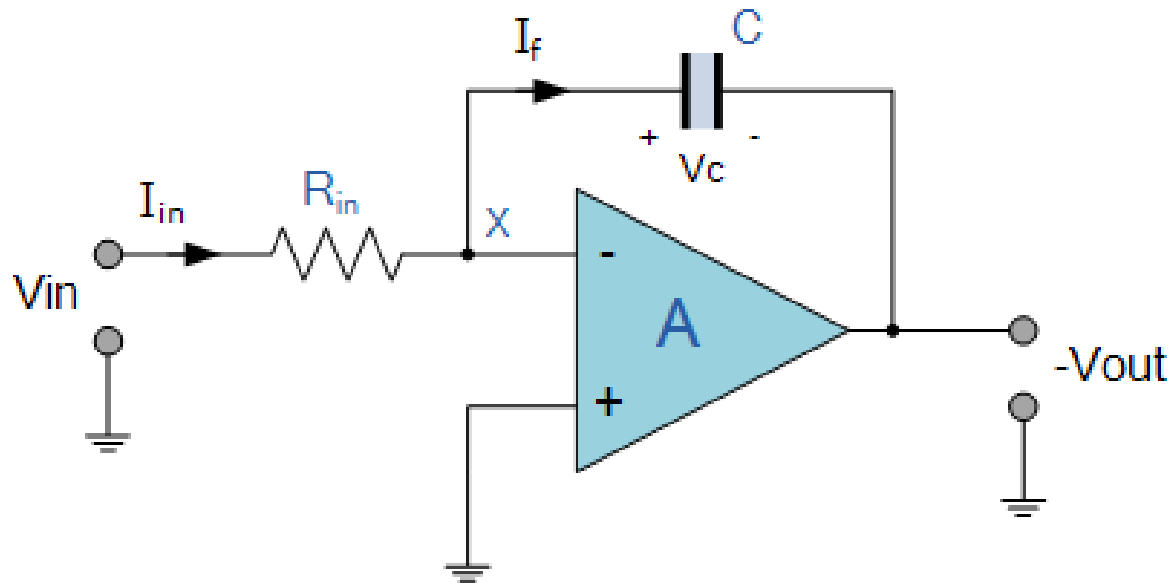

$$V_{out}(t) = -\frac{1}{R_{in}C} \int_0^t V_{in}(t) dt$$

$$V_{out}(\omega) = -\frac{1}{j\omega R_{in}C} V_{in}(\omega)$$

Practical Integrator Circuit

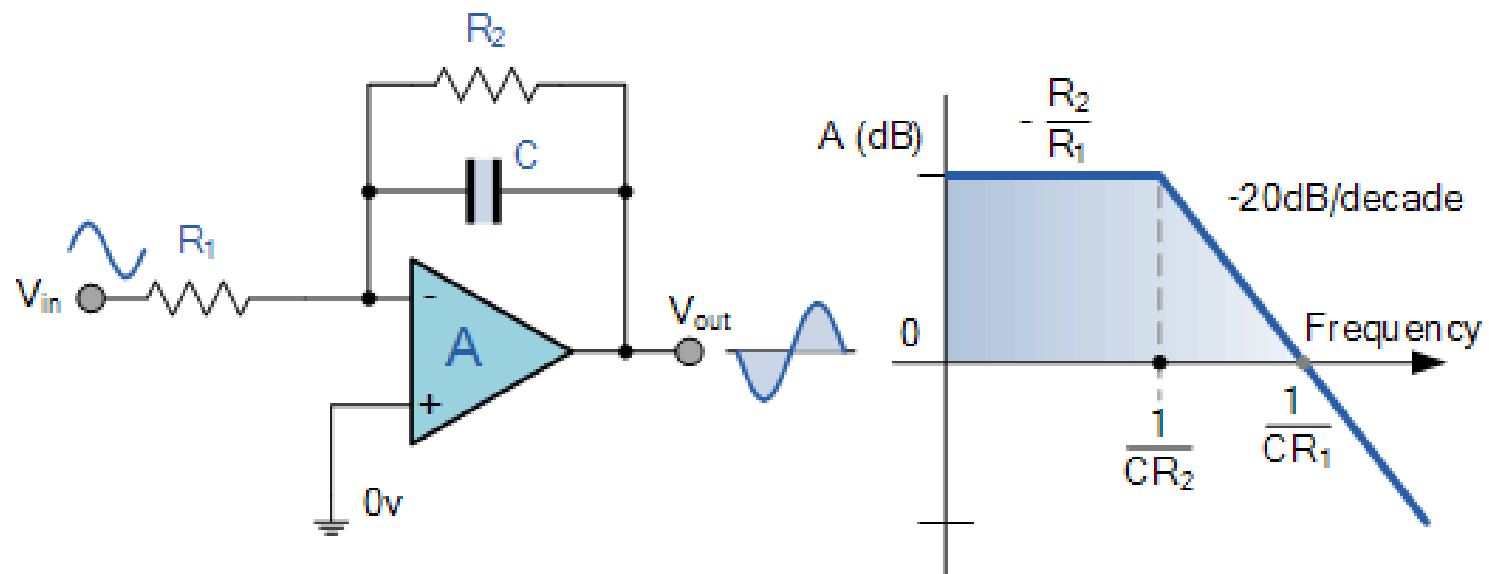


Practical Integrator Circuit

$$\text{DC Voltage Gain } (A_{v0}) = -\frac{R_2}{R_1}$$


$$\text{AC Voltage Gain } (A_v) = -\frac{R_2}{R_1} \times \frac{1}{(1 + \omega CR_2)}$$

$$\text{Corner Frequency } (\omega_0) = \frac{1}{CR_2}$$

Triangular Wave Generator

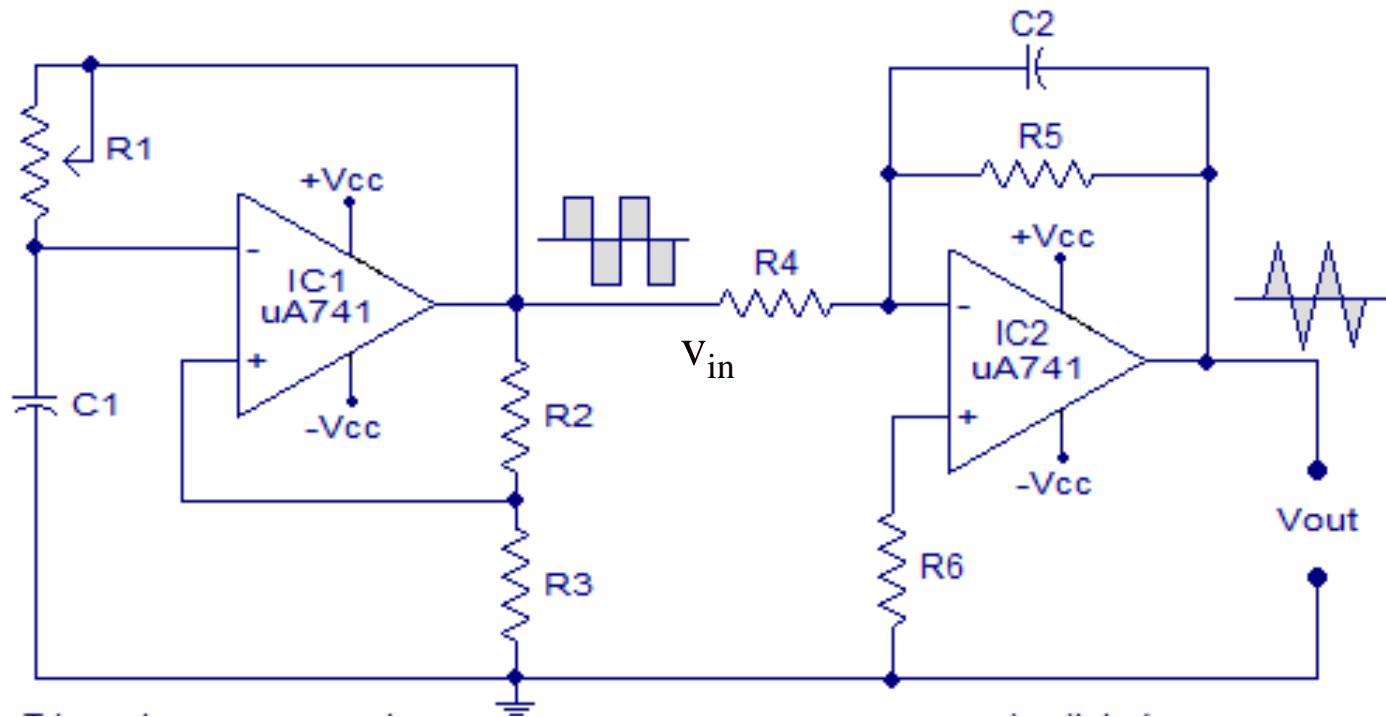


Triangular Wave Generator

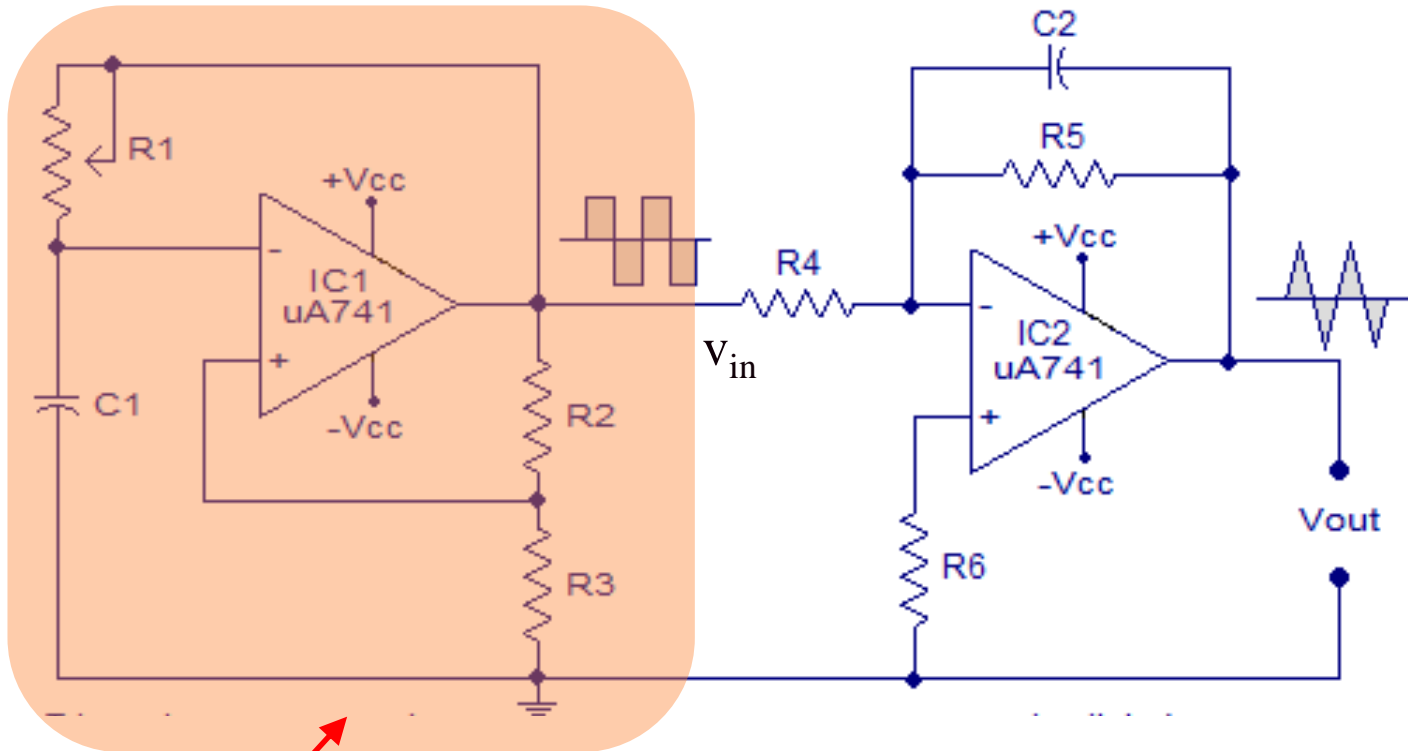

Square Wave Generator


Triangular Wave Generator

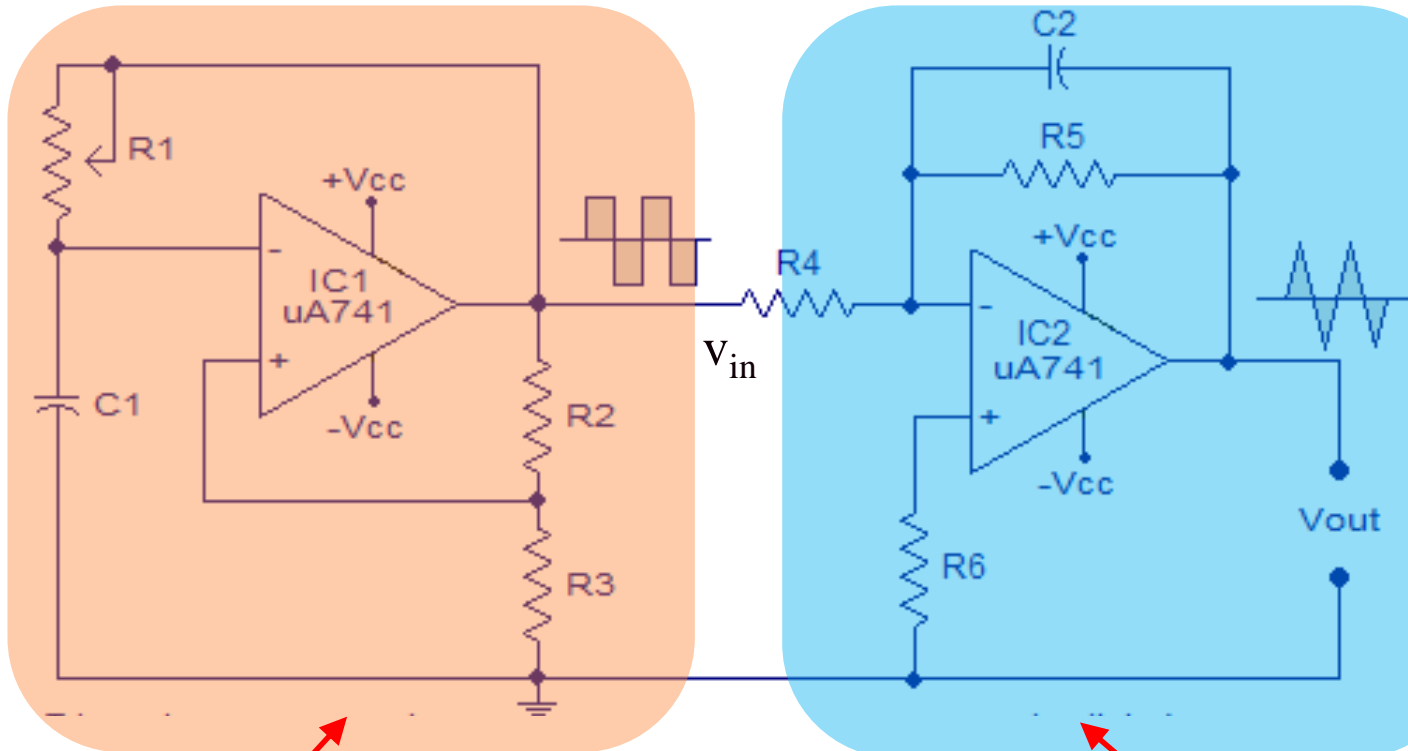


Square Wave Generator

Integrator

Triangular Wave Generator

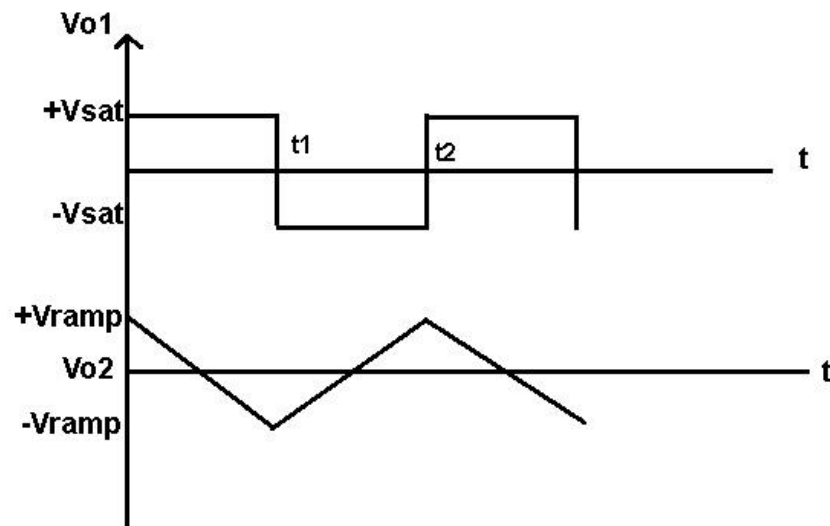


Triangular Wave Generator

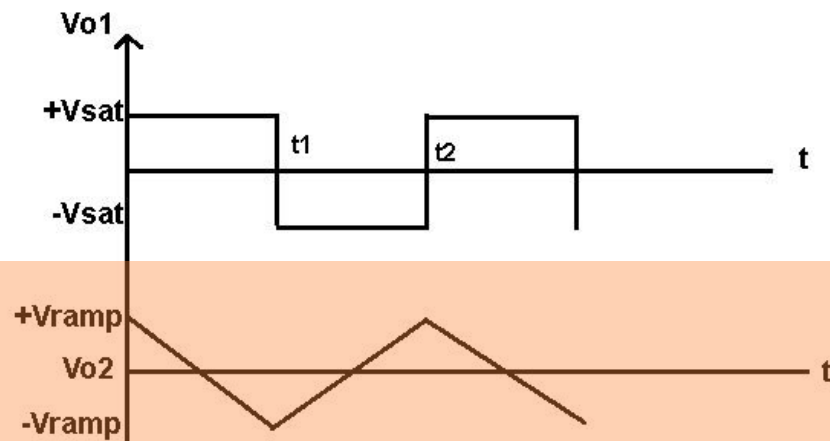


V_{out}

Triangular Wave Generator


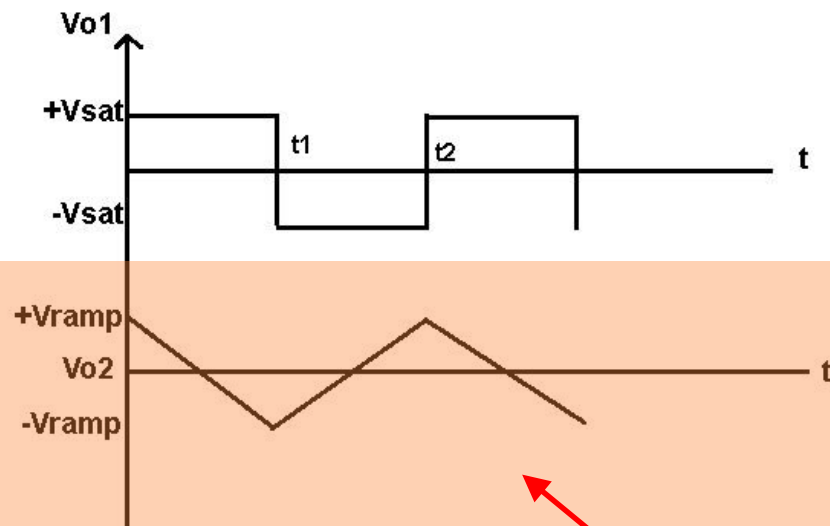


$$V_{out} = \left(\frac{-R_5 / R_4}{R_5 C_2 s + 1} \right) V_{in}$$

Triangular Wave Generator

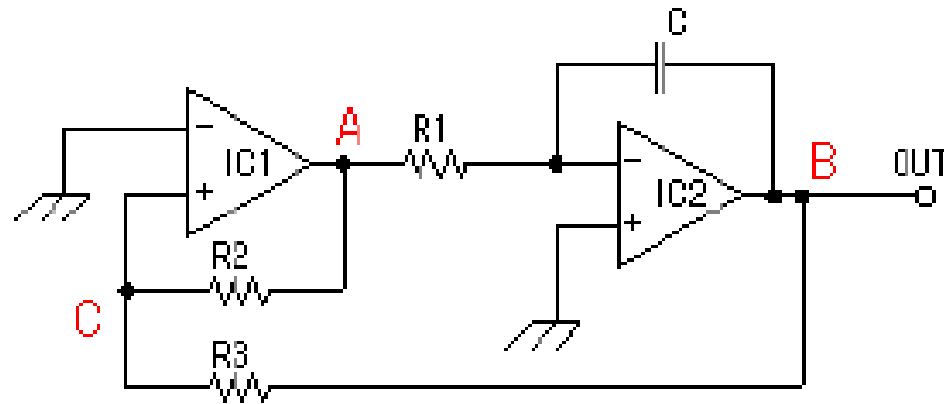


Triangular Wave Generator

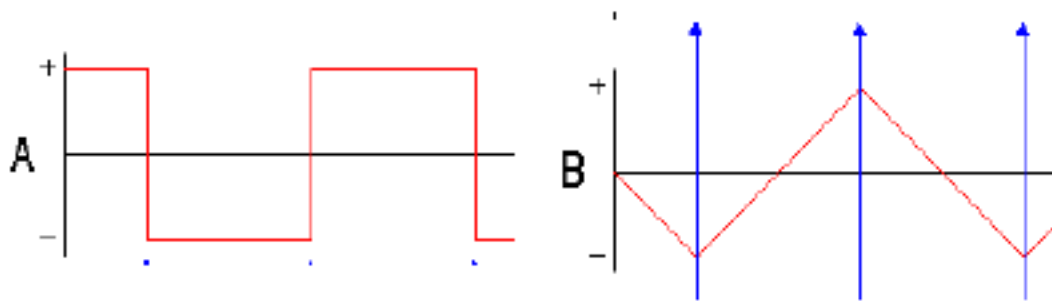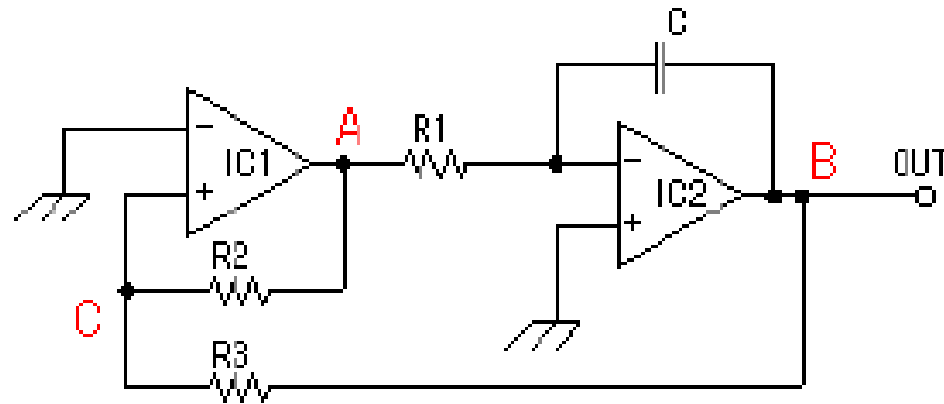

Log and Antilog Amplifier

Logarithmic Amplifier

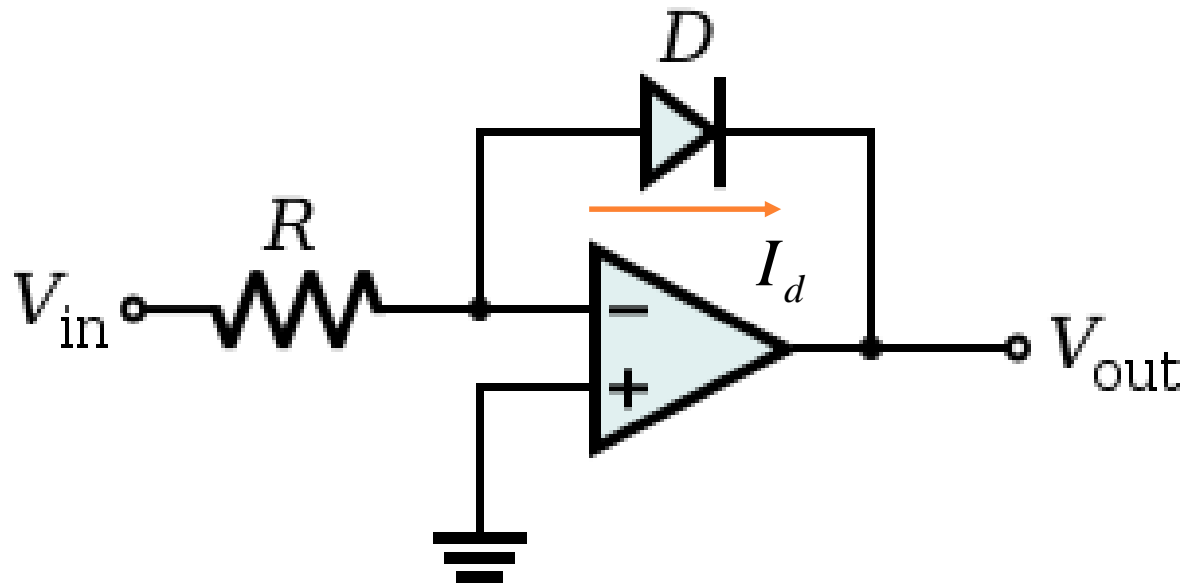

Diode Equation

$$i_D = I_0 \left(e^{\frac{qv_D}{nKT}} - 1 \right)$$

Diode Equation

$$i_D = I_0 \left(e^{\frac{qv_D}{nKT}} - 1 \right)$$

i_D = the net current flowing through the diode;

I_0 = "dark saturation current", the diode leakage current in the absence of light;

v_D = applied voltage across the terminals of the diode;

q = absolute value of electron charge (1.6×10^{-19} C);

k = Boltzmann's constant (1.38×10^{-23} J/K);

T = absolute temperature in Kelvin (K); and

n = empirical constant, 1 for Ge and 2 for Si diode.

Diode Equation

$$i_D = I_0 \left(e^{\frac{qv_D}{nKT}} - 1 \right)$$

i_D = the net current flowing through the diode;

I_0 = "dark saturation current", the diode leakage current in the absence of light;

v_D = applied voltage across the terminals of the diode;

q = absolute value of electron charge (1.6×10^{-19} C);

k = Boltzmann's constant (1.38×10^{-23} J/K);

T = absolute temperature in Kelvin (K); and

n = empirical constant, 1 for Ge and 2 for Si diode.

At 300 K, $kT/q = 26$ mV, the thermal voltage.

Diode Equation

$$i_D = I_0 \left(e^{\left(\frac{v_D}{0.026} \right)} - 1 \right)$$

where v_D is the voltage applied across diode in volts.

If diode is forward biased

$$i_D \cong I_0 e^{\left(\frac{v_D}{0.026} \right)}$$

Analysis

Applying KCL at inverting input

Analysis

Applying KCL at inverting input

$$\frac{0 - V_{\text{in}}}{R} + I_d = 0 \Rightarrow I_d = \frac{V_{\text{in}}}{R}$$

Analysis

Applying KCL at inverting input

$$\frac{0 - V_{\text{in}}}{R} + I_d = 0 \Rightarrow I_d = \frac{V_{\text{in}}}{R}$$

But

$$I_d = I_0 (e^{(v_d / v_T)} - 1)$$

Analysis

Applying KCL at inverting input

$$\frac{0 - V_{\text{in}}}{R} + I_d = 0 \Rightarrow I_d = \frac{V_{\text{in}}}{R}$$

But

$$I_d = I_0 (e^{(v_d / v_T)} - 1)$$

When diode is forward biased

$$I_d \cong I_0 (e^{(v_d / v_T)})$$

Analysis

Analysis

Here $V_d = -V_{out}$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

$$e^{(-V_{out} / V_T)} = \frac{V_{in}}{I_0 R}$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

$$e^{(-V_{out} / V_T)} = \frac{V_{in}}{I_0 R}$$

$$V_{out} = -V_T \ln\left(\frac{V_{in}}{I_0 R}\right) = k_1 \ln\left(\frac{V_{in}}{k_2}\right)$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

$$e^{(-V_{out} / V_T)} = \frac{V_{in}}{I_0 R}$$

$$V_{out} = -V_T \ln\left(\frac{V_{in}}{I_0 R}\right) = k_1 \ln\left(\frac{V_{in}}{k_2}\right)$$

where

$$k_1 = -V_T \text{ and } k_2 = I_0 R$$