

Tutorial Sheet-8

JEC103

Q1 Draw the circuit of a 555 Timer to implement monostable multivibrator. Draw the waveforms and derive the expression for pulse width duration at output of 555 Timer.

Q2 Using a 10nF capacitor C , find the value of R that yields an output pulse of duration $100\mu\text{s}$ in the 555 Timer monostable circuit.

Q3 Draw the circuit diagram of a 555 Timer to implement astable multivibrator. Draw the appropriate waveforms and derive expression time period of oscillations and duty ratio

(Q4.) For the 555 Timer astable multivibrator, with a 1nF capacitor, find the values of R_A and R_B that results in an oscillation frequency of 100 kHz and a duty cycle (or ratio) of 75%.