


# **Basic Electronic Circuits**

## **(IEC-103)**


### **Lecture-06**

# **Op-Amp Circuits**

# Example

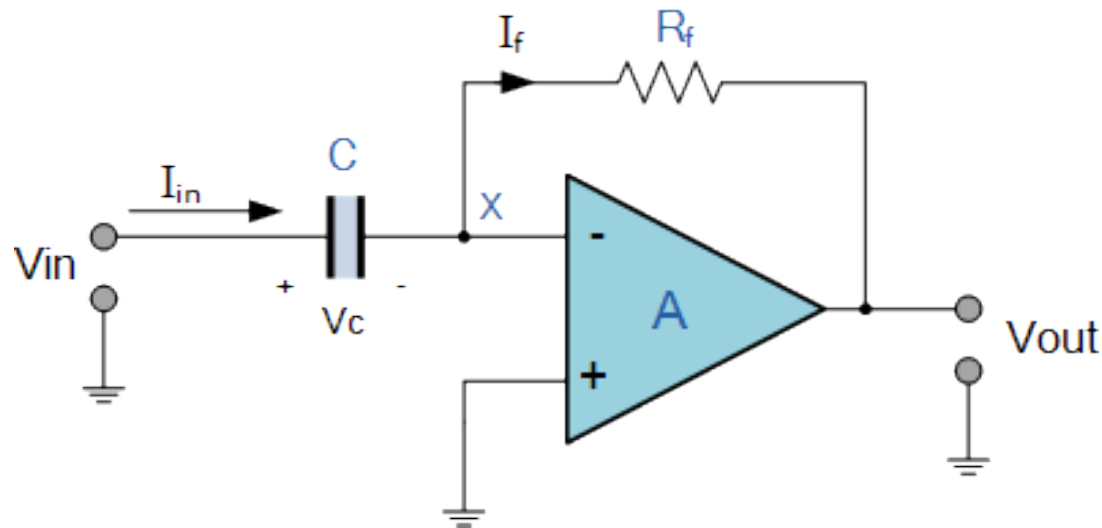


# Example (Continued)

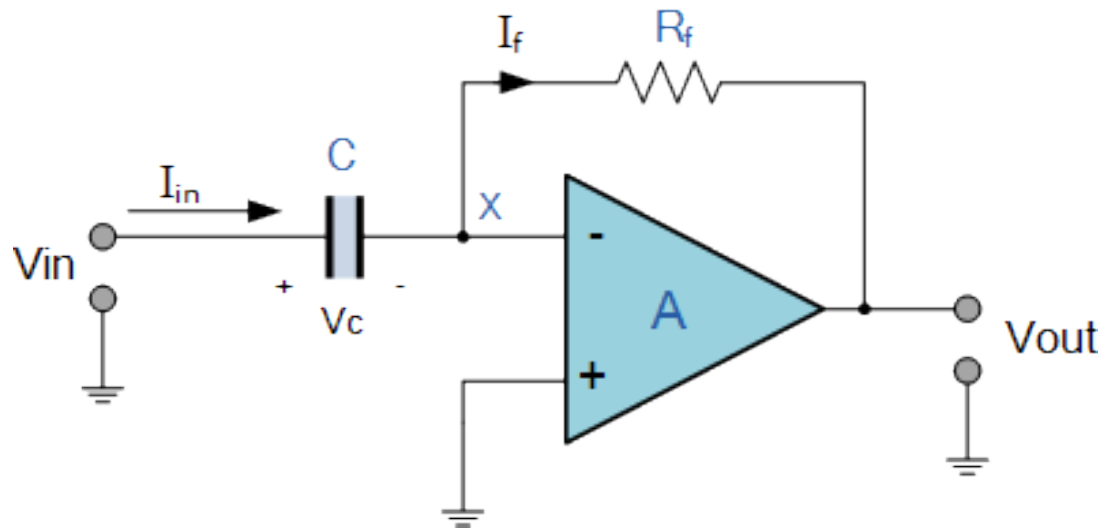

$$V_{out} = -R_f C \frac{dV_{in}}{dt}$$


# Example (Continued)

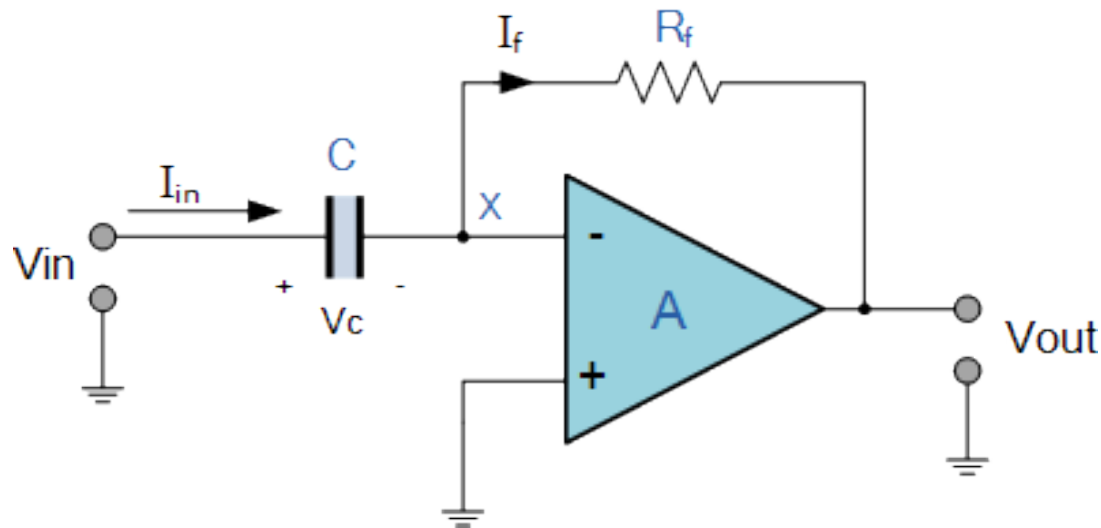

$$V_{out} = -R_f C \frac{dV_{in}}{dt}$$


**Differentiator**

# Example

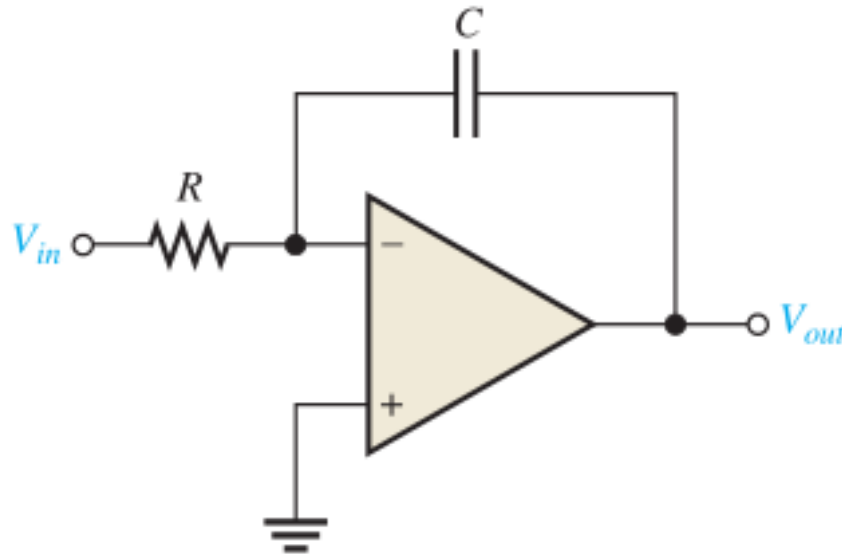




# Example (Continued)

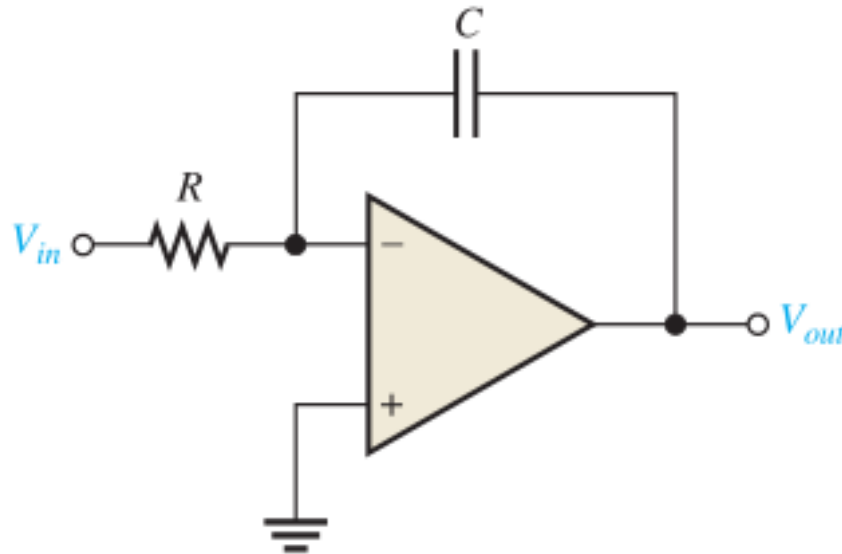

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

# Example (Continued)

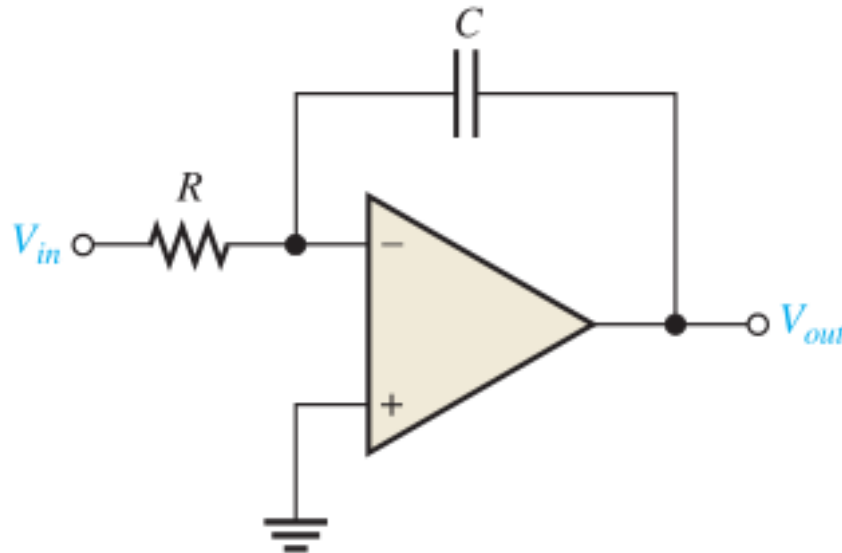


$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$


**Integrator**




# Integrator

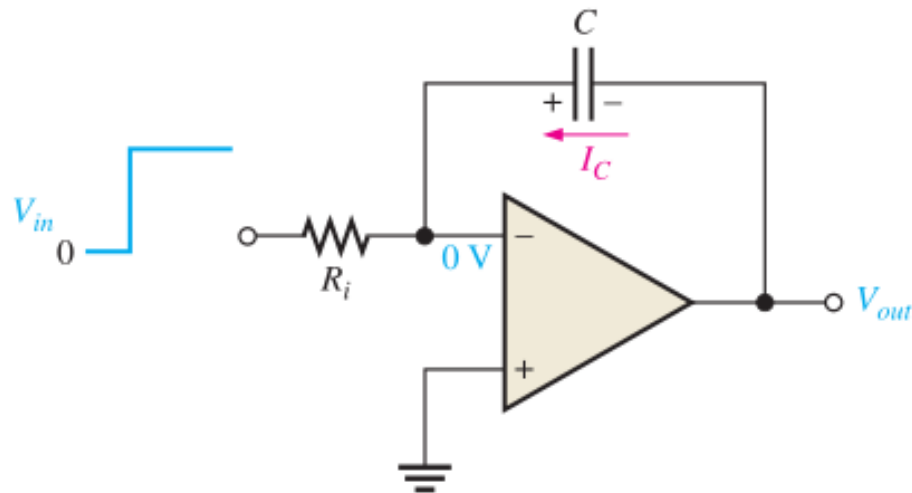

# Integrator

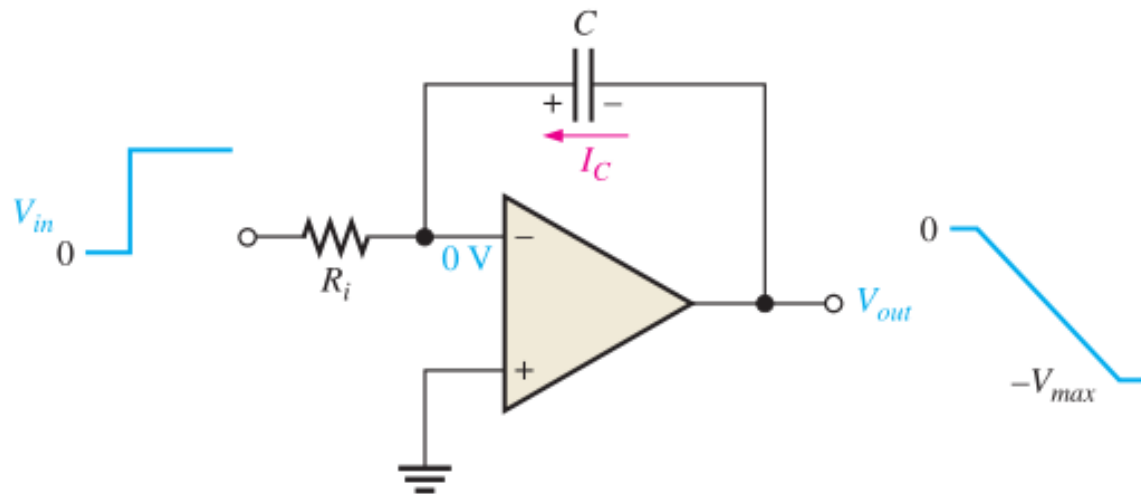


# Integrator

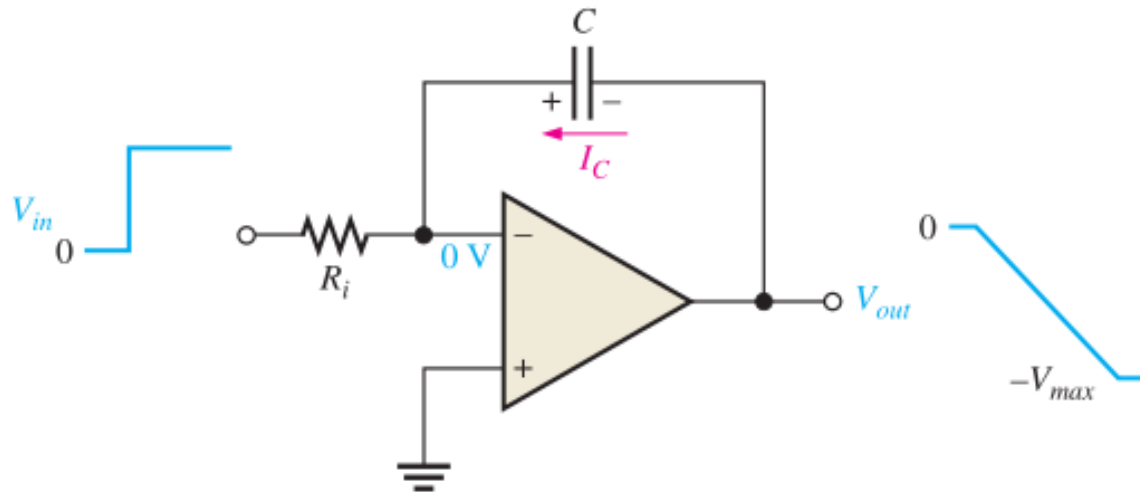


**A constant input voltage produces a ramp on the output of the integrator before it saturates.**
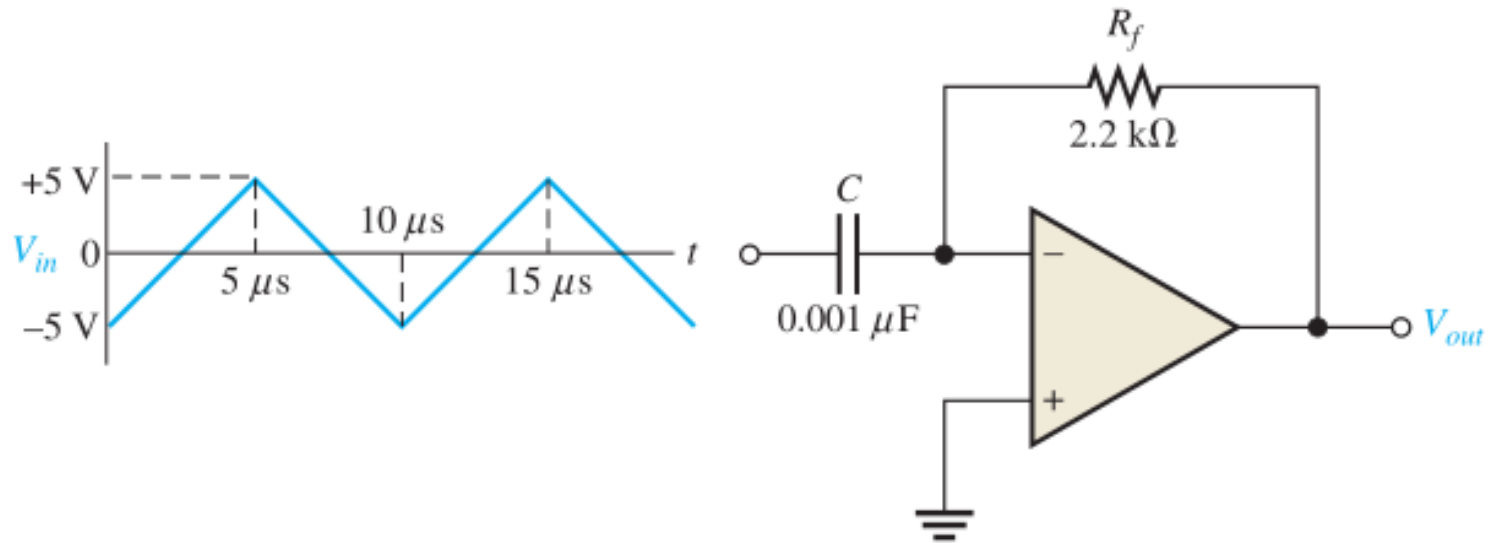
# Example

Determine the output voltage of the op-amp ckt.




# Example

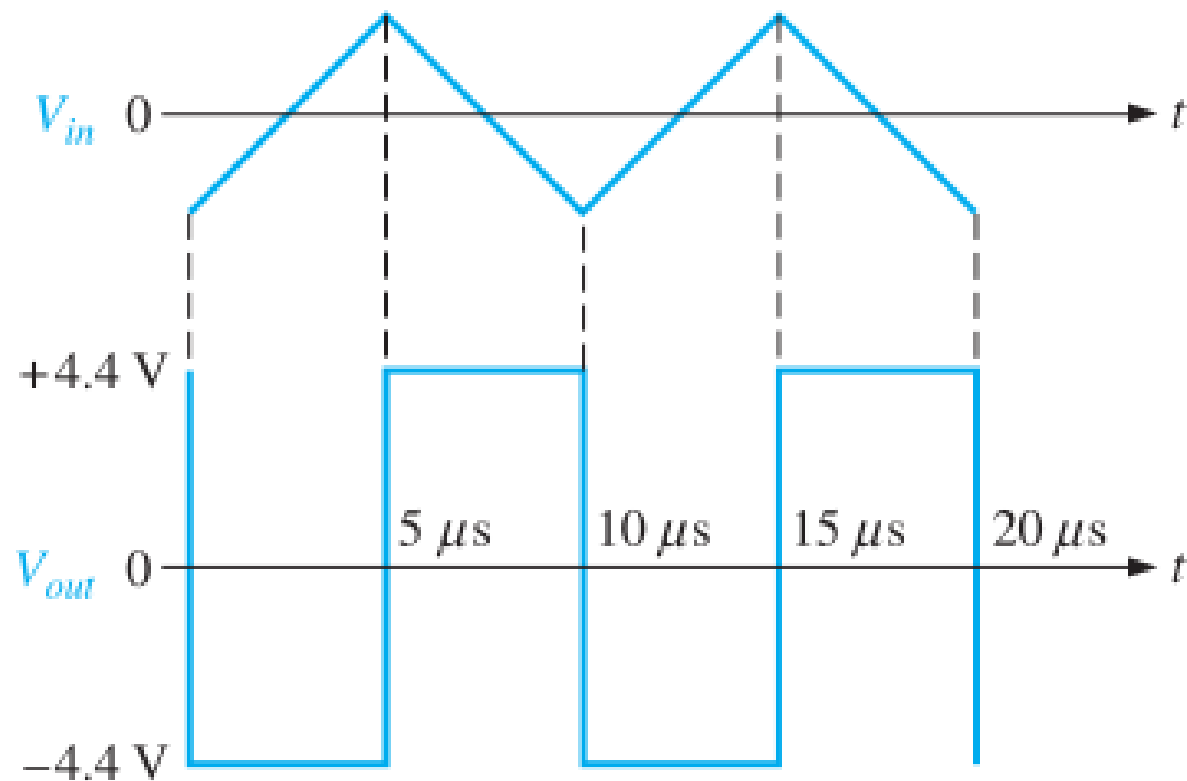


# **Non-linear Applications**



# Comparators

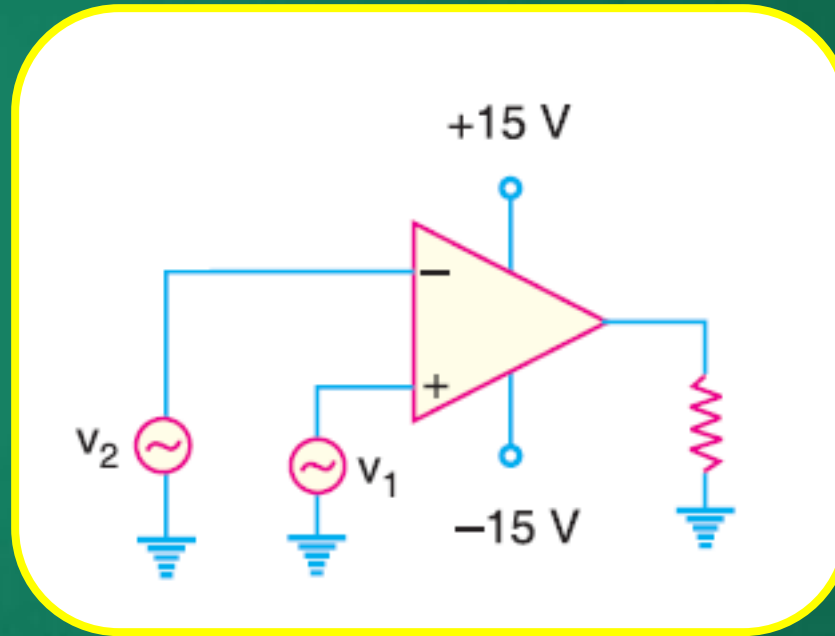


# Comparators

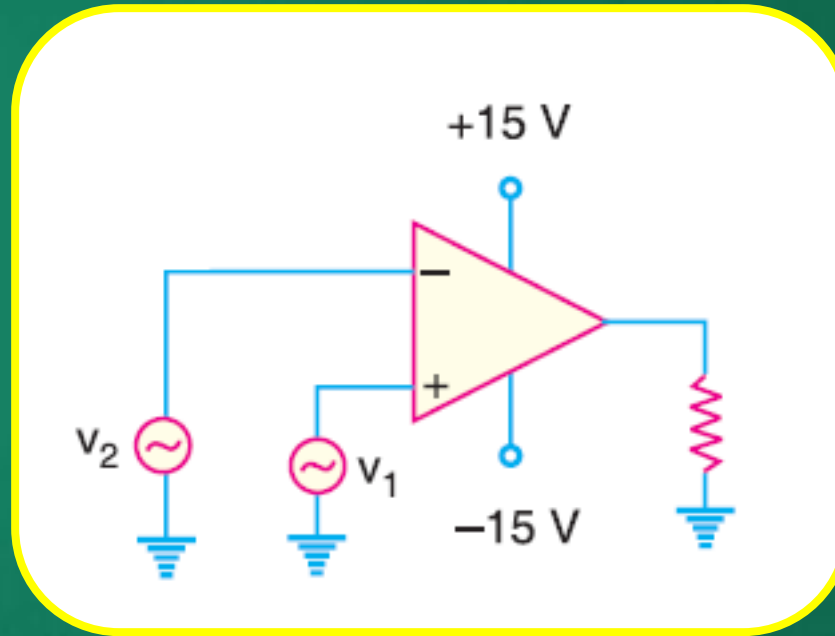

- ❑ **A comparator is an op-amp circuit without negative feedback and takes the advantage of very high open-loop gain.**

# Comparators

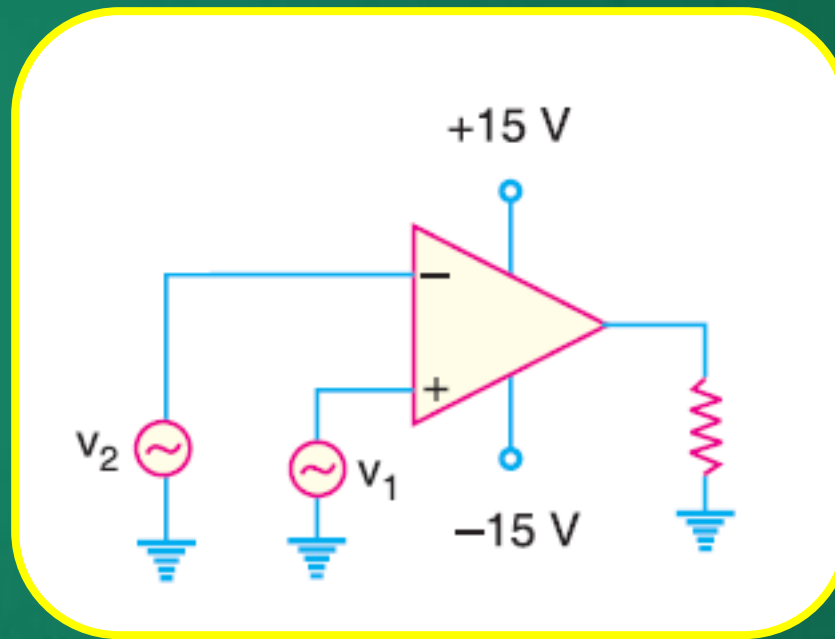


- ❑ **A comparator is an op-amp circuit without negative feedback and takes the advantage of very high open-loop gain.**
- ❑ **It is operated in a non-linear mode.**

# Comparators



$$+V_{sat} = +V_{supply} - 2 = 15 - 2 = +13 \text{ V}$$

$$-V_{sat} = -V_{supply} + 2 = -15 + 2 = -13 \text{ V}$$

# Comparator (Square Wave Generator)

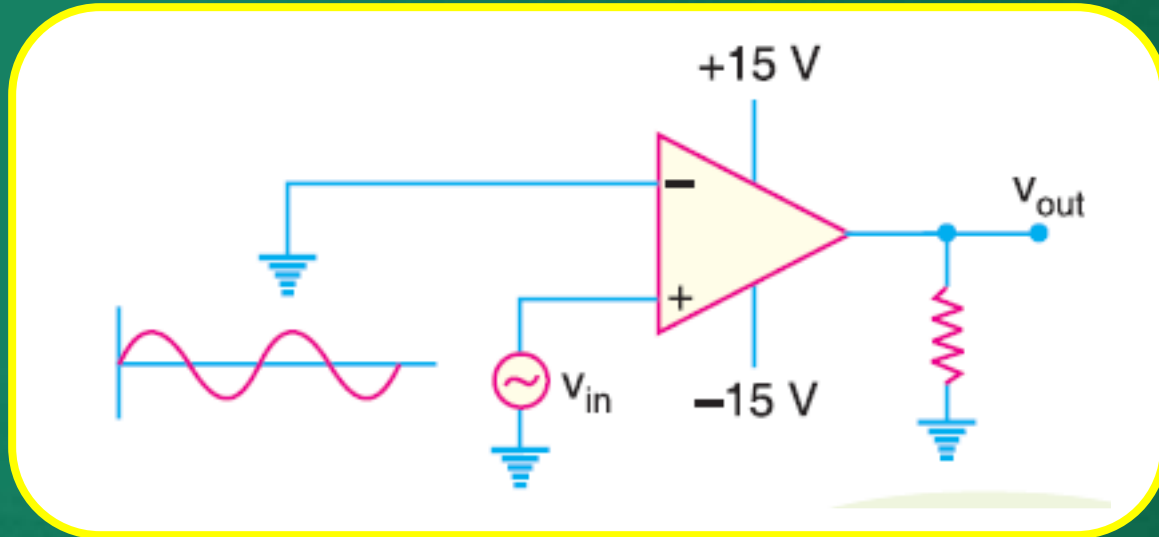


# Comparator (Square Wave Generator)

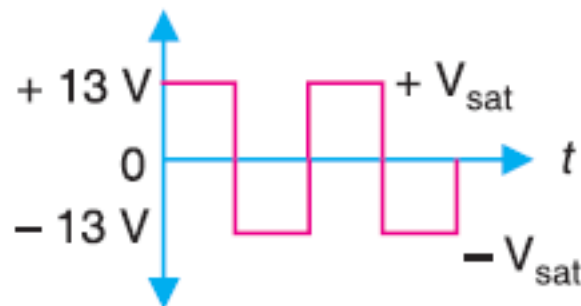
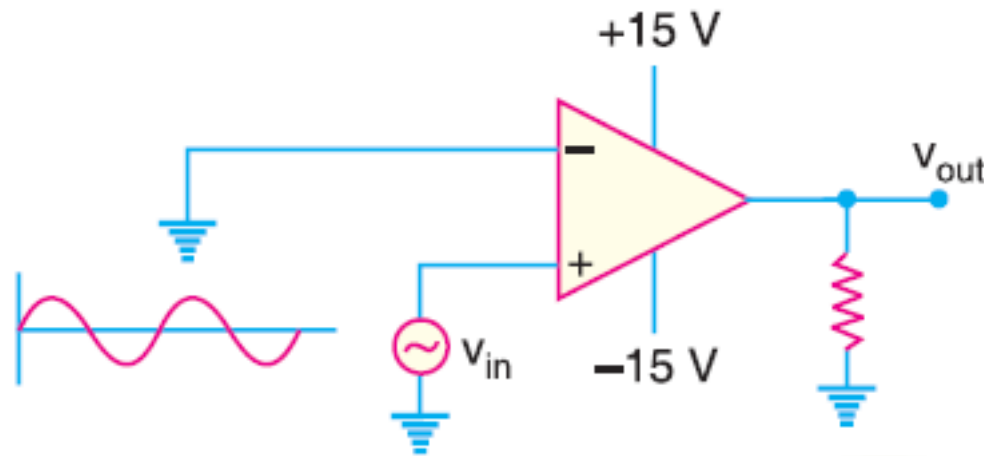





# Comparator (Zero Crossing Detector)

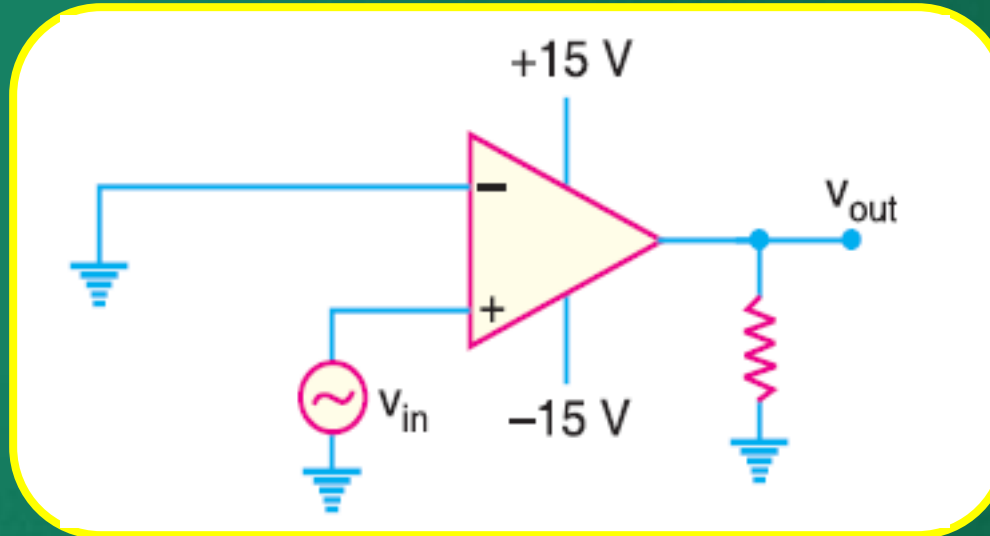

# Comparator (Zero Crossing Detector)

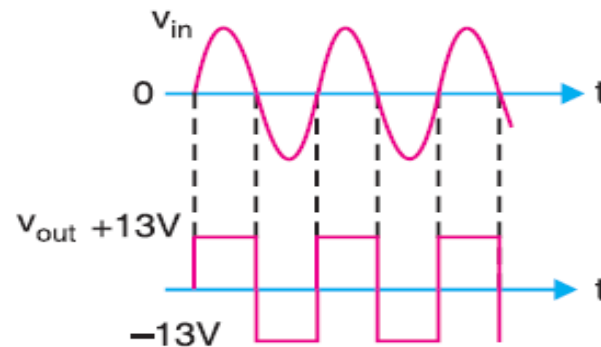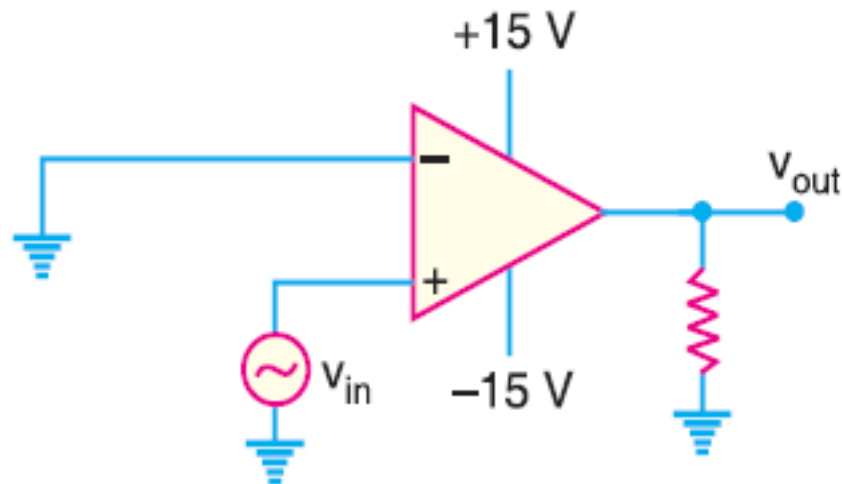


# Comparator (Level Detector)

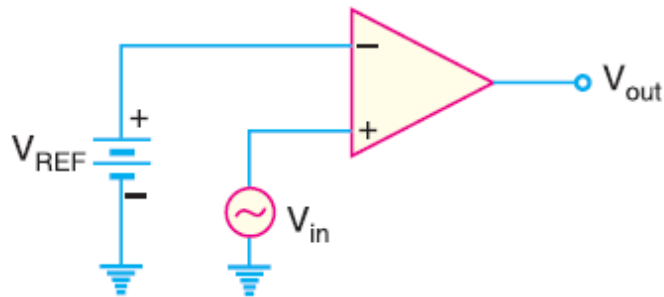


(i) Battery reference

# Comparator (Level Detector)

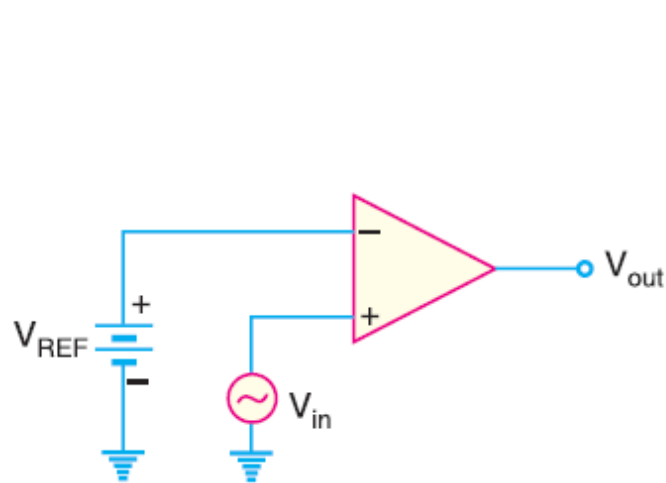


(i) Battery reference

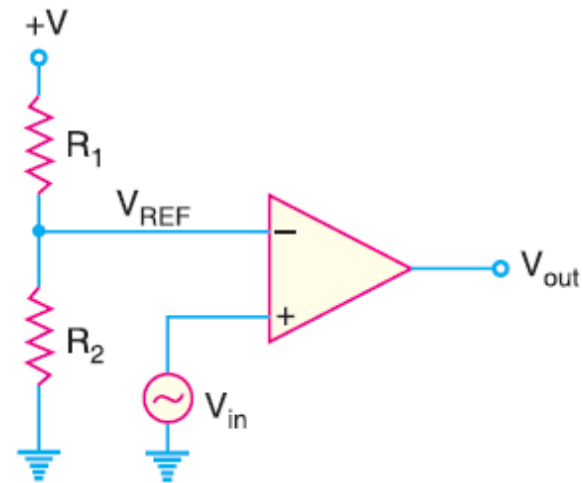

(ii) Voltage-divider reference

# Comparator (Level Detector)

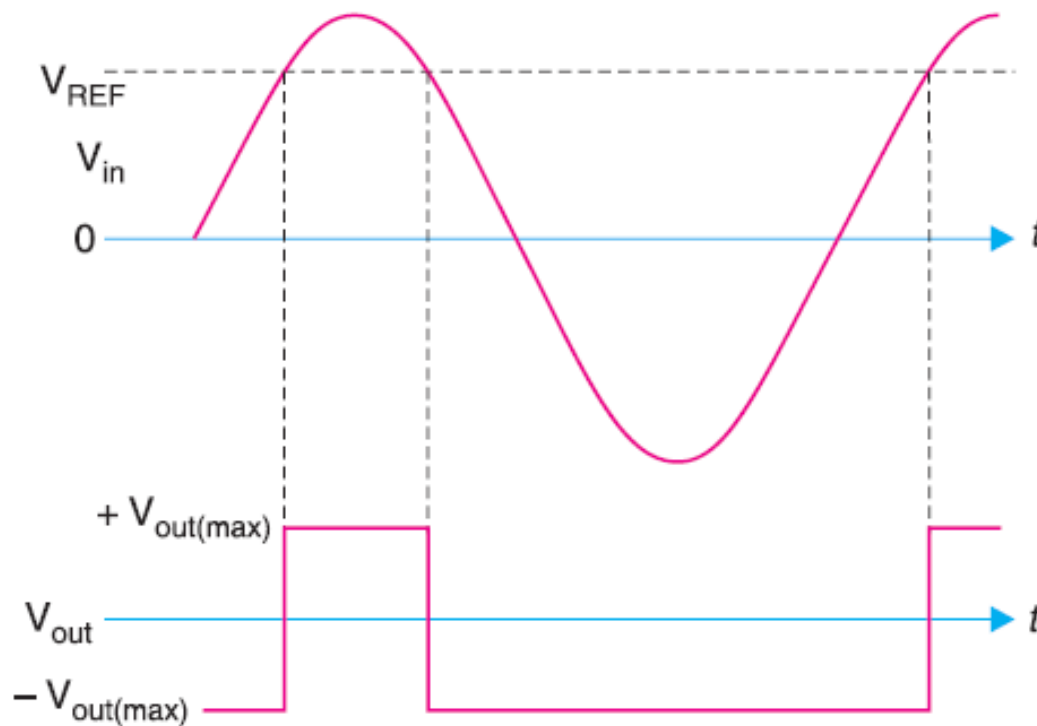

# Feedback



# Feedback

- **2 types of feedback: regenerative (+ve feedback) degenerative (-ve feedback).**

# Feedback

- ❑ **2 types of feedback: regenerative (+ve feedback) degenerative (-ve feedback).**
- ❑ **Unless we want your circuit to oscillate, we use NEGATIVE FEEDBACK.**

# Feedback

- ❑ **2 types of feedback: regenerative (+ve feedback) degenerative (-ve feedback).**
- ❑ **Unless we want your circuit to oscillate, we use NEGATIVE FEEDBACK.**
- ❑ **This idea negative feedback was first used in the late 1920's when building amplifiers with certain gain was difficult.**

# Feedback

- ❑ **2 types of feedback: regenerative (+ve feedback) degenerative (-ve feedback).**
- ❑ **Unless we want your circuit to oscillate, we use NEGATIVE FEEDBACK.**
- ❑ **This idea negative feedback was first used in the late 1920's when building amplifiers with certain gain was difficult.**
- ❑ **Harold Black invented negative feedback.**

# Properties of Feedback

- **The gain of the circuit is made less sensitive to the values of individual components.**



# Properties of Feedback

- ❑ The gain of the circuit is made less sensitive to the values of individual components.
- ❑ Nonlinear distortion can be reduced.



# Properties of Feedback

- ☐ The gain of the circuit is made less sensitive to the values of individual components.
- ☐ Nonlinear distortion can be reduced.
- ☐ The effects of noise can be reduced (but not the noise itself).

# Properties of Feedback

- ☐ The gain of the circuit is made less sensitive to the values of individual components.
- ☐ Nonlinear distortion can be reduced.
- ☐ The effects of noise can be reduced (but not the noise itself).
- ☐ The input and output impedances of the amplifier can be modified.

# Properties of Feedback

- ☐ The gain of the circuit is made less sensitive to the values of individual components.
- ☐ Nonlinear distortion can be reduced.
- ☐ The effects of noise can be reduced (but not the noise itself).
- ☐ The input and output impedances of the amplifier can be modified.
- ☐ The bandwidth of an amplifier can be extended.

# Implementation of Feedback


- **Portion of output is fed back to the inverting terminal of the amplifier.**

# Implementation of Feedback

- ☐ **Portion of output is fed back to the inverting terminal of the amplifier.**
- ☐ **If we use negative feedback, overall gain of the amplifier is always less than the maximum achievable by the amplifier without feedback.**



# Basic Block Diagram

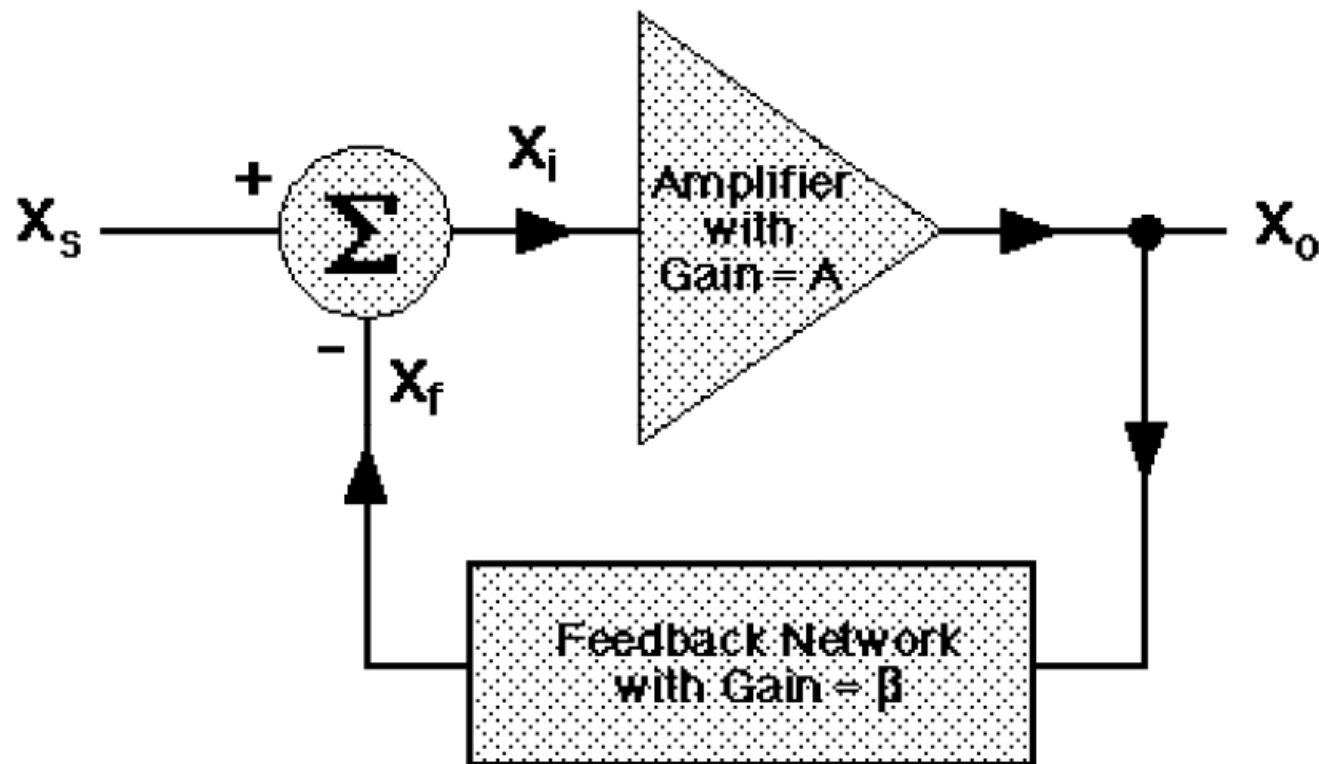



# Closed Loop Gain

$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} \text{ (for very large } A\text{)}$$

# Closed Loop Bandwidth

Open loop gain

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

# Closed Loop Bandwidth

Open loop gain

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

If we use amplifier with negative feedback

# Closed Loop Bandwidth

**Open loop gain**

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

**If we use amplifier with negative feedback**

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)}$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}}$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$



# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

**where**

$$\omega_{Hf} = \omega_H(1 + \beta A_0)$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

where

$$\omega_{Hf} = \omega_H(1 + \beta A_0)$$

$$A_{of} = \frac{A_0}{(1 + \beta A_0)}$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

where


$$\omega_{Hf} = \omega_H(1 + \beta A_0)$$

$$A_{of} = \frac{A_0}{(1 + \beta A_0)}$$


**The cut-off frequency is increased by a factor  $(1 + A_0\beta)$**

# **Types of Amplifiers**

# Ideal Voltage Amplifier

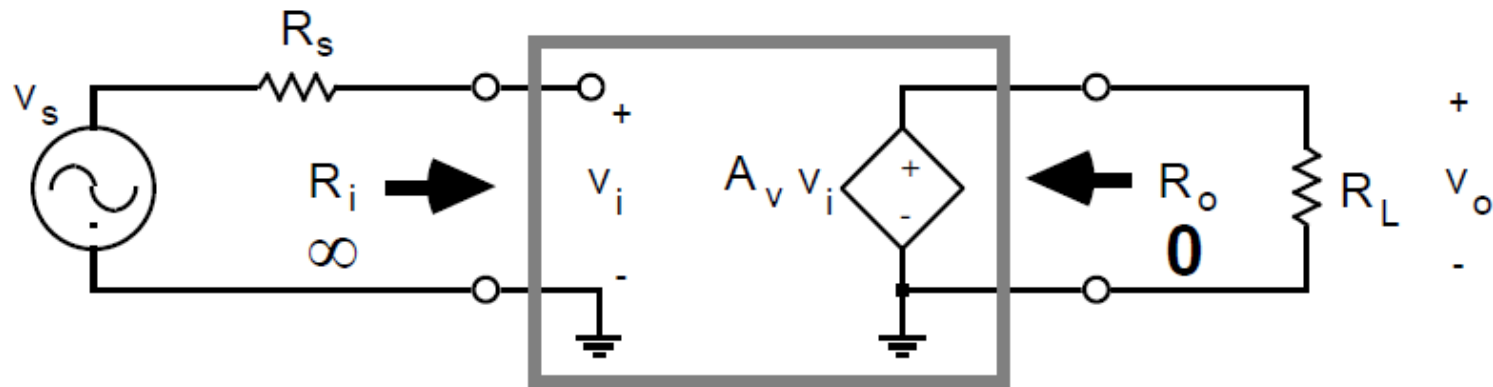


# Ideal Transconductance Amplifier

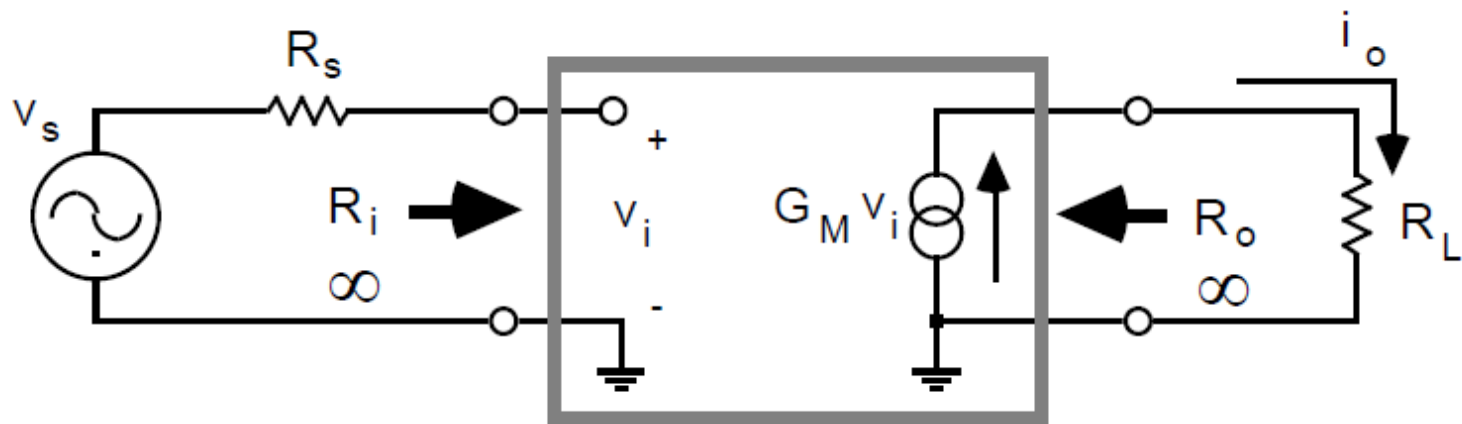




# Ideal Transresistance Amplifier

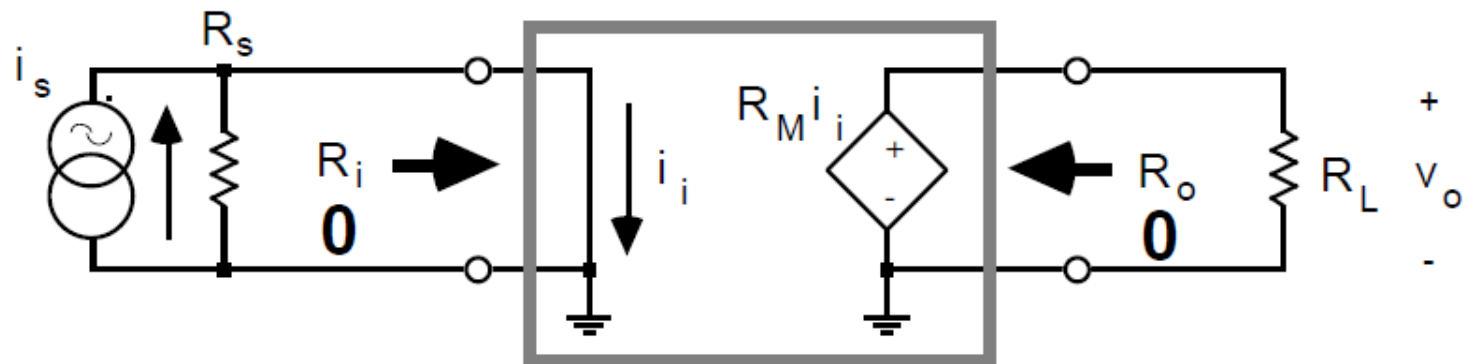

# Ideal Current Amplifier

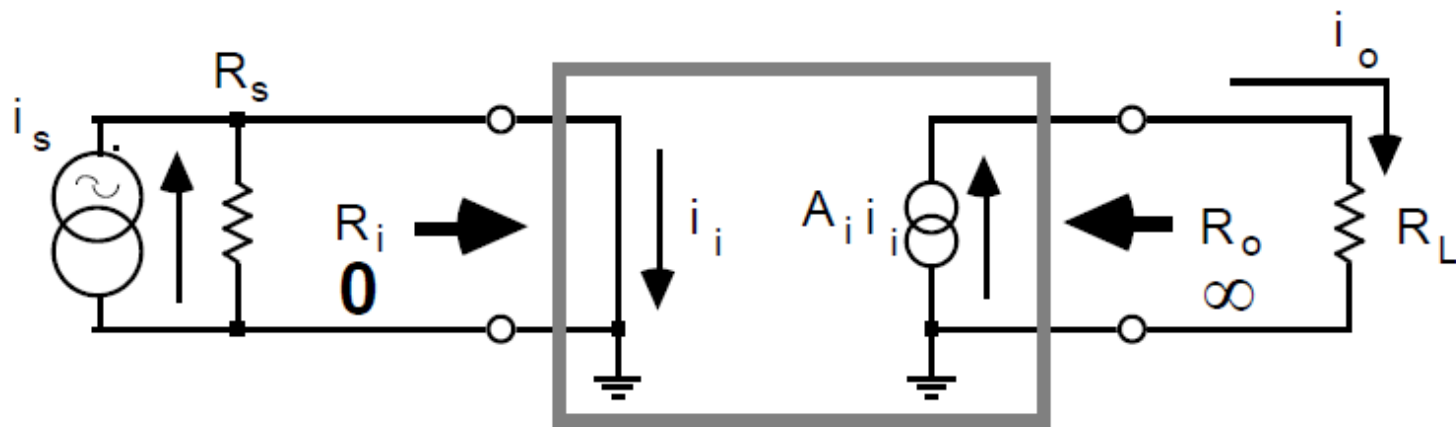


# Ideal Amplifiers


Type of Amplifier	Gain Expression	Ideal Input Impedance	Ideal Output Impedance
Voltage	$A_v = V_o/V_s$ Voltage Gain (dimensionless)	$Z_i = \infty$	$Z_o = 0$
Transconductance	$G_m = I_o/V_s$ Transconductance (Siemens)	$Z_i = \infty$	$Z_o = \infty$
Transresistance	$R_m = V_o/I_s$ Transresistance (Ohms)	$Z_i = 0$	$Z_o = 0$
Current	$A_i = I_o/I_s$ Current Gain (dimensionless)	$Z_i = 0$	$Z_o = \infty$

# Types of Mixers

# Basic Block Diagram

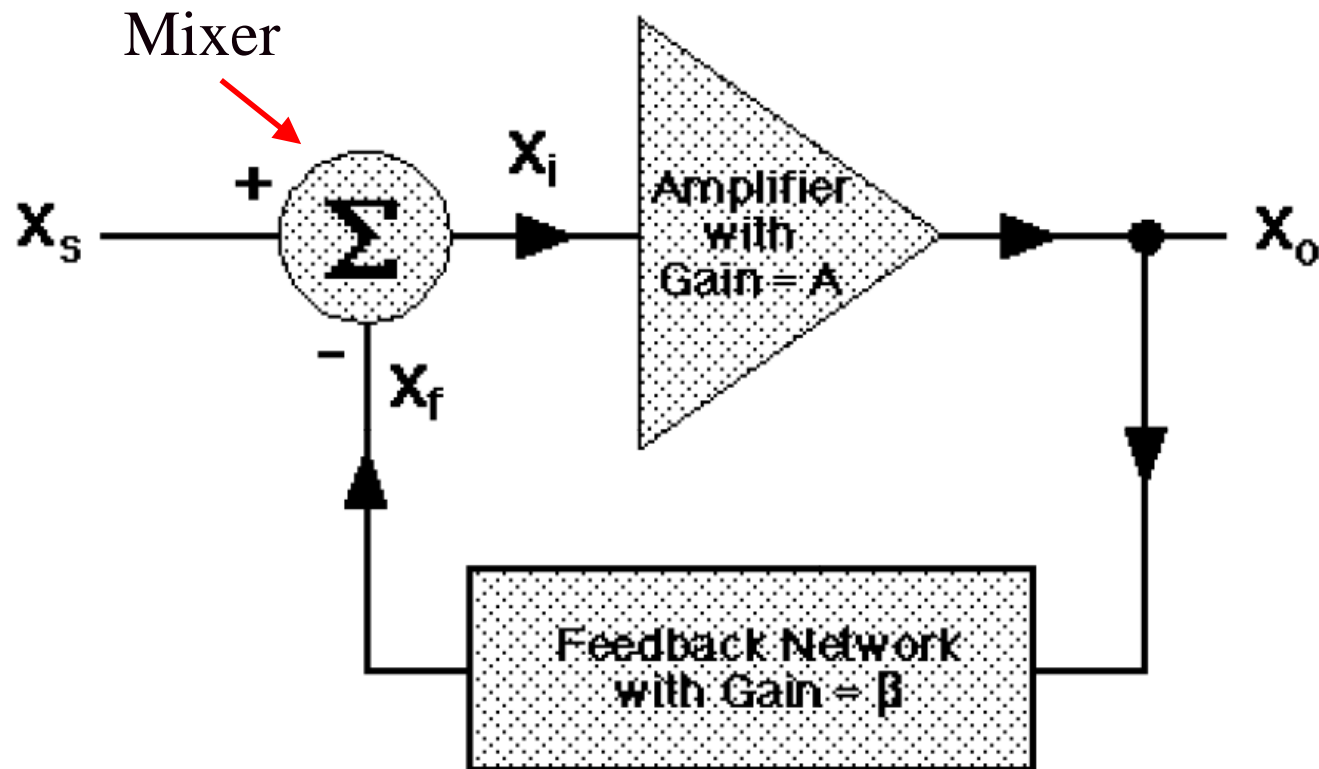


# Series Mixer

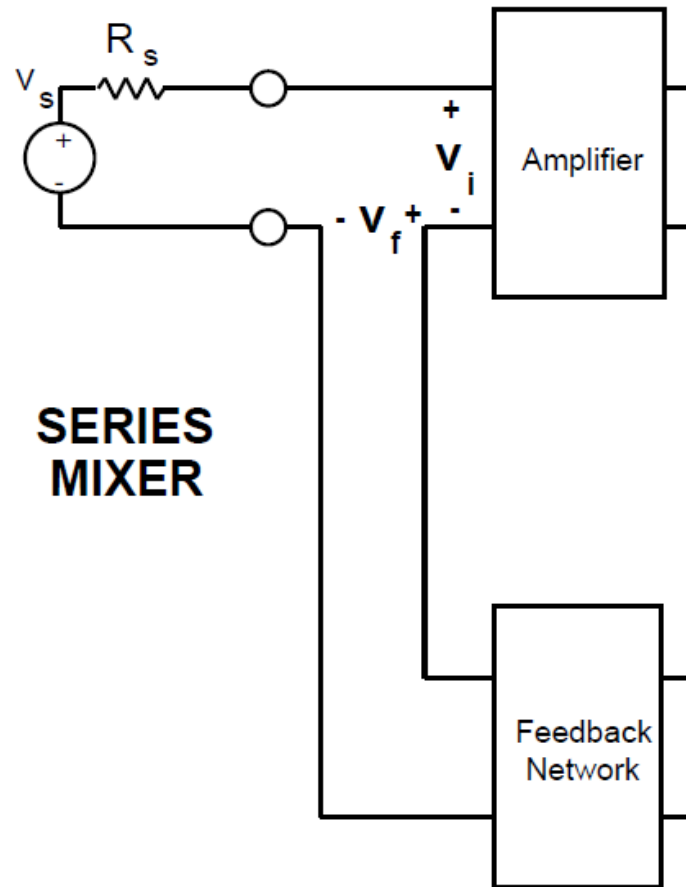




# Shunt Mixer

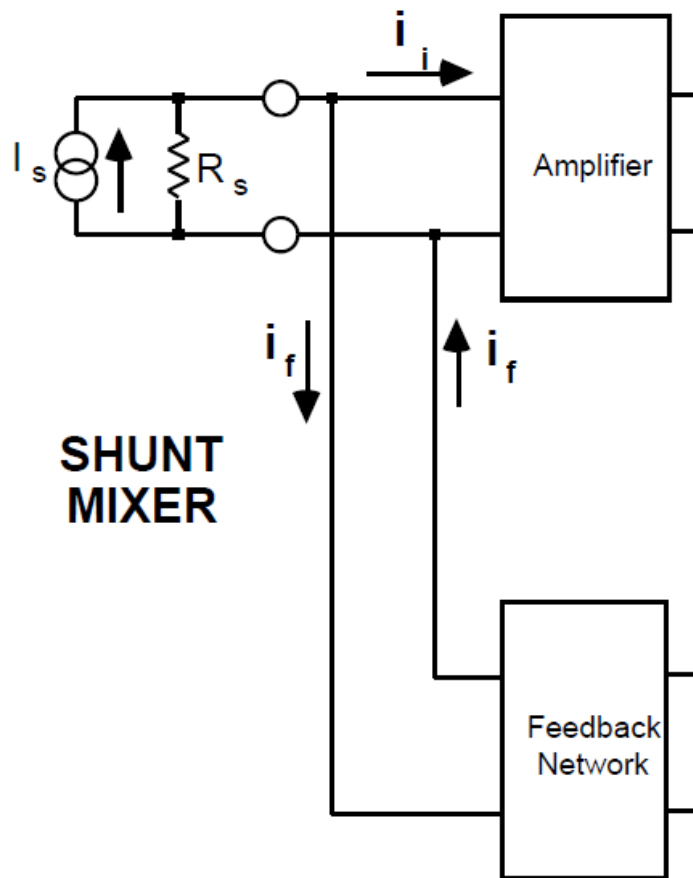


# **Types of Samplers**

# Basic Block Diagram

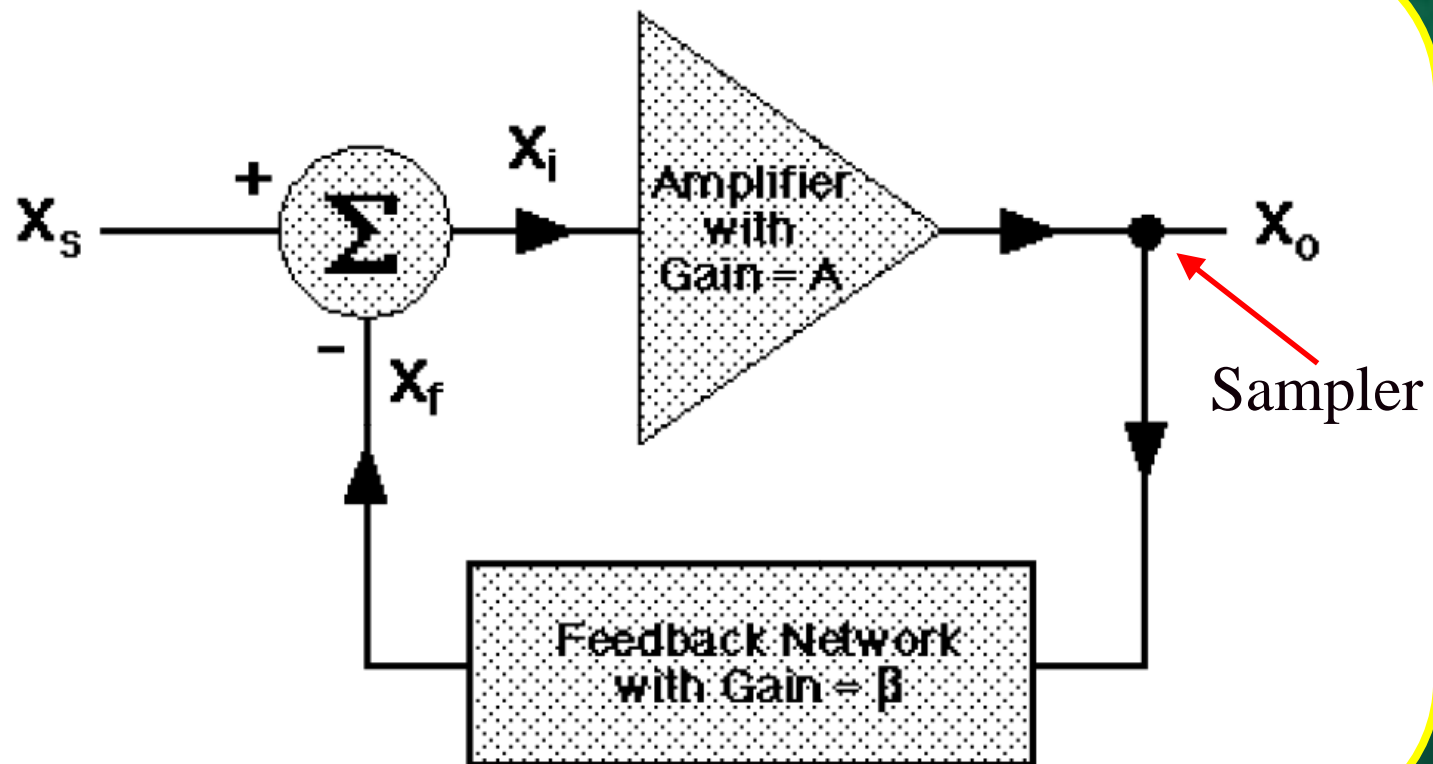

# Shunt Sampler

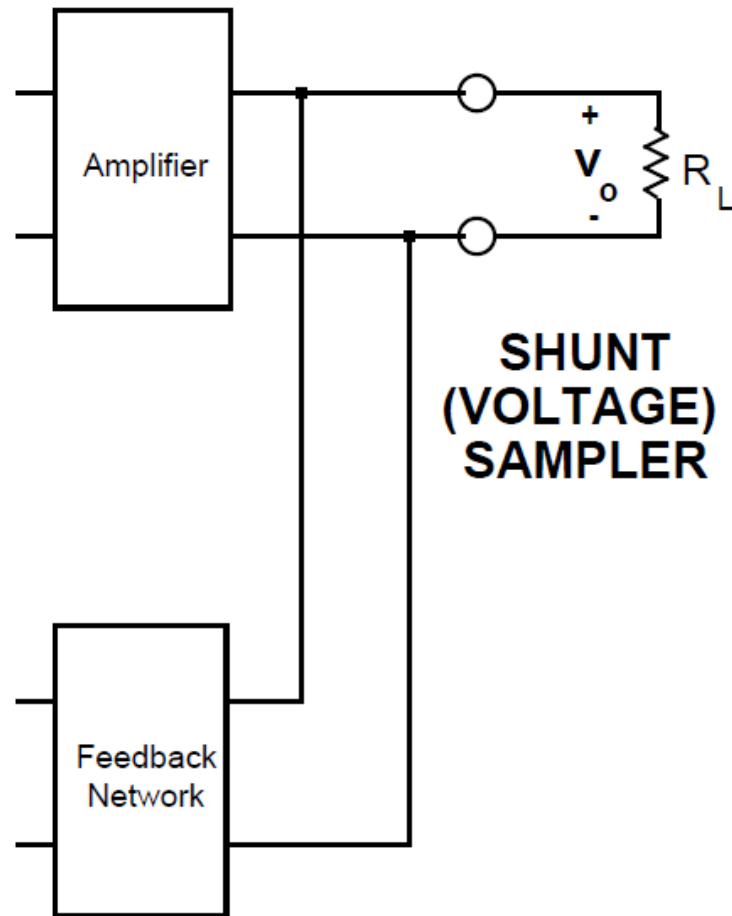

# Series Sampler

