

Tutorial Sheet - 9

IECI03

(Q1) Determine the dc current gain β_{DC} and emitter current

I_E of a transistor whose $I_B = 50 \mu A$ and $I_C = 3.65 mA$

Q2 Sketch an ideal family of collector curves for the circuit shown in Fig. Q2a) for $I_B = 5\mu A$ to $25\mu A$ in $5\mu A$ increments. Assume $\beta_{DC} = 100$ and that V_{CE} does not exceed breakdown.

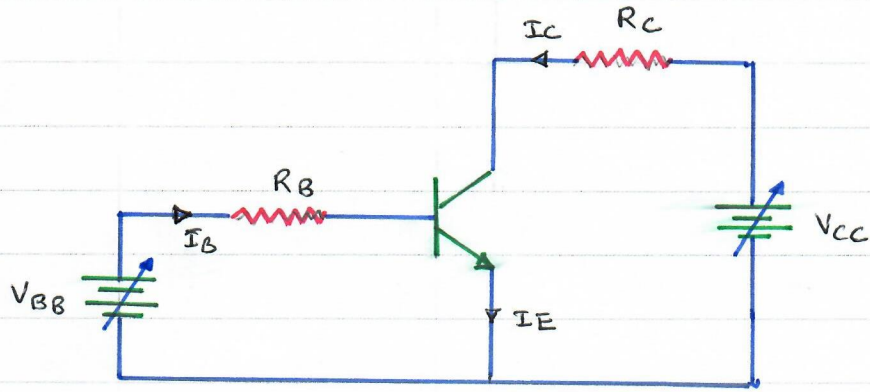


Fig. Q2a)

Q3 Determine the values of I_B , I_C , I_E , V_{BE} , V_{CE} and V_{CB} in the circuit shown in Fig. Q below. The transistor is a silicon transistor with $\beta_{ac} = 150$.

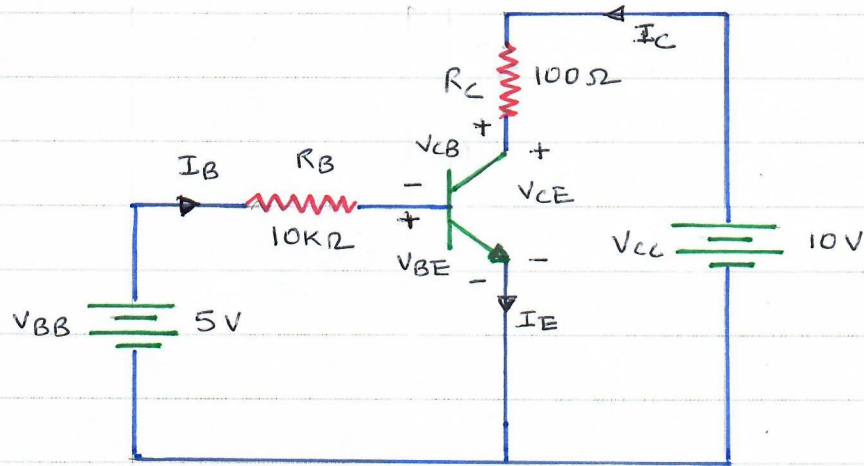


Fig. Q

(Q4) For the transistor circuit shown in Fig. Q4, find

- V_{CB} , Is collector base junction forward or reverse biased
- Power consumed by transistor.

Neglect leakage current.

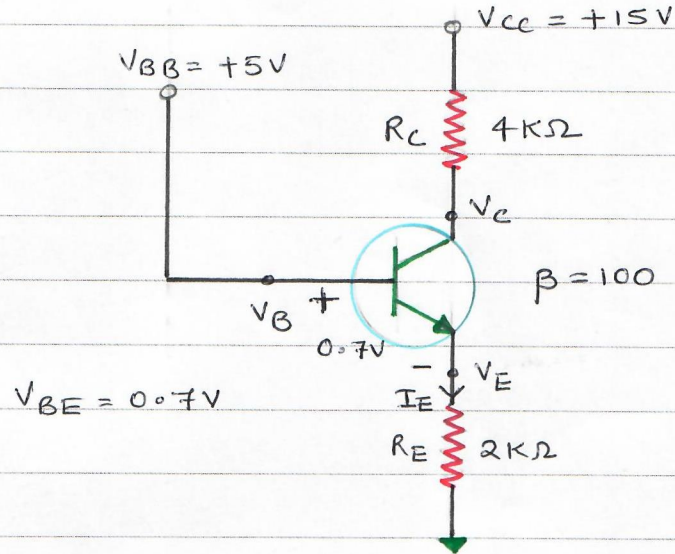


Fig. Q4