


Basic Electronic Circuits

(IEC-103)

Lecture-19

Small Signal Analysis


Basic Common Emitter Amplifier

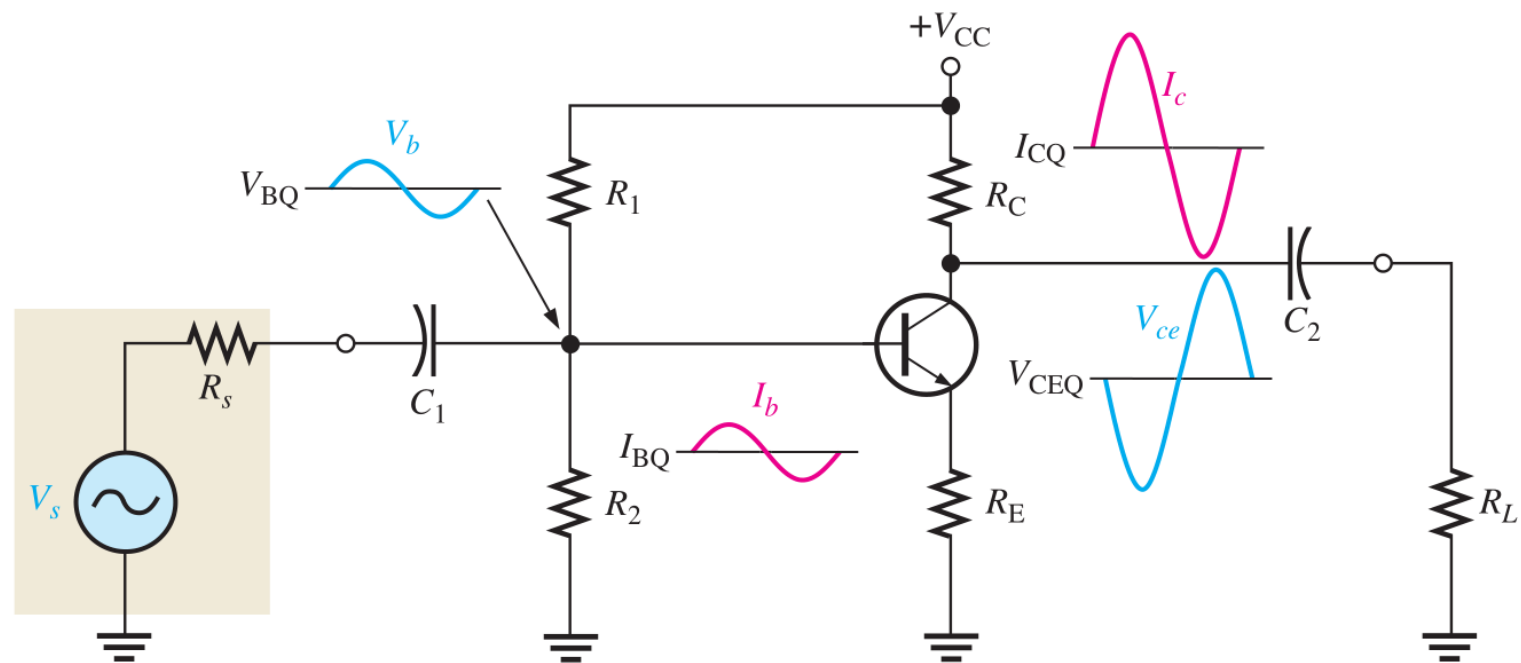

Notation in Transistor Analysis


S. No	Variable	Instantaneous AC	DC	Total
1	Emitter Current	i_e	I_E	i_E
2	Collector Current	i_c	I_C	i_C
3	Base Current	i_b	I_B	i_B
4	Collector-emitter Voltage	v_{ce}	V_{CE}	v_{CE}
5	Emitter-base Voltage	v_{eb}	V_{EB}	v_{EB}

Small Signal Hybrid- π Equiv. Circuit

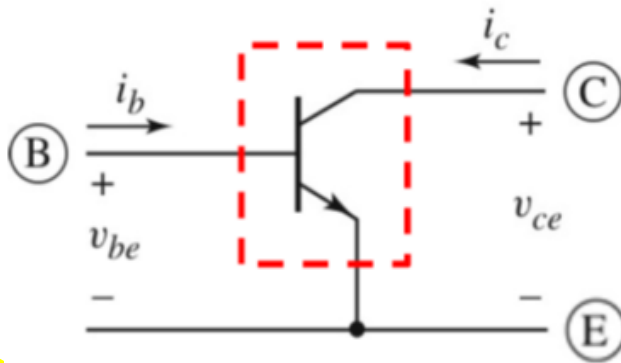

BJT as a 2 port network


Small Signal Hybrid- π Equiv. Circuit

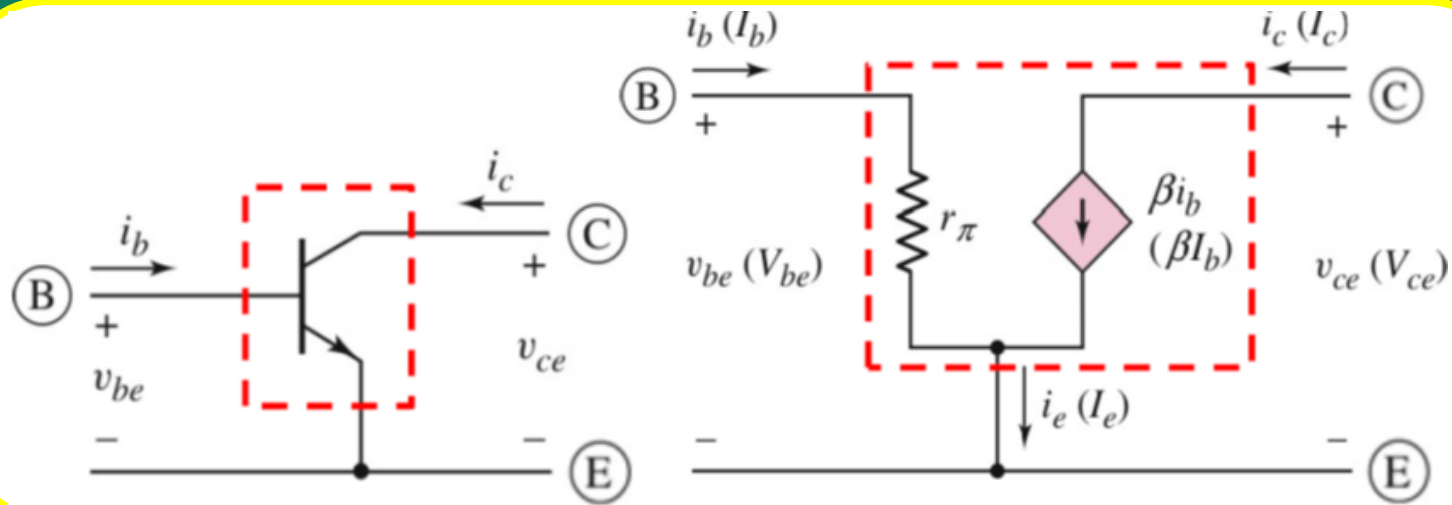

BJT as a 2 port network

Small signal hybrid π equivalent circuit

Small Signal Hybrid- π Equiv. Circuit

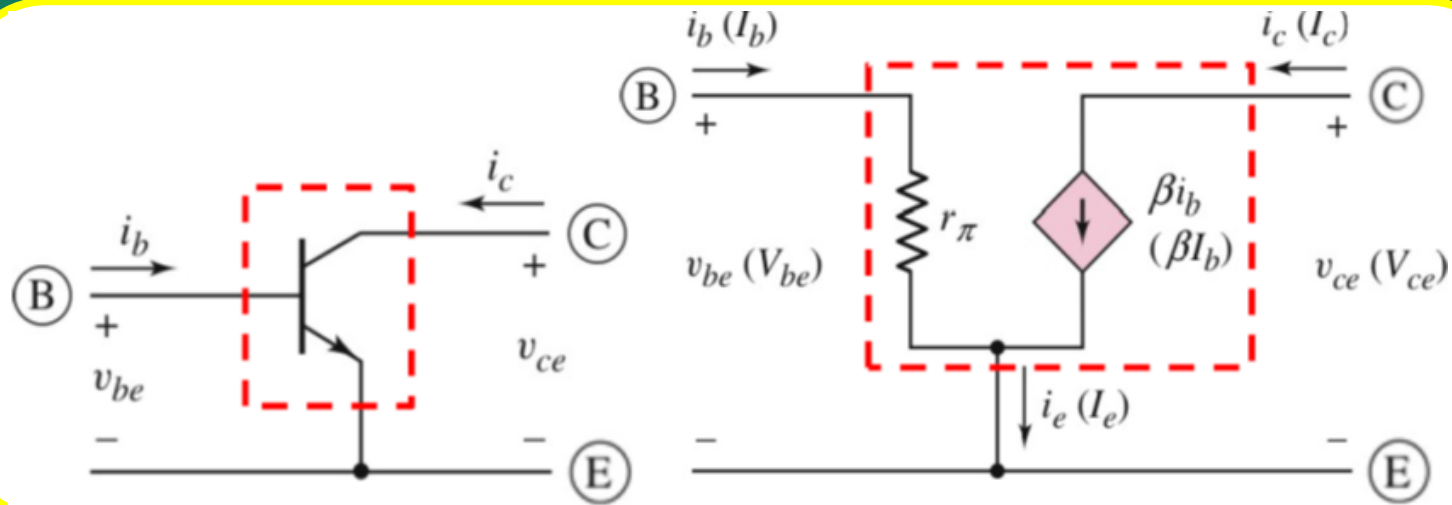


BJT as a 2 port network

Small signal hybrid π equivalent circuit

$\beta = \text{Common emitter current gain} = i_c / i_b$

Small Signal Hybrid- π Equiv. Circuit

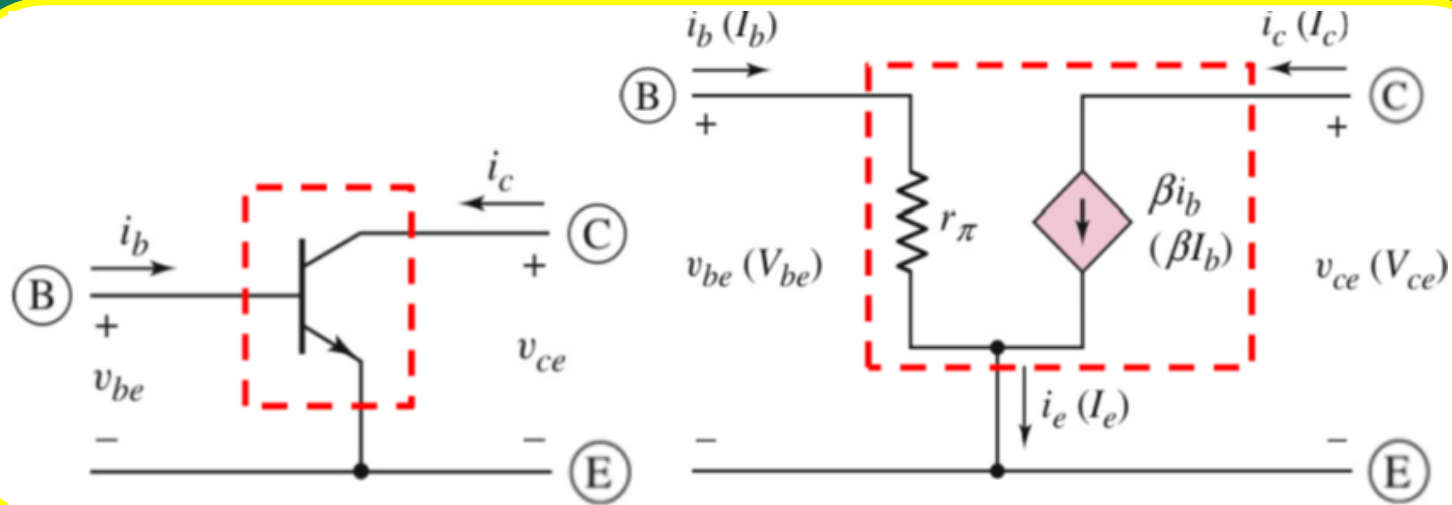

BJT as a 2 port network


Small signal hybrid π equivalent circuit

$\beta = \text{Common emitter current gain} = i_c / i_b$

$$r_\pi = v_{be} / i_b = V_T / I_{BQ}$$


$= \beta V_T / I_{CQ} = \text{small signal resistance, where } V_T \text{ is the thermal voltage}$

Small Signal Hybrid- π Equiv. Circuit

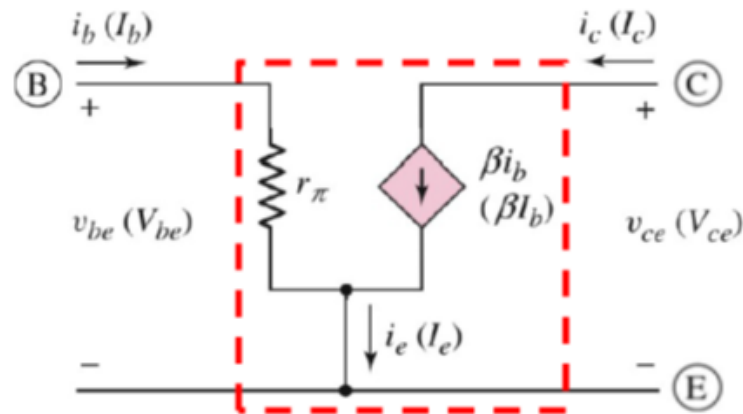

With current gain parameter


Small Signal Hybrid- π Equiv. Circuit

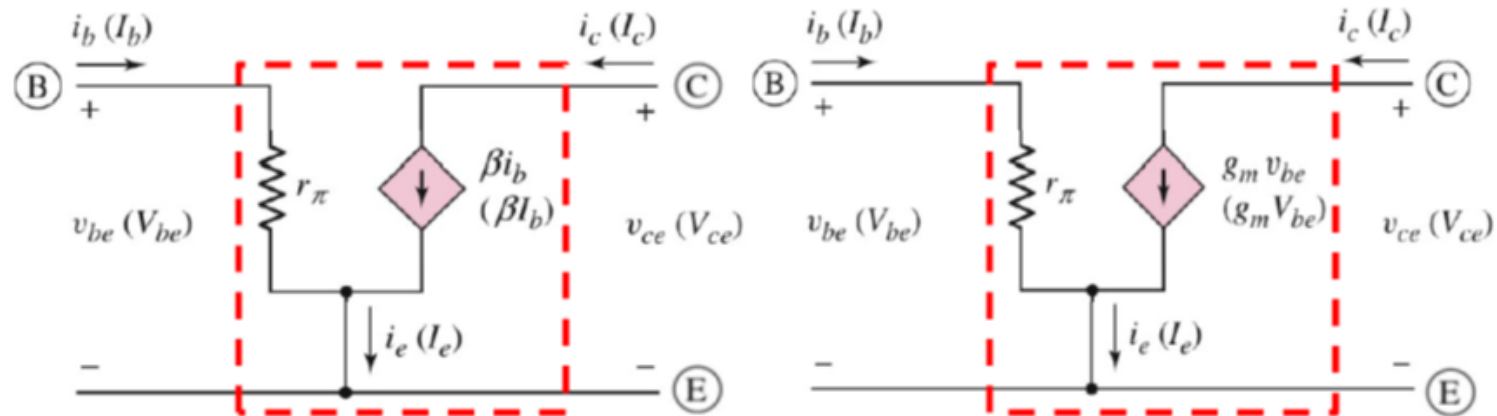

With current gain parameter

With transconductance parameter

Small Signal Hybrid- π Equiv. Circuit

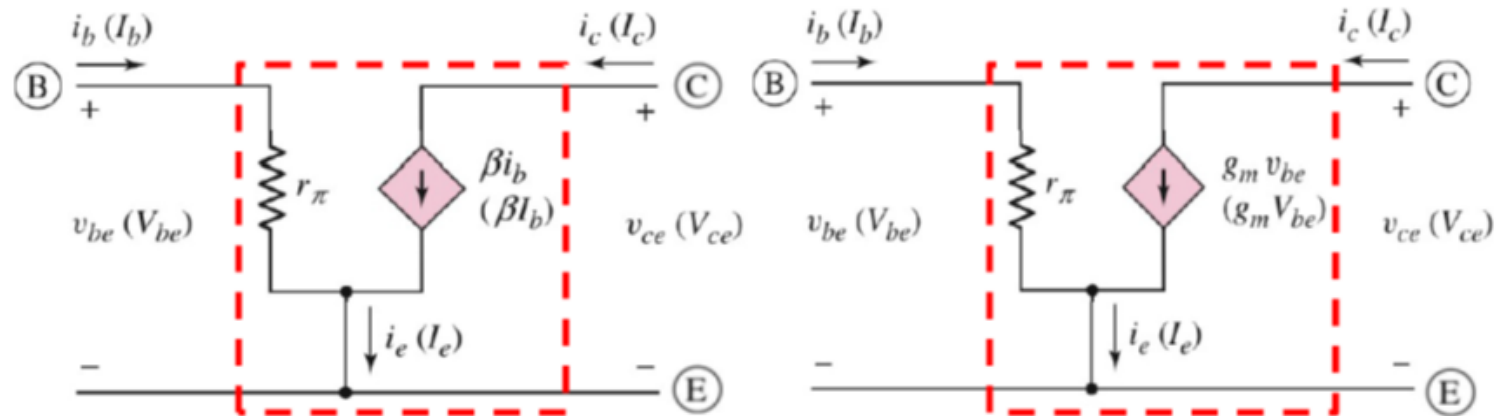


With current gain parameter

With transconductance parameter

$$g_m = \beta / r_\pi = I_{CQ} / V_T = \text{transconductance}$$

Small Signal Hybrid- π Equiv. Circuit

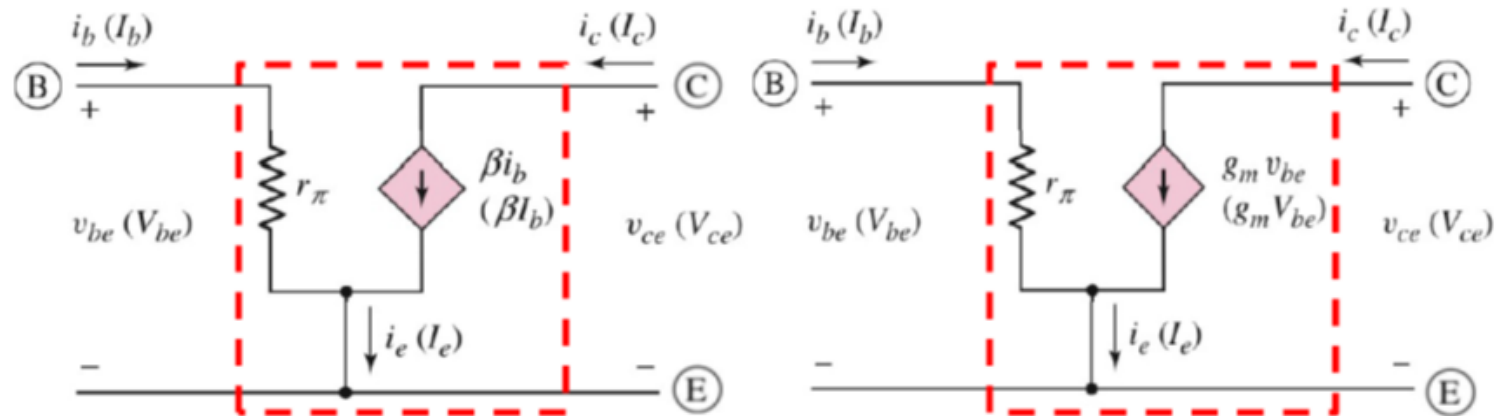


With current gain parameter

With transconductance parameter


$$g_m = \beta / r_\pi = I_{CQ} / V_T = \text{transconductance}$$

i_c is assumed to be independent of v_{ce} which is not the case in practice and the assumption will be released later to include the "Early effect"


Another Representation

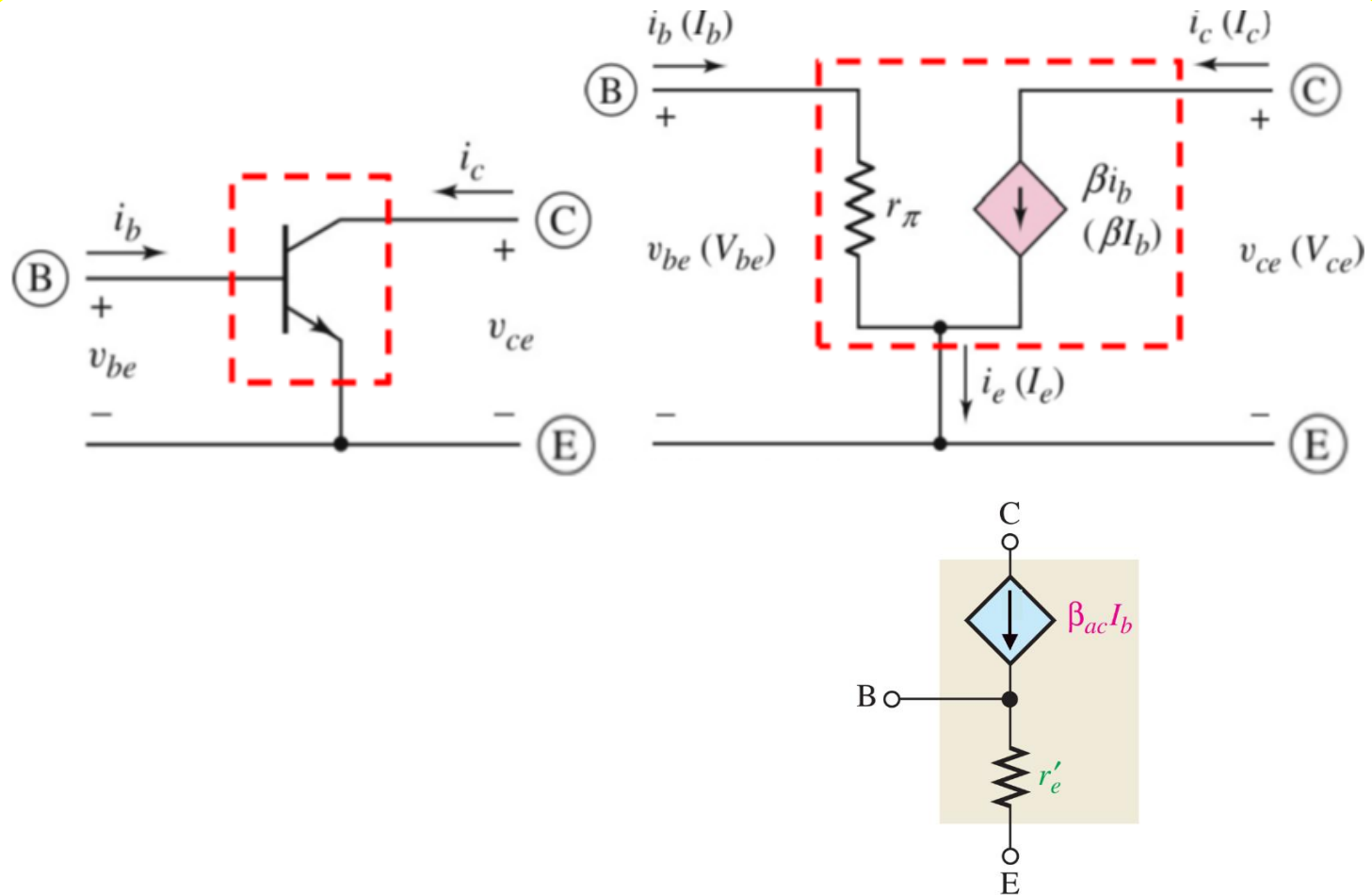

Another Representation

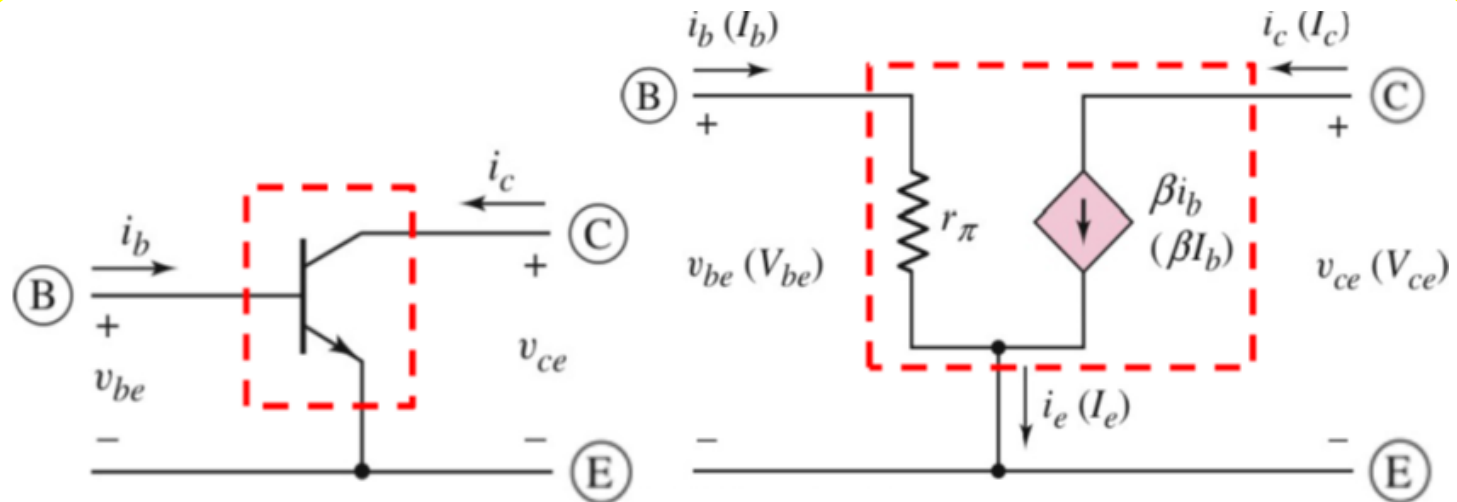

$$r_e = \frac{25\text{mV}}{I_E}$$

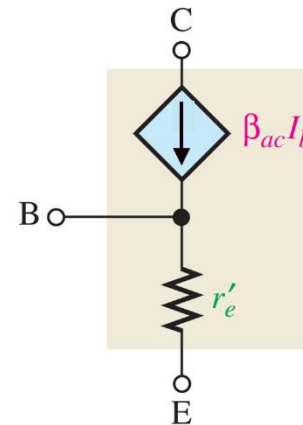

DC and AC Load Lines

DC and AC Load Lines

- Load line is drawn on the characteristic curve (current vs voltage) in a nonlinear device like diode or transistor.

DC and AC Load Lines

- ❑ Load line is drawn on the characteristic curve (current vs voltage) in a nonlinear device like diode or transistor.
- ❑ It represents the constraint put on the voltage and current in the nonlinear device by the external circuit.

DC and AC Load Lines

- ❑ Load line is drawn on the characteristic curve (current vs voltage) in a nonlinear device like diode or transistor.
- ❑ It represents the constraint put on the voltage and current in the nonlinear device by the external circuit.
- ❑ DC load line is the load line of the DC equivalent circuit.


DC and AC Load Lines

- ☐ **Load line is drawn on the characteristic curve (current vs voltage) in a nonlinear device like diode or transistor.**
- ☐ **It represents the constraint put on the voltage and current in the nonlinear device by the external circuit.**
- ☐ **DC load line is the load line of the DC equivalent circuit.**
- ☐ **The load line equation is used to determine the correct DC operating point, often called the Q point.**


DC and AC Load Lines

- ❑ Load line is drawn on the characteristic curve (current vs voltage) in a nonlinear device like diode or transistor.
- ❑ It represents the constraint put on the voltage and current in the nonlinear device by the external circuit.
- ❑ DC load line is the load line of the DC equivalent circuit.
- ❑ The load line equation is used to determine the correct DC operating point, often called the Q point.
- ❑ AC load line is a straight line with a slope equal to the AC impedance passing through the Q point.

DC And AC Load Line

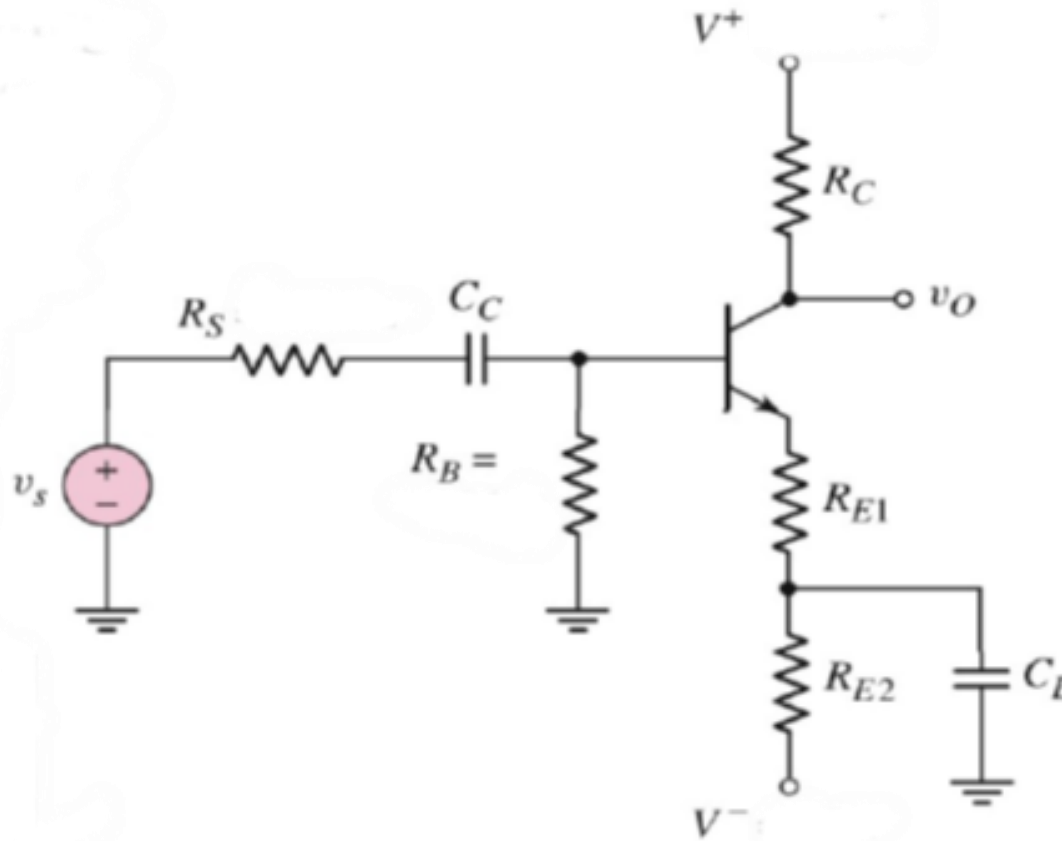

DC Equivalent Circuit

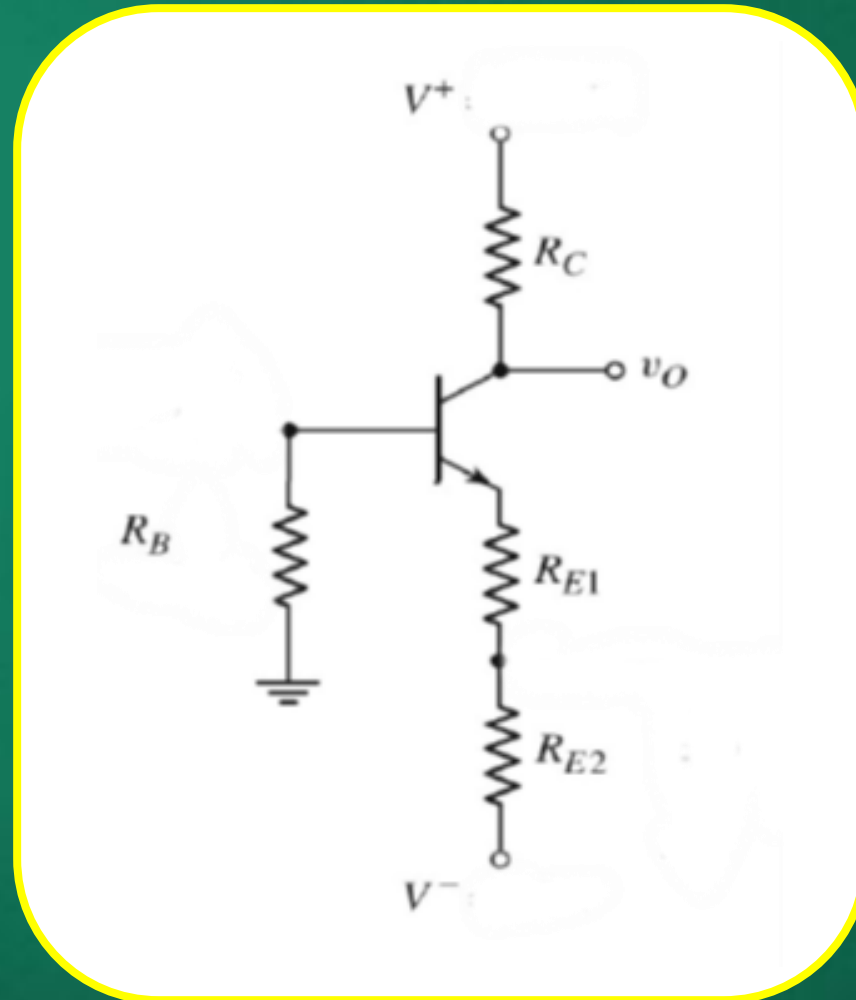

DC Load Line

DC Load Line

DC load line is found by writing KVL equations for DC equivalent circuit.

DC Load Line

DC load line is found by writing KVL equations for DC equivalent circuit.

$$V^+ - I_C R_C - V_{CE} - I_E (R_{E1} + R_{E2}) = V^-$$

DC Load Line

DC load line is found by writing KVL equations for DC equivalent circuit.

$$V^+ - I_C R_C - V_{CE} - I_E (R_{E1} + R_{E2}) = V^-$$

If $\beta \gg 1$, $I_E \approx I_C$

DC Load Line

DC load line is found by writing KVL equations for DC equivalent circuit.

$$V^+ - I_C R_C - V_{CE} - I_E (R_{E1} + R_{E2}) = V^-$$

If $\beta \gg 1$, $I_E \approx I_C$

$$V^+ - I_C R_C - V_{CE} - I_C (R_{E1} + R_{E2}) = V^-$$

DC Load Line

DC load line is found by writing KVL equations for DC equivalent circuit.

$$V^+ - I_C R_C - V_{CE} - I_E (R_{E1} + R_{E2}) = V^-$$

If $\beta \gg 1$, $I_E \approx I_C$

$$V^+ - I_C R_C - V_{CE} - I_C (R_{E1} + R_{E2}) = V^-$$

$$V_{CE}(\text{off}) = V^+ - V^-$$

DC Load Line

DC load line is found by writing KVL equations for DC equivalent circuit.

$$V^+ - I_C R_C - V_{CE} - I_E (R_{E1} + R_{E2}) = V^-$$

If $\beta \gg 1$, $I_E \approx I_C$

$$V^+ - I_C R_C - V_{CE} - I_C (R_{E1} + R_{E2}) = V^-$$

$$V_{CE}(\text{off}) = V^+ - V^-$$


$$I_C(\text{sat}) = \frac{V^+ - V^-}{R_C + R_{E1} + R_{E2}}$$

DC and AC Load Lines

Slope of the DC load line

$$-\frac{1}{R_C + R_{E1} + R_{E2}}$$

AC Equivalent Circuit

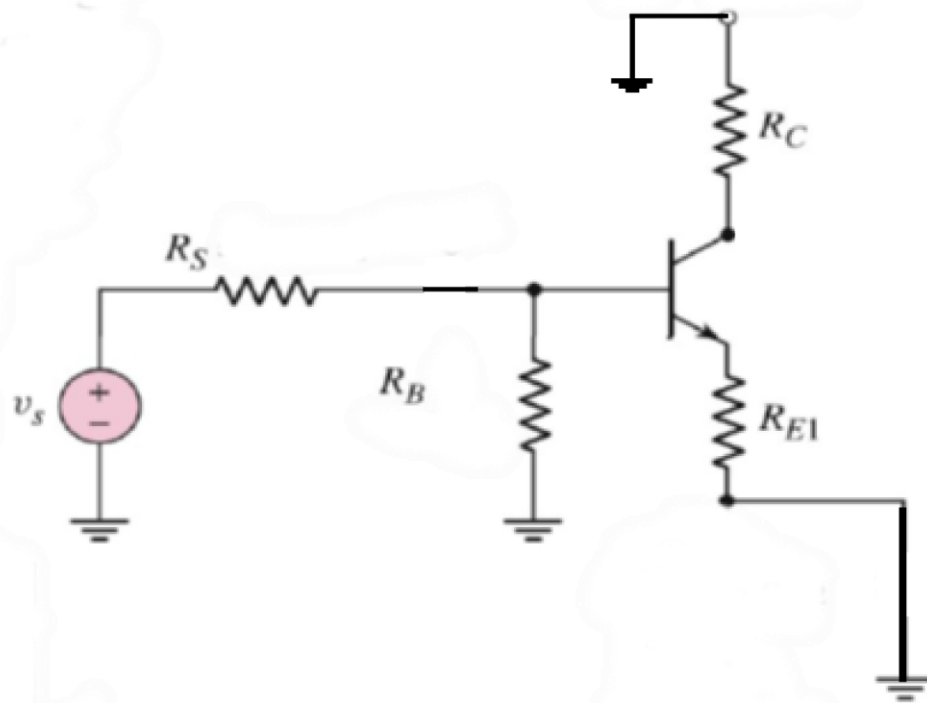

AC Load Line

AC Load Line

AC load line is found by writing KVL equations for AC equivalent circuit.

AC Load Line

AC load line is found by writing KVL equations for AC equivalent circuit.

$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$

AC Load Line

AC load line is found by writing KVL equations for AC equivalent circuit.

$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$

If $\beta \gg 1$, $i_e \approx i_c$

AC Load Line

AC load line is found by writing KVL equations for AC equivalent circuit.

$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$

If $\beta \gg 1$, $i_e \approx i_c$

$$v_{ce} = -i_c (R_C + R_{E1})$$

AC Load Line

AC load line is found by writing KVL equations for AC equivalent circuit.

$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$

If $\beta \gg 1$, $i_e \approx i_c$

$$v_{ce} = -i_c (R_C + R_{E1})$$

Slope of the DC load line

AC Load Line

AC load line is found by writing KVL equations for AC equivalent circuit.

$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$


If $\beta \gg 1$, $i_e \approx i_c$

$$v_{ce} = -i_c (R_C + R_{E1})$$


Slope of the DC load line

$$-\frac{1}{R_C + R_{E1}}$$

Max. Output Symmetrical Swing

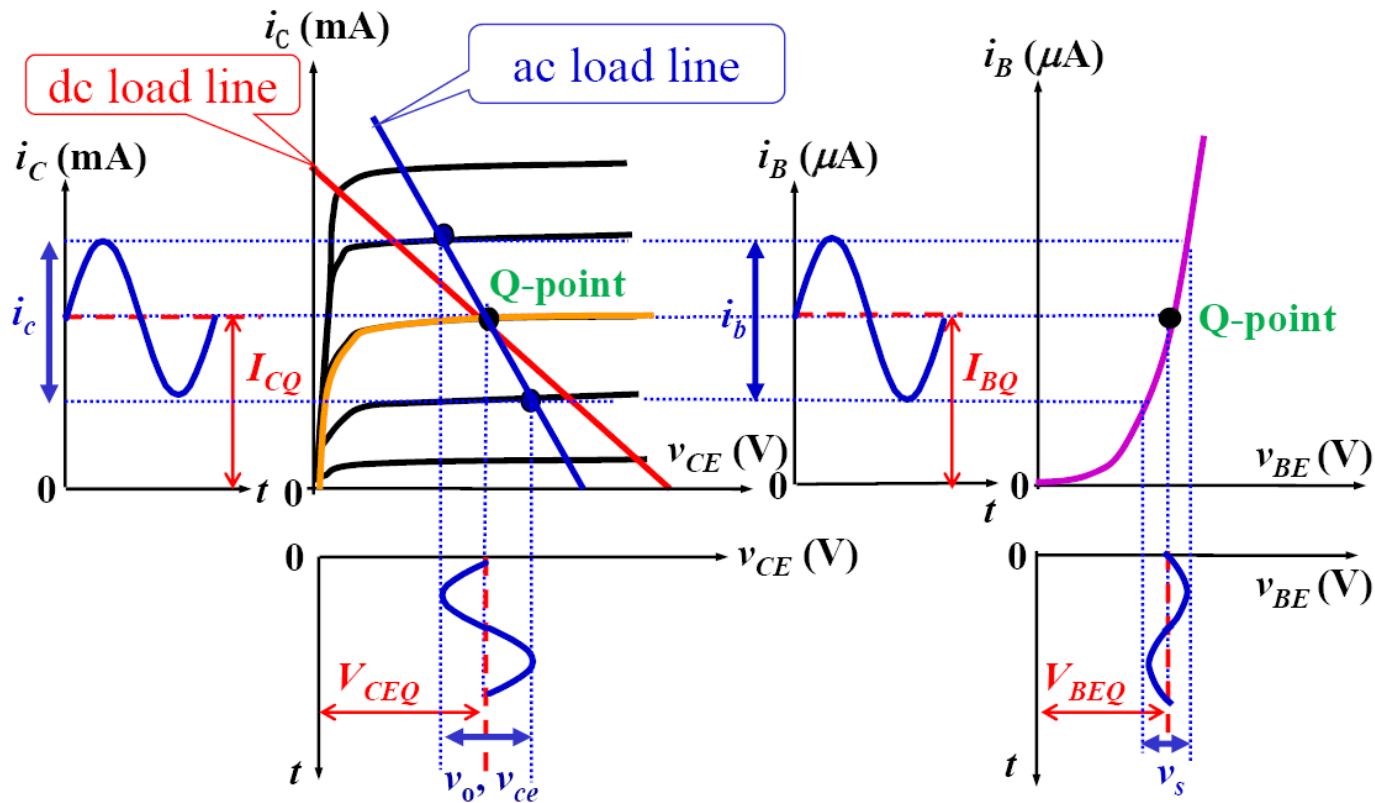

Saturation

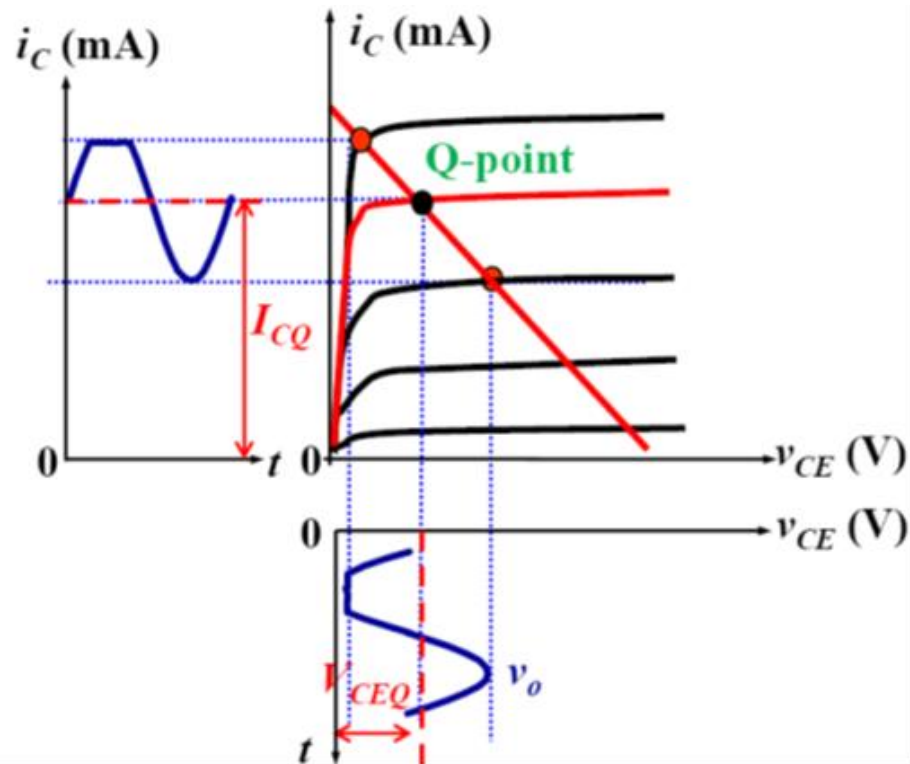

Saturation

- ❑ If the Q-point is not set properly, the transistor may enter into saturation or cutoff resulting in nonlinear distortion.


Saturation

- ❑ If the Q-point is not set properly, the transistor may enter into saturation or cutoff resulting in nonlinear distortion.
- ❑ If the Q-point is set too high, the BJT gets into saturation and a reduction of I_{BQ} is required.


Saturation

- ❑ If the Q-point is not set properly, the transistor may enter into saturation or cutoff resulting in nonlinear distortion.
- ❑ If the Q-point is set too high, the BJT gets into saturation and a reduction of I_{BQ} is required.
- ❑ Even with a proper Q-point setting, if the signal amplitude is too large, distortion will also result, and a reduction of signal amplitude is required.

Cutoff

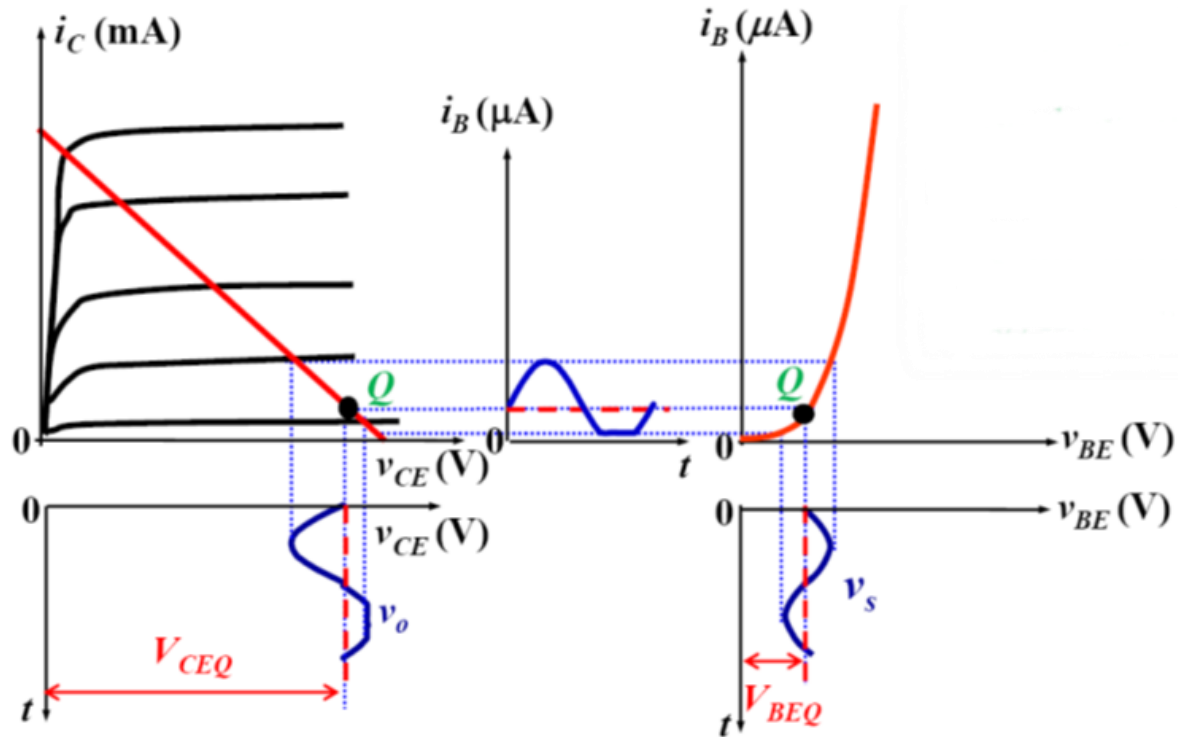

Cutoff

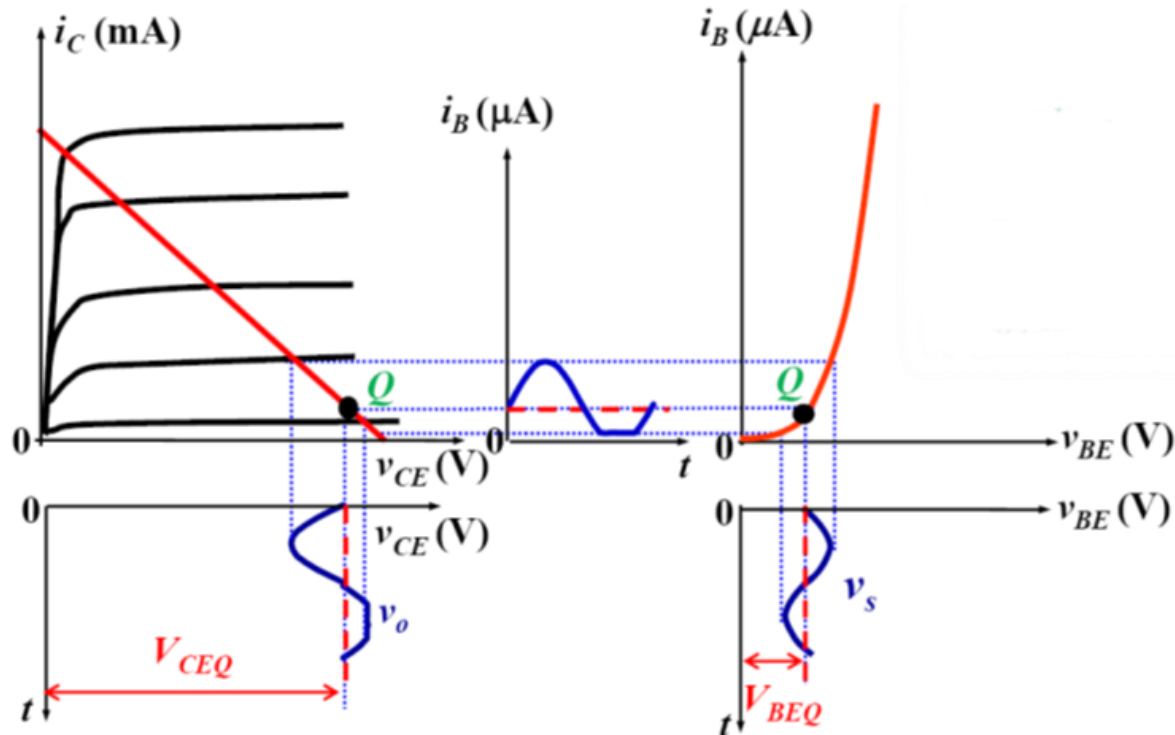

❑ If the Q-point is too low, the BJT gets into cutoff, and an increase in I_{BQ} is required.

Multistage Amplifiers

Multistage Amplifiers

- ❑ Many applications cannot be handled with single-transistor amplifiers in order to meet the specification of a given amplification factor, input resistance and output resistance

Multistage Amplifiers


- ❑ Many applications cannot be handled with single-transistor amplifiers in order to meet the specification of a given amplification factor, input resistance and output resistance
- ❑ **Solution** – transistor amplifier circuits can be connected in series or cascaded amplifiers

Multistage Amplifiers

- ❑ Many applications cannot be handled with single-transistor amplifiers in order to meet the specification of a given amplification factor, input resistance and output resistance
- ❑ **Solution** – transistor amplifier circuits can be connected in series or cascaded amplifiers
- ❑ This is done either to increase the overall small-signal voltage gain or provide an overall voltage gain greater than 1 with a very low output resistance


Multistage Amp Configuration

Cascade/RC coupling

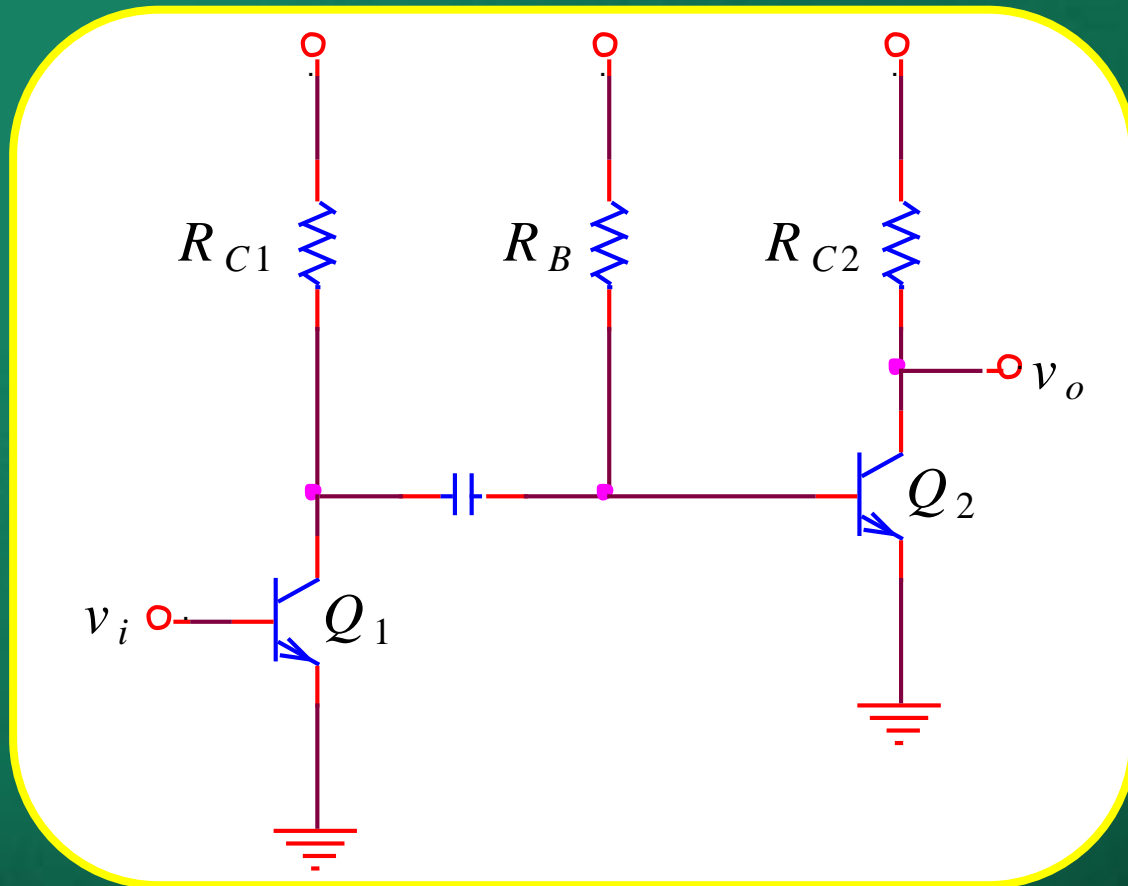


Multistage Amp Configuration

Cascade/RC coupling

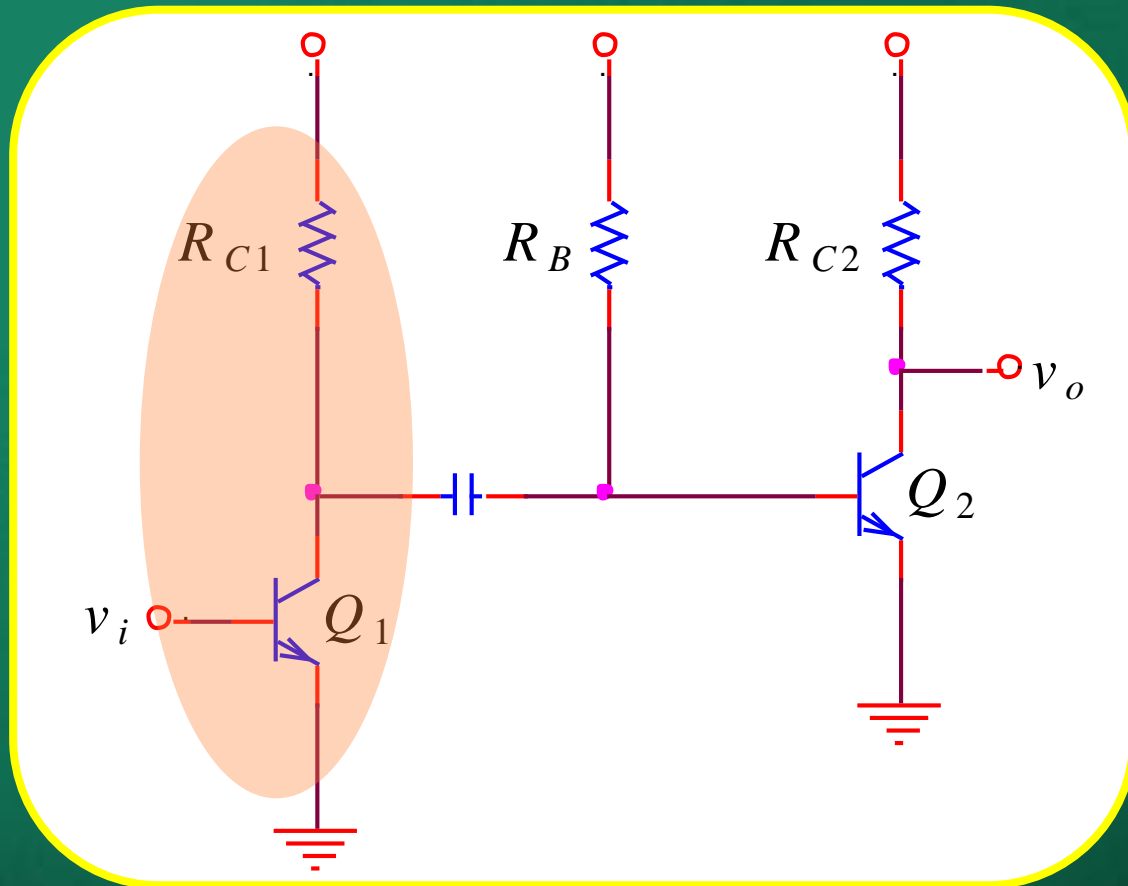


Multistage Amp Configuration

Cascade/RC coupling

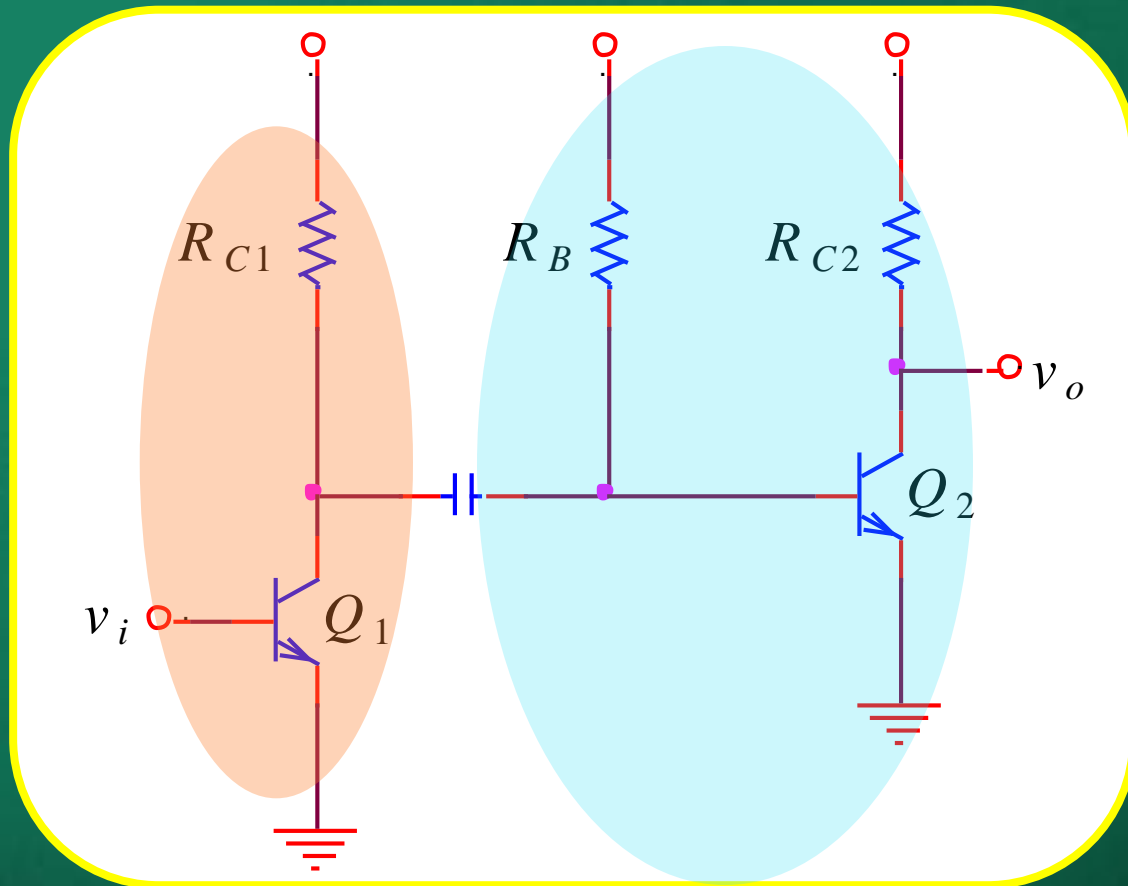


Multistage Amp Configuration

Cascode

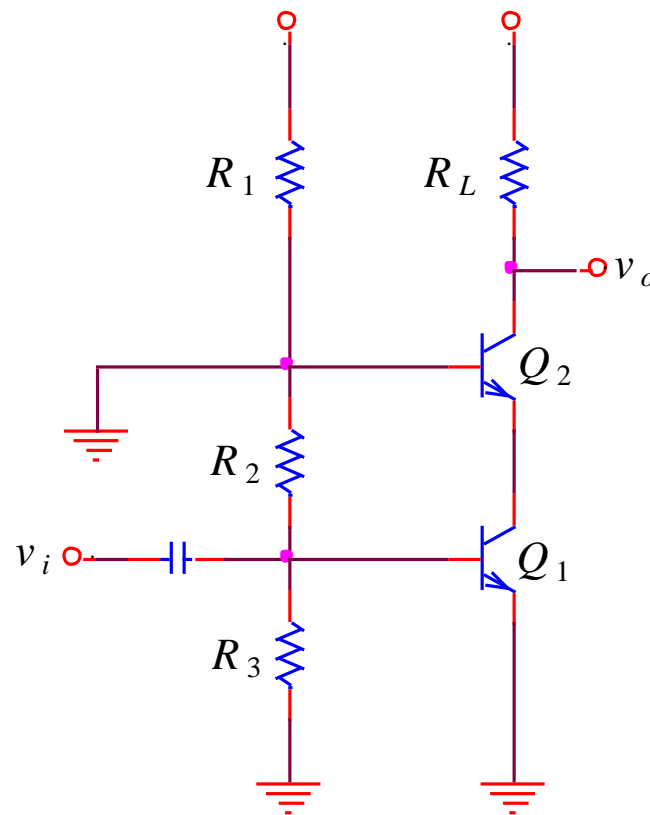


Multistage Amp Configuration

Cascode

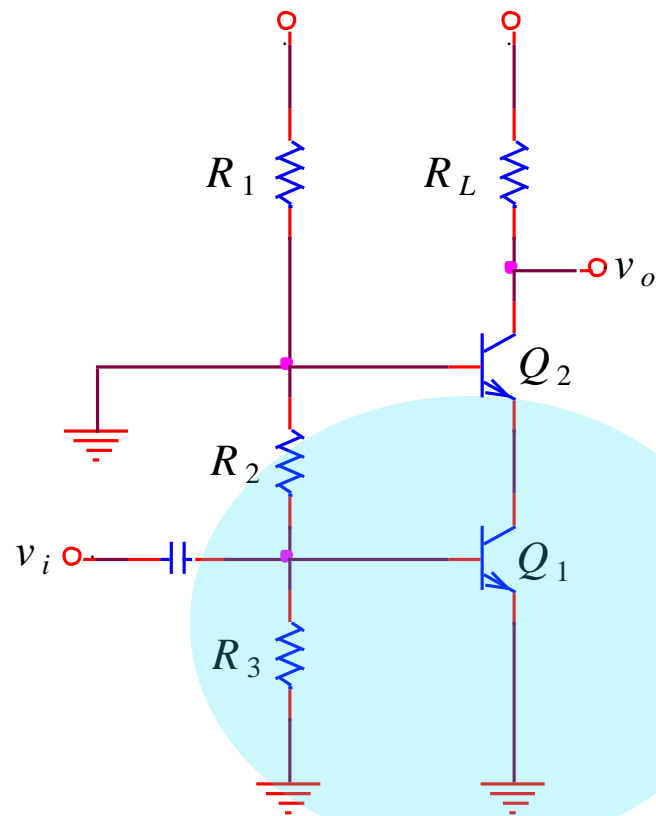


Multistage Amp Configuration

Cascode

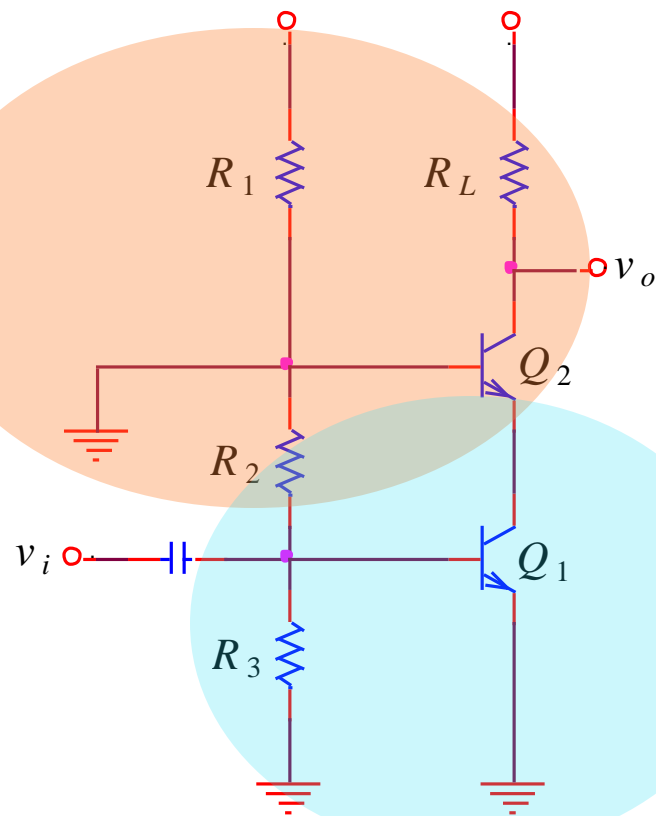


Multistage Amp Configuration

Darlington/Direct coupling

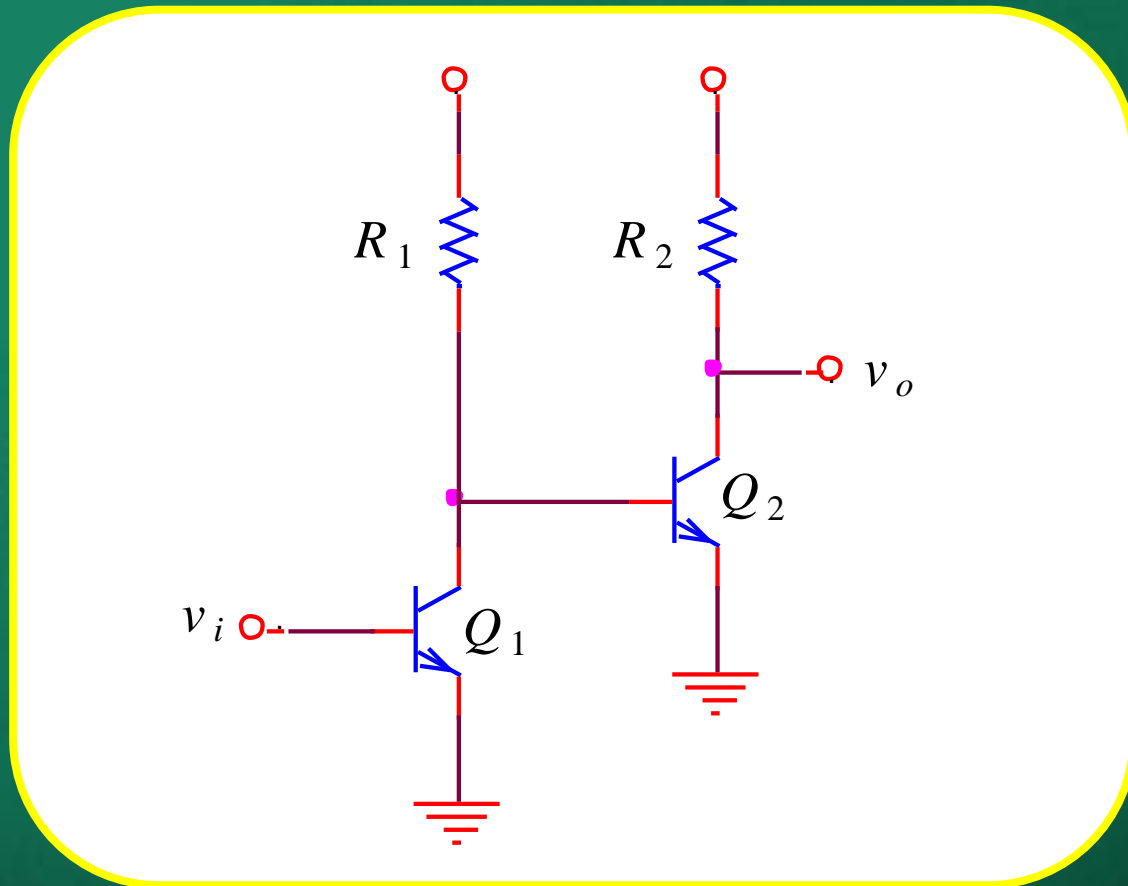


Multistage Amp Configuration

Darlington/Direct coupling

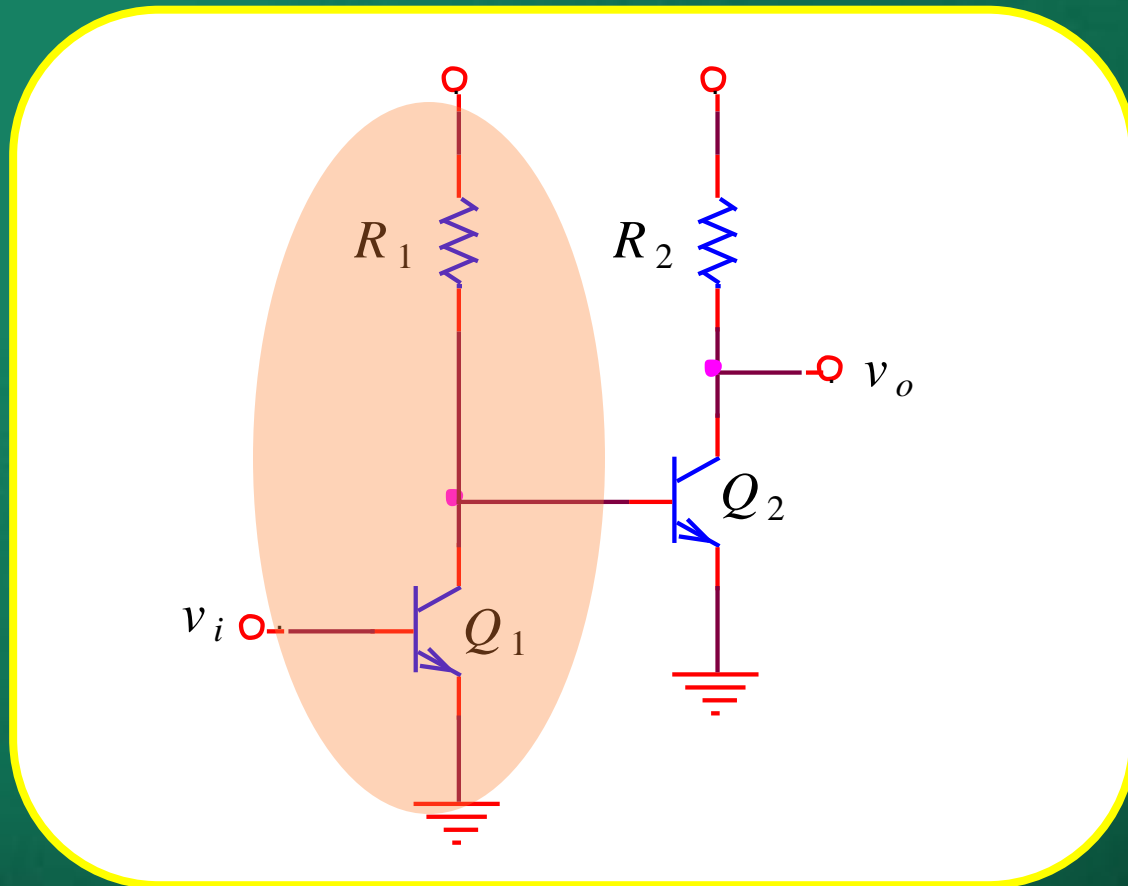


Multistage Amp Configuration

Darlington/Direct coupling

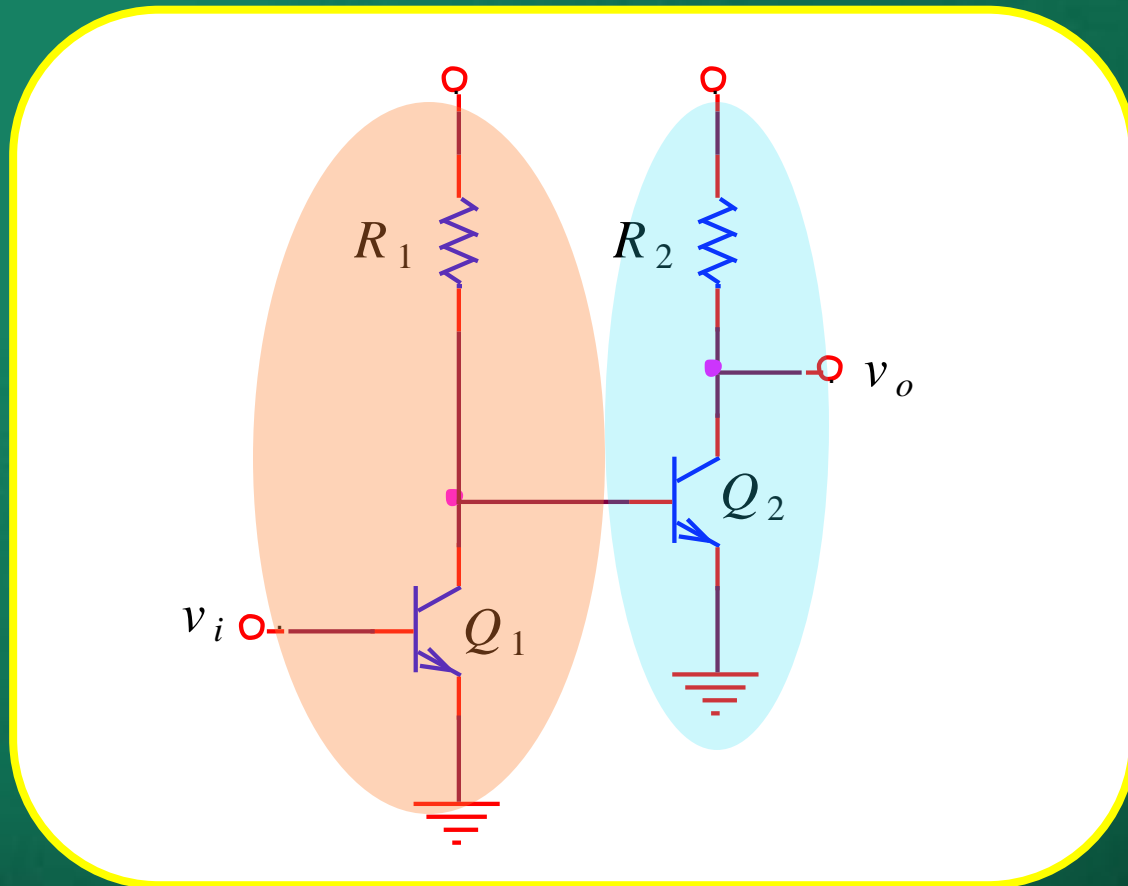


Multistage Amp Configuration

Transformer coupling

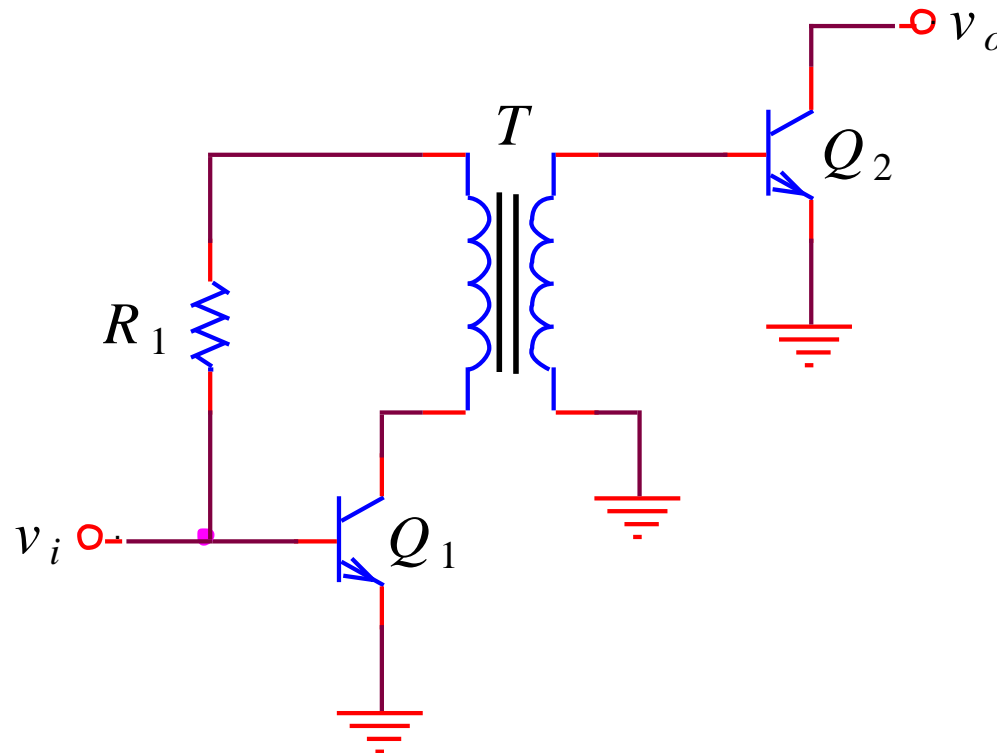


Multistage Amp Configuration

Transformer coupling

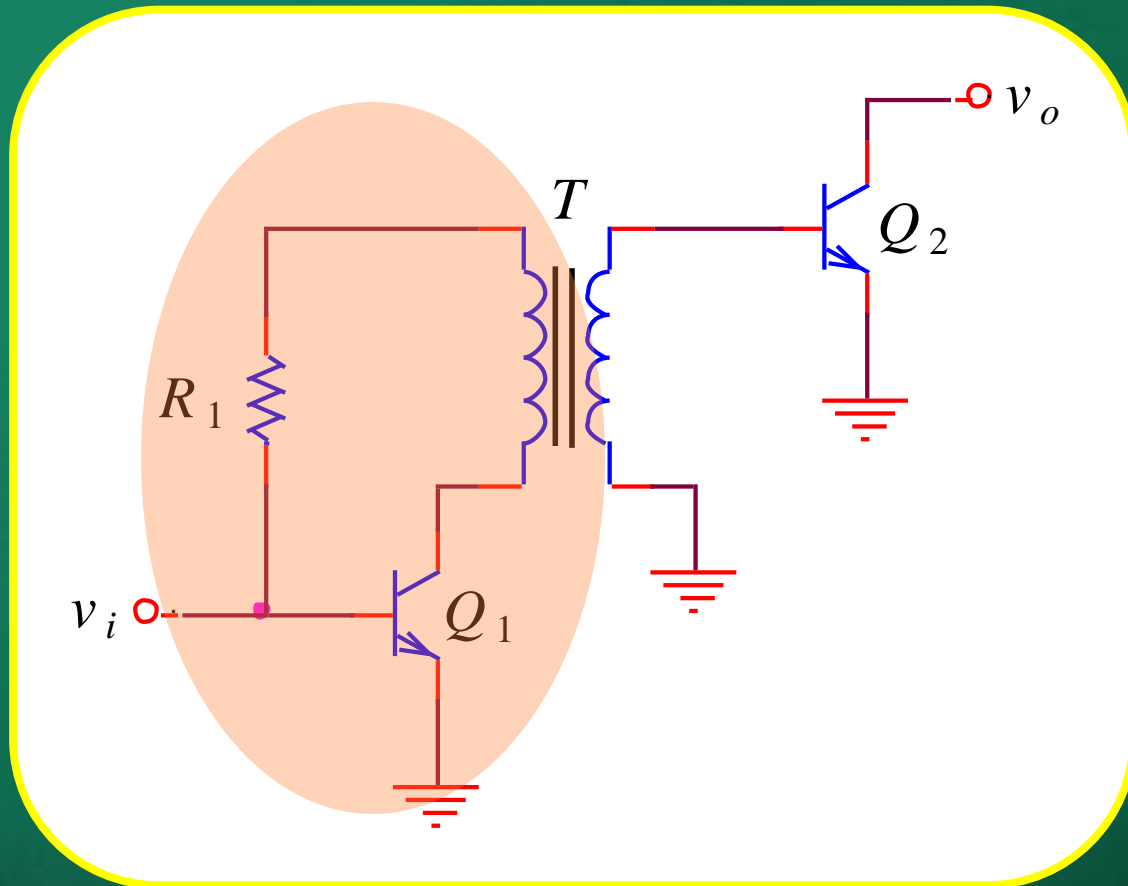

Multistage Amp Configuration

Transformer coupling

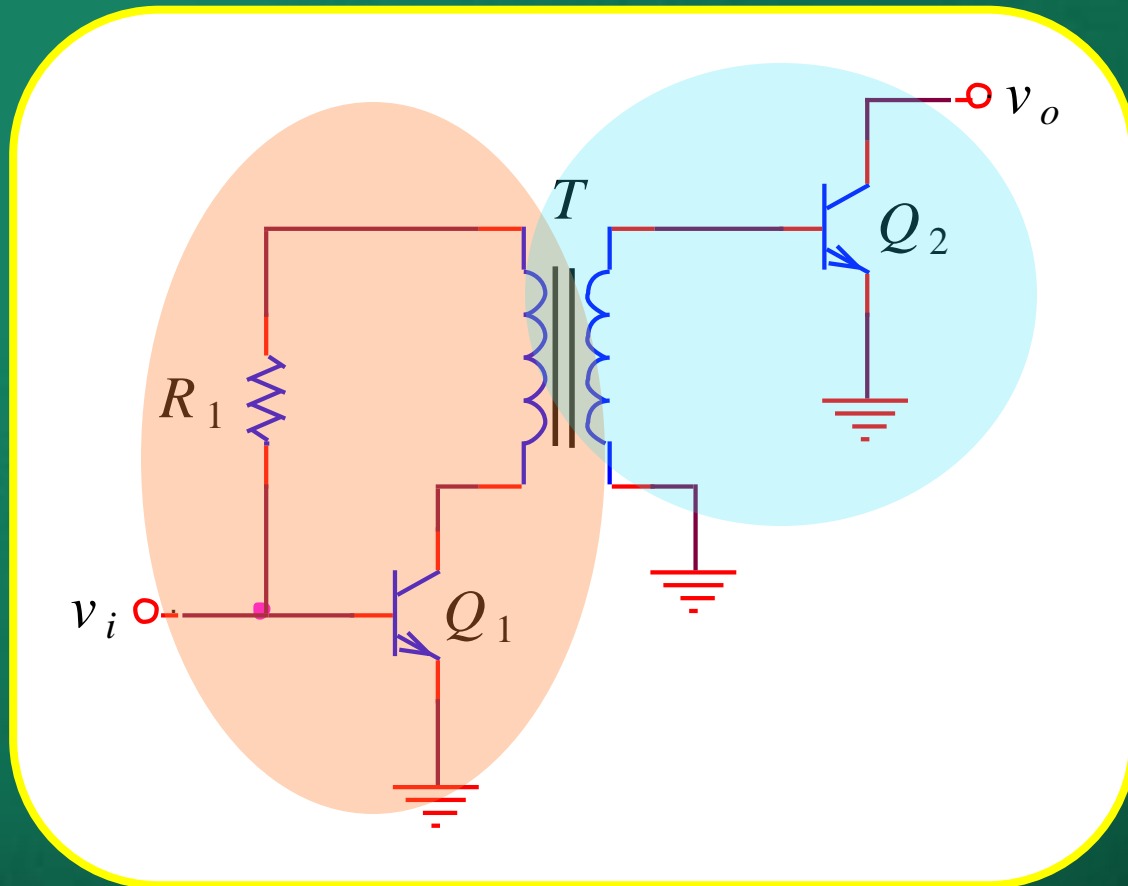

Cascade Connection

Cascade Connection

- ❑ The most widely used configuration.

Cascade Connection

- ❑ **The most widely used configuration.**
- ❑ **Coupling a signal from one stage to the another stage and block dc voltage from one stage to the another stage.**

Cascade Connection


- ❑ **The most widely used configuration.**
- ❑ **Coupling a signal from one stage to the another stage and block dc voltage from one stage to the another stage.**
- ❑ **The signal developed across the collector resistor of each stage is coupled into the base of the next stage.**

Cascade Connection

- ❑ **The most widely used configuration.**
- ❑ **Coupling a signal from one stage to the another stage and block dc voltage from one stage to the another stage.**
- ❑ **The signal developed across the collector resistor of each stage is coupled into the base of the next stage.**
- ❑ **The overall gain = product of the individual gain.**

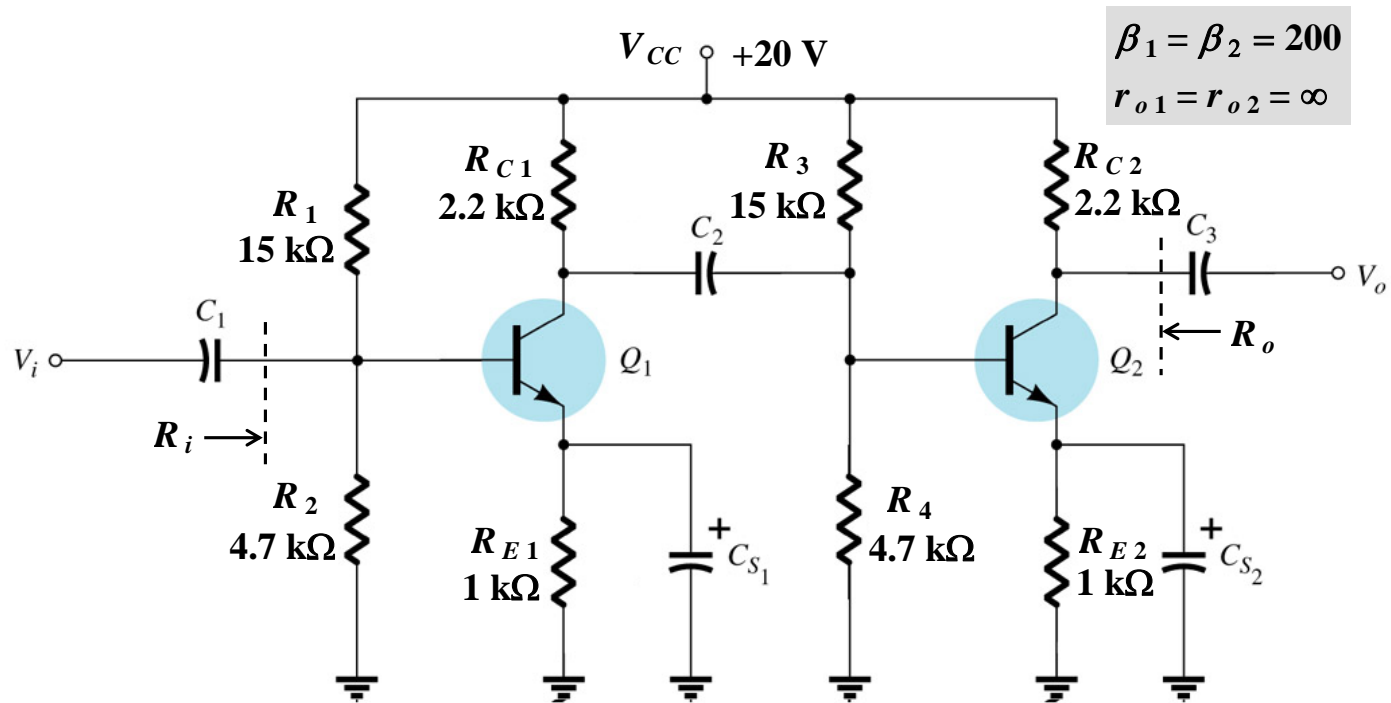
Example

Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



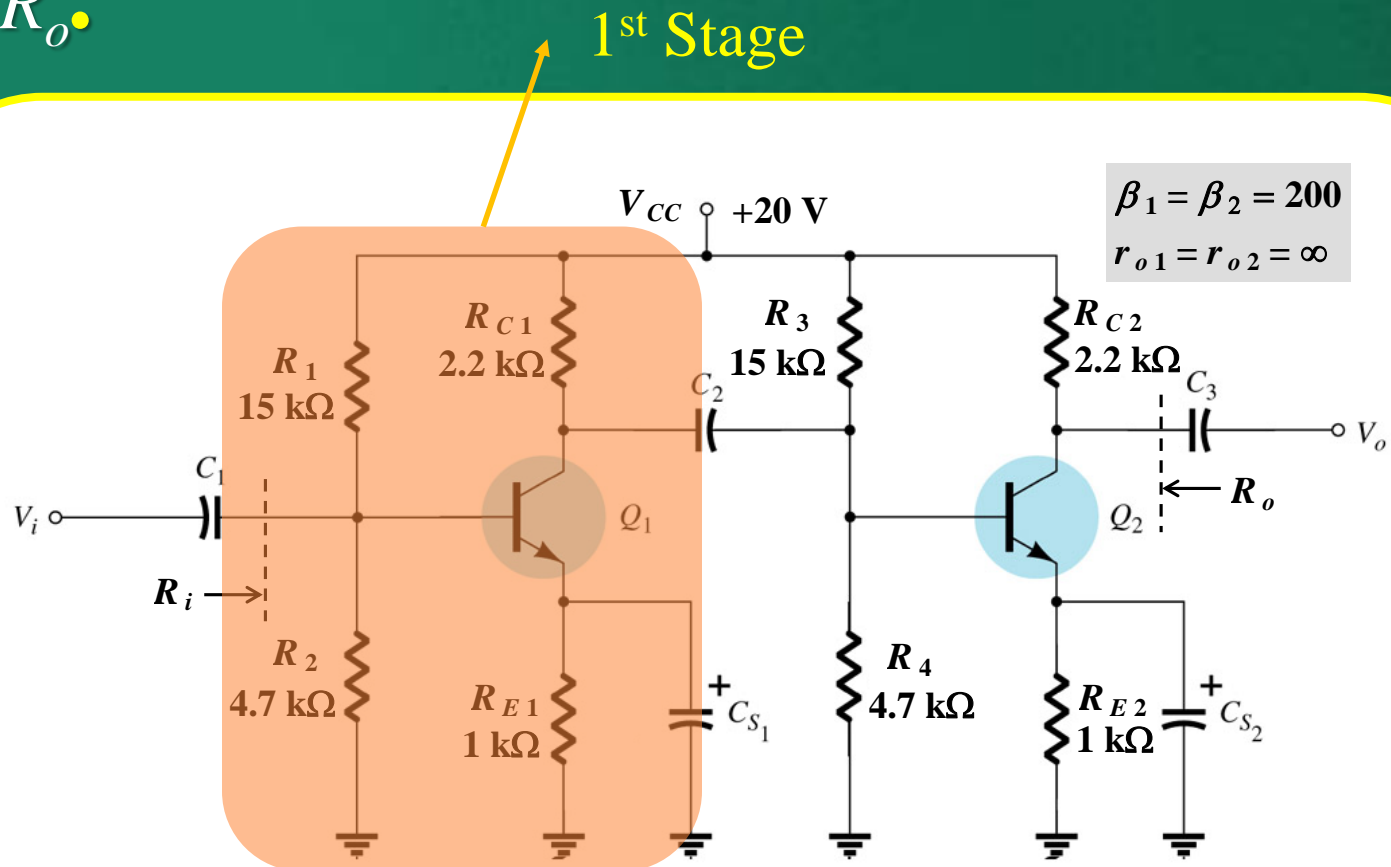
Example

Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



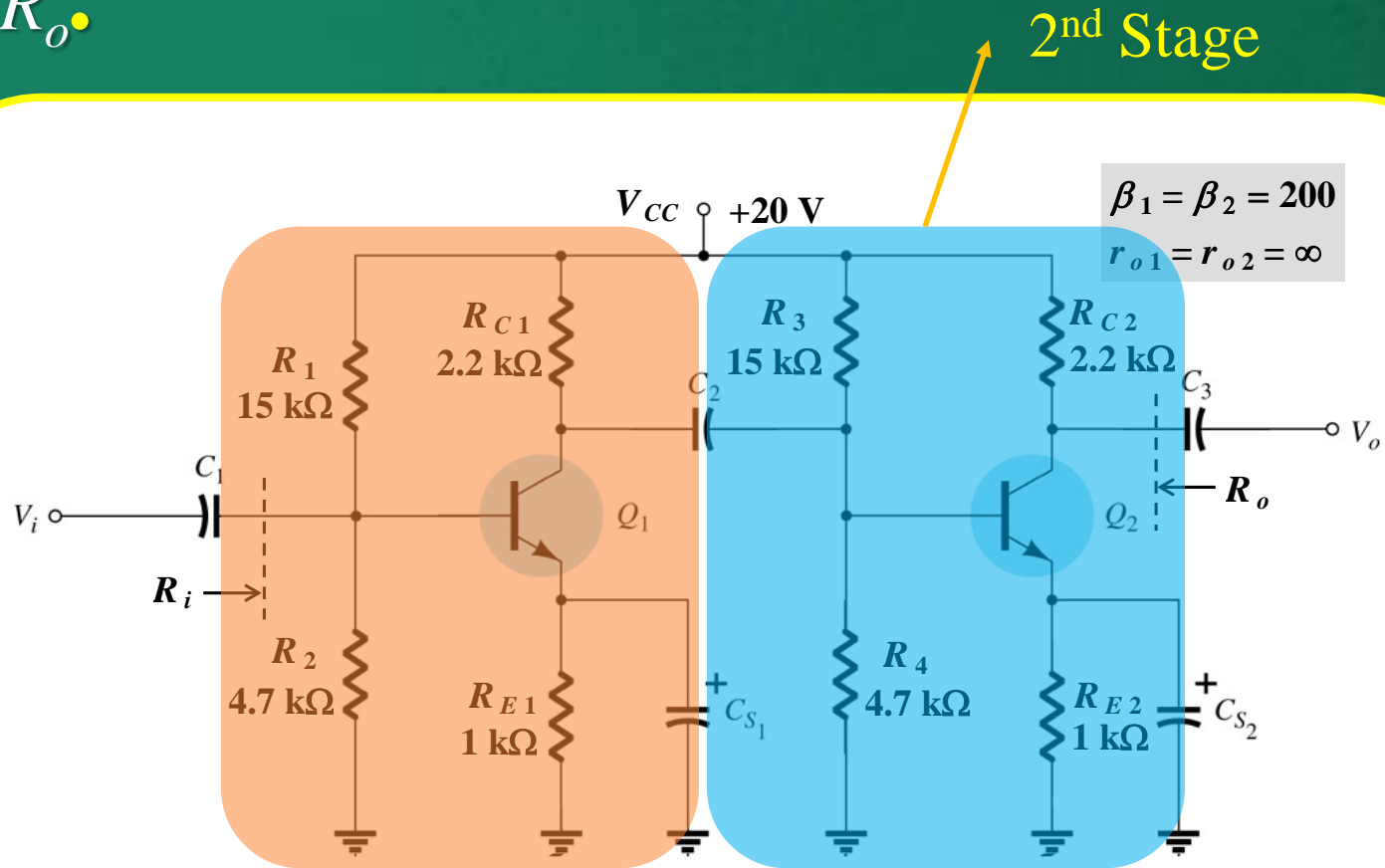Example


Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



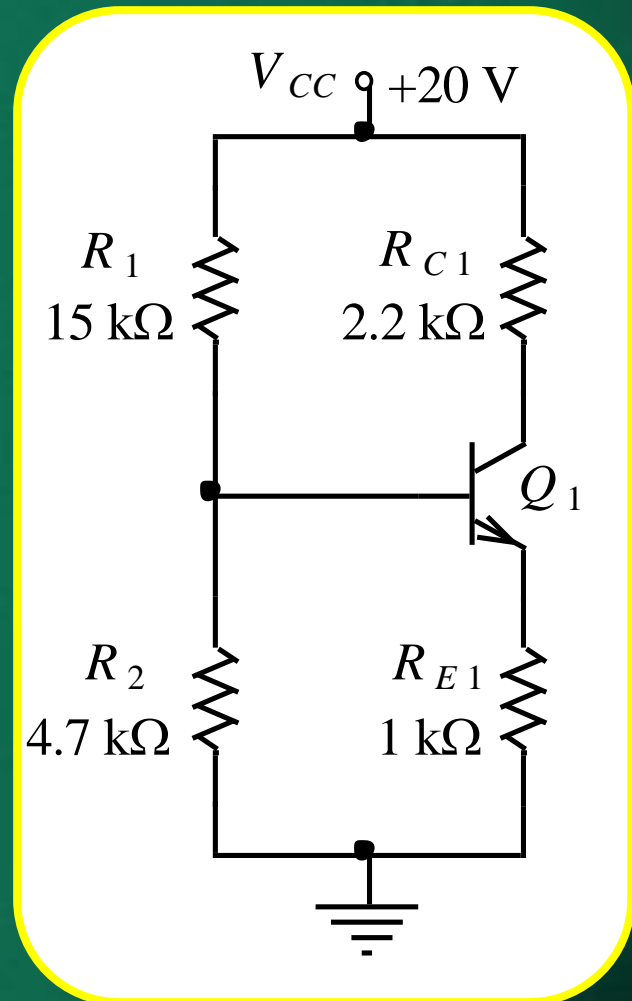Example (continued)


DC analysis

The circuit under DC condition (stage 1 and 2 are identical)



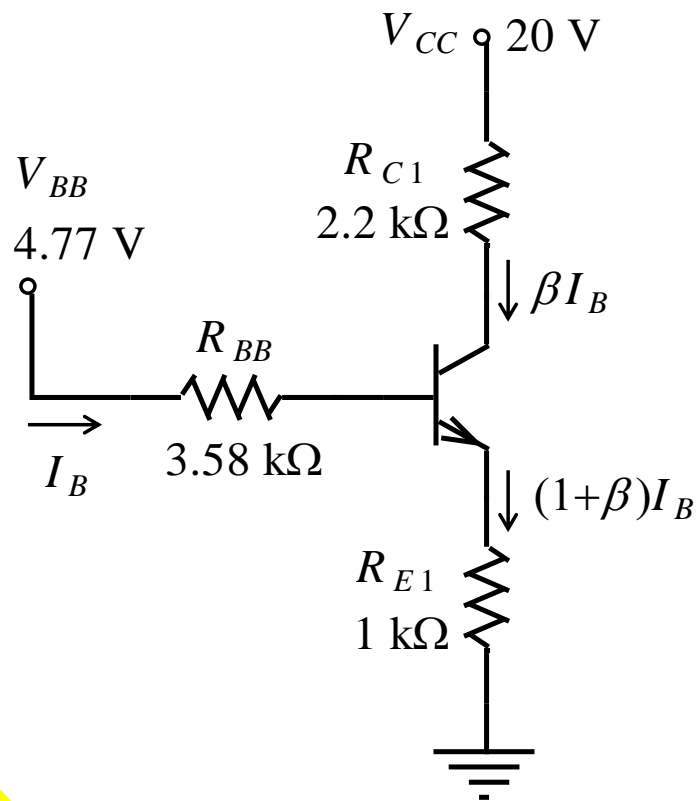Example (continued)

Applying Thévenin's theorem, the circuit becomes



$$I_{BQ1} = I_{BQ2} = 19.89 \mu\text{A}$$

$$I_{CQ1} = I_{CQ2} = 3.979 \text{ mA}$$


$$r_{\pi1} = r_{\pi2} = 1.307 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = 0.153 \text{ A/V}$$

Example (continued)

AC analysis


The small-signal equivalent circuit

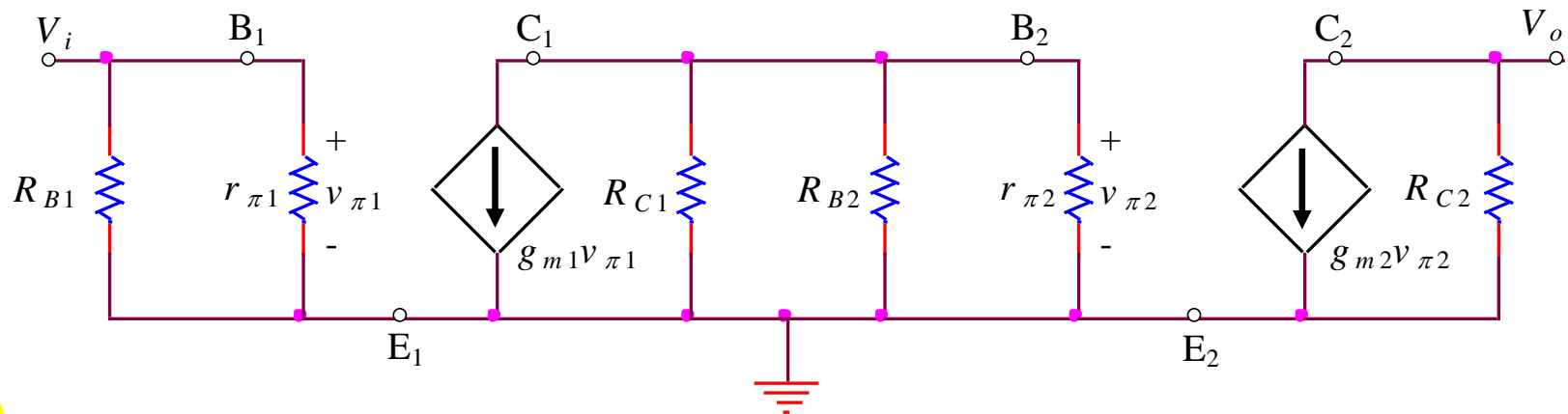

Example (continued)

AC analysis


The small-signal equivalent circuit

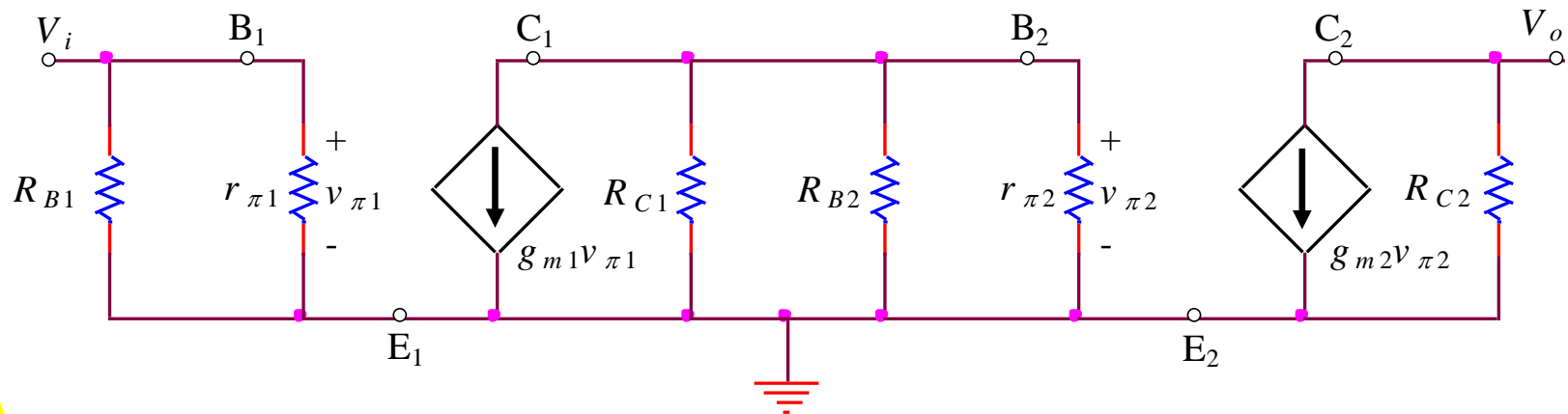

Example (continued)

AC analysis

The small-signal equivalent circuit

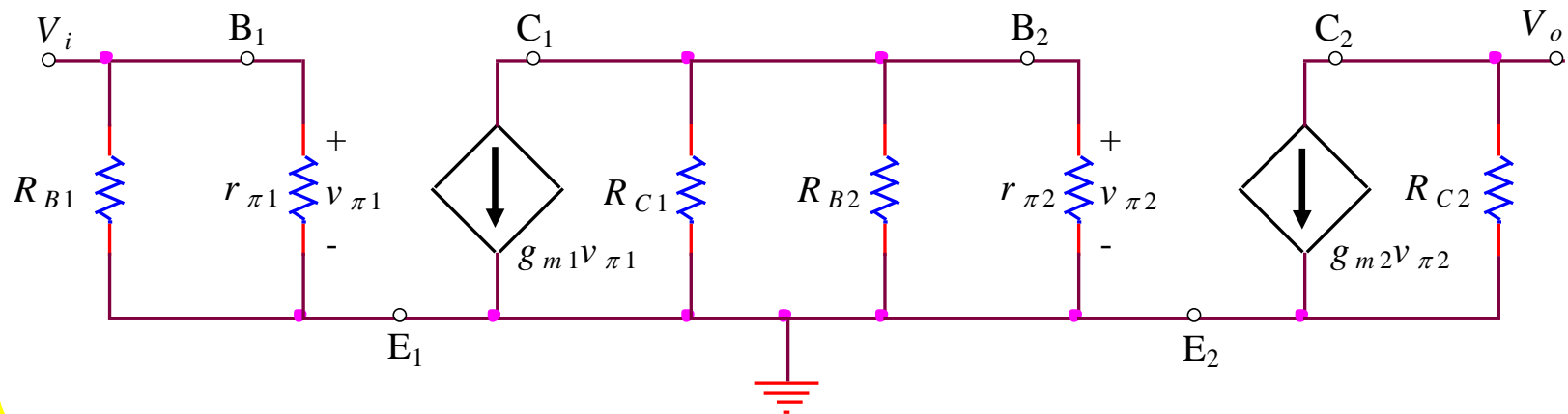

$$R_{B1} = R_1 // R_2$$

$$R_{B2} = R_3 // R_4$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

$$v_{\pi2} = -g_{m1}v_{\pi1}(R_{C1} // R_{B2} // r_{\pi2})$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

$$v_{\pi2} = -g_{m1}v_{\pi1}(R_{C1} // R_{B2} // r_{\pi2})$$

$$= -g_{m1}V_i(R_{C1} // R_{B2} // r_{\pi2})$$

$$[v_{\pi1} = V_i]$$

Example (continued)

$$V_o = -g_{m2} v_{\pi 2} R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi 2}} = -g_{m2} R_{C2}$$

$$v_{\pi 2} = -g_{m1} v_{\pi 1} (R_{C1} // R_{B2} // r_{\pi 2})$$

$$= -g_{m1} V_i (R_{C1} // R_{B2} // r_{\pi 2})$$

$$[v_{\pi 1} = V_i]$$

$$A_1 = \frac{v_{\pi 2}}{V_i} = -g_{m2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Example (continued)

The small-signal voltage gain

$$A = A_1 A_2 = g_{m1} g_{m2} R_{C2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Example (continued)

The small-signal voltage gain

$$A = A_1 A_2 = g_{m1} g_{m2} R_{C2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Substituting values

$$R_{B1} = R_{B2} = R_3 // R_4 = 15 // 4.7 = 3.579 \text{ k}\Omega$$

$$R_{C1} // R_{B2} // r_{\pi 2} = 2.2 // 3.579 // 1.307 = 667 \text{ }\Omega$$

$$A = 0.153 \times 0.153 \times 2200 \times 667 = 34350 \text{ V/V}$$

Example (continued)

The input resistance

$$R_{in} = R_{B1} // r_{\pi 1} = 3.579 // 1.307 = 0.957 \text{ k}\Omega$$

Example (continued)

The input resistance

$$R_{in} = R_{B1} // r_{\pi 1} = 3.579 // 1.307 = 0.957 \text{ k}\Omega$$

The output resistance

$$R_o = R_{C2} = 2.2 \text{ k}\Omega$$