


# **Basic Electronic Circuits**

## **(IEC-103)**


### **Lecture-12**

# **DC Power Supplies**

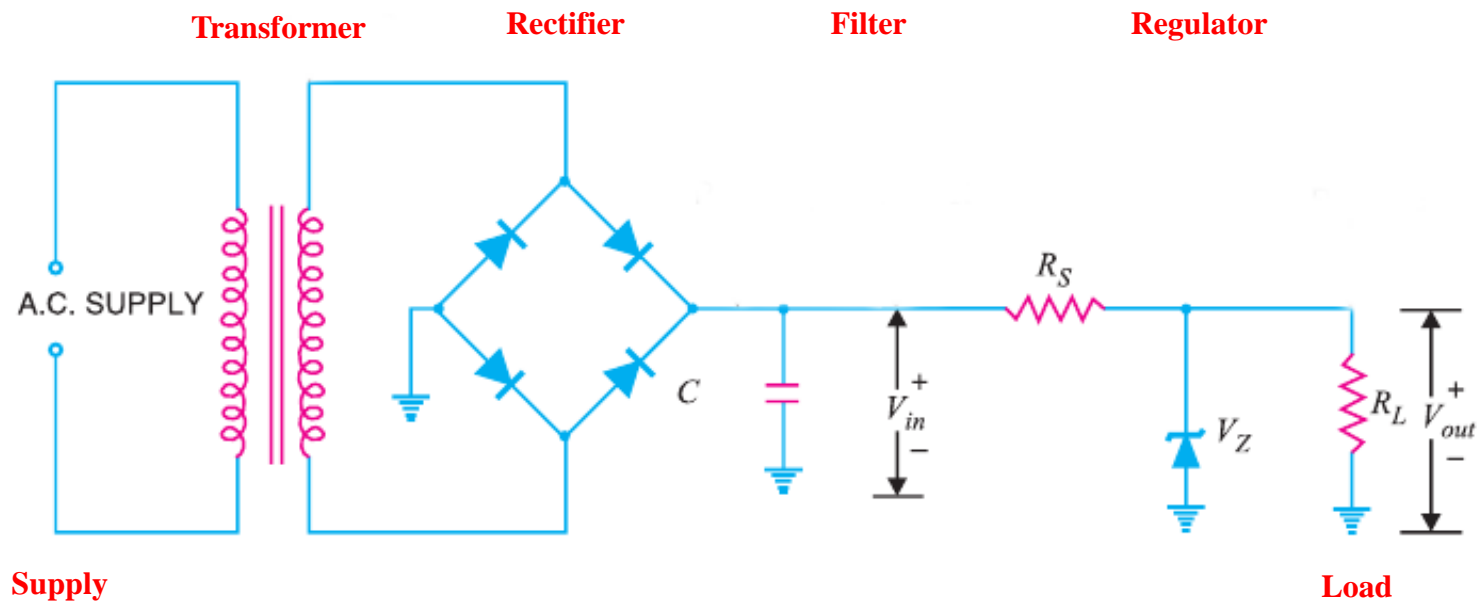
# Circuit Diagram of a Simple Regulated Power Supply



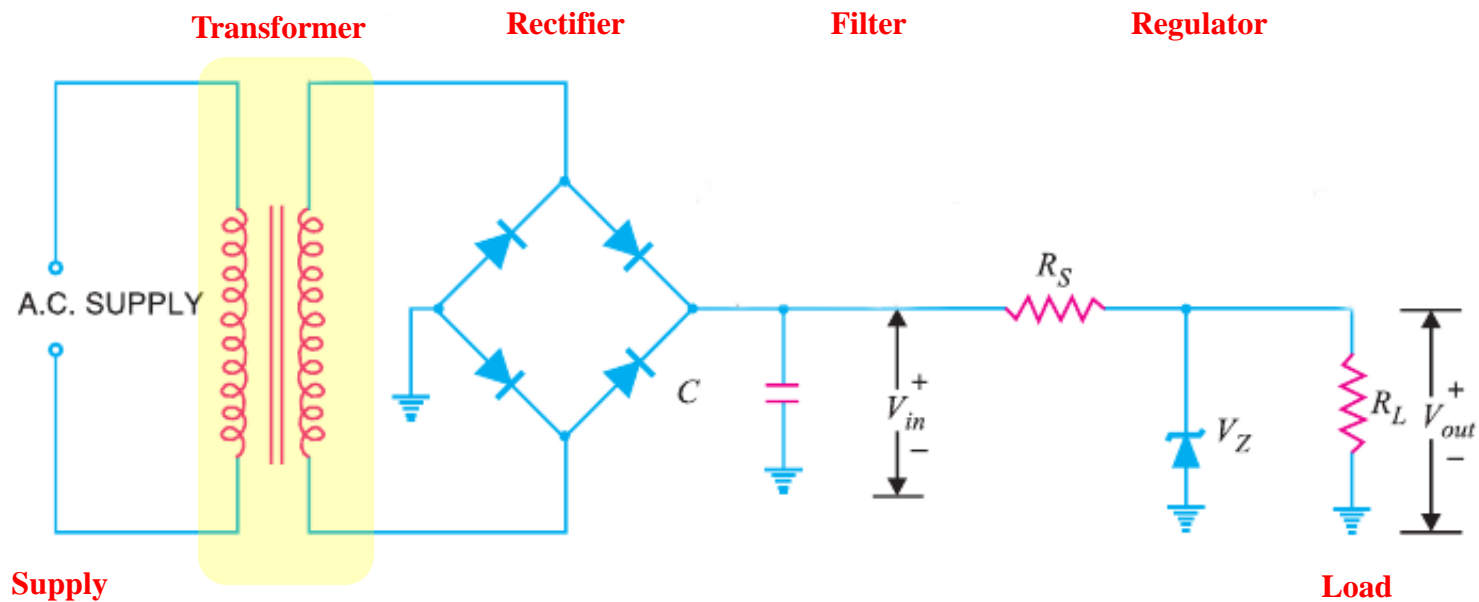
# Circuit Diagram of a Simple Regulated Power Supply


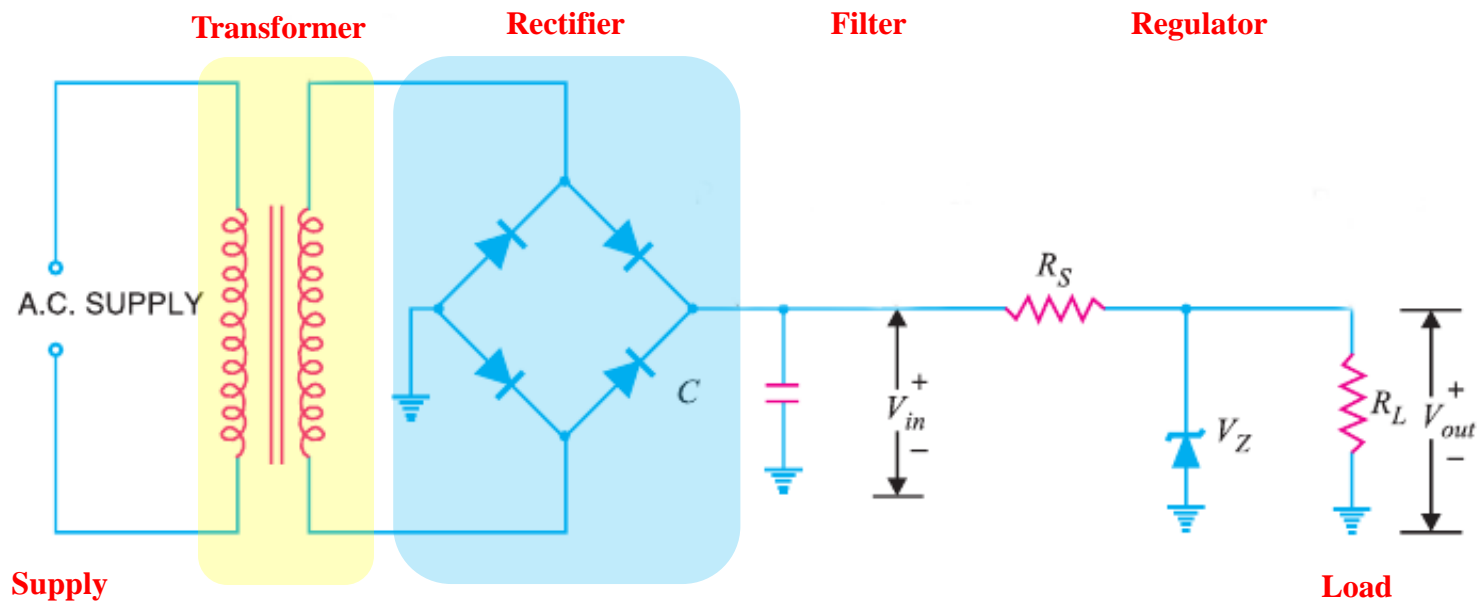
# Circuit Diagram of a Simple Regulated Power Supply



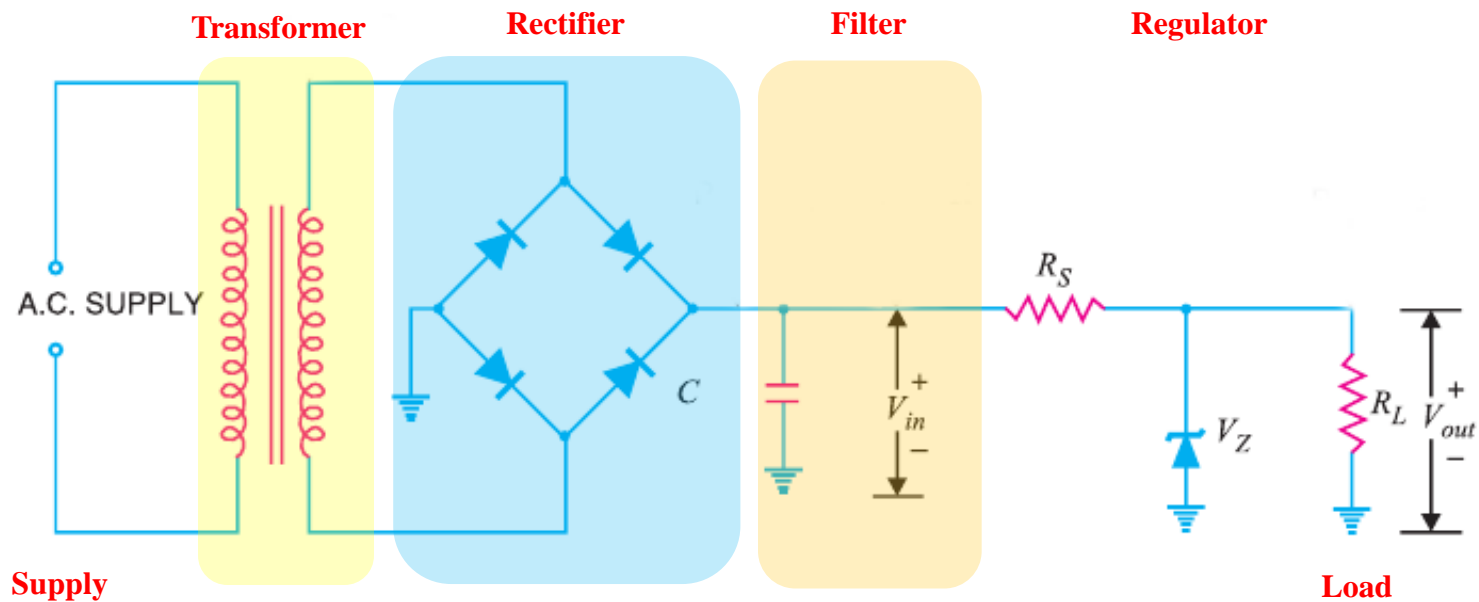
# Circuit Diagram of a Simple Regulated Power Supply





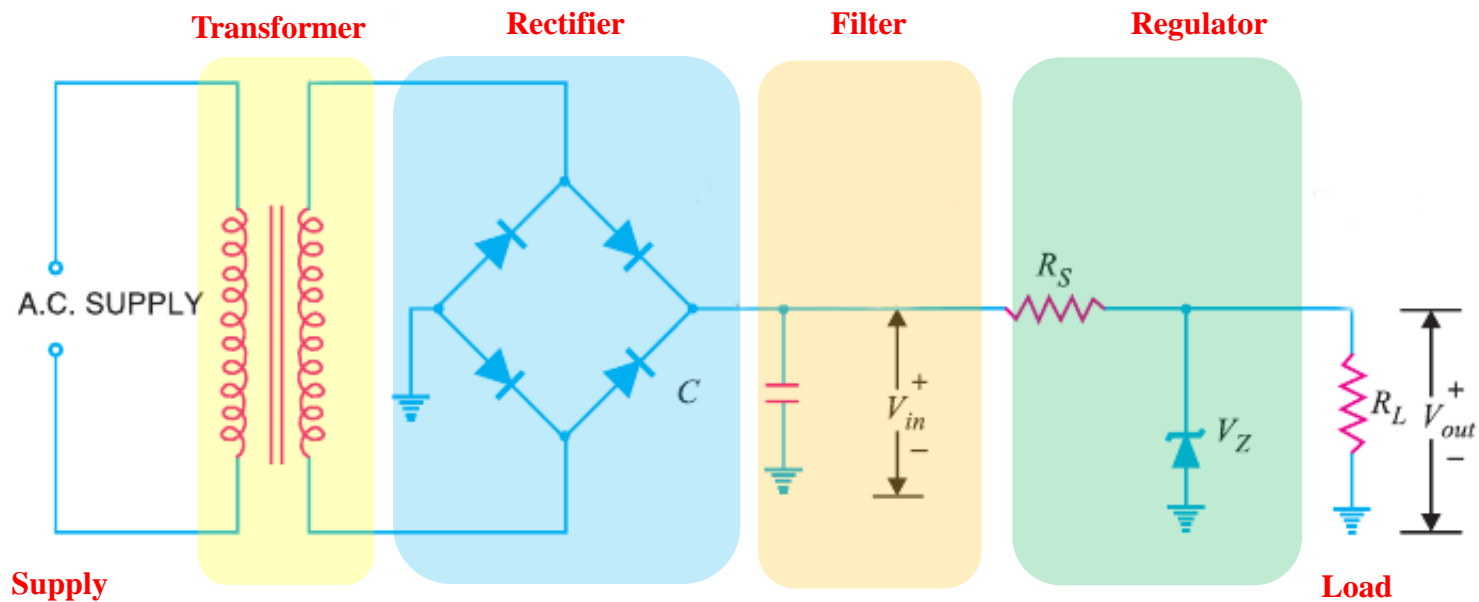
# Circuit Diagram of a Simple Regulated Power Supply




# Output Waveform after each Stage

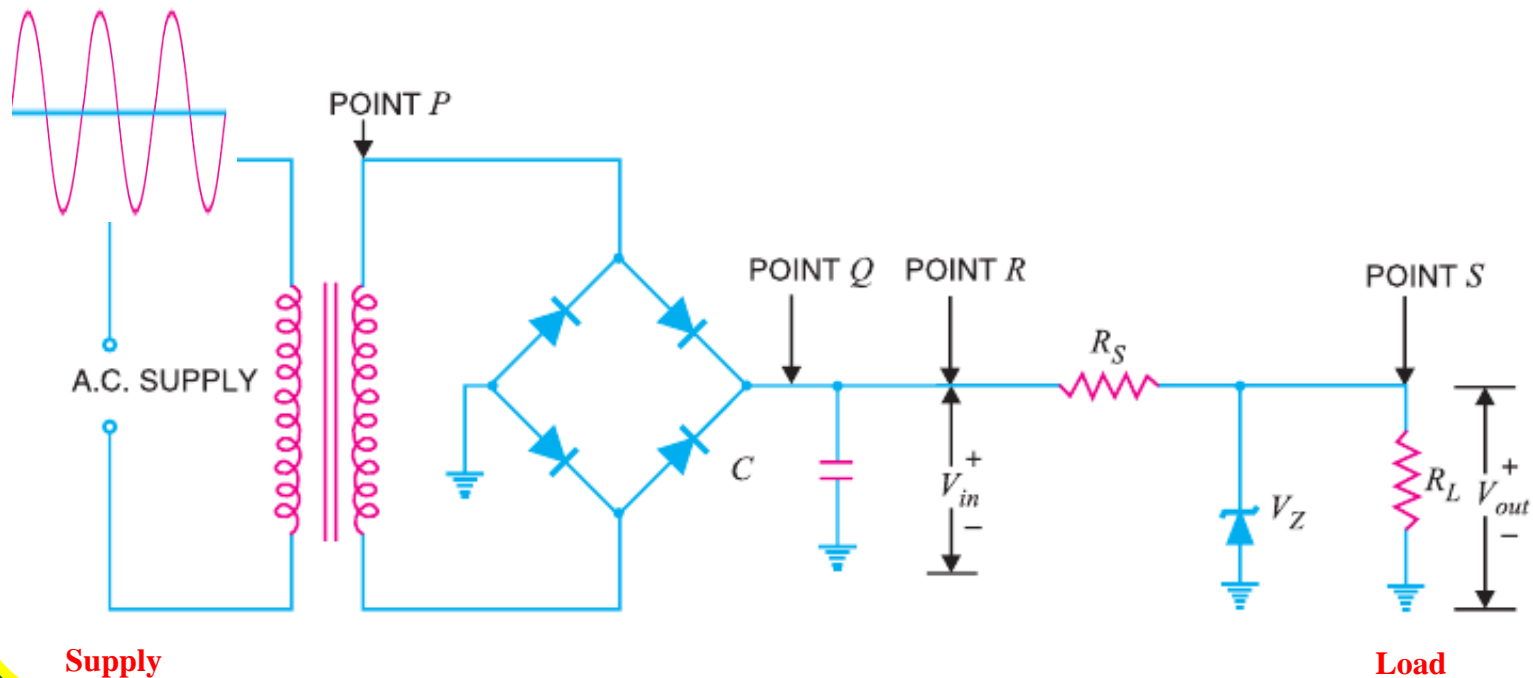





# Output Waveform after each Stage

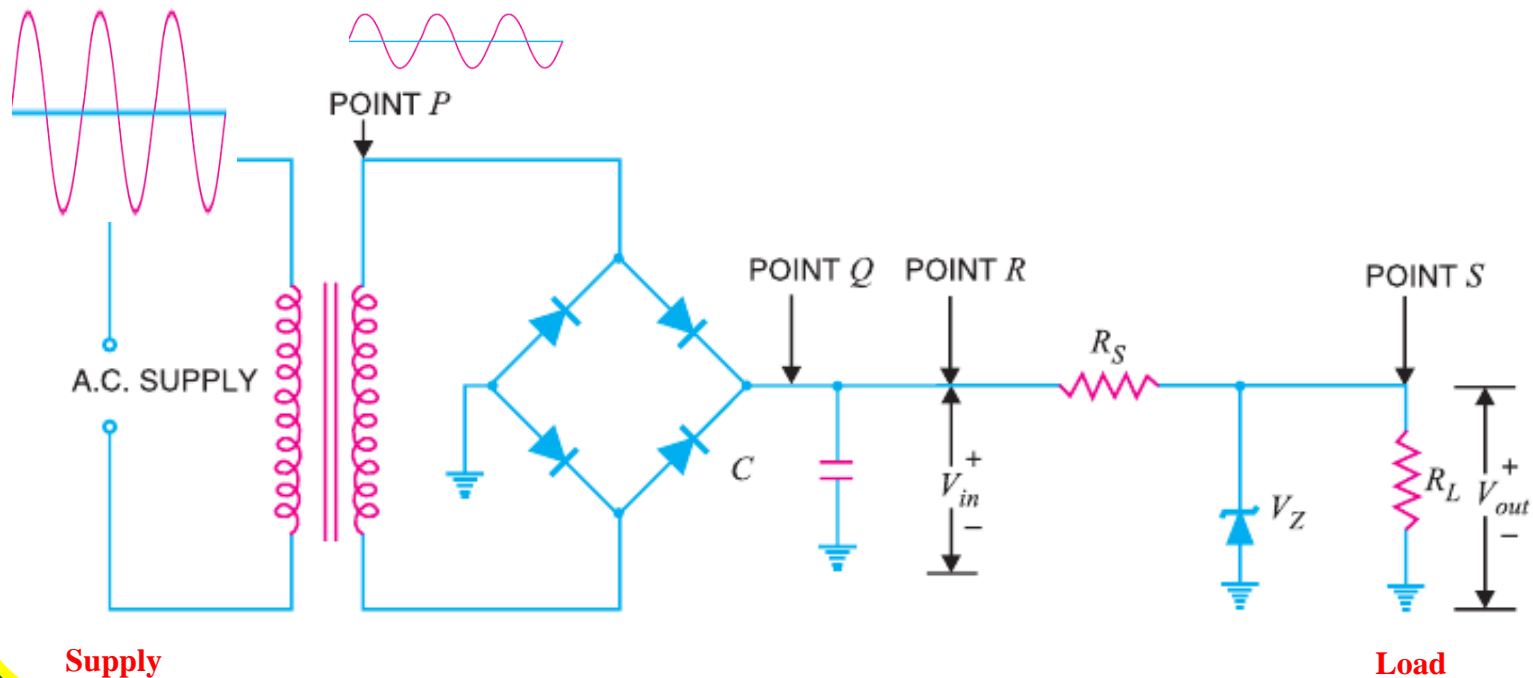


# Output Waveform after each Stage

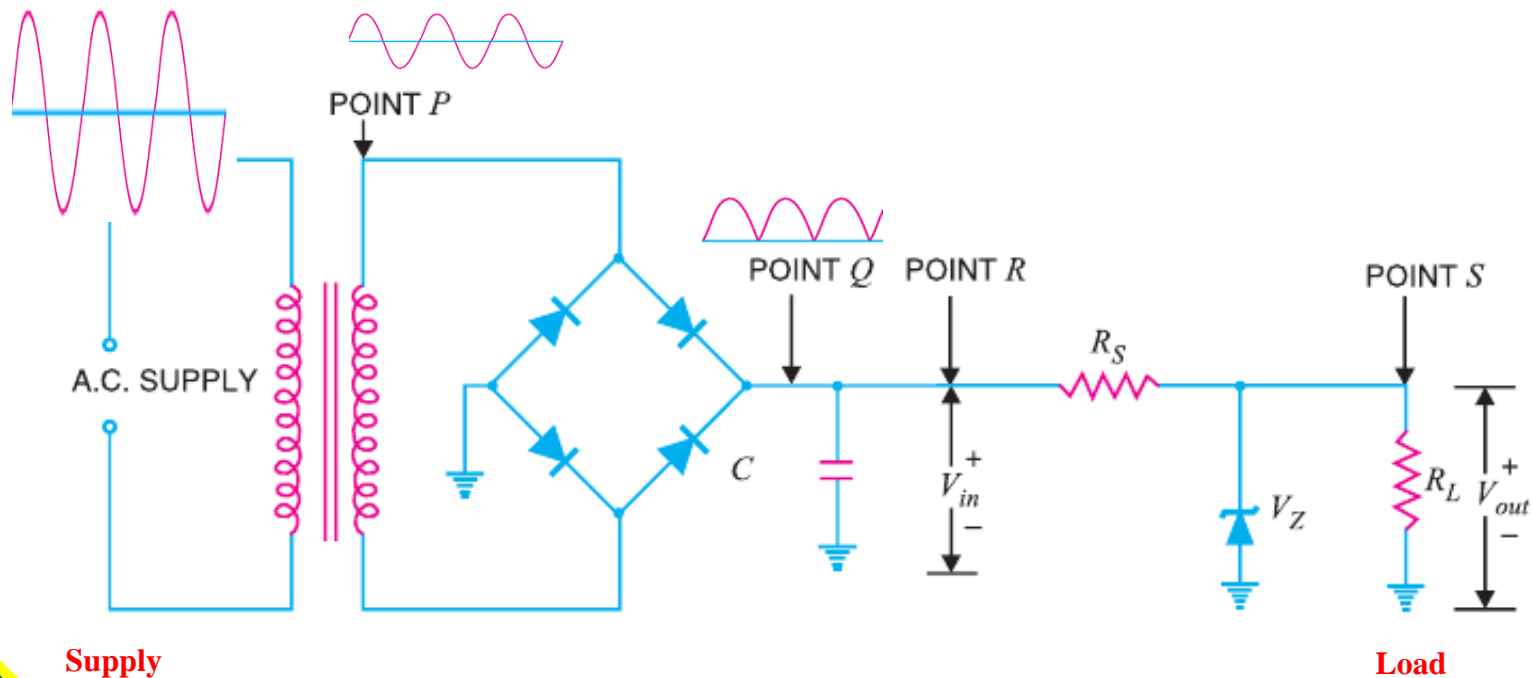

# Output Waveform after each Stage

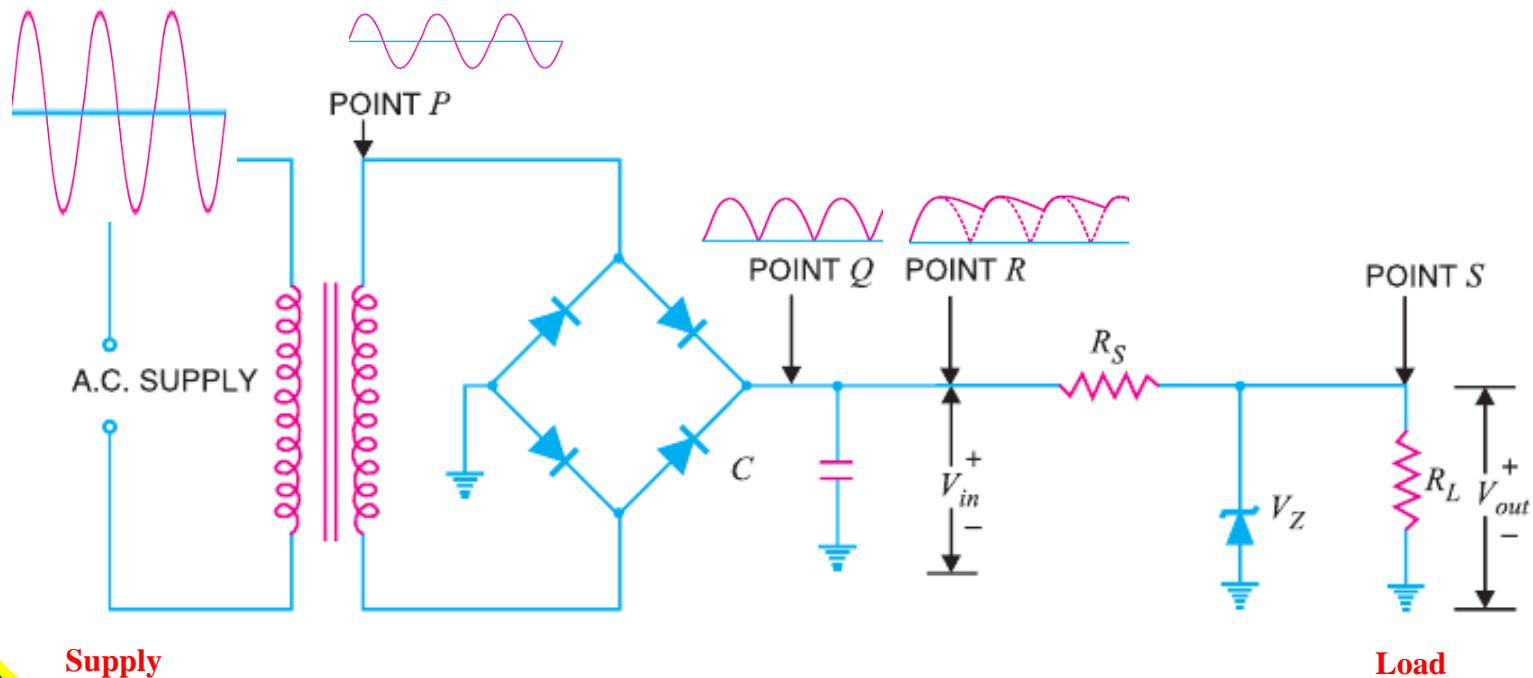

# Output Waveform after each Stage

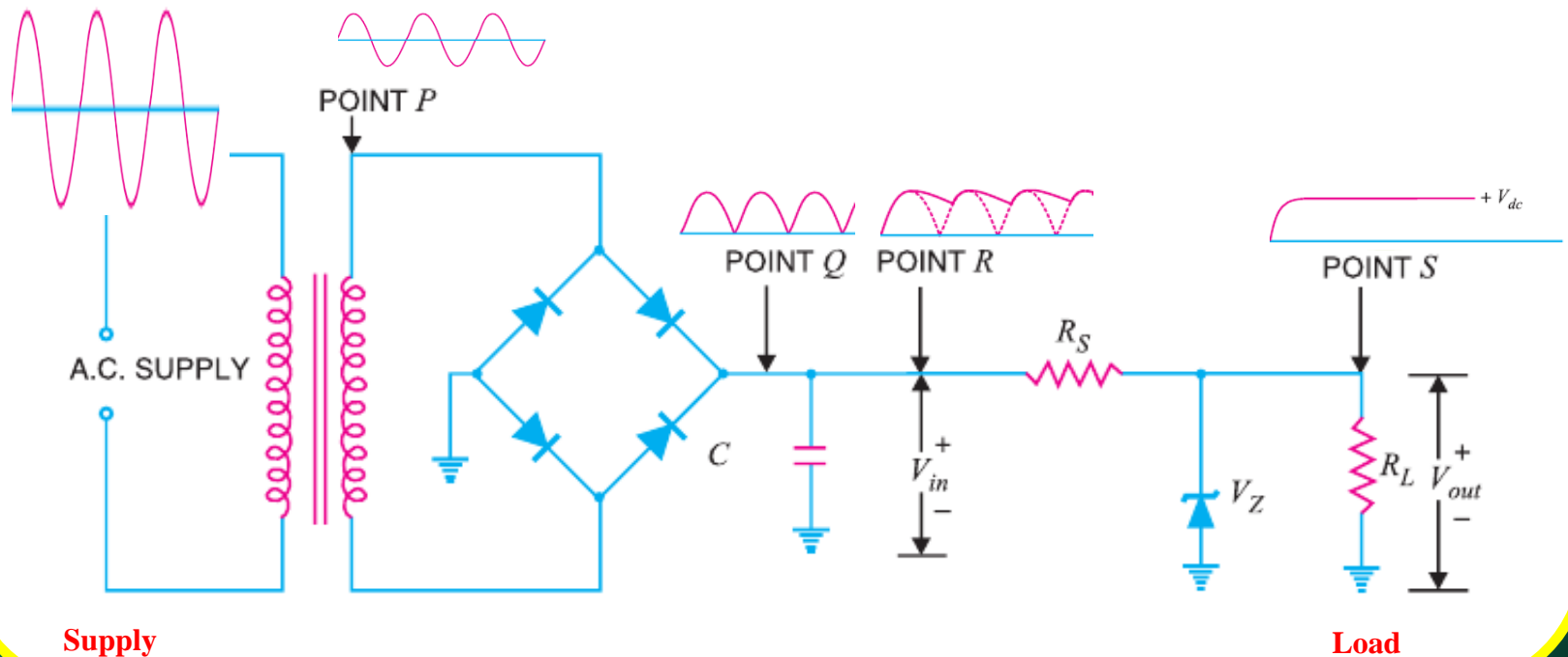

# Quality of a Power Supply

# Quality of a Power Supply

- ❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.



# Quality of a Power Supply

❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

# Quality of a Power Supply

- ❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

- ❑ **Load Regulation:** Is the capability to maintain a constant voltage (or current) level on the output channel of a power supply despite changes in the load.

# Quality of a Power Supply

- ❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.


$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

- ❑ **Load Regulation:** Is the capability to maintain a constant voltage (or current) level on the output channel of a power supply despite changes in the load.

$$\% LR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$


# **No Load & Full Load for a Voltage Source**

# No Load & Full Load

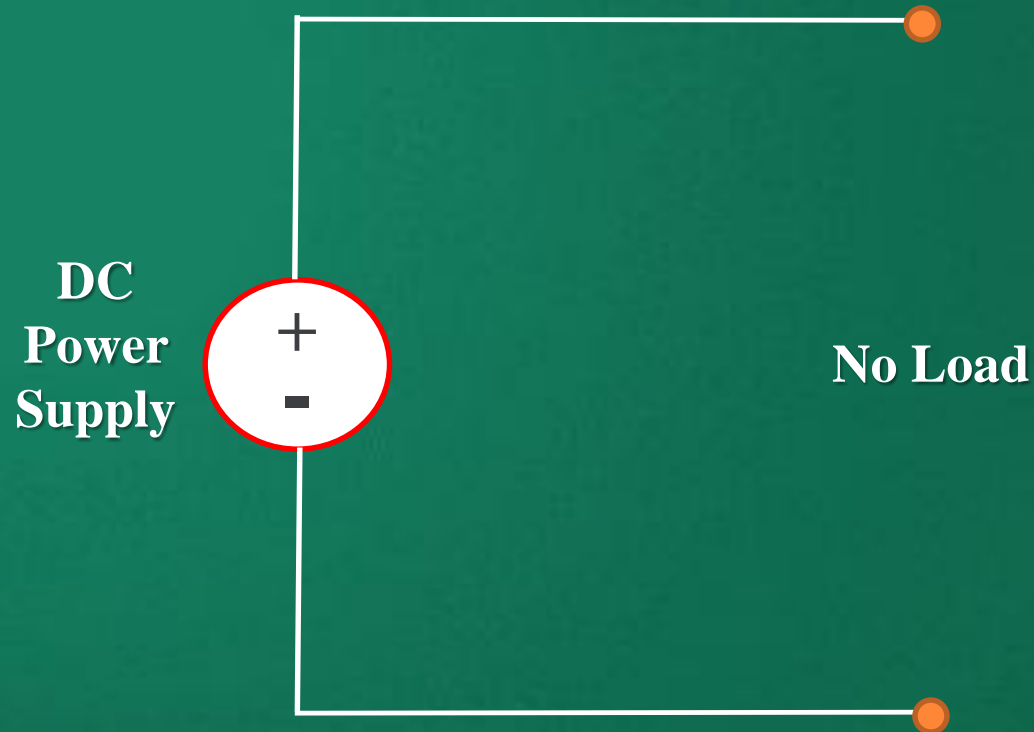



# No Load & Full Load

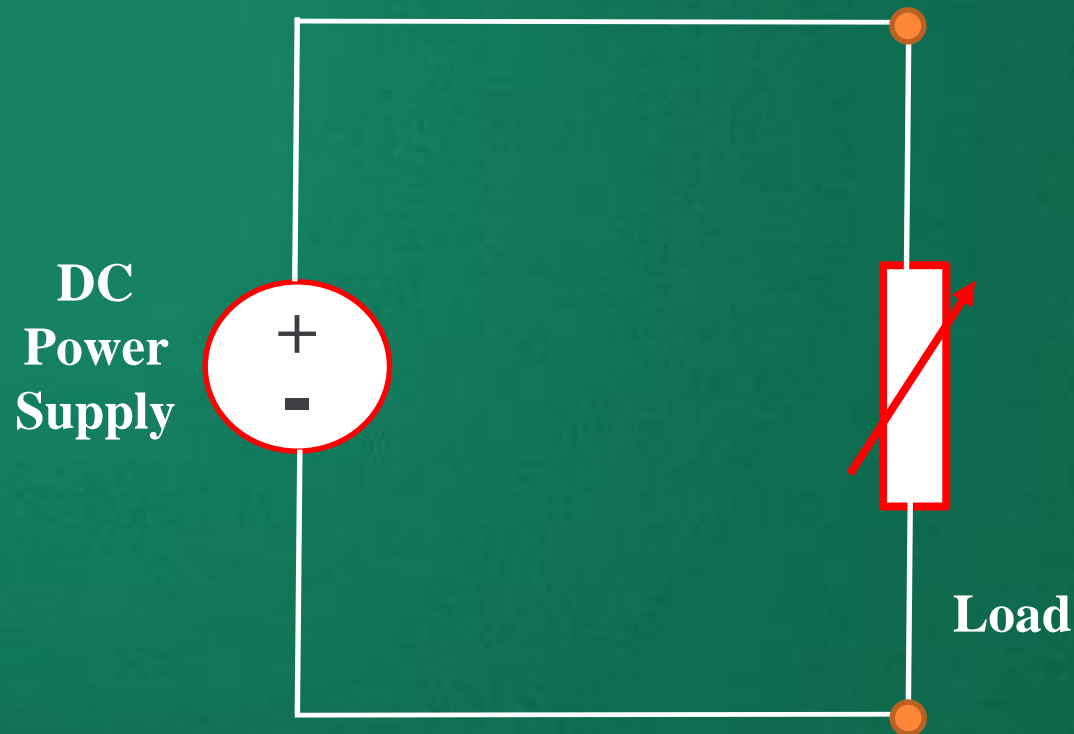



# Transformers

# Transformers

# Transformers

- **Transformer is an AC device which can step up or step down AC voltages.**

# Transformers


- ❑ **Transformer is an AC device which can step up or step down AC voltages.**
- ❑ **Secondly transformer isolates the rectifier circuit from power line and thus reduces the risk of electric shock.**

# Transformers

- ❑ Transformer is an AC device which can step up or step down AC voltages.
- ❑ Secondly transformer isolates the rectifier circuit from power line and thus reduces the risk of electric shock.




**Without Centre Tap**

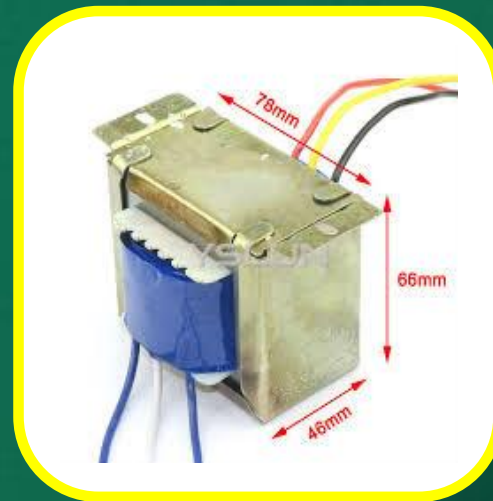

**With Centre Tap**




# Transformer

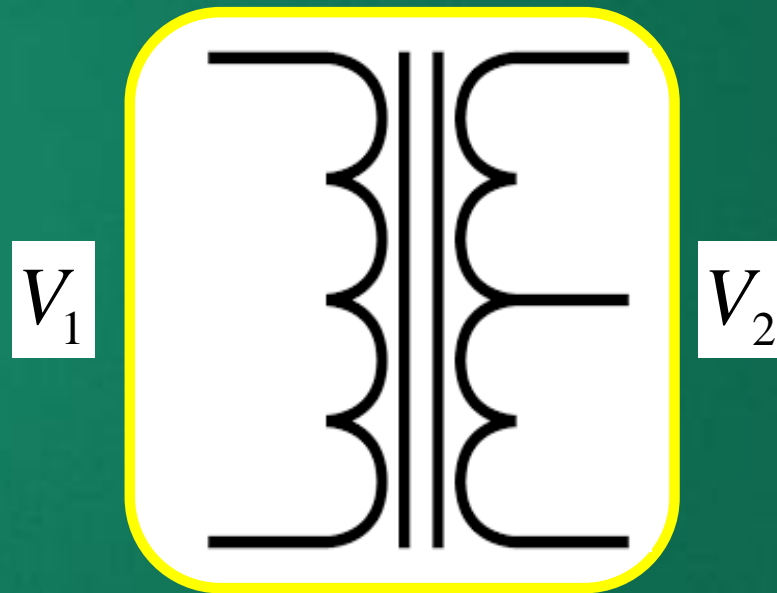



# Transformer

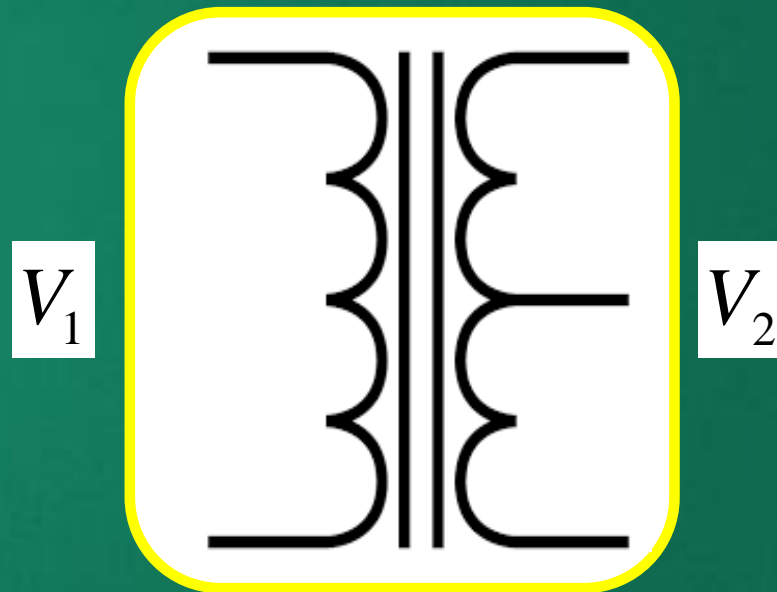

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

# Rectifiers

# Rectifiers

# Rectifiers

- The rectifier converts the AC sinusoidal signal into a pulsating DC wave.

# Rectifiers

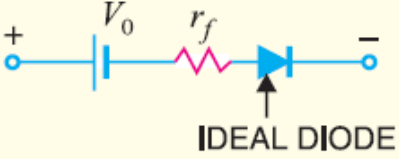
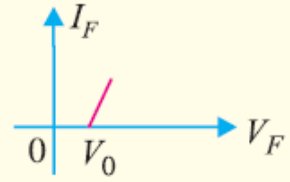
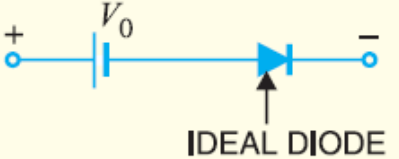
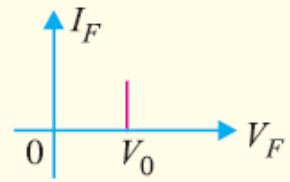

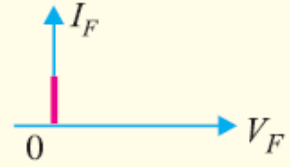
- ❑ The rectifier converts the AC sinusoidal signal into a pulsating DC wave.
- ❑ There are several forms of rectifiers in use and all of them use diodes.

# Rectifiers

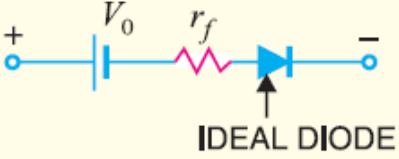
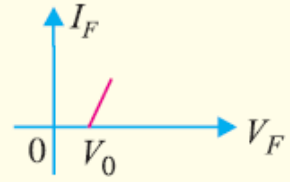
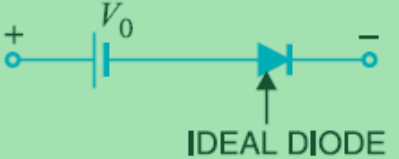
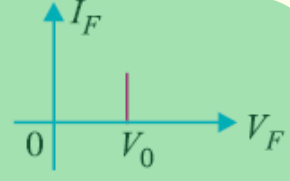

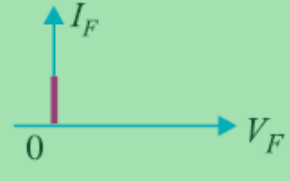
- ❑ The rectifier converts the AC sinusoidal signal into a pulsating DC wave.
- ❑ There are several forms of rectifiers in use and all of them use diodes.
- ❑ Can be classified into two types
  - Half wave rectifiers
  - Full wave rectifiers




# Diode Equivalent Circuits

S.No.	Type	Model	Characteristic
1.	Approximate model		
2.	Simplified model		
3.	Ideal Model		


# Diode Equivalent Circuits

S.No.	Type	Model	Characteristic
1.	Approximate model		
2.	Simplified model		
3.	Ideal Model		


# Half Wave Rectifier

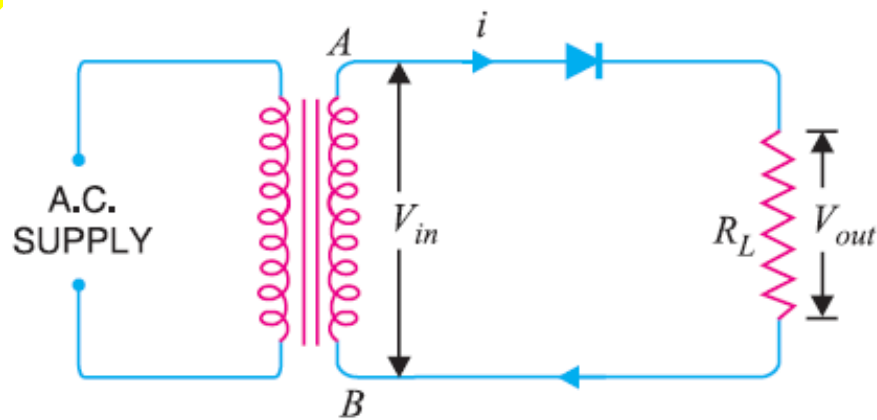

# Half Wave Rectifier



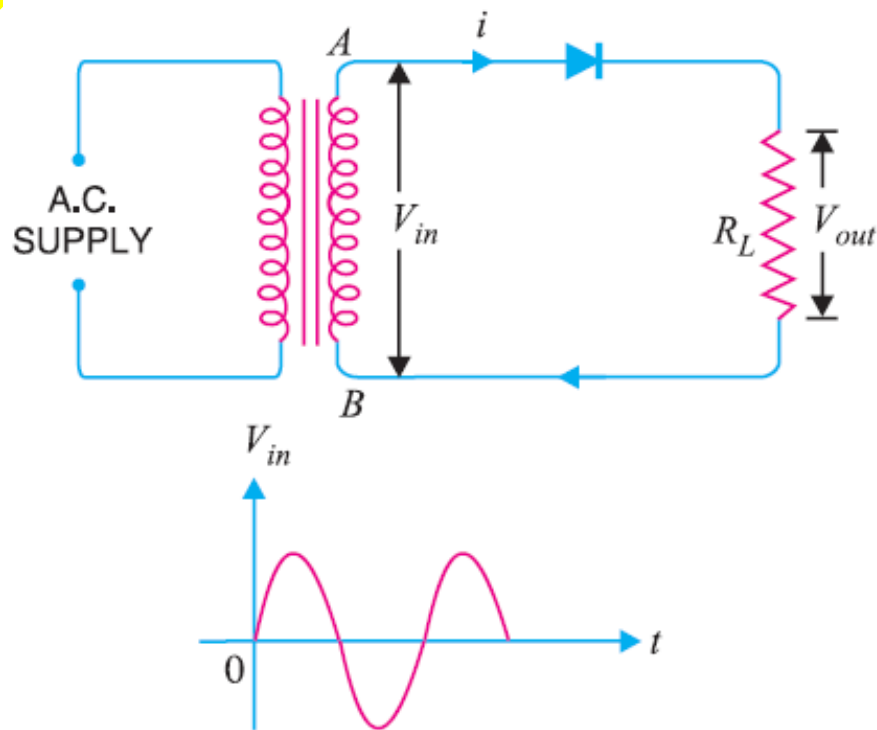


# Half Wave Rectifier

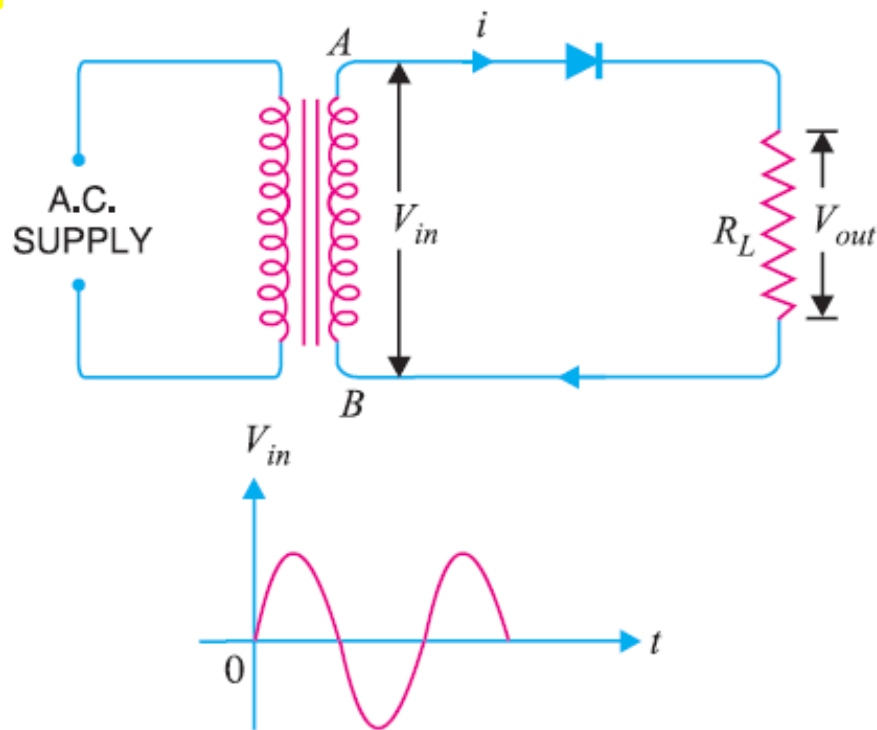



# Half Wave Rectifier

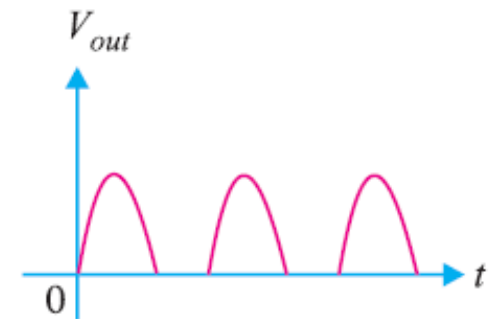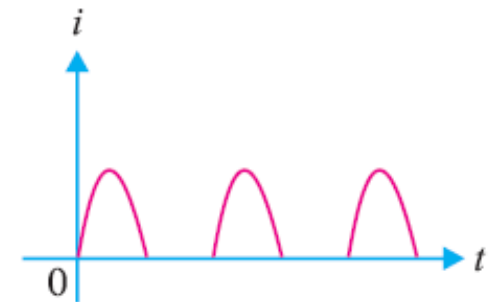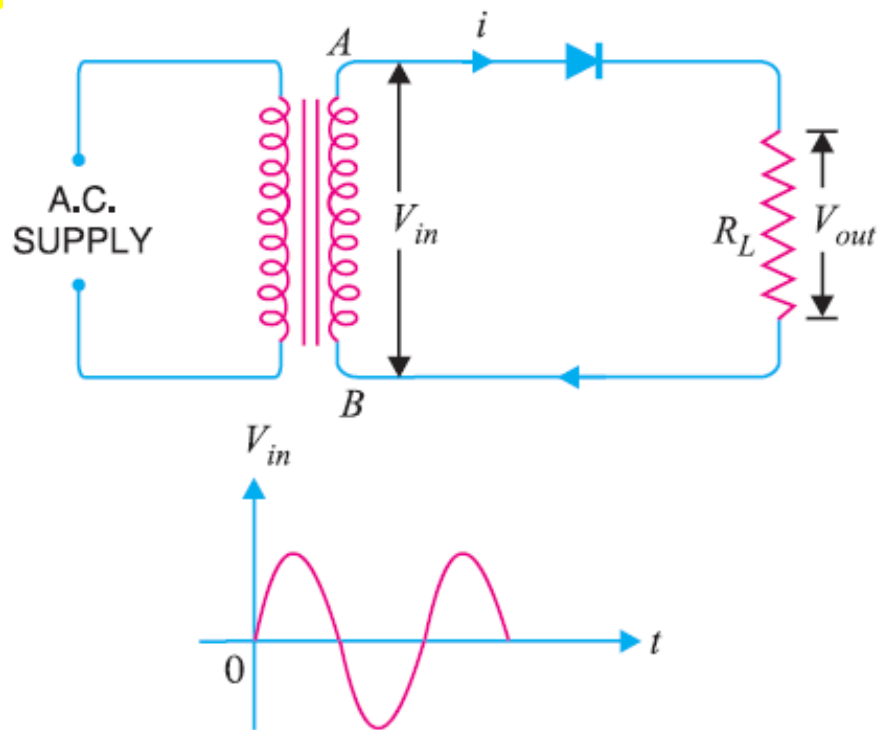

# Half Wave Rectifier

# Half Wave Rectifier

## □ Ripple Factor

# Half Wave Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2} \sqrt{\pi^2 - 4} = 1.21$$

# Half Wave Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2} \sqrt{\pi^2 - 4} = 1.21$$

□ The ripple content is high, so an elaborate filter is required to produce steady current.



# Half Wave Rectifier

## □ Ripple Factor


$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2} \sqrt{\pi^2 - 4} = 1.21$$

- The ripple content is high, so an elaborate filter is required to produce steady current.
- It delivers power only half the time, therefore output is low.

# Full Wave Rectifiers

## □ Full Wave Rectifiers



- Centre-Tap Full Wave Rectifier

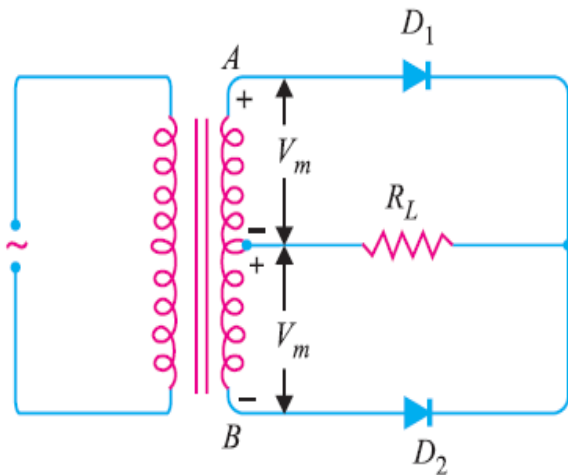


# Full Wave Rectifiers
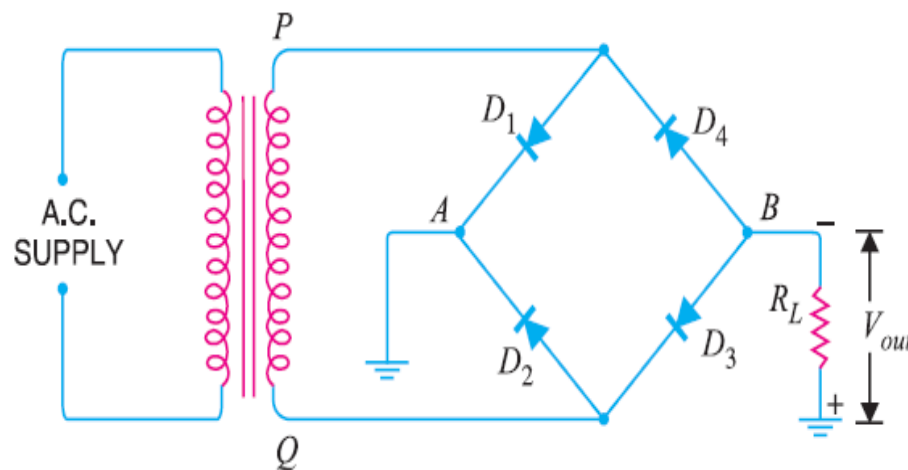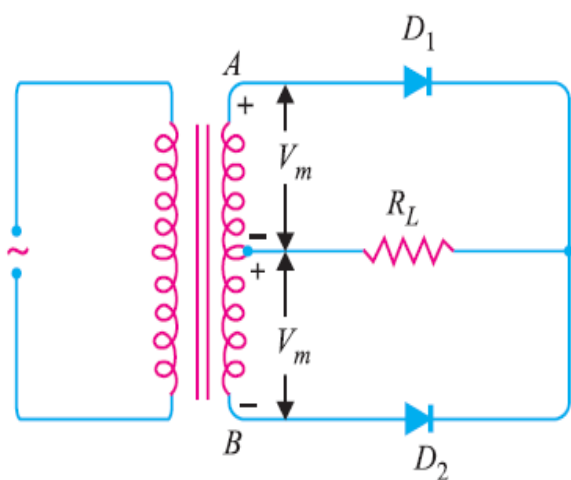
## □ Full Wave Rectifiers



- Centre-Tap Full Wave Rectifier
- Full Wave Bridge Rectifier



# Centre-Tap Full Wave Rectifier

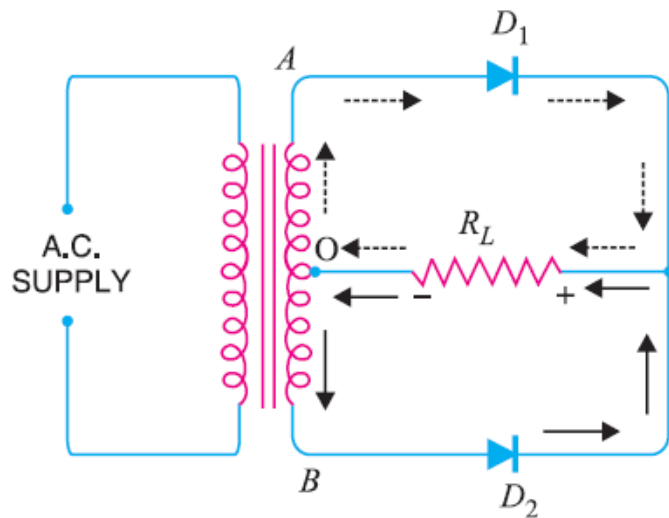

# Centre-Tap Full Wave Rectifier

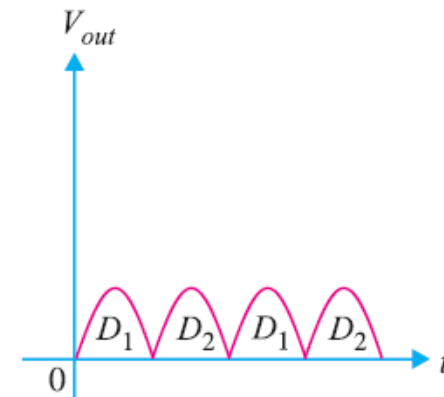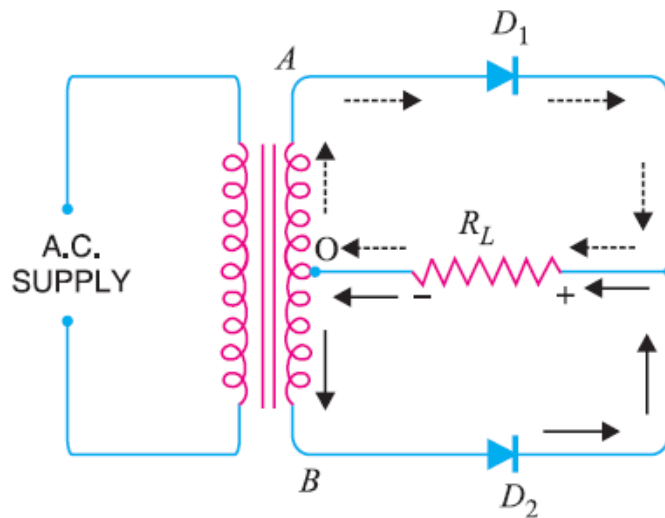

# Centre-Tap Full Wave Rectifier



# Centre-Tap Full Wave Rectifier

□ **Ripple Factor**

# Centre-Tap Full Wave Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

# Centre-Tap Full Wave Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

## □ Transformer with centre-tap is needed.

# Centre-Tap Full Wave Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

□ Transformer with centre-tap is needed.

□ The diodes must have high PIV ( $2V_m$ ).

# Centre-Tap Full Wave Rectifier

## ❑ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$


❑ Transformer with centre-tap is needed.

❑ The diodes must have high PIV ( $2V_m$ ).

❑ The DC output is small because each diode utilizes only one half of the transformer's secondary voltage



# Full Wave Bridge Rectifier

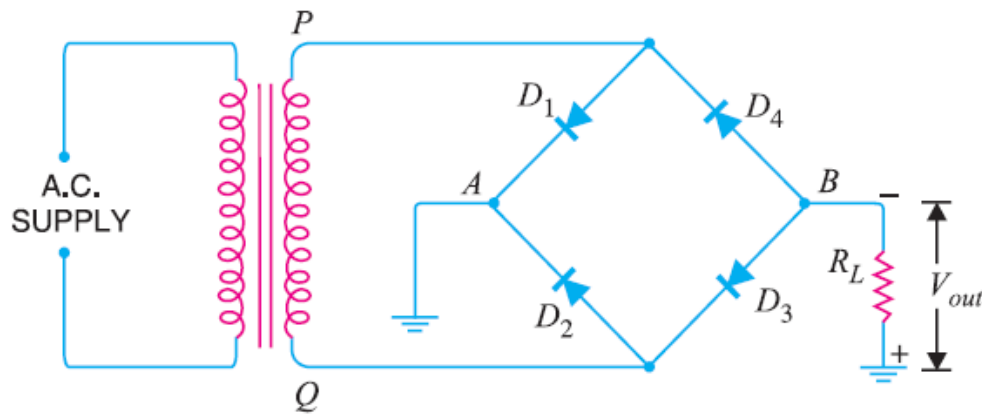



# Full Wave Bridge Rectifier

# Full Wave Bridge Rectifier

## □ Ripple Factor

# Full Wave Bridge Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

# Full Wave Bridge Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

## □ Need for centre tapped transformer is eliminated

# Full Wave Bridge Rectifier

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

□ Need for centre tapped transformer is eliminated

□ The output is twice that of centre tap circuit for same secondary voltage.



# Full Wave Bridge Rectifier

## ❑ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

- ❑ Need for centre tapped transformer is eliminated
- ❑ The output is twice that of centre tap circuit for same secondary voltage.
- ❑ The PIV is half that of centre tap circuit (for same DC output).



# Full Wave Bridge Rectifier

## ❑ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

- ❑ Need for centre tapped transformer is eliminated
- ❑ The output is twice that of centre tap circuit for same secondary voltage.
- ❑ The PIV is half that of centre tap circuit (for same DC output).
- ❑ It requires 4 diodes.

# Rectifier Efficiency

$$\text{Rectifier Efficiency} = \frac{\text{DC Power Output}}{\text{Input AC Power}}$$

# Rectifier Efficiency

$$\text{Rectifier Efficiency} = \frac{\text{DC Power Output}}{\text{Input AC Power}}$$

**Assuming diodes to be ideal.**

# Rectifier Efficiency

$$\text{Rectifier Efficiency} = \frac{\text{DC Power Output}}{\text{Input AC Power}}$$

**Assuming diodes to be ideal.**

**Rectifier efficiency of half wave rectifier is 40.6%.**

# Rectifier Efficiency

$$\text{Rectifier Efficiency} = \frac{\text{DC Power Output}}{\text{Input AC Power}}$$

**Assuming diodes to be ideal.**

**Rectifier efficiency of half wave rectifier is 40.6%.**

**Rectifier efficiency of full wave rectifier is 81.2%.**



# Filters



# Filters

# Filters

- ❑ The rectifier produces a pulsating DC with high ripple content.

# Filters



- ❑ The rectifier produces a pulsating DC with high ripple content.
- ❑ There filter is used to reduce pulsations and create almost a smooth DC output across the load.

# Filters

- ❑ The rectifier produces a pulsating DC with high ripple content.
- ❑ There filter is used to reduce pulsations and create almost a smooth DC output across the load.
- ❑ The most common filter is a large capacitor

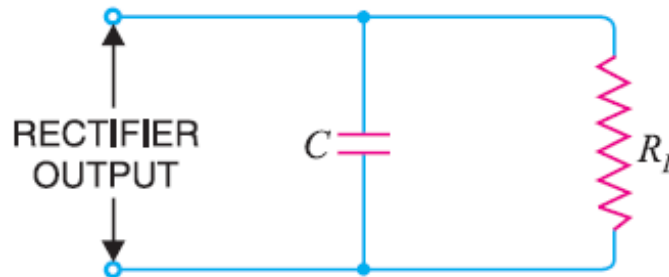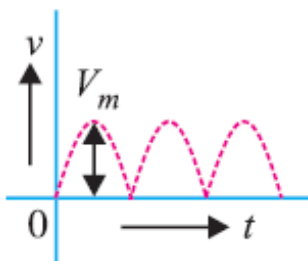
# Filters

- ❑ The rectifier produces a pulsating DC with high ripple content.
- ❑ There filter is used to reduce pulsations and create almost a smooth DC output across the load.
- ❑ The most common filter is a large capacitor






# Capacitor Filter

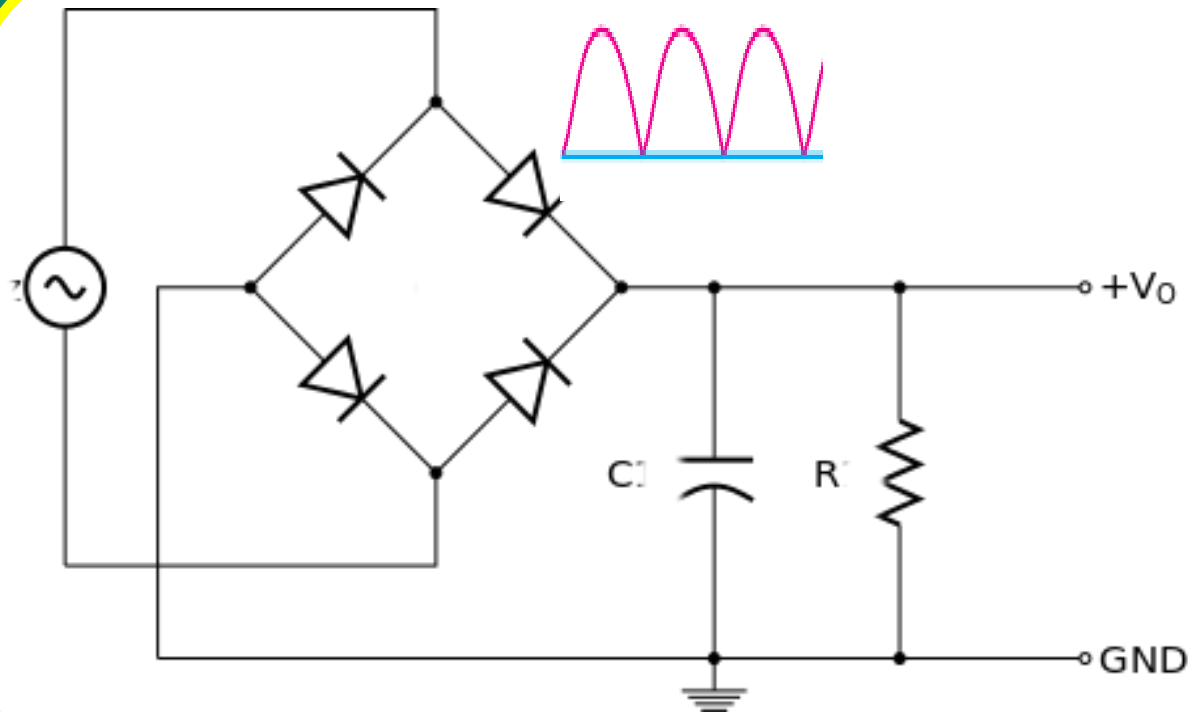



# Capacitor Filter

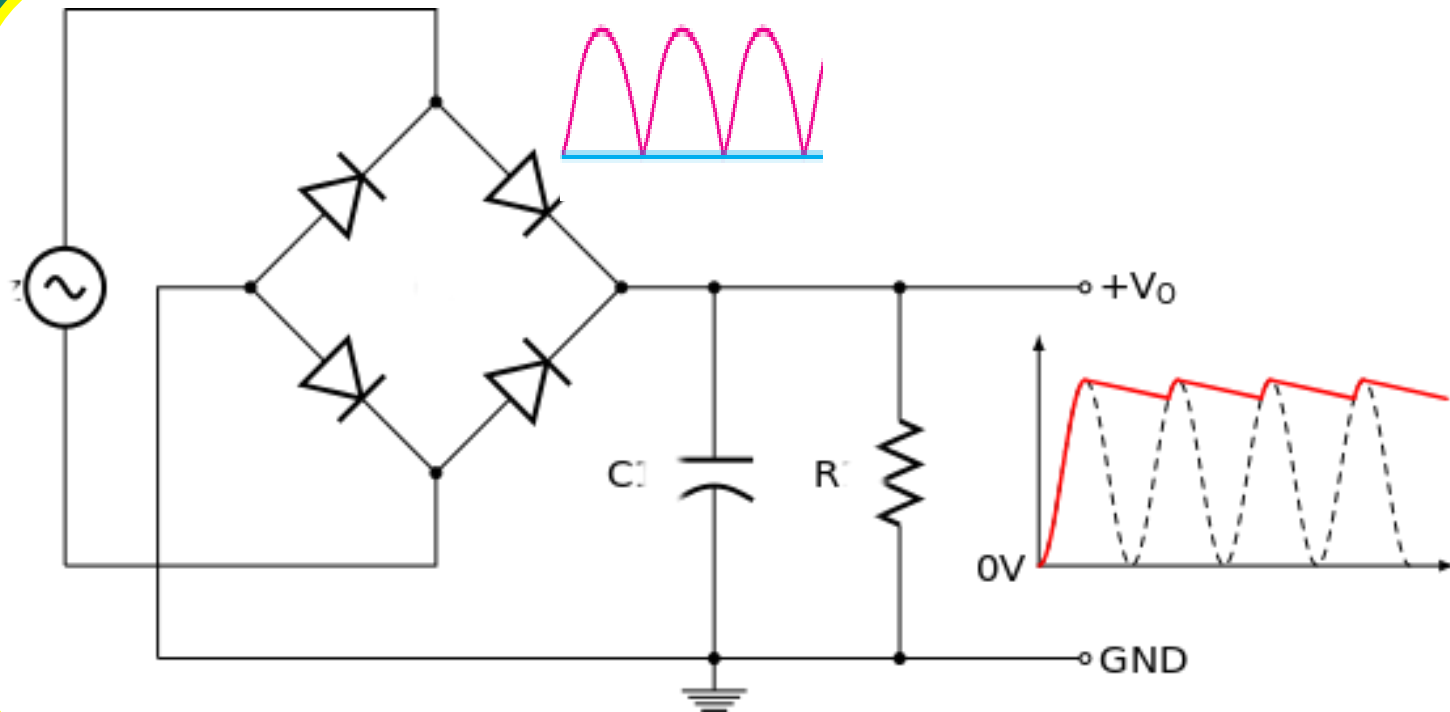

# Capacitor Filter

## □ Ripple Factor (Full Wave Rectifier)

# Capacitor Filter

## □ Ripple Factor (Full Wave Rectifier)

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{4\sqrt{3} fRC}$$

# Capacitor Filter

## □ Ripple Factor (Full Wave Rectifier)

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{4\sqrt{3} fRC}$$

□ Larger the value of capacitor, lesser will be the ripple.

# Capacitor Filter


## ❑ Ripple Factor (Full Wave Rectifier)

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{4\sqrt{3} fRC}$$

❑ Larger the value of capacitor, lesser will be the ripple.


❑ If the load is connected across the filter, the power supply is termed as unregulated power supply.

# Half Wave Rectifier with Filter

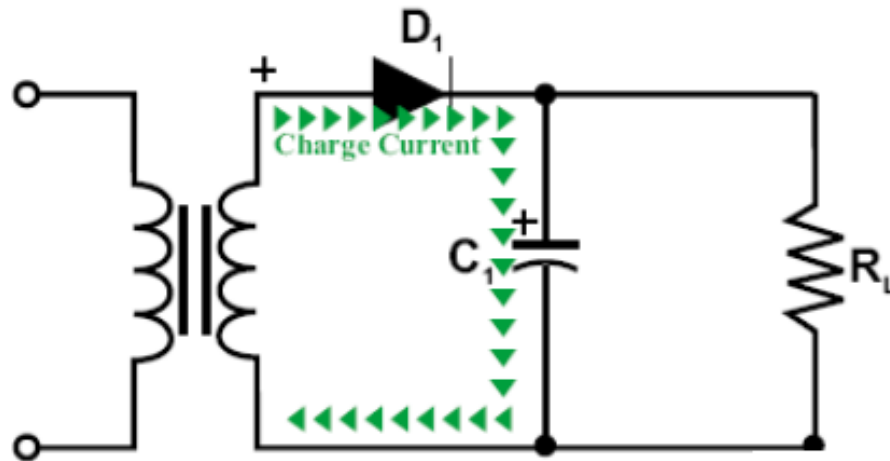




# Half Wave Rectifier with Filter

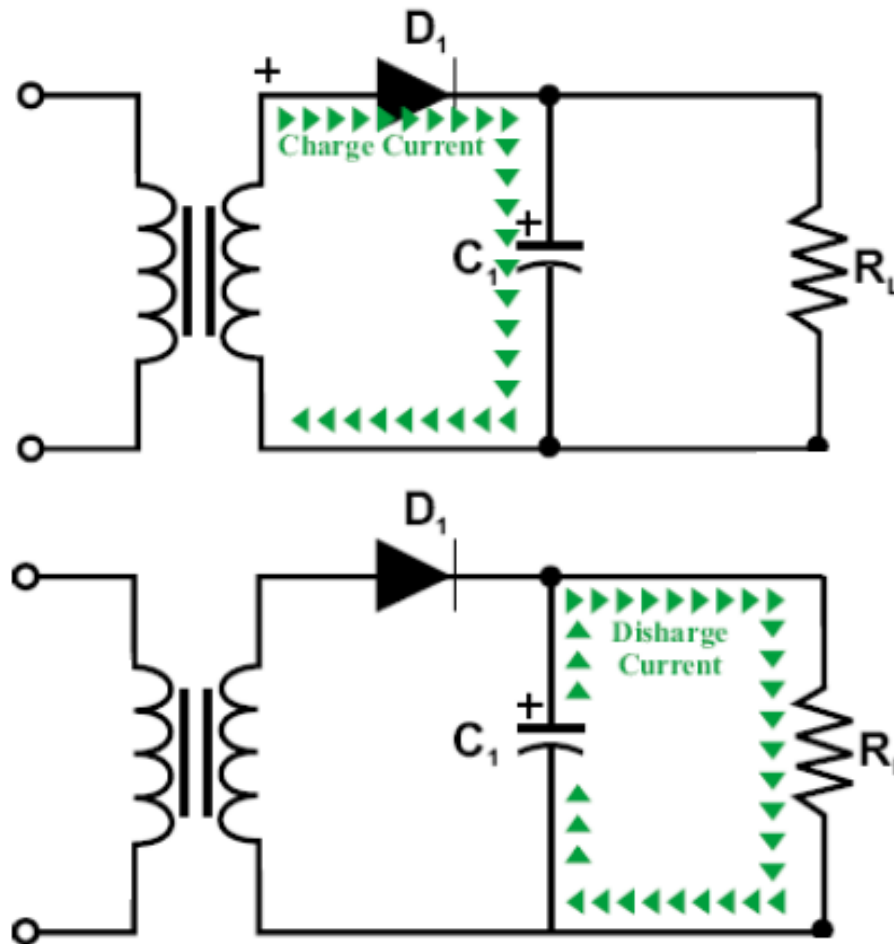

# Half Wave Rectifier with Filter

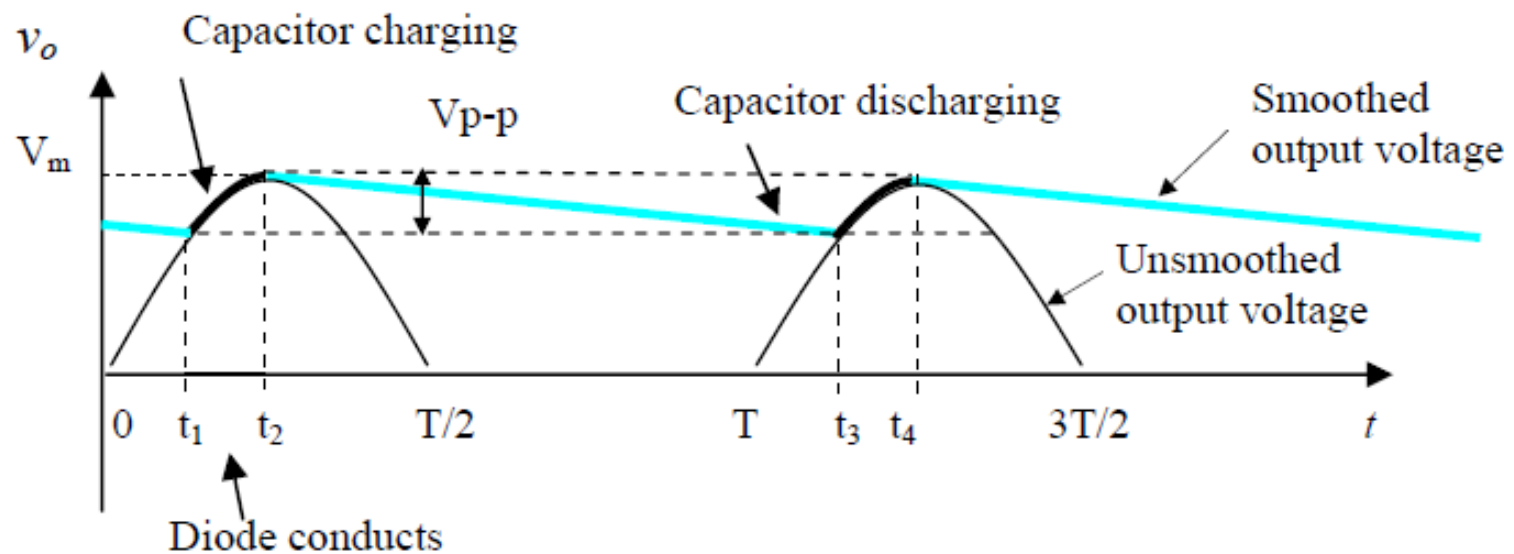

# Half Wave Rectifier with Filter

- Charge removed from the capacitor during discharge cycle ( $t_2$  to  $t_3$ )

# Half Wave Rectifier with Filter

- Charge removed from the capacitor during discharge cycle ( $t_2$  to  $t_3$ )

$$\Delta Q = I_L(t_3 - t_2) \cong I_L T$$

# Half Wave Rectifier with Filter

- Charge removed from the capacitor during discharge cycle ( $t_2$  to  $t_3$ )

$$\Delta Q = I_L(t_3 - t_2) \cong I_L T$$

where  $I_L$  is the average load current and  $T$  is the time period of the AC voltage.



# Half Wave Rectifier with Filter

- Charge removed from the capacitor during discharge cycle ( $t_2$  to  $t_3$ )

$$\Delta Q = I_L(t_3 - t_2) \cong I_L T$$

where  $I_L$  is the average load current and  $T$  is the time period of the AC voltage.

$$I_L = \frac{V_{avg}}{R_L} \cong \frac{V_m}{R_L}$$



# Half Wave Rectifier with Filter

- Charge removed from the capacitor can also be expressed as

# Half Wave Rectifier with Filter

- Charge removed from the capacitor can also be expressed as

$$\Delta Q = V_{p-p} C$$

# Half Wave Rectifier with Filter

- Charge removed from the capacitor can also be expressed as

$$\Delta Q = V_{p-p} C$$

where  $V_{p-p}$  is peak to peak ripple.

# Half Wave Rectifier with Filter

- Charge removed from the capacitor can also be expressed as

$$\Delta Q = V_{p-p} C$$

where  $V_{p-p}$  is peak to peak ripple.

- Therefore C can be calculated as

# Half Wave Rectifier with Filter

- Charge removed from the capacitor can also be expressed as

$$\Delta Q = V_{p-p} C$$

where  $V_{p-p}$  is peak to peak ripple.

- Therefore  $C$  can be calculated as

$$C = \frac{I_L T}{V_{p-p}} \text{ Farads}$$



# Half Wave Rectifier with Filter

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2\sqrt{3} fRC}$$



# Half Wave Rectifier with Filter

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2\sqrt{3} fRC}$$

□ Larger the value of capacitor, lesser will be the ripple.


# Half Wave Rectifier with Filter

## □ Ripple Factor


$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2\sqrt{3} fRC}$$

- Larger the value of capacitor, lesser will be the ripple.
- If the load is connected across the filter (without regulator), the power supply is termed as unregulated power supply.

# Full Wave Rectifier with Filter

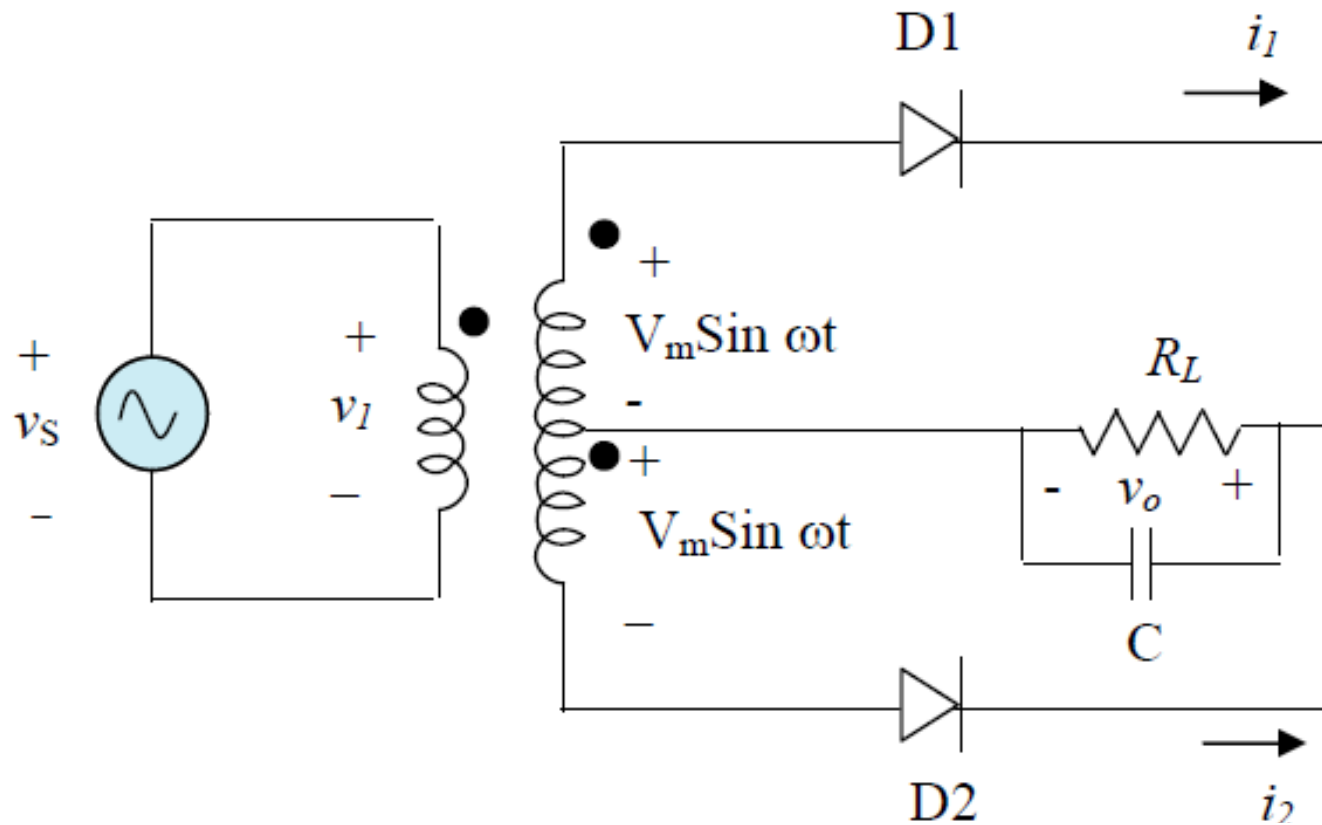

# Full Wave Rectifier with Filter

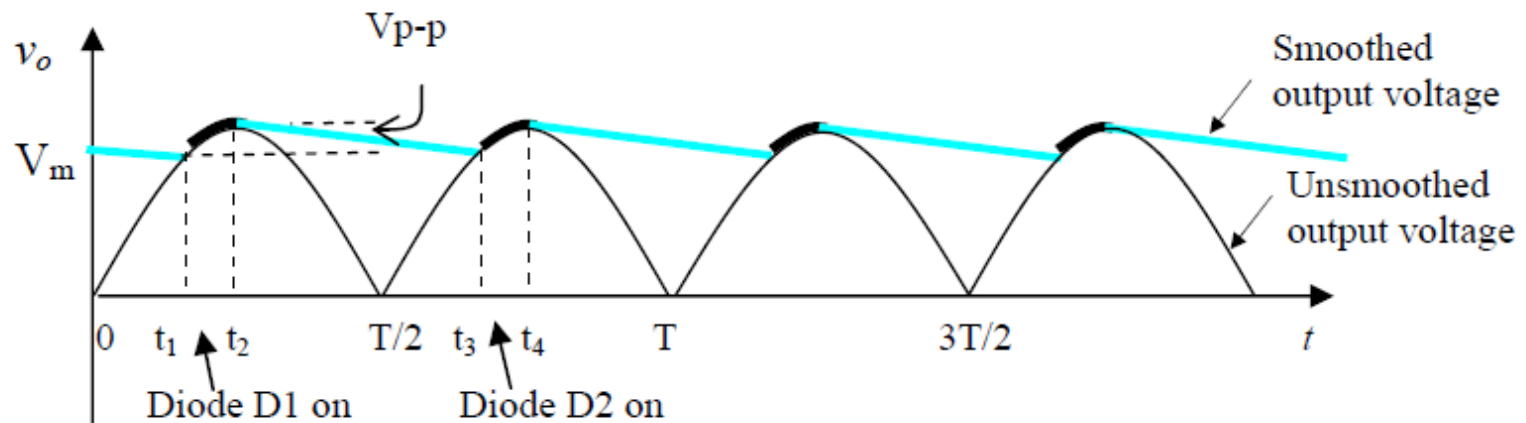

# Full Wave Rectifier with Filter

## ☐ Ripple Factor



# Full Wave Rectifier with Filter

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{4\sqrt{3} fRC}$$



# Full Wave Rectifier with Filter

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{4\sqrt{3} fRC}$$

□ Larger the value of capacitor, lesser will be the ripple.

# Full Wave Rectifier with Filter

## □ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{4\sqrt{3} fRC}$$

□ Larger the value of capacitor, lesser will be the ripple.

□ If the load is connected across the filter, the power supply is termed as unregulated power supply.