

Basic Electronic Circuits Lab

(IEC-103)

Experiment-06

Objective

To build a Wein bridge oscillator.



Components

- **Op-amp ICs (741)**
- **Resistances** ($1\text{K}\Omega$ (2), $1.5\text{K}\Omega$, $2.2\text{K}\Omega$ (2), & $1\text{K}\Omega$ pot)
- **Capacitors** ($0.1\ \mu\text{F}$ (2) **and** $0.01\ \mu\text{F}$ (2))
- **Breadboard**
- **Connecting wires**


Equipment

- **Regulated Power supplies (± 12 V) to power up op-amp.**
- **CRO for voltage measurements.**


741 Op Amp IC

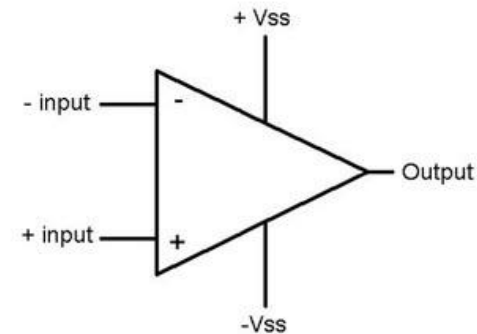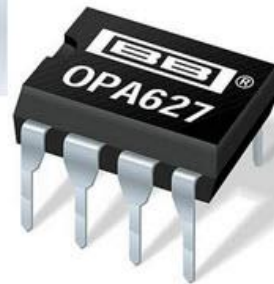

OP-AMP

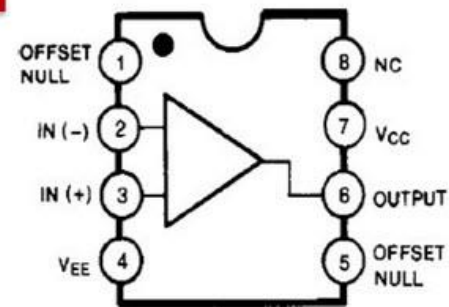


741 Op Amp IC (Pin Diagram)

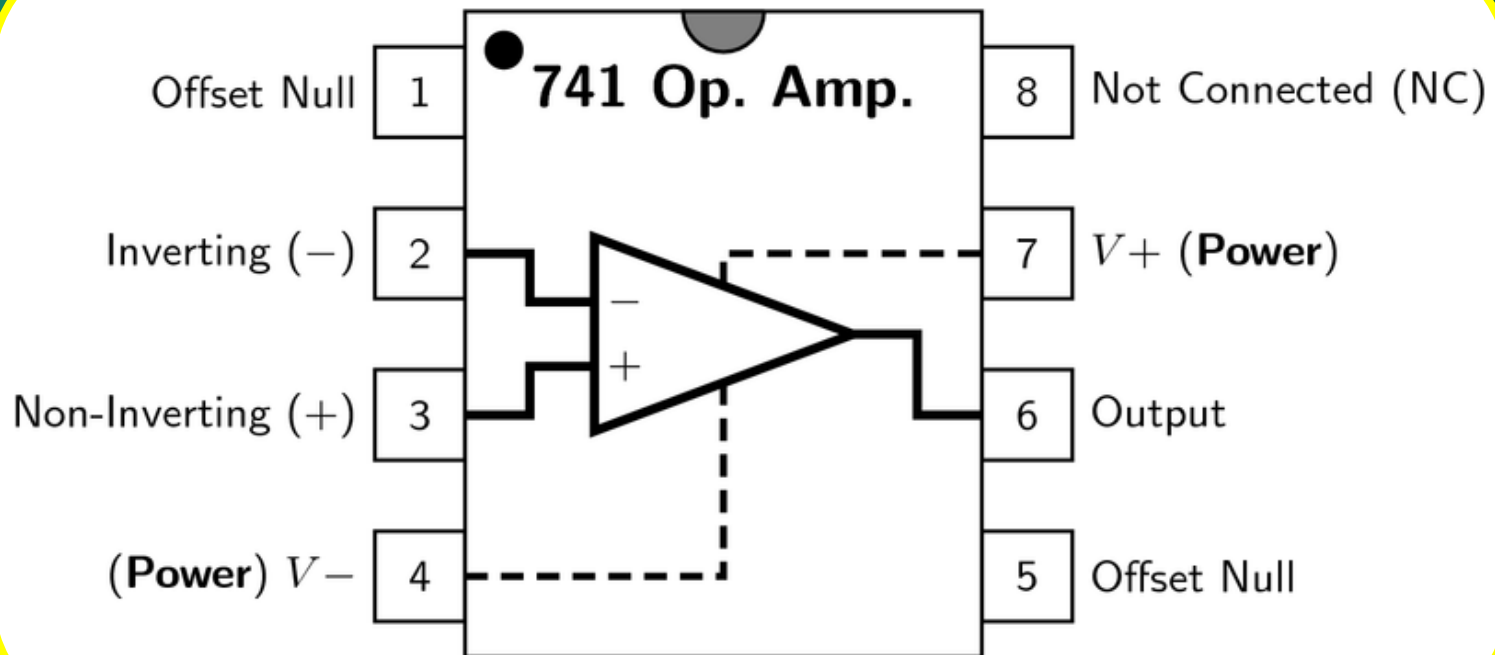


Power Supply (Fixed)

Power Supply

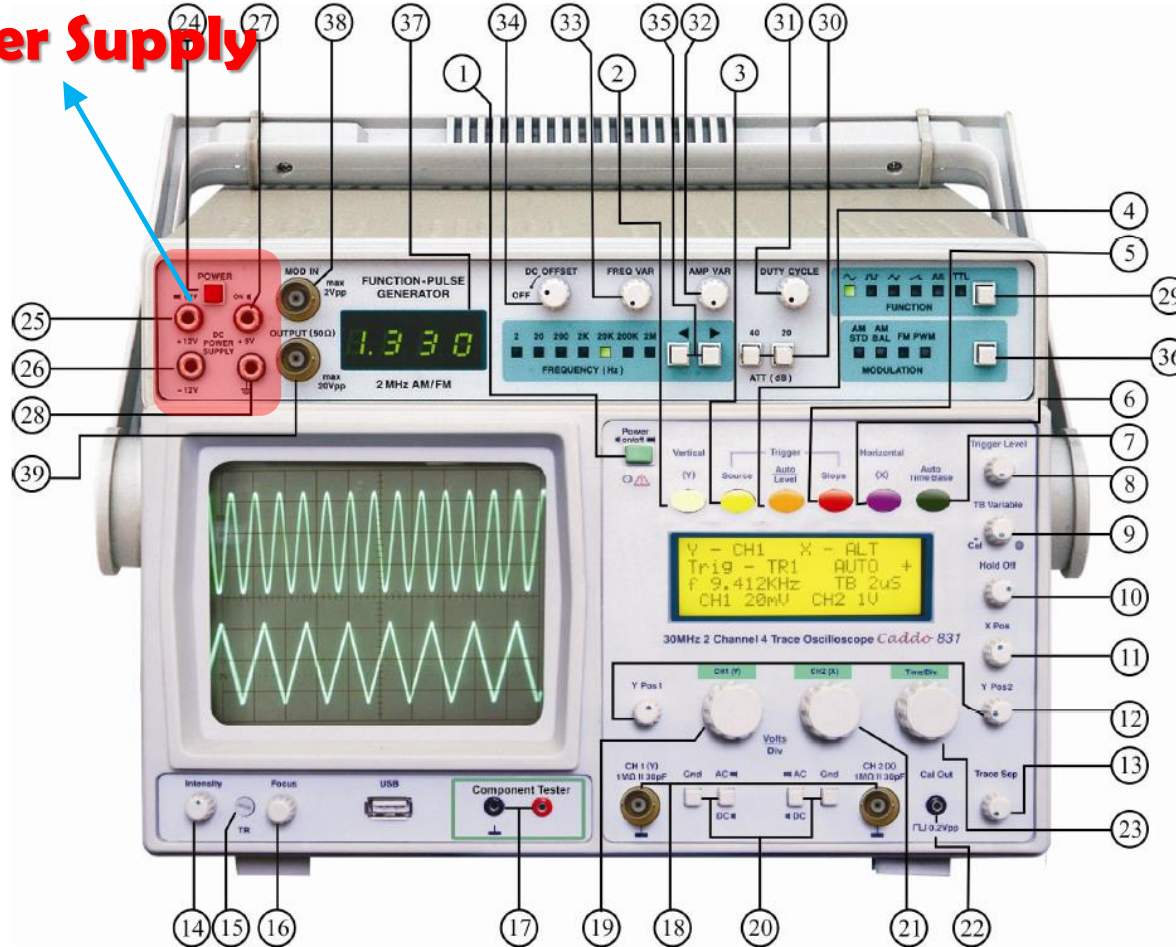


Oscilloscope

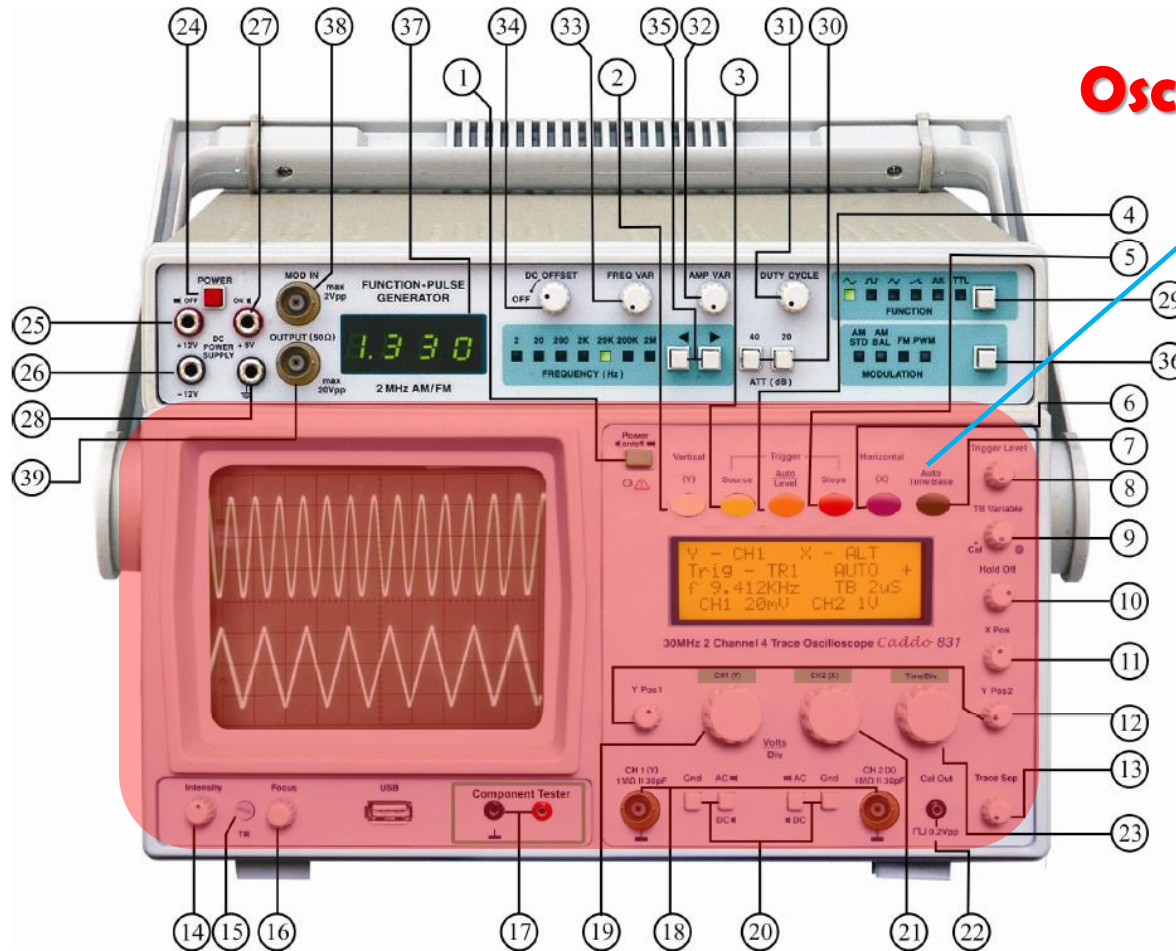

Oscilloscope

Wein Bridge Oscillator

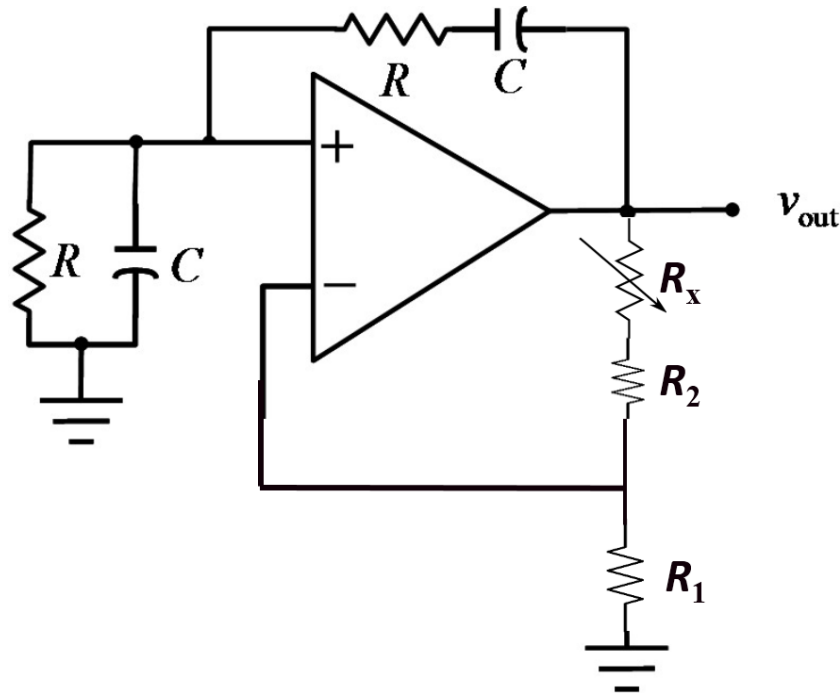

$R = (1 \text{ k}\Omega, 2 \text{ k}\Omega)$, $C = (0.1 \text{ }\mu\text{F}, 0.01 \text{ }\mu\text{F})$, $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$ and $R_x = 1 \text{ k}\Omega$ pot

Wein Bridge Oscillator (f)

Frequency of the oscillations

$$f = \frac{1}{2\pi RC}$$

Observations

Sr. No.	R	C	R ₁	R ₂	R _x	T (measured)	f = 1/T	f (theoretical)
1	1 KΩ	0.1 μF	1 KΩ	1.5 KΩ	1 KΩ pot			
2	1 KΩ	0.01 μF	1 KΩ	1.5 KΩ	1 KΩ pot			
3	2.2 KΩ	0.1 μF	1 KΩ	1.5 KΩ	1 KΩ pot			
3	2.2 KΩ	0.01 μF	1 KΩ	1.5 KΩ	1 KΩ pot			