

Solutions to Tutorial Sheet-9

IEC103

Q1. Determine the dc current gain  $\beta_{DC}$  and emitter current  $I_E$  of a transistor whose  $I_B = 50 \mu A$  and  $I_C = 3.65 mA$

Sol. 
$$\beta_{DC} = \frac{I_C}{I_B} = \frac{3.65 mA}{50 \mu A} = \frac{3.65}{50} \times 10^3 = 73$$

$$\begin{aligned} I_E &= I_C + I_B = 3.65 mA + 50 \mu A \\ &= 3.65 + 0.05 mA \\ &= 3.7 mA \end{aligned}$$

Q2) Sketch an ideal family of collector curves for the circuit shown in Fig. Q2a) for  $I_B = 5\mu A$  to  $25\mu A$  in  $5\mu A$  increments. Assume  $\beta_{DC} = 100$  and that  $V_{CE}$  does not exceed breakdown.

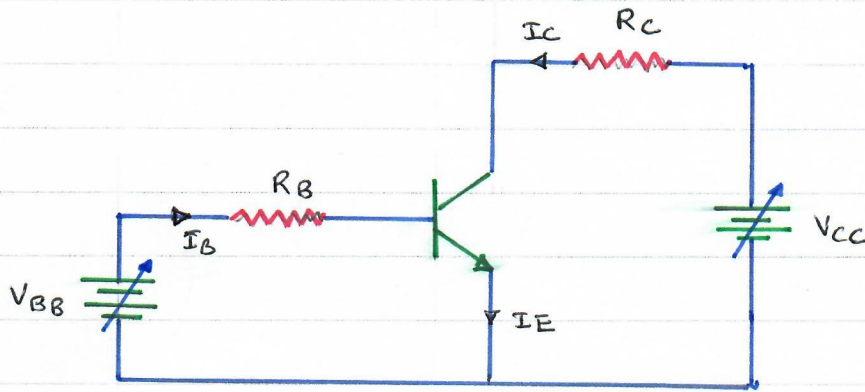


Fig. Q2a)

Sol. Using the relationship  $I_C = \beta_{DC} I_B$  values of  $I_C$  are calculated and tabulated in the Table below. The resulting curves are plotted in Fig. Q

$I_B$	$I_C$
$5\mu A$	$0.5mA$
$10\mu A$	$1.0mA$
$15\mu A$	$1.5mA$
$20\mu A$	$2.0mA$
$25\mu A$	$2.5mA$

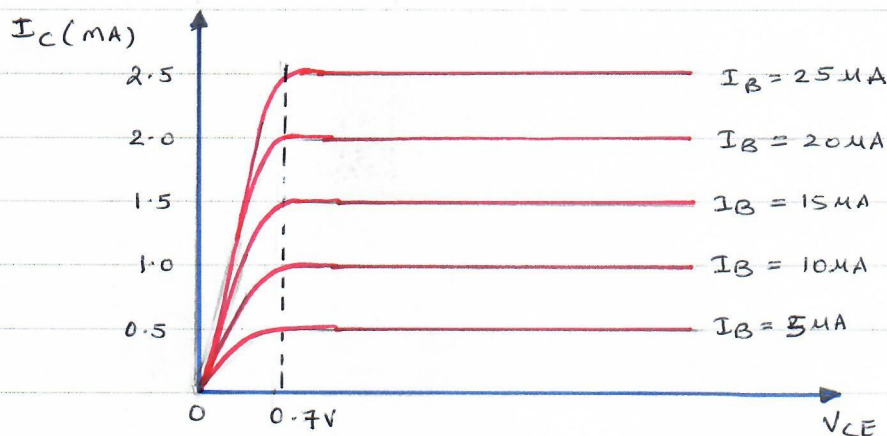


Fig. Q2b)

Q3. Determine the values of  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$  and  $V_{CB}$  in the circuit shown in Fig. Q below. The transistor is a silicon transistor with  $\beta_{DC} = 150$ .

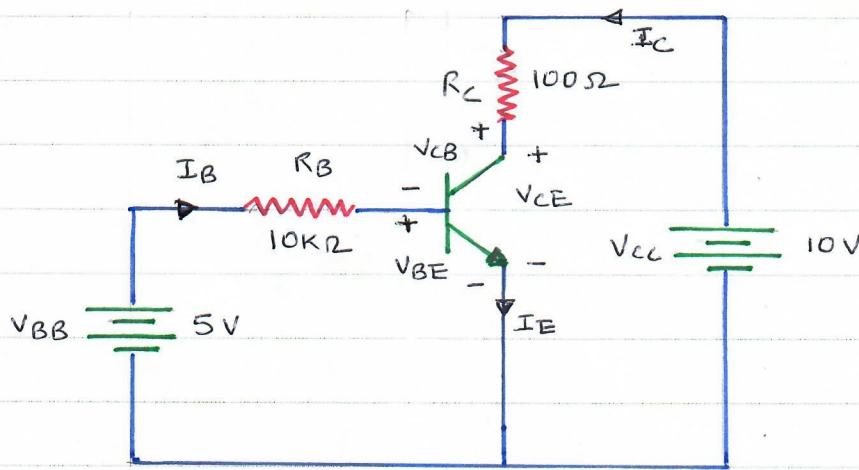


Fig. Q

Sol. 
$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 - 0.7}{10K} = \frac{4.3}{10} \text{ mA} = 0.43 \text{ mA}$$

$$I_C = \beta_{DC} I_B = 150 \times 0.43 \text{ mA} = 64.5 \text{ mA}$$

$$I_E = I_C + I_B = 64.5 + 0.43 \text{ mA} = 64.93 \text{ mA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_C = 10 - 64.5 \times 10^{-3} \times 100 = 3.55 \text{ V}$$


$$V_{CB} = V_{CE} - V_{BE} = 3.55 - 0.7 = 2.85 \text{ V}$$



(Q4) For the transistor circuit shown in Fig. Q4, find

- $V_{CB}$ , is collector base junction forward or reverse biased
- Power consumed by transistor.

Neglect leakage current.

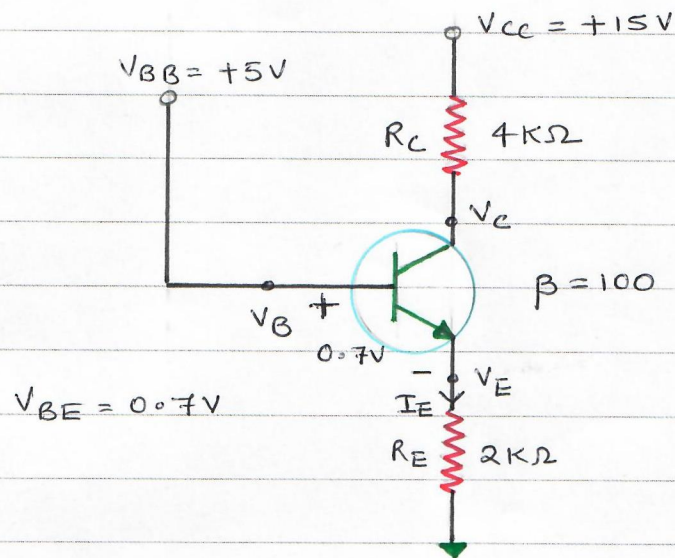

Sol.

i)

$$V_B = V_{BE} + I_E R_E$$

$$= 0.7 + I_E \times 2 \times 10^3 = 5$$

$$\Rightarrow I_E = \frac{5 - 0.7}{2} \text{ mA} = \frac{4.3}{2} = 2.15 \text{ mA}$$

$$\beta = \frac{\alpha}{1 - \alpha} \Rightarrow \alpha = \frac{\beta}{1 + \beta} = \frac{100}{101}$$

$$I_C = \alpha I_E = \frac{100}{101} \times 2.15 \text{ mA} = \frac{2.15}{101} \text{ mA} = 2.1287 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C$$

$$= 15 - \frac{2.15}{101} \times 10^{-3} \times 4 \times 10^3$$

$$= 15 - \frac{8.60}{101} = 6.4851 \text{ V}$$

$$V_{CB} = V_C - V_B = 6.4851 - 5 = 1.4851$$

The transistor is an NPN transistor, collector is at higher potential

than base, so the collector-base junction is reverse biased.

ii) Power dissipated by the transistor is difference between the input power by the supplies and the power dissipated by resistors.

$$P_{\text{transistor}} = P_{\text{supply}} - P_{\text{resistors}}$$

$$P_{\text{supplied}} = V_{BB} I_B + V_{CC} I_C$$

↪

$$I_B = \frac{I_C}{\beta} = \left( \frac{215}{101} \right) \text{ mA} = \frac{215}{101 \times 100} \text{ mA} = 21.287 \mu\text{A}$$

$$V_{BB} = 5\text{V}; V_{CC} = 15\text{V}; I_B = 21.287 \mu\text{A}; I_C = 2.1287 \text{ mA}$$

$$P_{\text{supplied}} = 5 \times 21.287 \times 10^{-6} + 15 \times 2.1287 \times 10^{-3} = 0.032037 \text{ W}$$

$$\begin{aligned} P_{\text{resistors}} &= I_C^2 R_C + I_E^2 R_E \\ &= (2.1287 \times 10^{-3})^2 \times 4 \times 10^3 + (2.15 \times 10^{-3})^2 \times 2 \times 10^3 \\ &= 4.5314 \times 10^{-6} \times 4 \times 10^3 + 4.6225 \times 10^{-6} \times 2 \times 10^3 \\ &= 18.126 \times 10^{-3} + 9.245 \times 10^{-3} \\ &= 27.37 \times 10^{-3} = 0.027371 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{\text{transistor}} &= P_{\text{supplied}} - P_{\text{resistors}} \\ &= 0.032037 - 0.027371 \\ &= 0.004666 \text{ W} \\ &= 4.666 \text{ mW} \end{aligned}$$