

Solutions to Quiz-1 Paper (Group-B)

IEC103

Q1) Find the input resistance of between the terminals B and G_1 in the circuit shown in Fig. Q1.


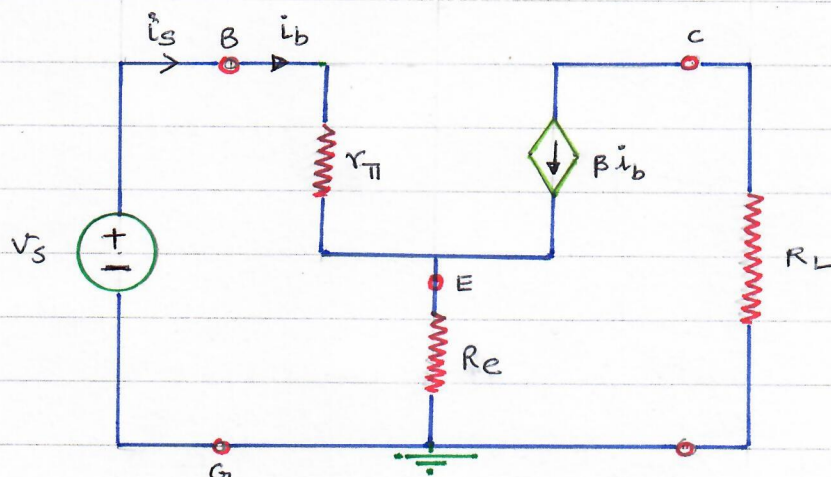


Fig. Q1

Sol.

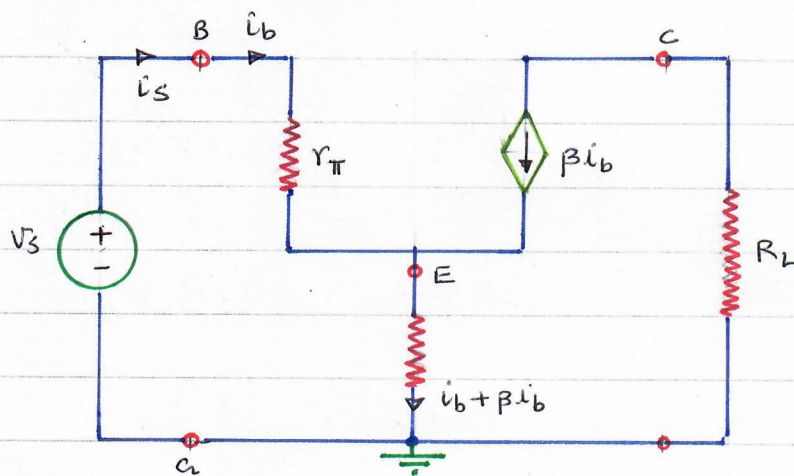

Input resistance between terminals B and G_1 is the resistance seen by the source V_S .

$$R_{in} = \frac{V_S}{i_s}$$

$$\begin{aligned} V_S = V_{BG_1} &= r_{\pi} i_b + (\beta + 1) i_b R_e \\ &= [r_{\pi} + (\beta + 1) R_e] i_b \end{aligned}$$

$$i_s = i_b$$

$$\therefore V_S = [r_{\pi} + (\beta + 1) R_e] i_s$$

$$\Rightarrow R_{in} = V_S / i_s = r_{\pi} + (\beta + 1) R_e$$

Q2) Assuming op-amp to be ideal, find the current gain i_L/i_I , in the circuit shown in Fig. Q. Find the value of R required for having a current gain (i_L/i_I) equal to 20 A/A.


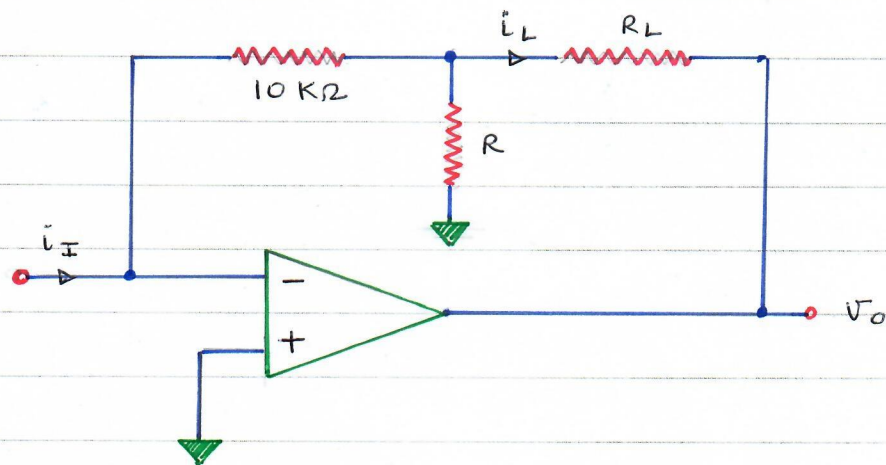


Fig. Q2

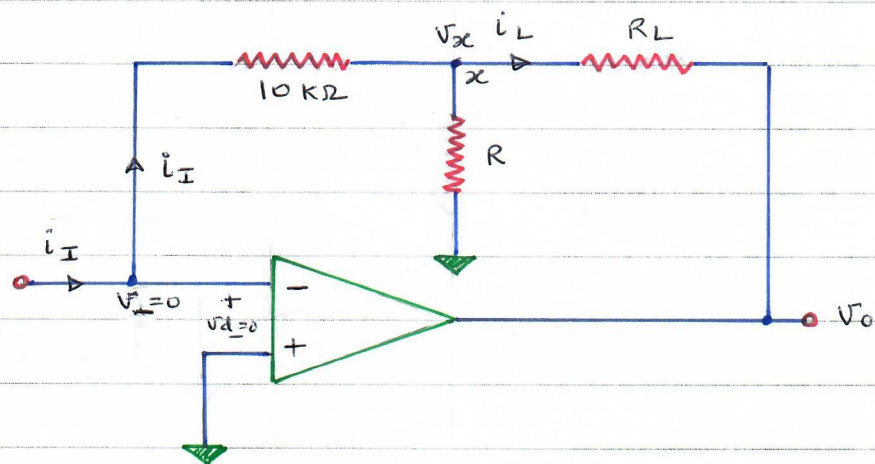Sol. Since the op-amp is ideal the differential voltage at the input terminals $V_d = V_+ - V_-$ is zero, and the current entering the terminals (input) is zero.



Applying KCL at node x

$$\frac{V_x - 0}{10K} + \frac{V_x}{R} + \frac{V_x - V_O}{R_L} = 0 \quad \dots (A)$$

$$\Rightarrow -i_I + \frac{V_x}{R} + i_L = 0 \quad \dots (B)$$

$$\text{but } V_x = -10K i_I$$

$$\therefore -i_I - \frac{10K i_I}{R} + i_L = 0$$

$$-i_I - \frac{10K i_I}{R} + i_L = 0$$

$$\Rightarrow i_I \left(1 + \frac{10K}{R} \right) = i_L$$

$$\Rightarrow \text{current gain} = \frac{i_L}{i_I} = 1 + \frac{10K}{R}$$

$$\text{If current gain} = 20$$

$$1 + \frac{10K}{R} = 20$$

$$\Rightarrow \frac{10K}{R} = 19$$

$$\Rightarrow R = \frac{10}{19} K \approx 526 \Omega$$

Q3 Find the voltage gain V_o/V_i of the circuit shown below in Fig. Q3

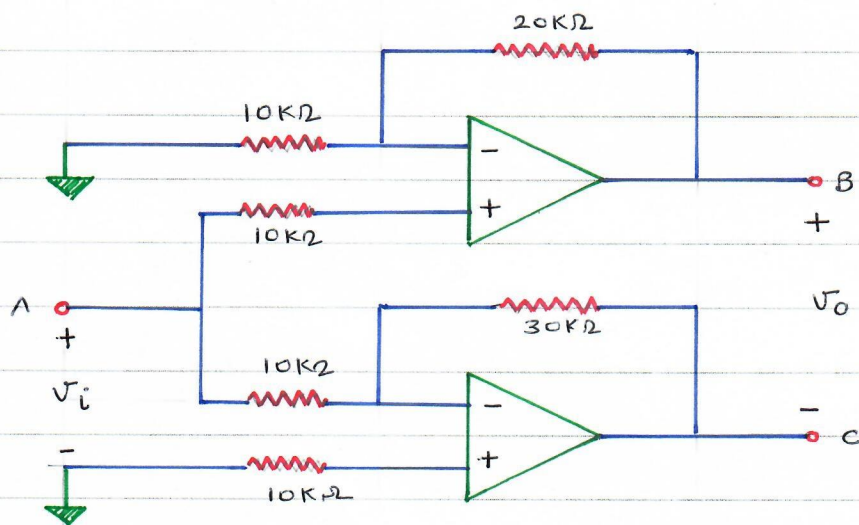


Fig. Q3

Sol.

The top circuit is a non-inverting amplifier and the lower one is an inverting amplifier.

The output of non-inverting amplifier is V_B and that of the inverting amplifier is V_C .

$$V_B = \left(1 + \frac{20K}{10K}\right) V_i = 3V_i$$

$$V_C = -\frac{30K}{10K} V_i = -3V_i$$

$$V_o = V_{BC} = V_B - V_C = 3V_i - (-3V_i) = 6V_i$$

$$\text{voltage gain} = A_v = \frac{V_o}{V_i} = 6$$