


Basic Electronic Circuits

(IEC-103)


Lecture-18

Small Signal Analysis


Analog Audio Amplifier

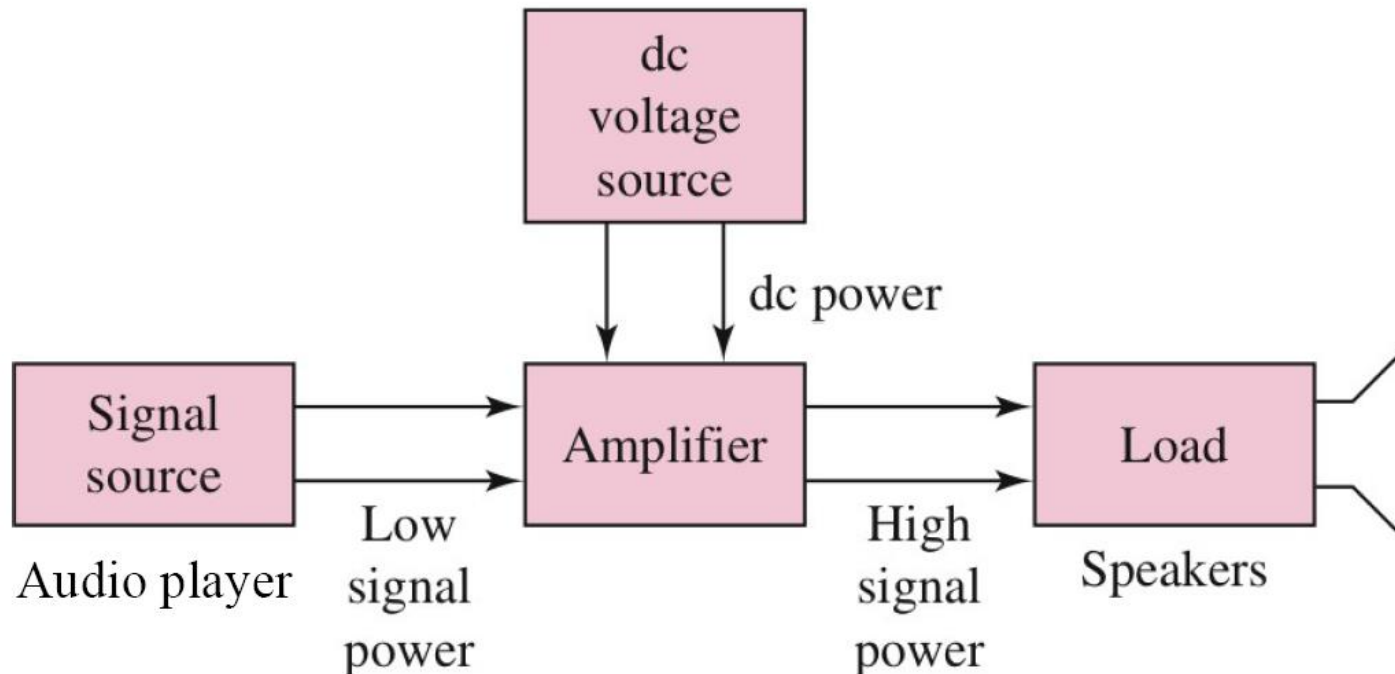


Analog Audio Amplifier

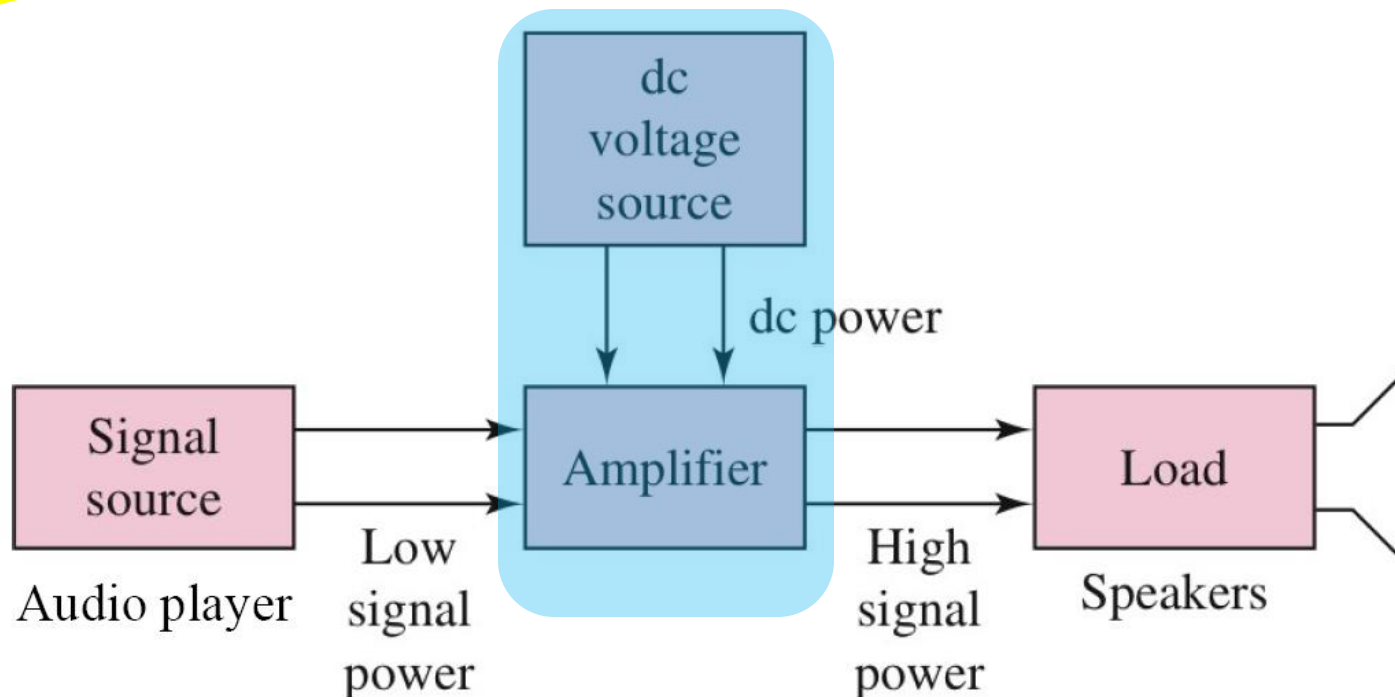

Analog Audio Amplifier

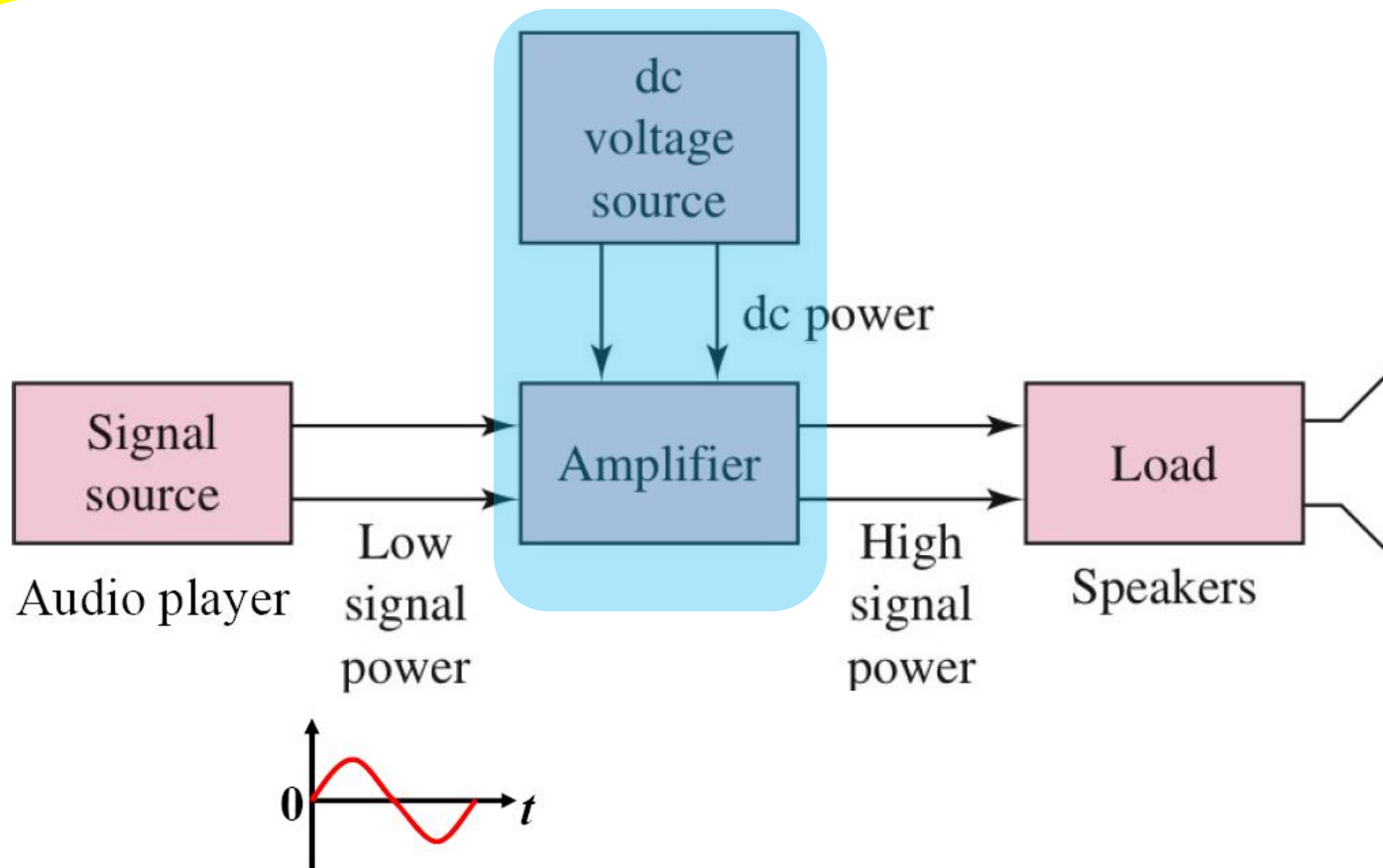

Analog Audio Amplifier

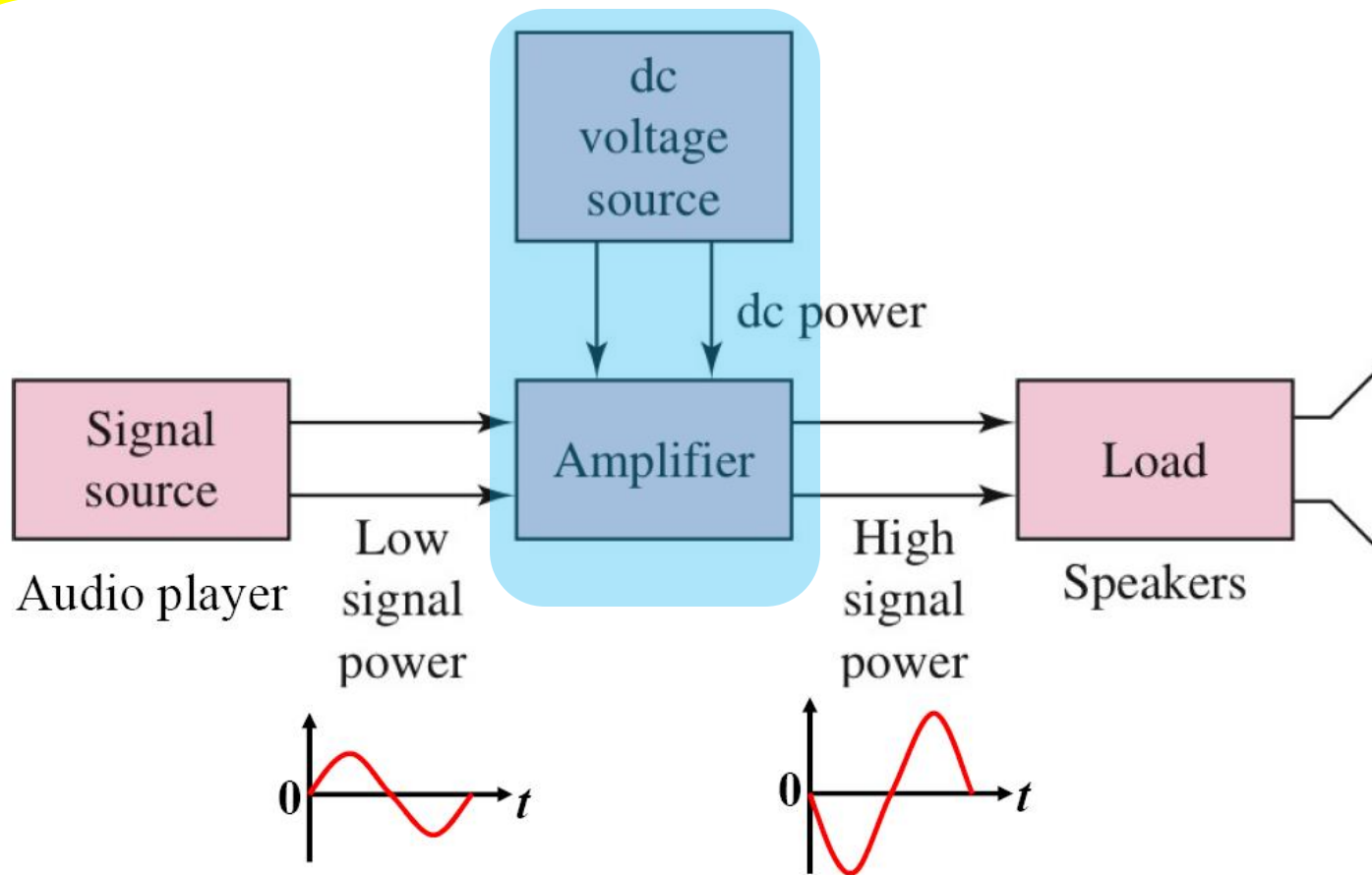

BJT Circuit Analysis

- **DC Analysis:** To fix DC operating point (Q point).
Also called biasing of transistor.


BJT Circuit Analysis

- ❑ **DC Analysis:** To fix DC operating point (Q point). Also called biasing of transistor.
- ❑ **Small Signal Analysis:** Analyze BJT circuits for signals being amplified. Small signal model is used for analysis.


BJT Circuit Analysis

- ❑ **DC Analysis:** To fix DC operating point (Q point). Also called biasing of transistor.
- ❑ **Small Signal Analysis:** Analyze BJT circuits for signals being amplified. Small signal model is used for analysis.
- ❑ **The transistor is biased such a way to operate it in active region if used in amplifier circuit.**

Large Signal Model (BJT) (Active Region)

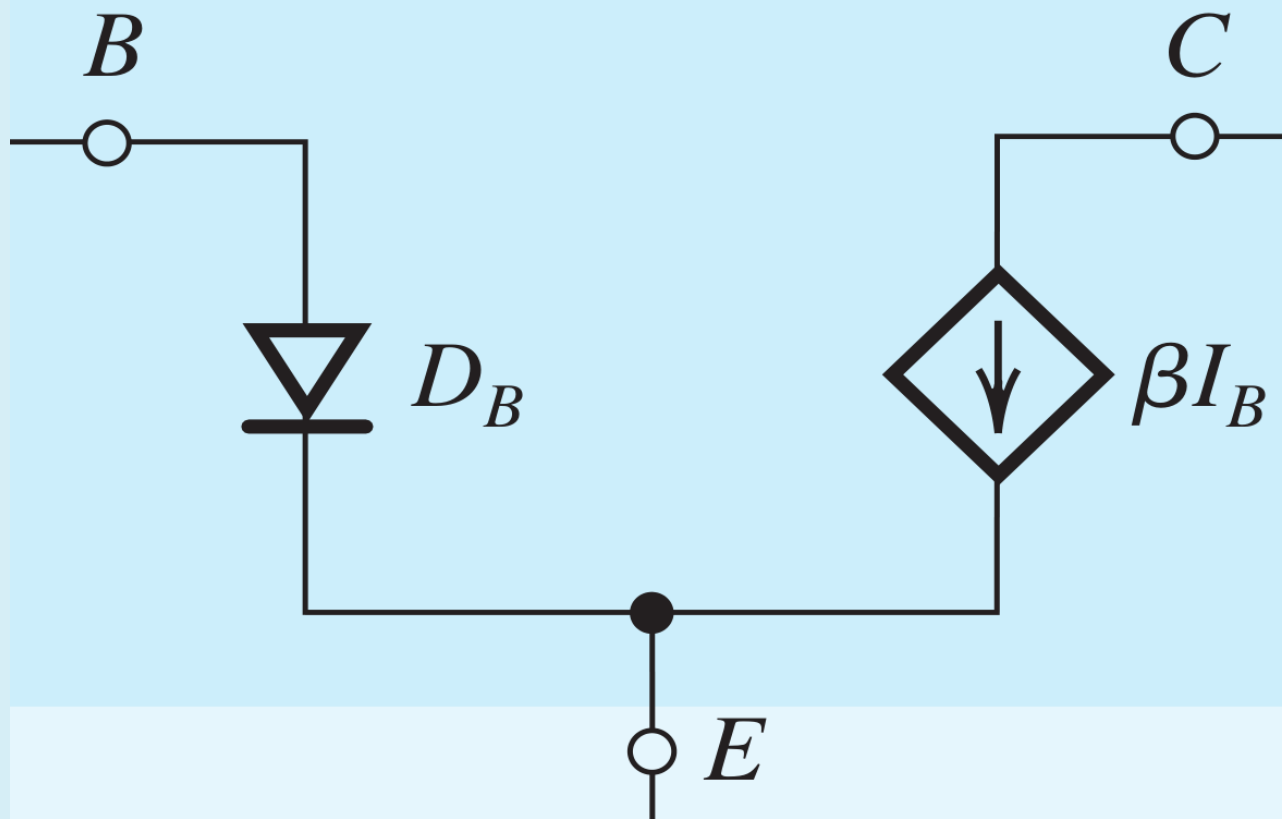


Large Signal DC Analysis (Active Region)


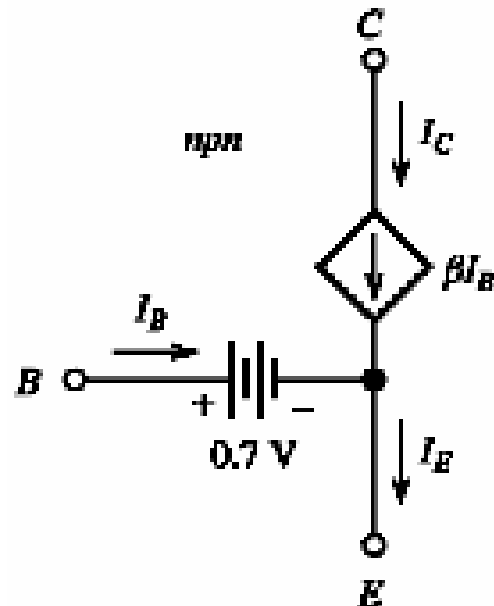


$$I_B > 0$$
$$V_{CE} > 0.2 \text{ V}$$

Large Signal DC Analysis (Active Region)

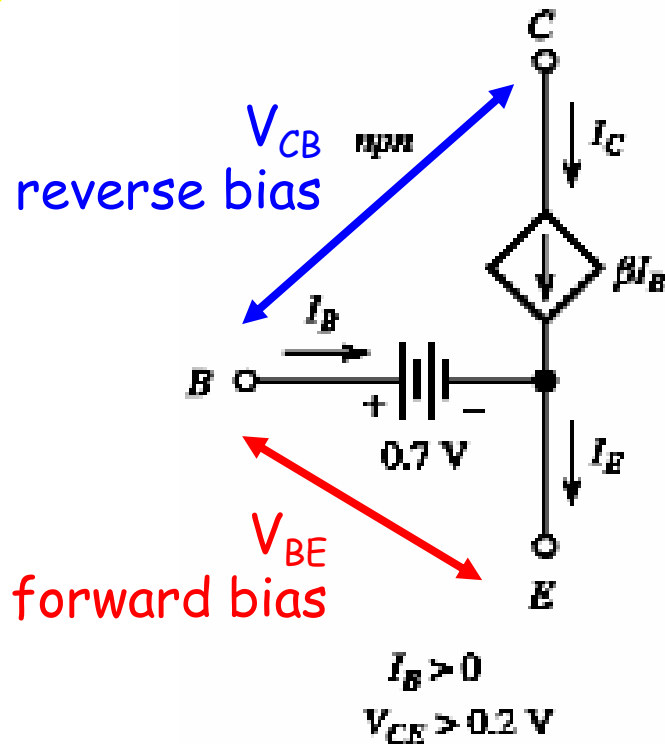


Large Signal DC Analysis (Active Region)

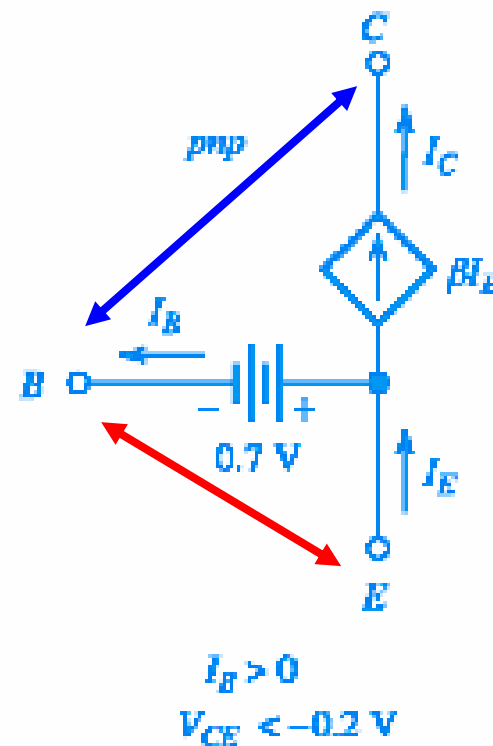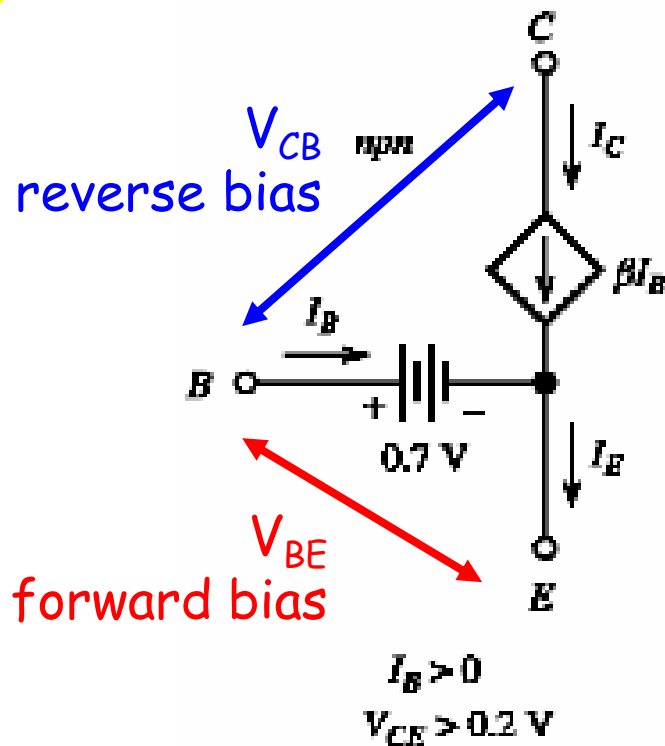

Analysis of BJT Amplifiers


Function of each component

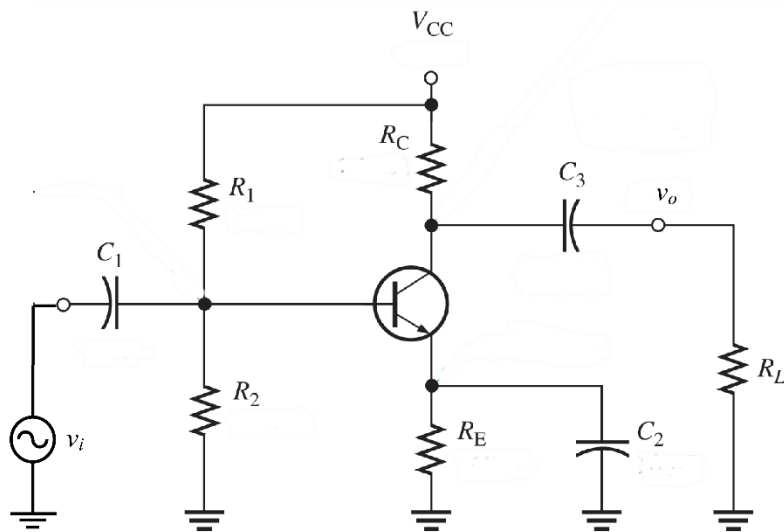

Analysis of BJT Amplifiers

Function of each component

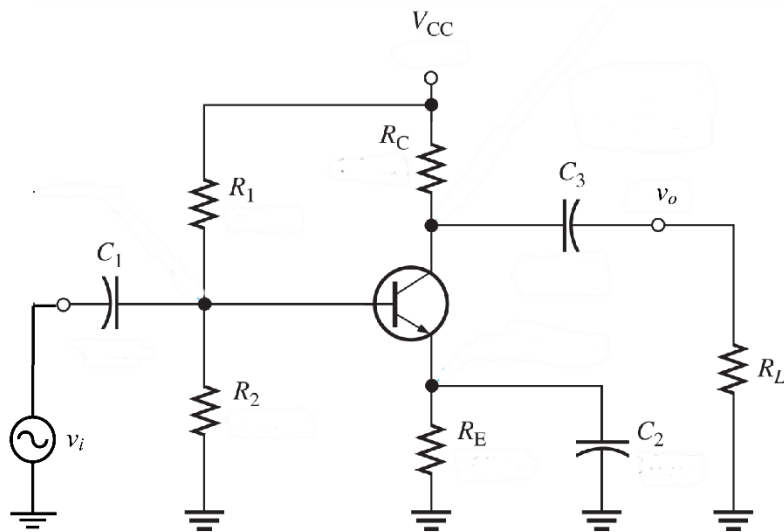- **Capacitors:** Act as an open circuit DC operation and short circuits to AC.




Analysis of BJT Amplifiers

Function of each component


- **Capacitors: Act as an open circuit DC operation and short circuits to AC.**

(If $f = 10 \text{ kHz}$ & $C = 10 \mu\text{F}$, then $|Z_c| = (2\pi fC)^{-1} = 8 \Omega$ which is usually smaller than $R_{TH} = R_1 \parallel R_2$).

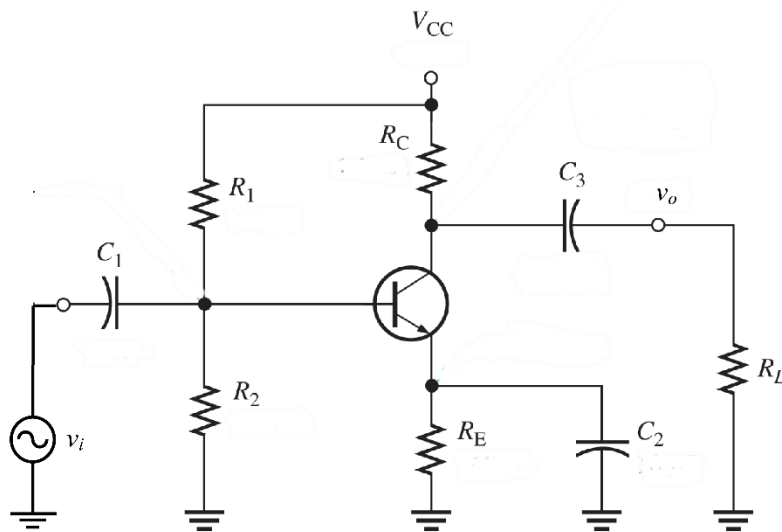

Analysis of BJT Amplifiers


Function of each component

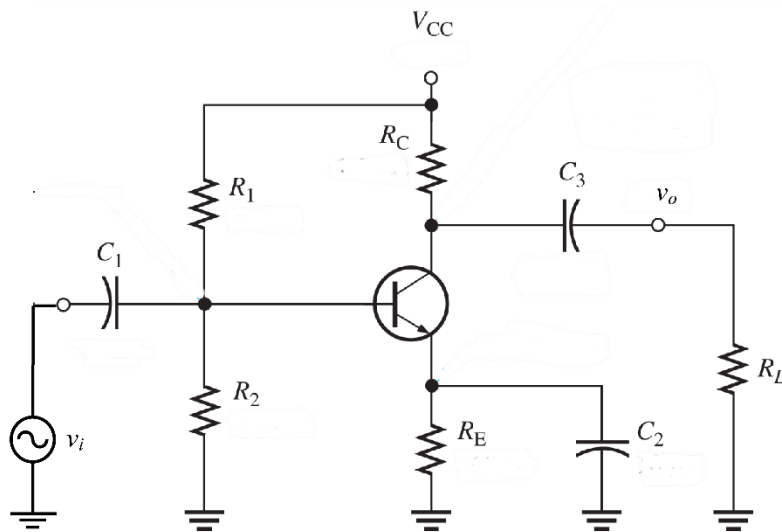

- **Capacitors:** Act as an open circuit DC operation and short circuits to AC.
(If $f = 10 \text{ kHz}$ & $C = 10 \mu\text{F}$, then $|Z_c| = (2\pi fC)^{-1} = 8 \Omega$ which is usually smaller than $R_{TH} = R_1 \parallel R_2$).
- **R_1 , R_2 , R_C , and R_E :** Setting DC biasing Q-Point.


Analysis of BJT Amplifiers

Function of each component

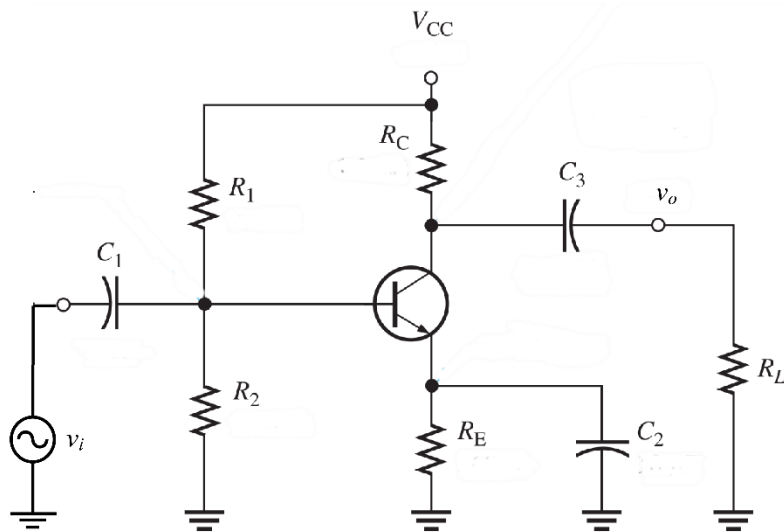

- **Capacitors:** Act as an open circuit DC operation and short circuits to AC.
(If $f = 10 \text{ kHz}$ & $C = 10 \mu\text{F}$, then $|Z_C| = (2\pi fC)^{-1} = 8 \Omega$ which is usually smaller than $R_{TH} = R_1 \parallel R_2$).
- **R_1 , R_2 , R_C , and R_E :** Setting DC biasing Q-Point.
- **R_C :** Converting i_c variation into v_{ce} (or v_o) variation (signal conversion).

DC & AC Analysis of Amplifiers

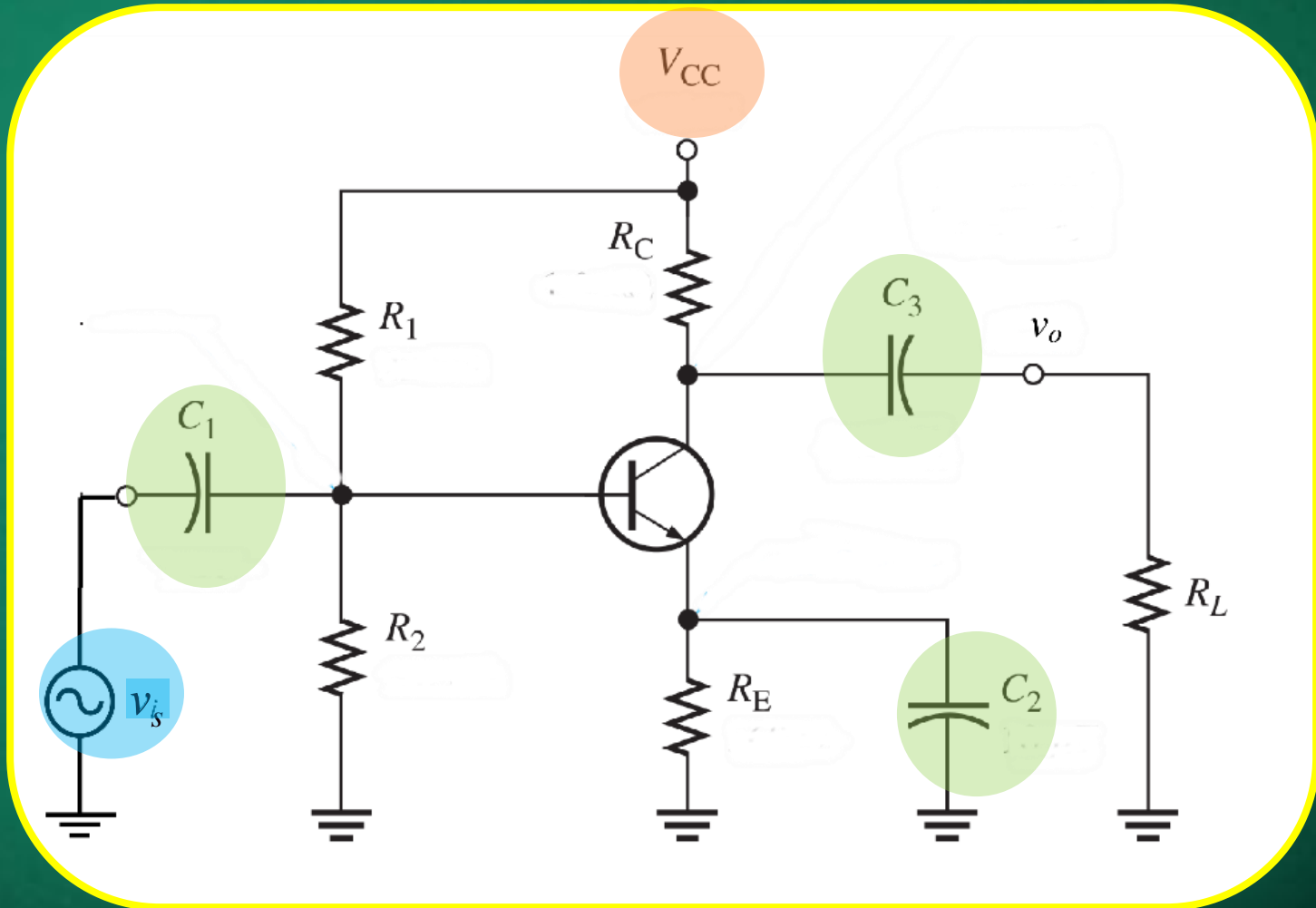

DC Equiv. Circuit & Analysis

**To determine DC operating point
(or Q-point)**

DC Equiv. Circuit & Analysis

**To determine DC operating point
(or Q-point)**

- **Reduce all signal sources to zero.**

DC Equiv. Circuit & Analysis

**To determine DC operating point
(or Q-point)**

- **Reduce all signal sources to zero.**
- **Open all the capacitors**

DC Equiv. Circuit & Analysis


**To determine DC operating point
(or Q-point)**

- **Reduce all signal sources to zero.**
- **Open all the capacitors**
- **Draw and analyze the DC equivalent.**

DC Equiv. Circuit & Analysis

To determine DC operating point (or Q-point)

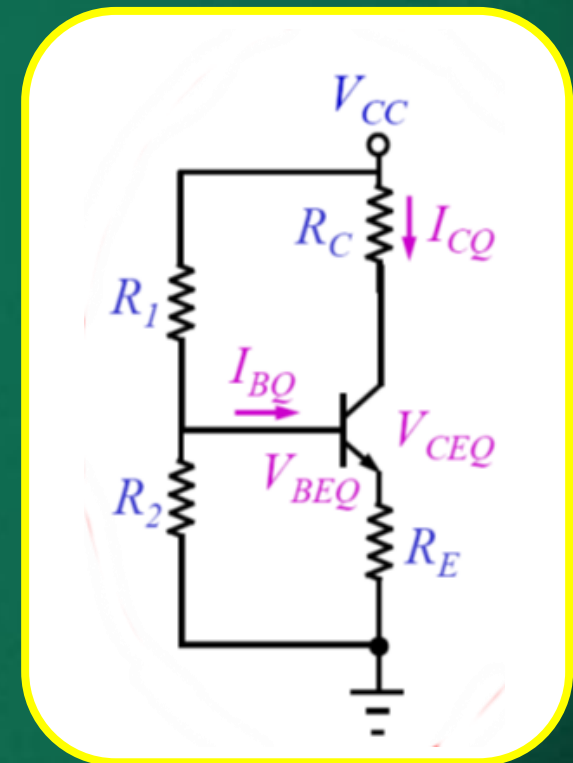- Reduce all signal sources to zero.
- Open all the capacitors
- Draw and analyze the DC equivalent.



AC Equiv. Circuit & Analysis

**To determine ac characteristics
(e.g., small signal voltage gain,
input impedance, output
impedance, frequency response
etc.**

AC Equiv. Circuit & Analysis

**To determine ac characteristics
(e.g., small signal voltage gain,
input impedance, output
impedance, frequency response
etc.**

- **Reduce all DC sources to zero.**

AC Equiv. Circuit & Analysis

**To determine ac characteristics
(e.g., small signal voltage gain,
input impedance, output
impedance, frequency response
etc.**

- **Reduce all DC sources to zero.**
- **Short all the capacitors**

AC Equiv. Circuit & Analysis


**To determine ac characteristics
(e.g., small signal voltage gain,
input impedance, output
impedance, frequency response
etc.**

- **Reduce all DC sources to zero.**
- **Short all the capacitors**
- **Draw and analyze the AC equivalent.**


AC Equiv. Circuit & Analysis

To determine ac characteristics (e.g., small signal voltage gain, input impedance, output impedance, frequency response etc.

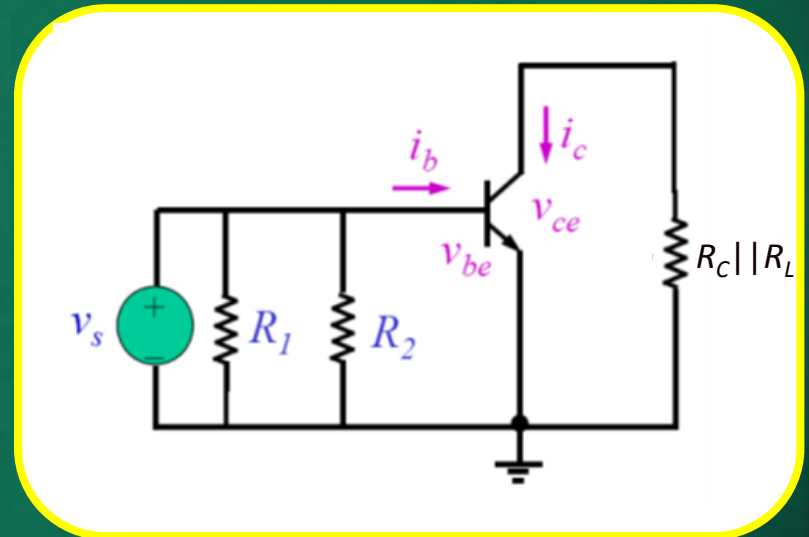- Reduce all DC sources to zero.
- Short all the capacitors
- Draw and analyze the AC equivalent.




Small Signal Hybrid- π Equiv. Circuit

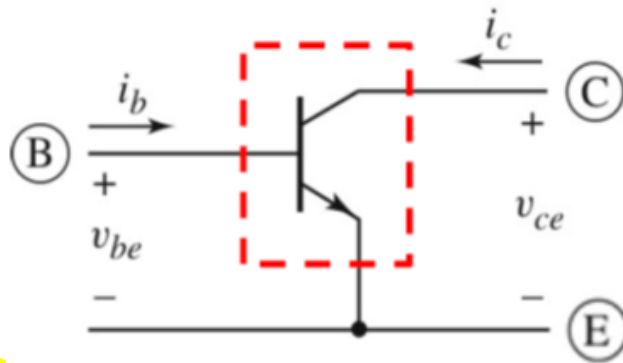

BJT as a 2 port network


Small Signal Hybrid- π Equiv. Circuit

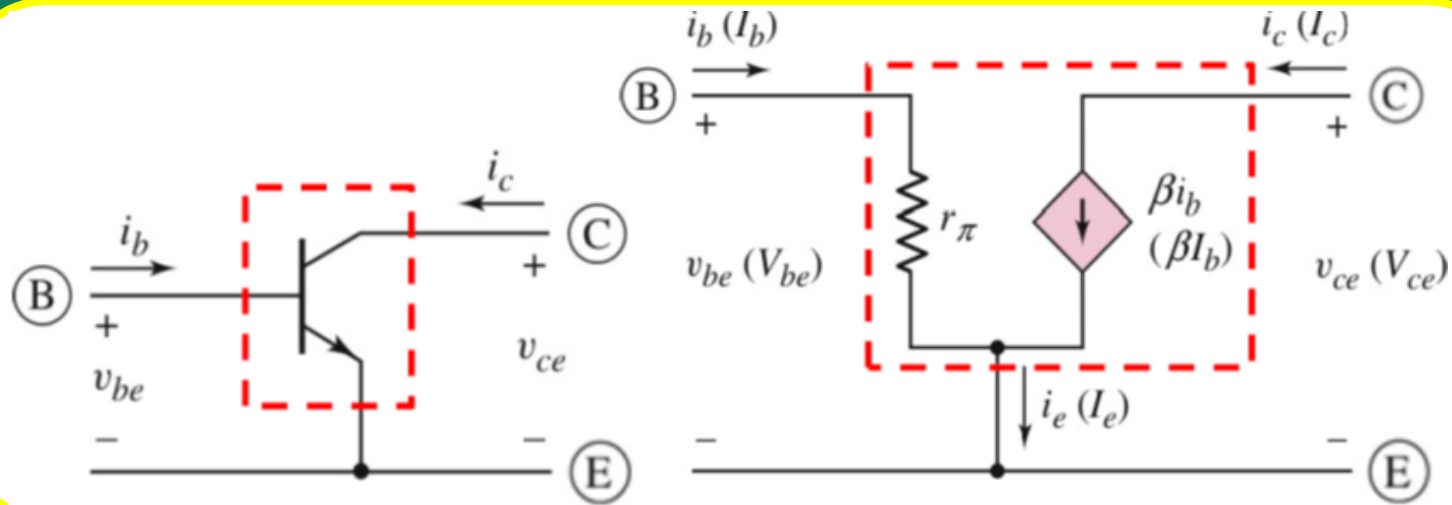

BJT as a 2 port network

Small signal hybrid π equivalent circuit

Small Signal Hybrid- π Equiv. Circuit

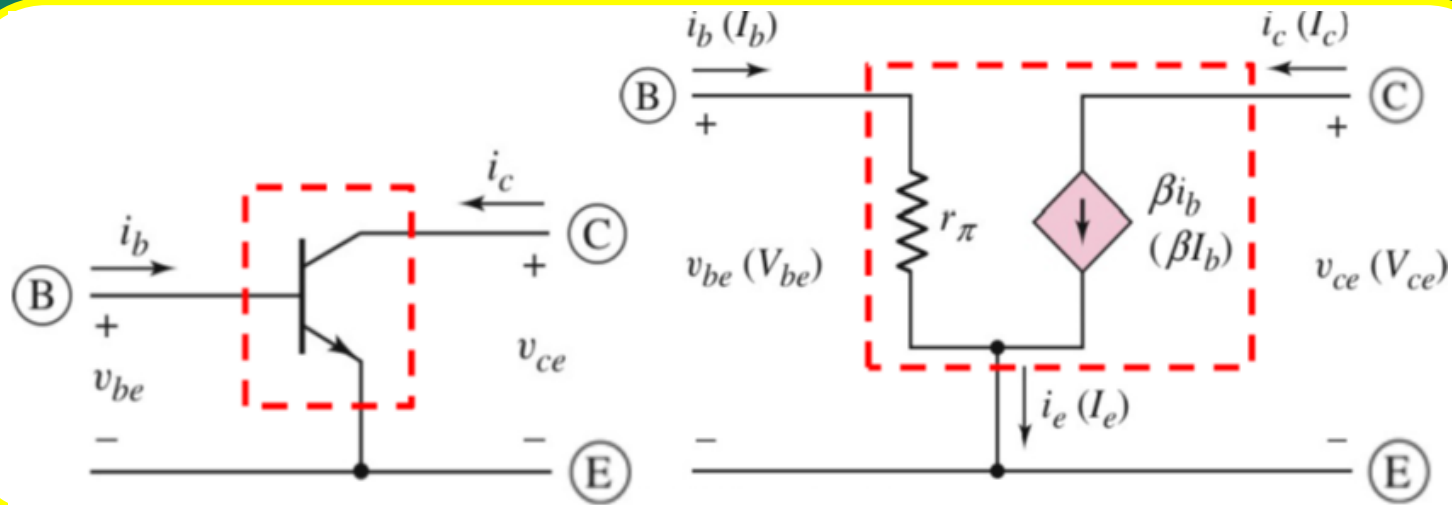


BJT as a 2 port network

Small signal hybrid π equivalent circuit

$\beta = \text{Common emitter current gain} = i_c / i_b$

Small Signal Hybrid- π Equiv. Circuit

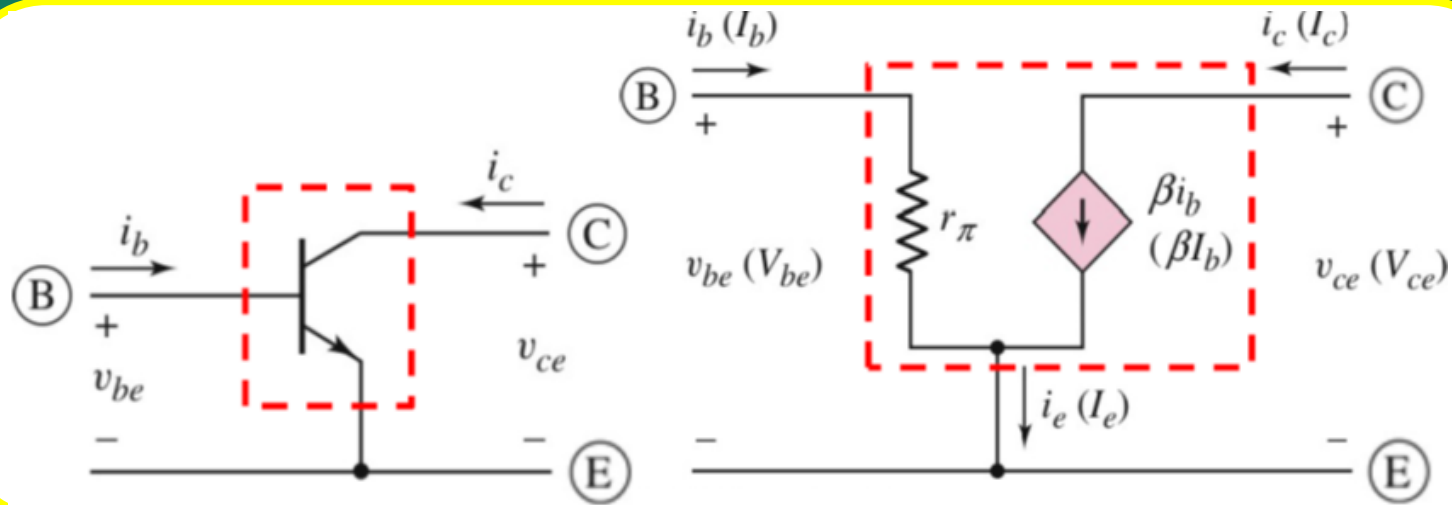

BJT as a 2 port network


Small signal hybrid π equivalent circuit

$\beta = \text{Common emitter current gain} = i_c / i_b$

$$r_\pi = v_{be} / i_b = V_T / I_{BQ}$$


$= \beta V_T / I_{CQ} = \text{small signal resistance, where } V_T \text{ is the thermal voltage}$

Small Signal Hybrid- π Equiv. Circuit

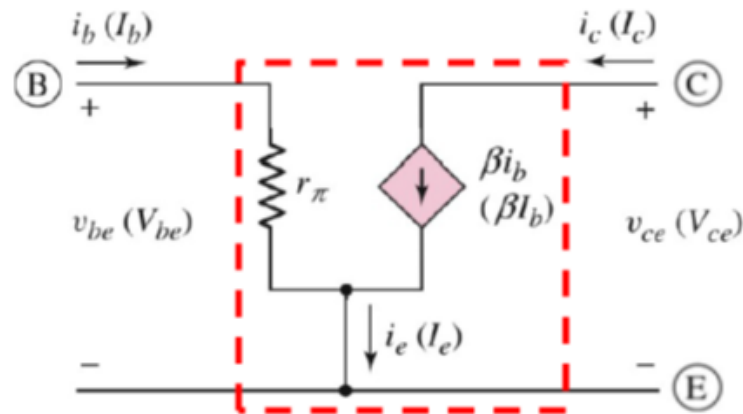

With current gain parameter


Small Signal Hybrid- π Equiv. Circuit

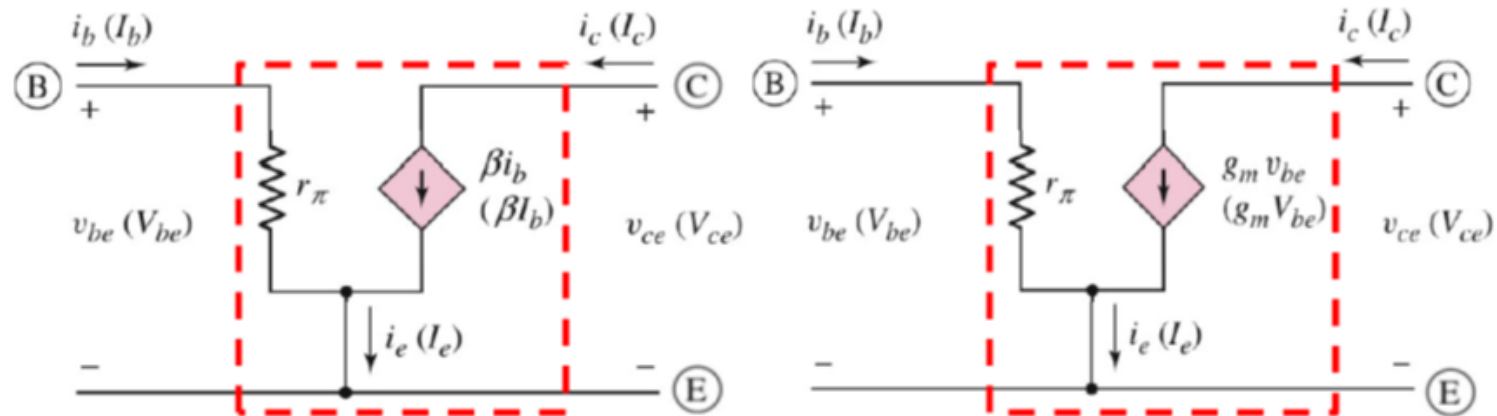

With current gain parameter

With transconductance parameter

Small Signal Hybrid- π Equiv. Circuit

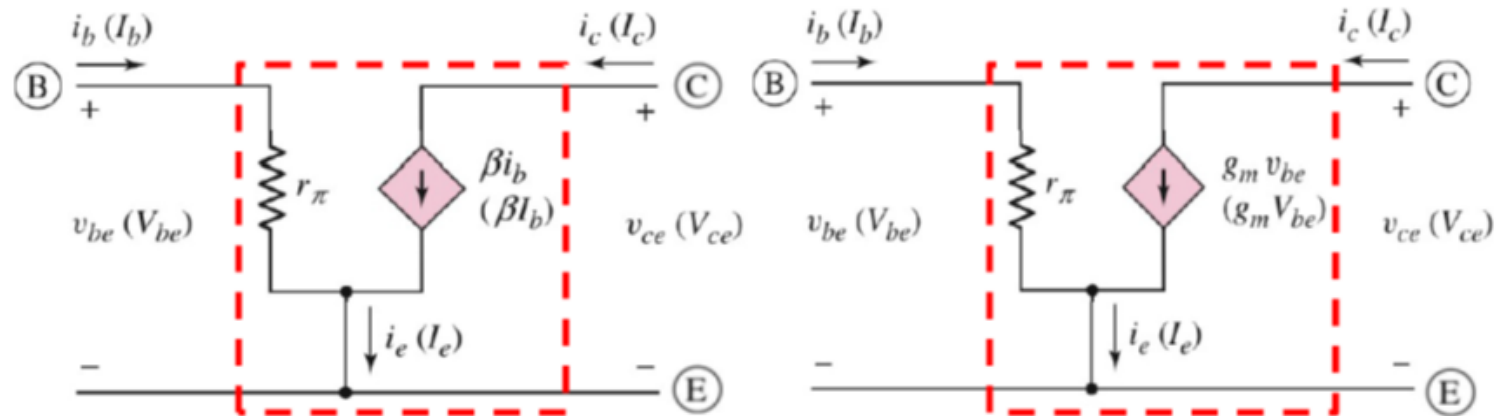


With current gain parameter

With transconductance parameter

$$g_m = \beta / r_\pi = I_{CQ} / V_T = \text{transconductance}$$

Small Signal Hybrid- π Equiv. Circuit

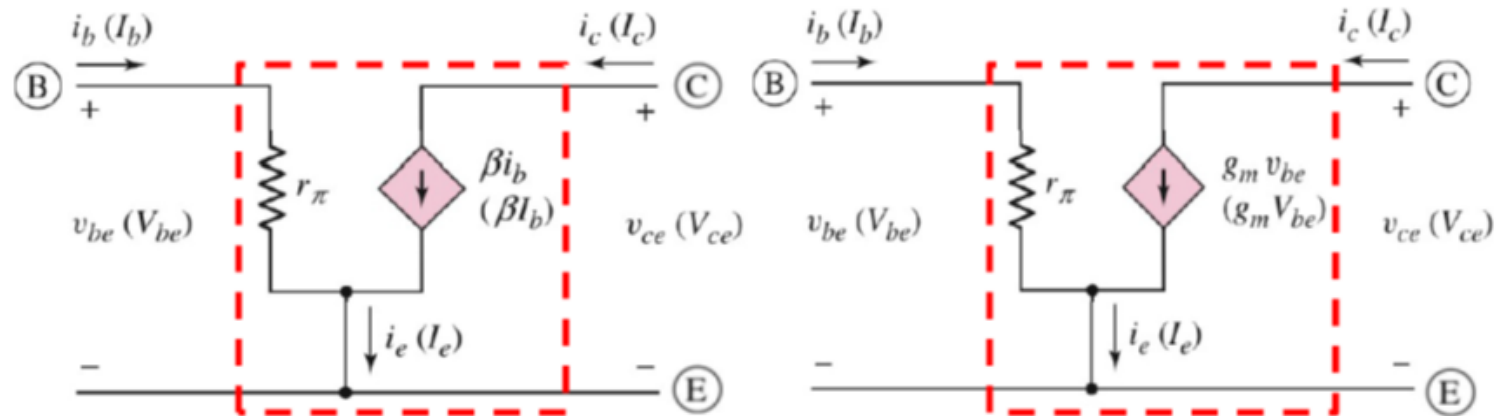


With current gain parameter

With transconductance parameter


$$g_m = \beta / r_\pi = I_{CQ} / V_T = \text{transconductance}$$

i_c is assumed to be independent of v_{ce} which is not the case in practice and the assumption will be released later to include the "Early effect"

Basic Characteristics of an Amplifier

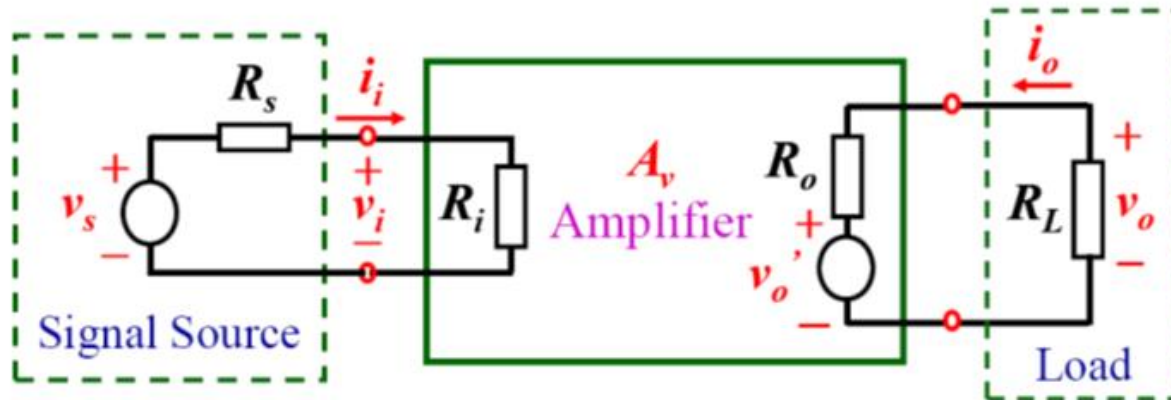


Basic Characteristics of an Amplifier

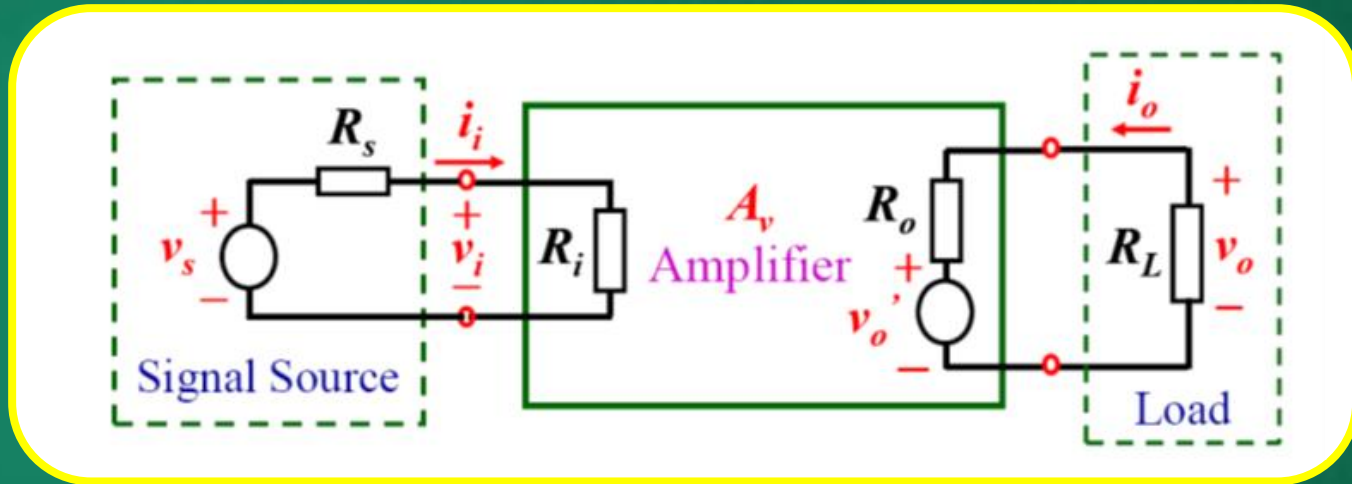

- **Overall Amplifier Gain**

$$A_v = \frac{v_o}{v_s}$$

Basic Characteristics of an Amplifier

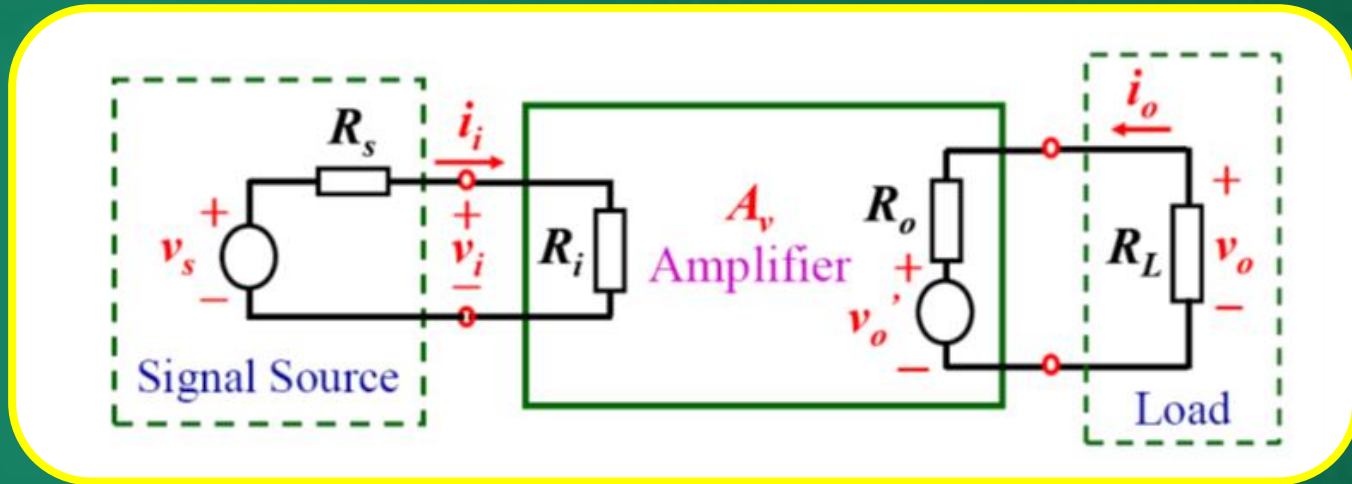


- **Overall Amplifier Gain**

$$A_v = \frac{v_o}{v_s}$$

- **Input Resistance**

$$R_i = \frac{v_i}{i_i}$$

Basic Characteristics of an Amplifier

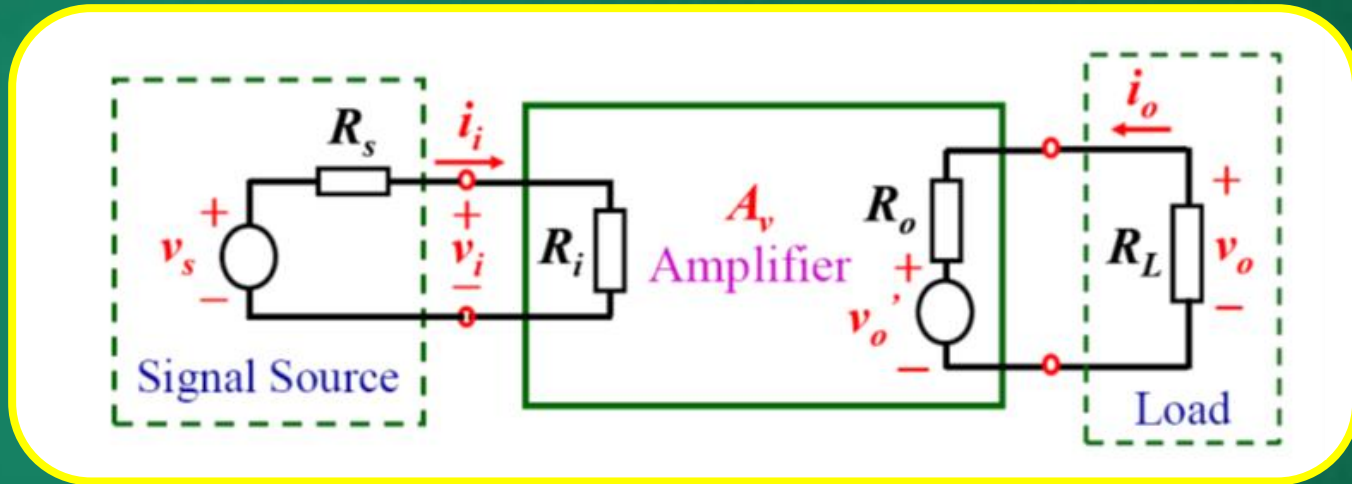

- Overall Amplifier Gain

$$A_v = \frac{v_o}{v_s}$$


- Input Resistance

$$R_i = \frac{v_i}{i_i}$$


- Output Resistance

$$R_o = \left. \frac{v_o}{i_o} \right|_{v_s=0}$$


Small Signal Voltage Gain

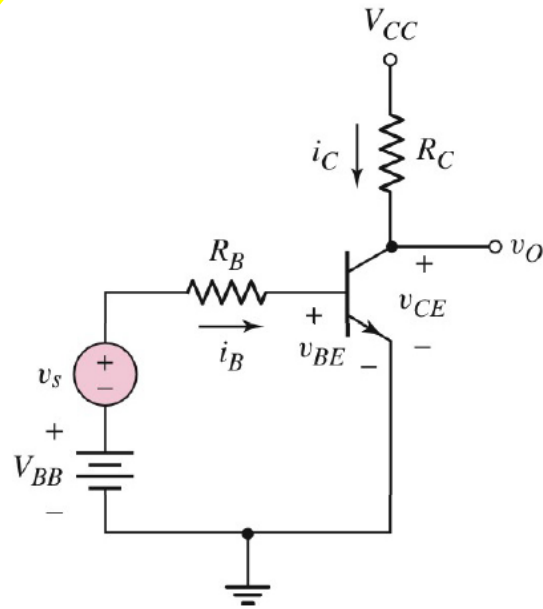


Small Signal Voltage Gain

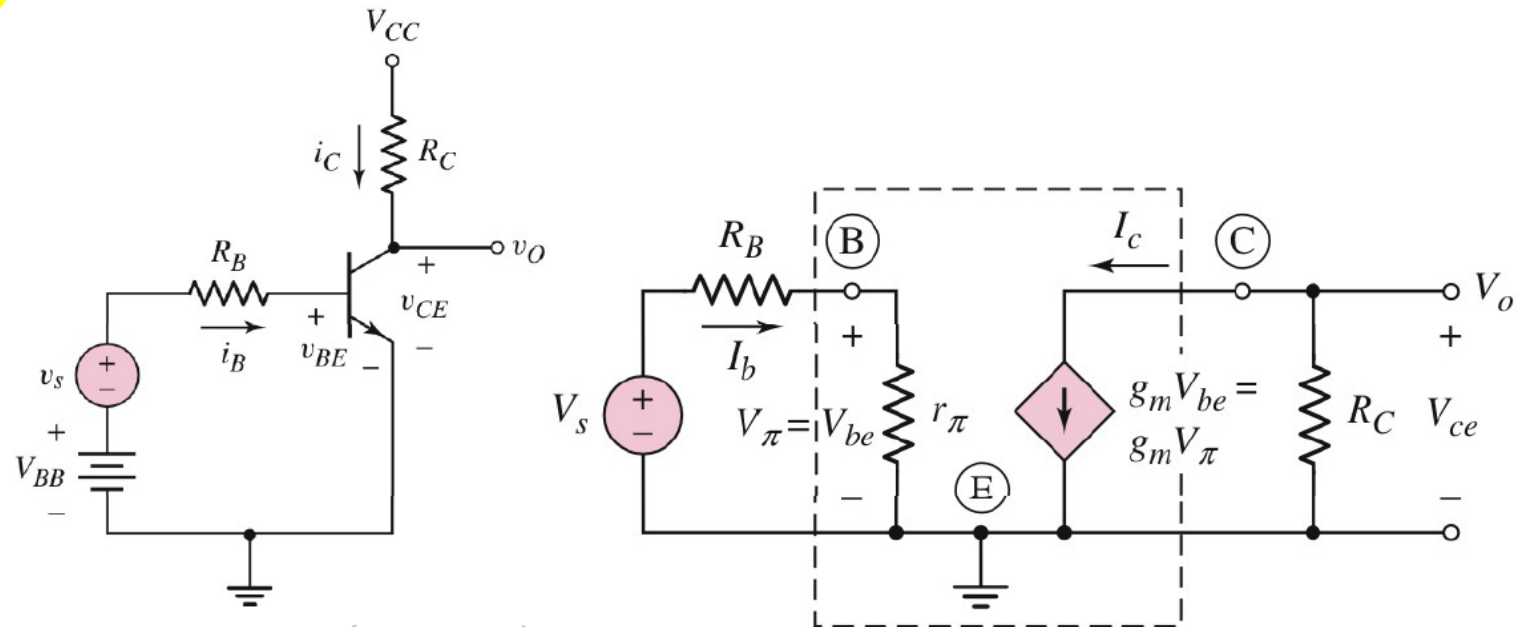


Small Signal Voltage Gain

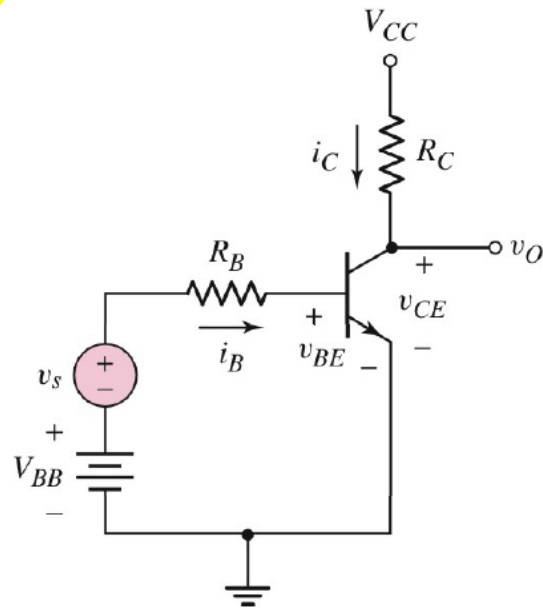
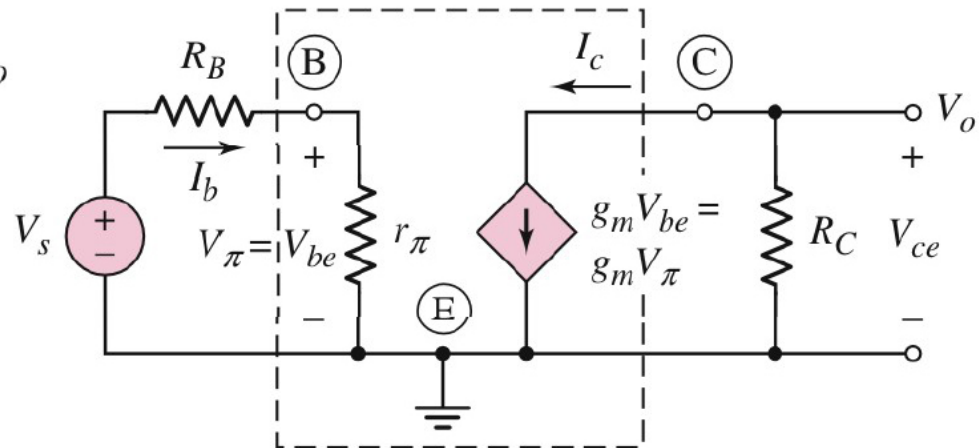
$$V_{\pi} = V_{be} = V_s \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right)$$





Small Signal Voltage Gain

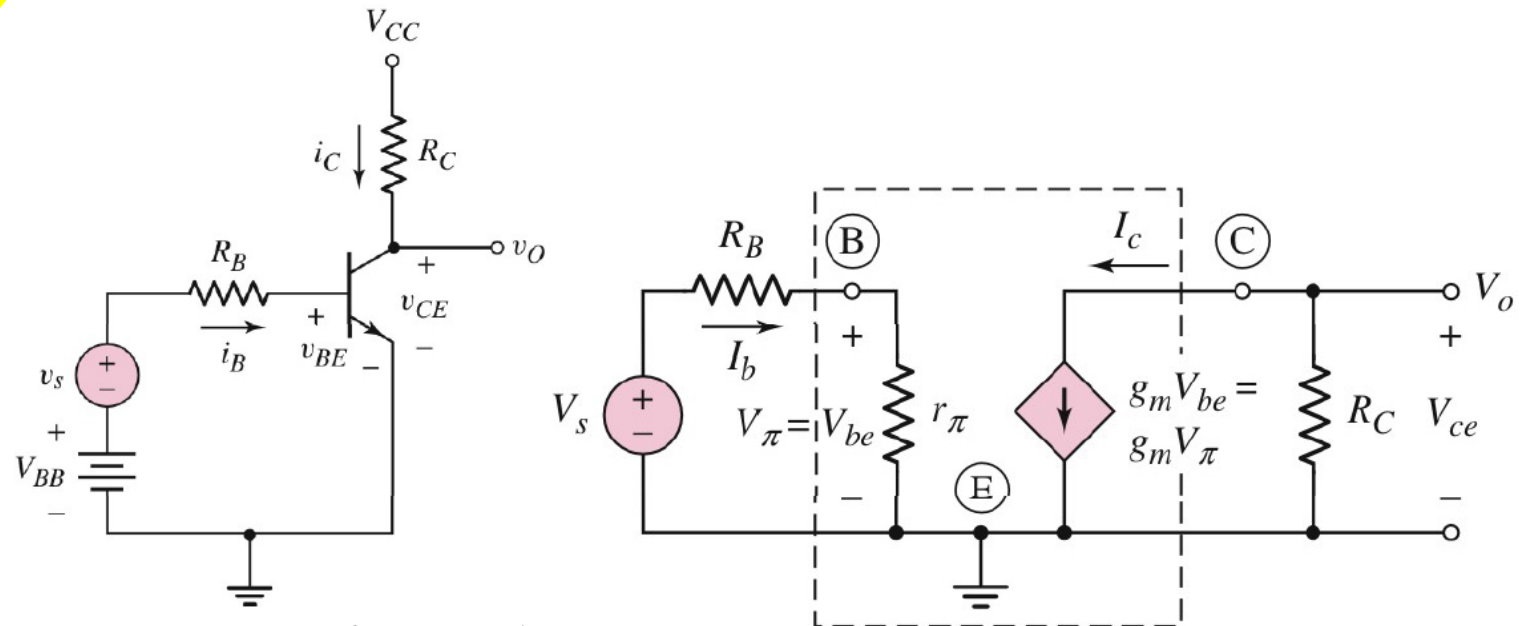

$$V_\pi = V_{be} = V_s \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$V_o = V_{ce} = -(g_m V_\pi) R_C = -(g_m V_{be}) R_C$$

Small Signal Voltage Gain

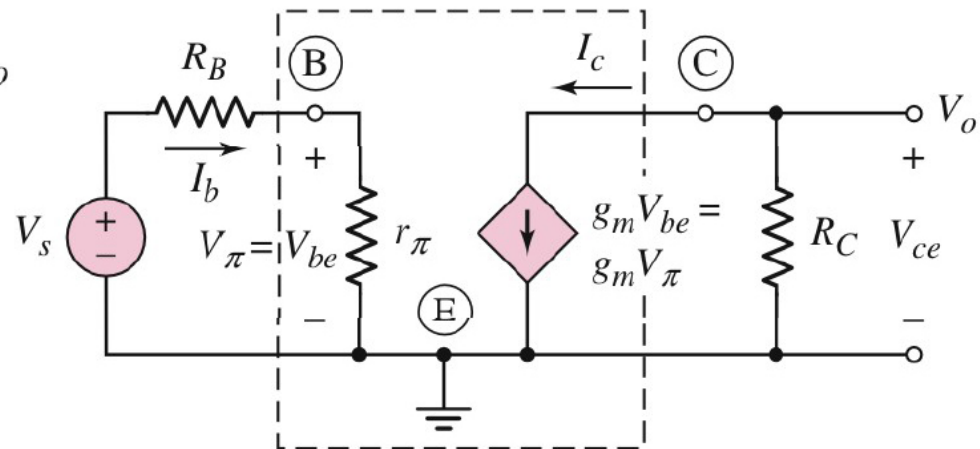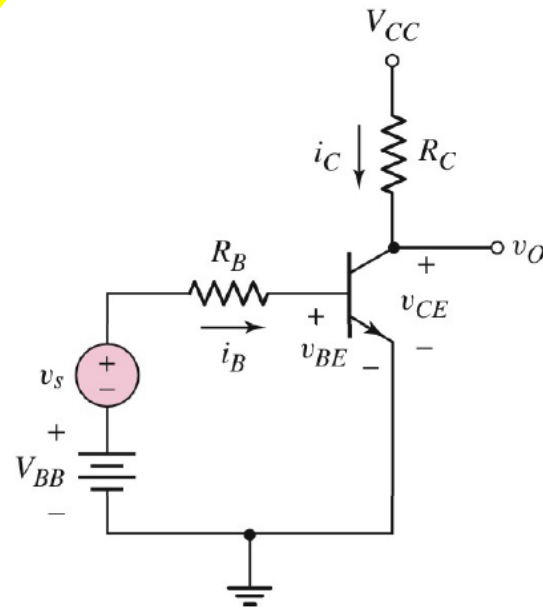


$$V_\pi = V_{be} = V_s \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$V_o = V_{ce} = -(g_m V_\pi) R_C = -(g_m V_{be}) R_C$$


Small-signal voltage gain:

$$A_v = \frac{V_o}{V_s} = -(g_m R_C) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

Input and Output Resistances

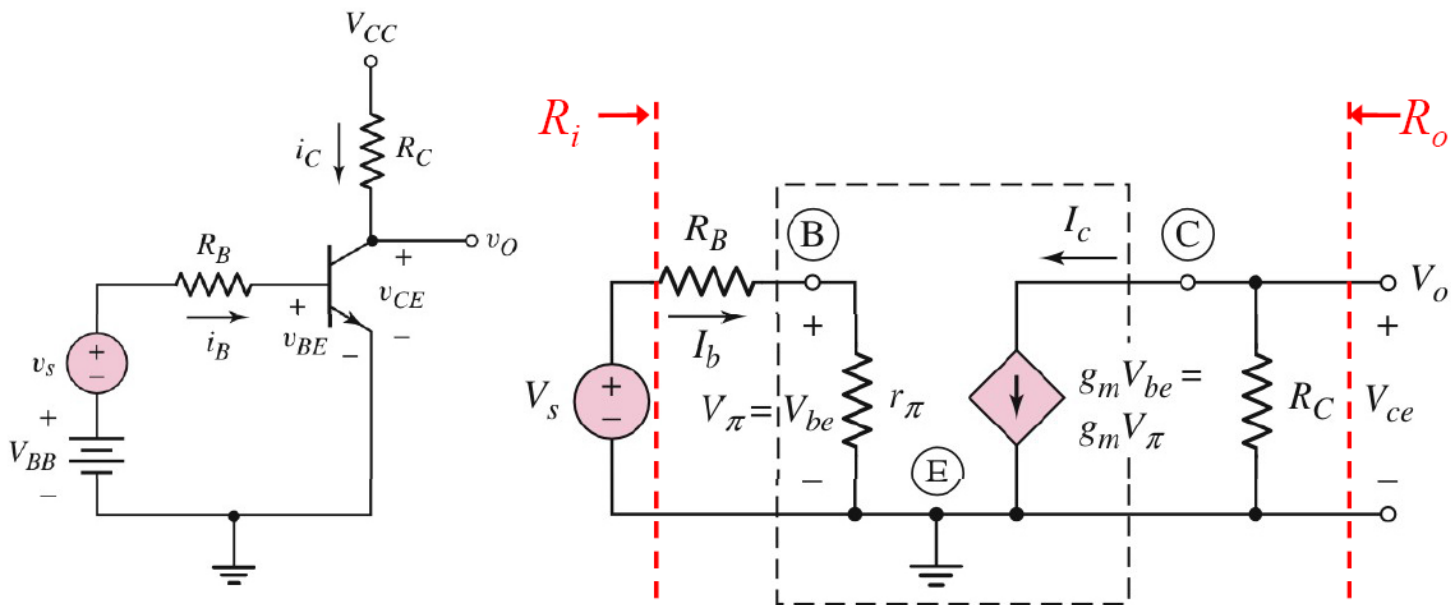


Input and Output Resistances

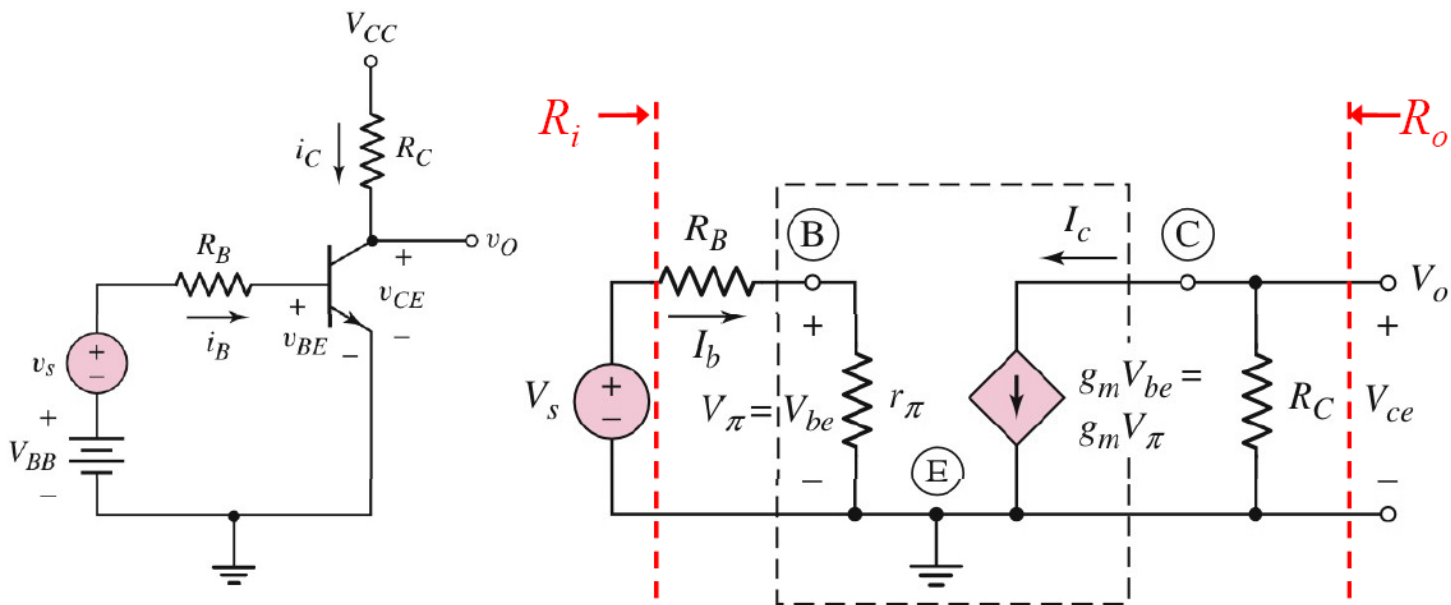

Input resistance: $R_i = R_B + r_\pi$

Input and Output Resistances

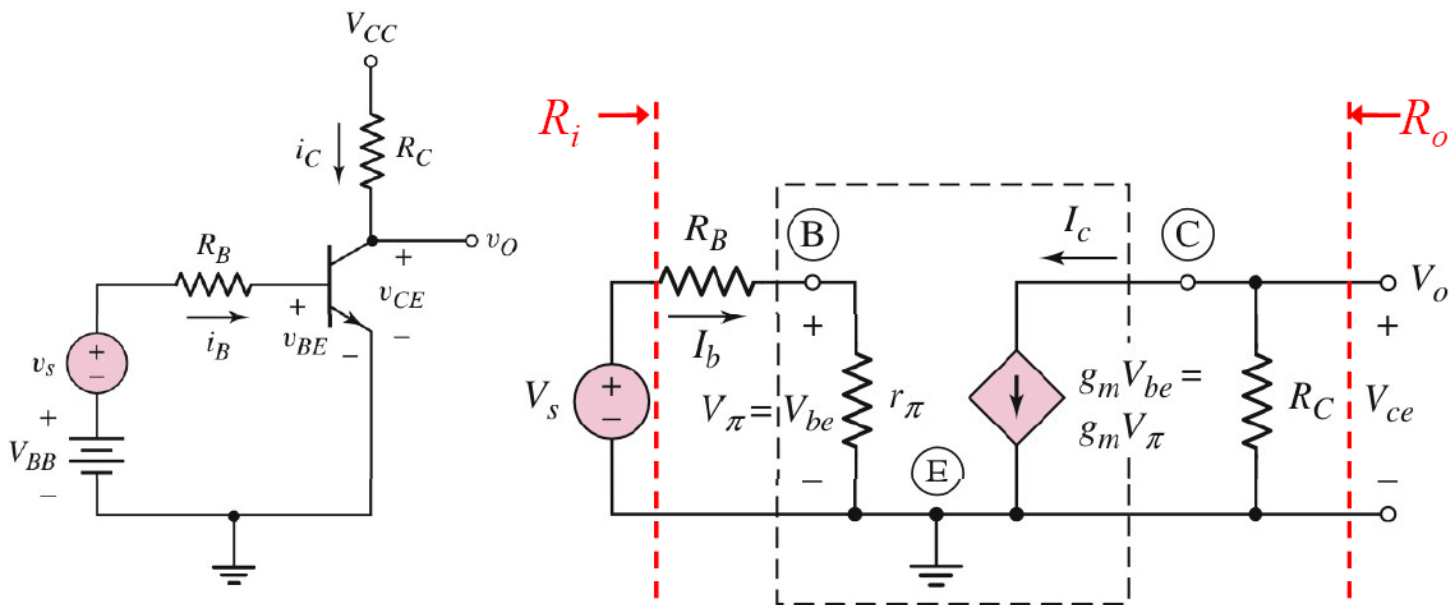

Input resistance: $R_i = R_B + r_\pi$

Output resistance: $R_o = R_C$

[Setting $V_s = 0$ (short), then $V_\pi = 0$ & $g_m V_\pi = 0$ (open)]

Example

- Calculate the small-signal voltage gain, input resistance & output resistance of the BJT amplifier circuit at 300 K. Assume that the BJT & circuit parameters are: $\beta = 100$, $V_{CC} = 12$ V, $V_{BE} = 0.7$ V, $R_C = 6$ k Ω , $R_B = 50$ k Ω & $V_{BB} = 1.2$ V.

