

# **Basic Electronic Circuits (IEC-103)**

## **Lecture-10**

# **Sinusoidal Oscillators**


# Types of Oscillators

- 1. Feedback Oscillator**
- 2. Relaxation Oscillators**

## ☐ **Feedback Oscillators**

- A fraction of output is feedback to the input with no net phase shift.**
- The loop gain must be maintained at 1 to maintain oscillations**
- Amplifier can be made of either discrete transistor or an op-amp.**

# Feedback Oscillators

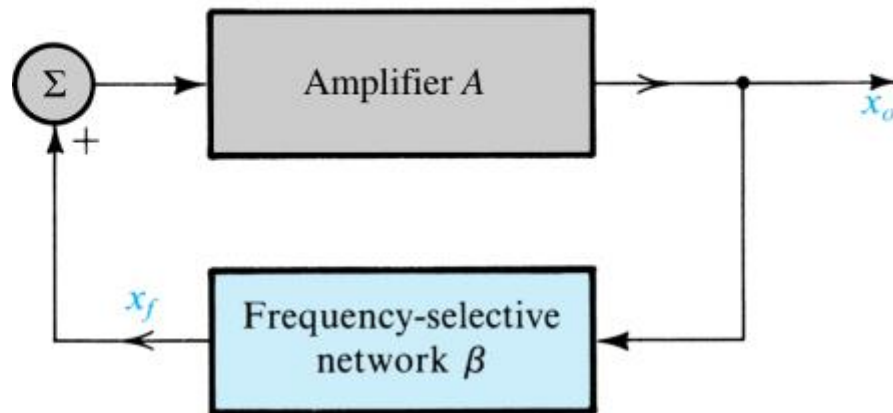

# Conditions for Oscillations

**Two conditions must be satisfied for sustained oscillations**



# Conditions for Oscillations

**Two conditions must be satisfied for sustained oscillations**


- 1. The phase shift around the feedback loop must be effectively  $0^\circ$ .**

# Conditions for Oscillations


**Two conditions must be satisfied for sustained oscillations**

- 1. The phase shift around the feedback loop must be effectively  $0^\circ$ .**
- 2. The voltage gain  $A\beta$  around the closed feedback loop (loop gain) must be equal to 1.**

# Conditions for Oscillations

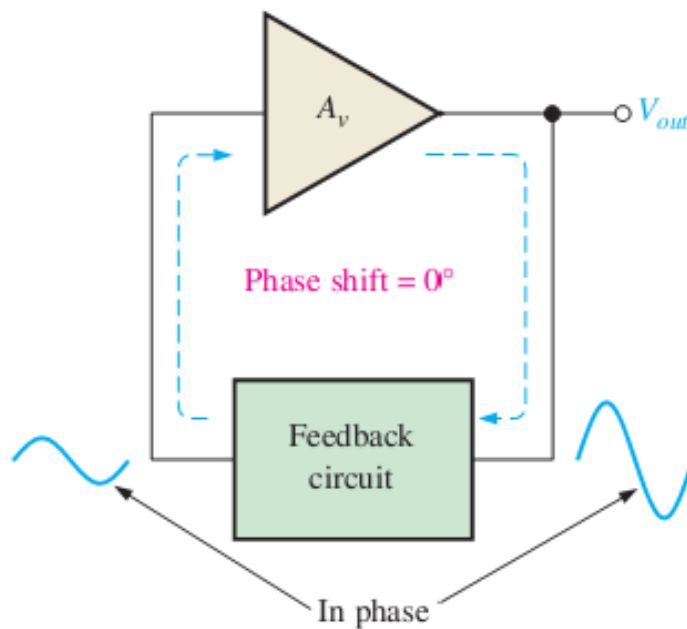

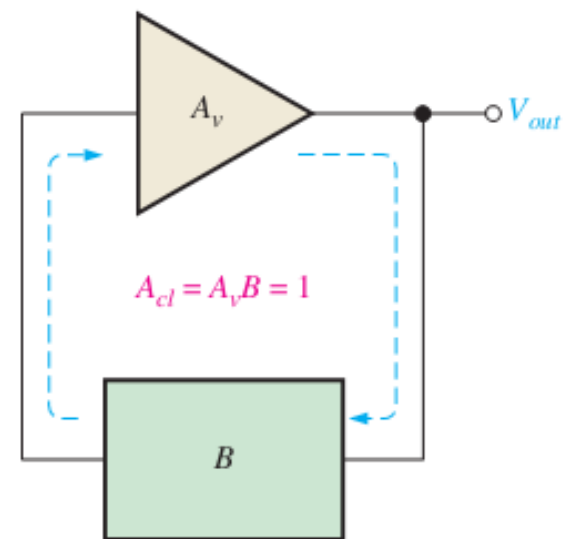(a) The phase shift around the loop is  $0^\circ$ .



(b) The closed loop gain is 1.



# RC and LC Oscillators

**RC Oscillators:** The frequency determining network contains only resistive and capacitive elements.

- Wein bridge oscillator
- Phase-shift oscillator
- Twin-T oscillator


# RC and LC Oscillators

**LC Oscillators:** The frequency determining network contains inductive and capacitive elements.


- **Hartly**
- **Colpitts**
- **Capp**
- **Pierce**

# RC Oscillators

# Wein Bridge Oscillator

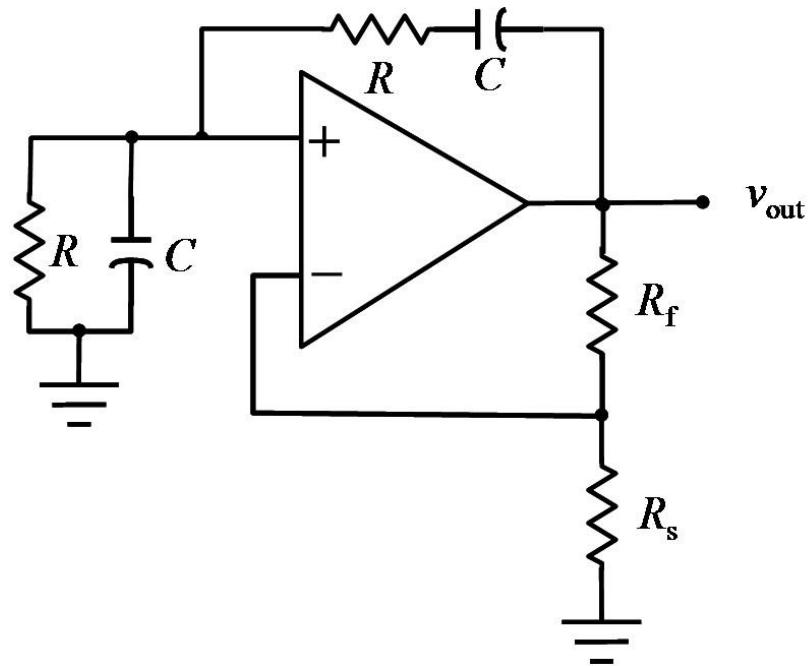


# Wein Bridge Oscillator

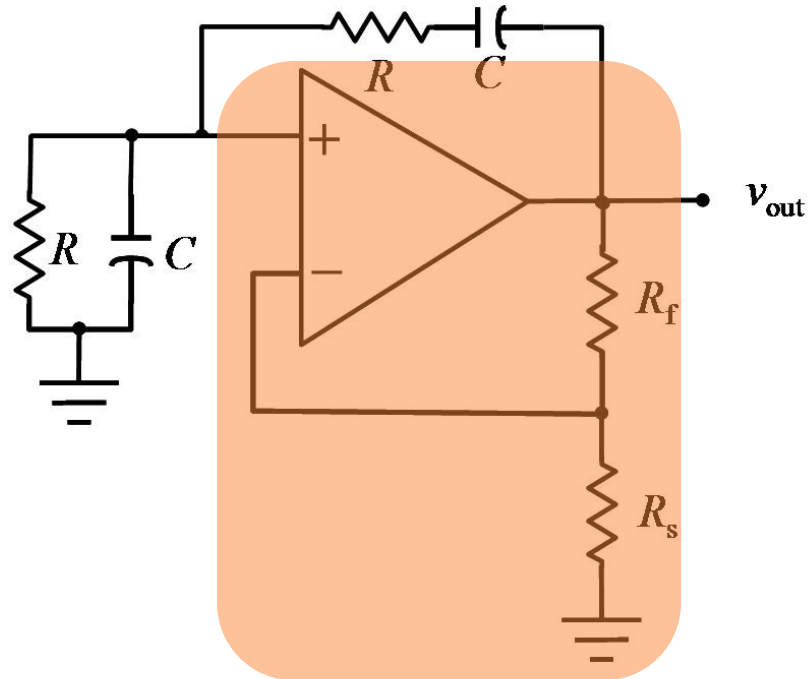




# Wein Bridge Oscillator

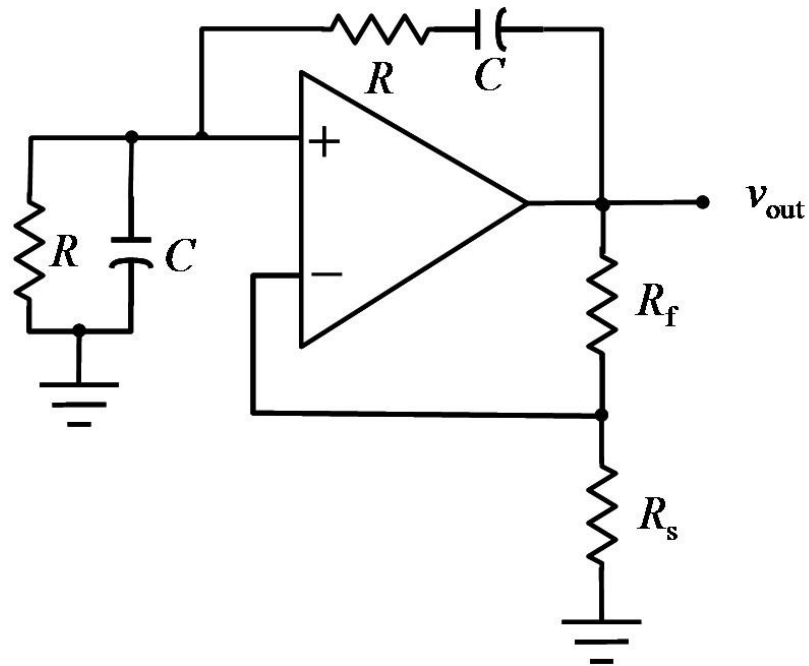

$$R_F = 2R_s$$


# Wein Bridge Oscillator

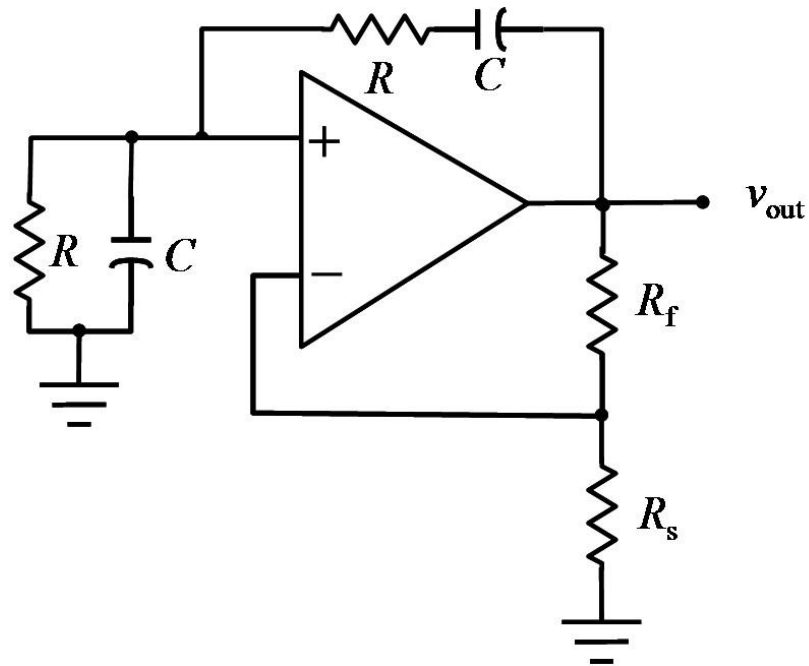


$$R_F = 2R_s$$

$$\omega = \frac{1}{RC}$$


# RC Phase Shift Oscillator

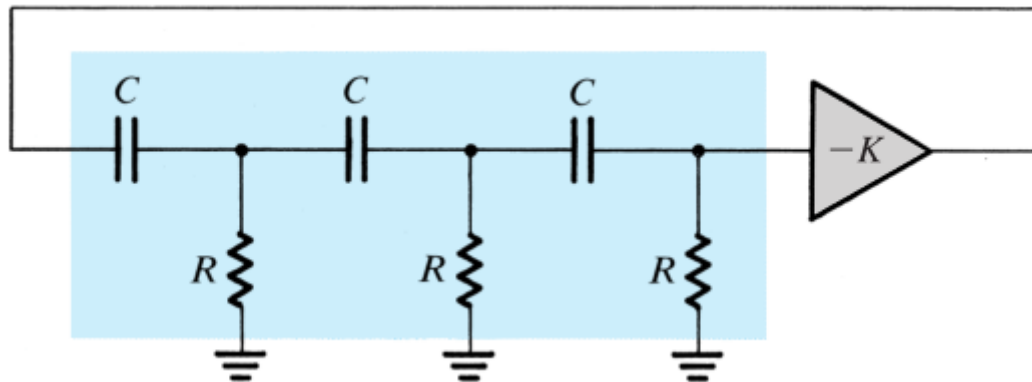

# RC Phase Shift Oscillator

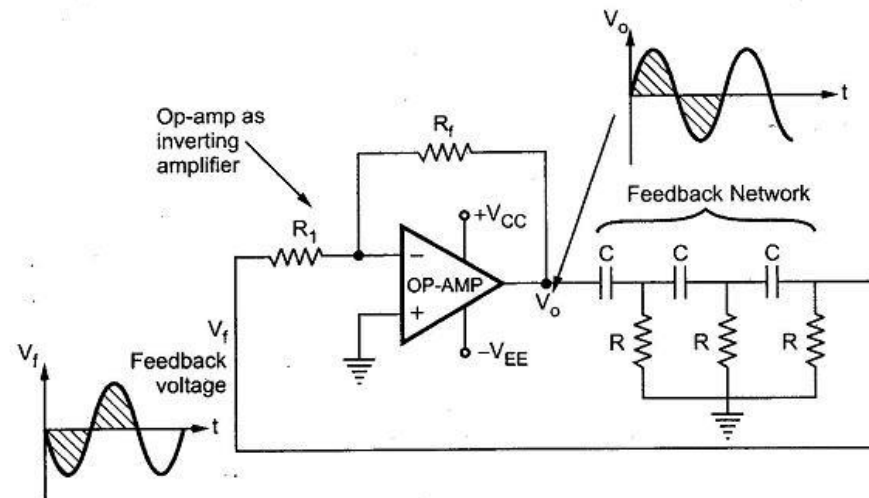


# RC Phase Shift Oscillator

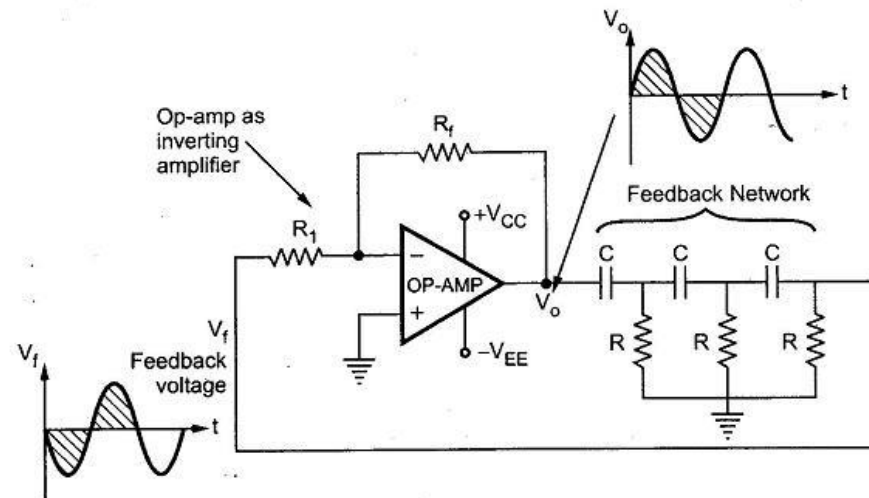

$$\frac{R_f}{R_1} = 29$$




# RC Phase Shift Oscillator

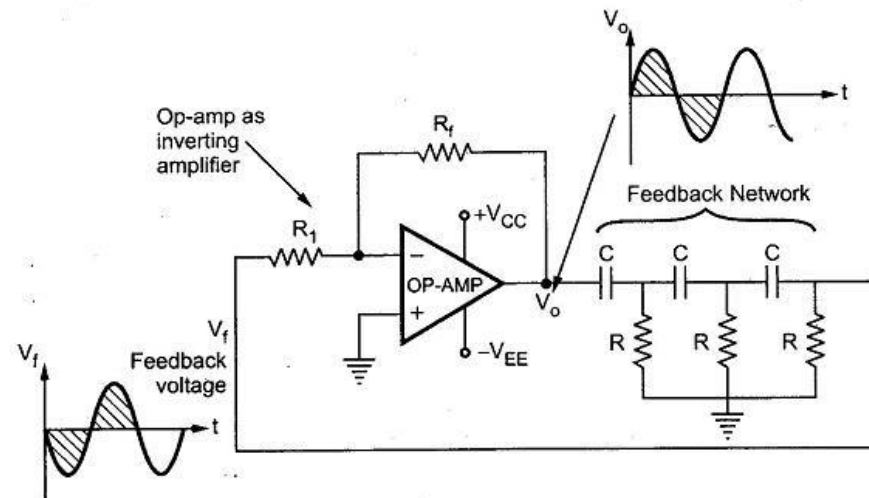

$$\frac{R_f}{R_1} = 29$$


$$\omega = \frac{1}{\sqrt{6RC}}$$

# Buffered Phase Shift Oscillator

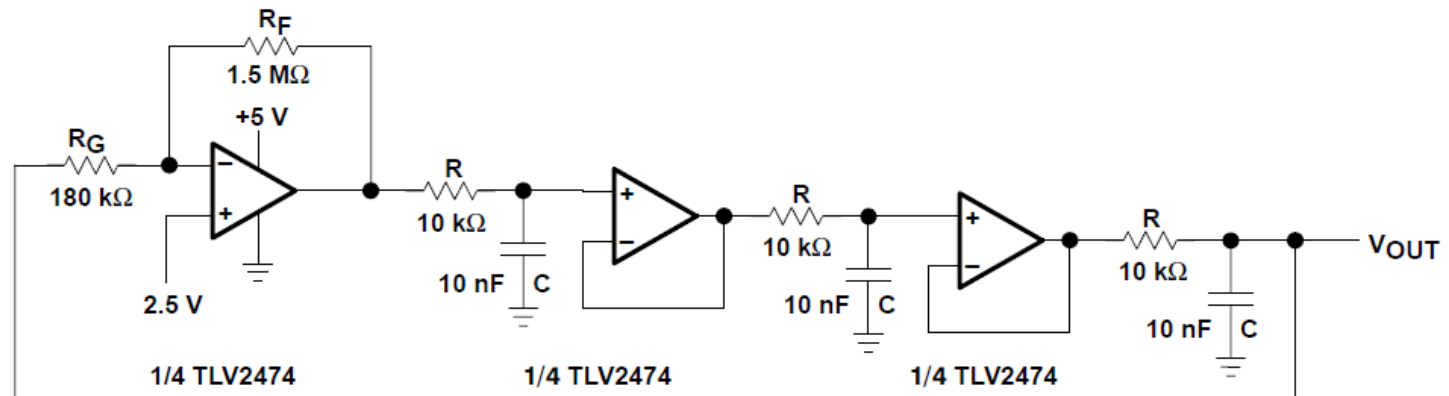


# LC Oscillators

# Transistor Oscillators

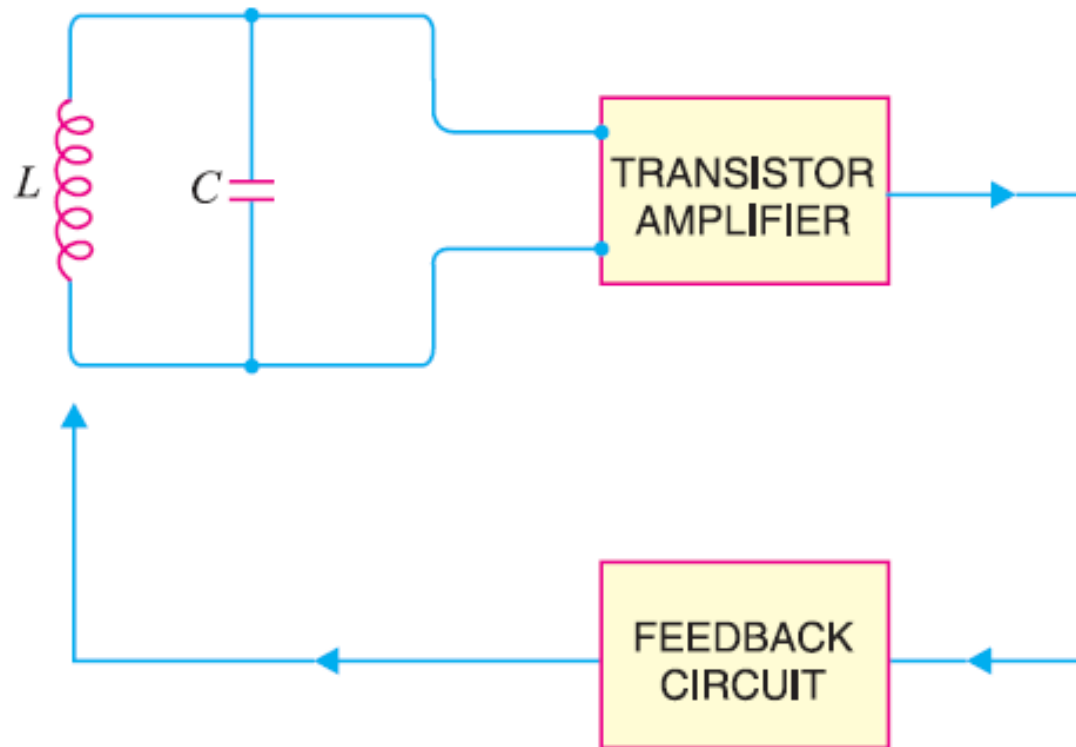


# Colpitt's Oscillator

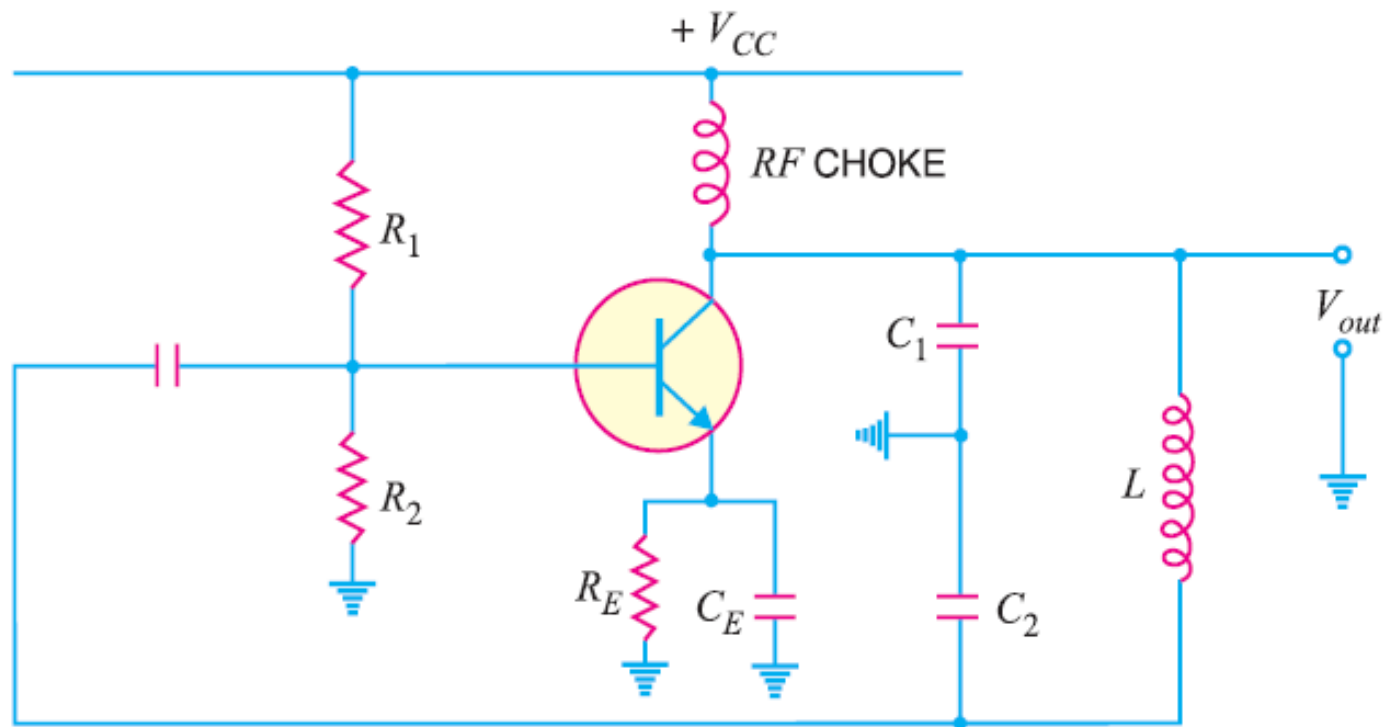




# Colpitt's Oscillator

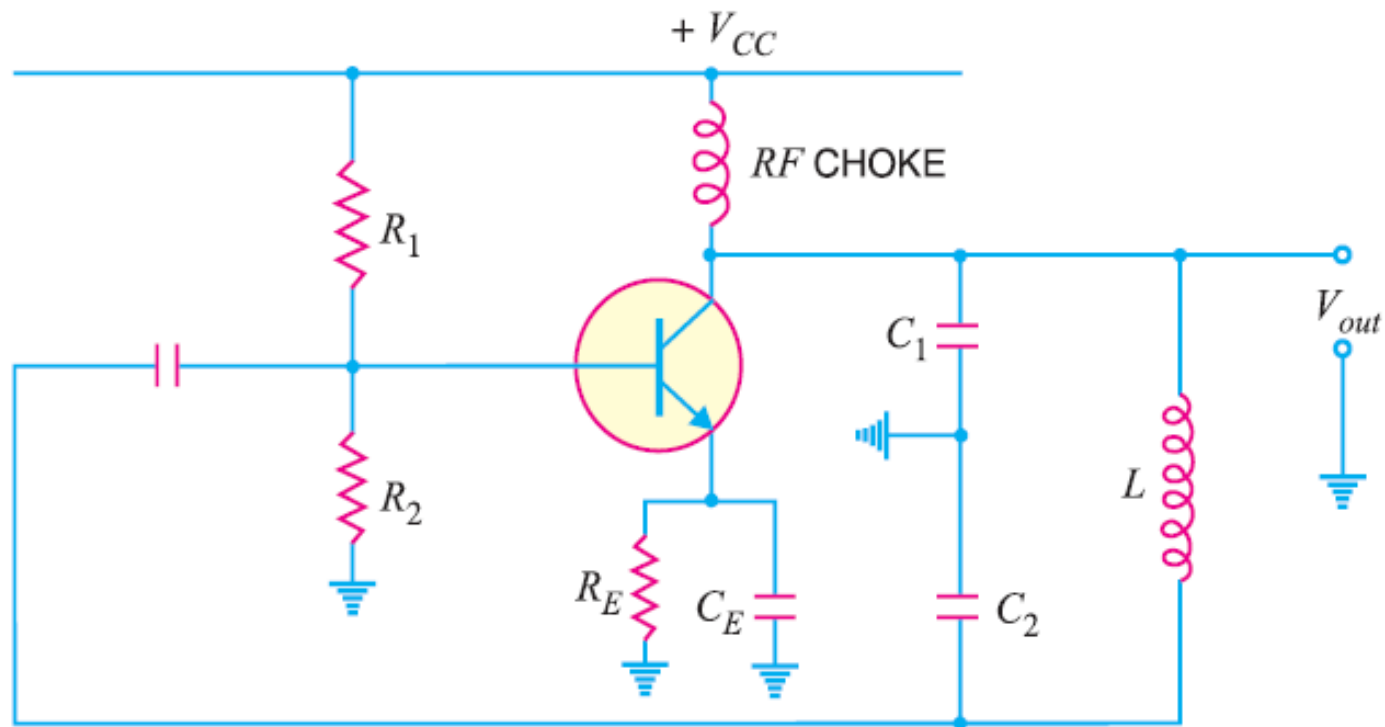

$$\omega = \frac{1}{\sqrt{LC_T}}$$


# Colpitt's Oscillator

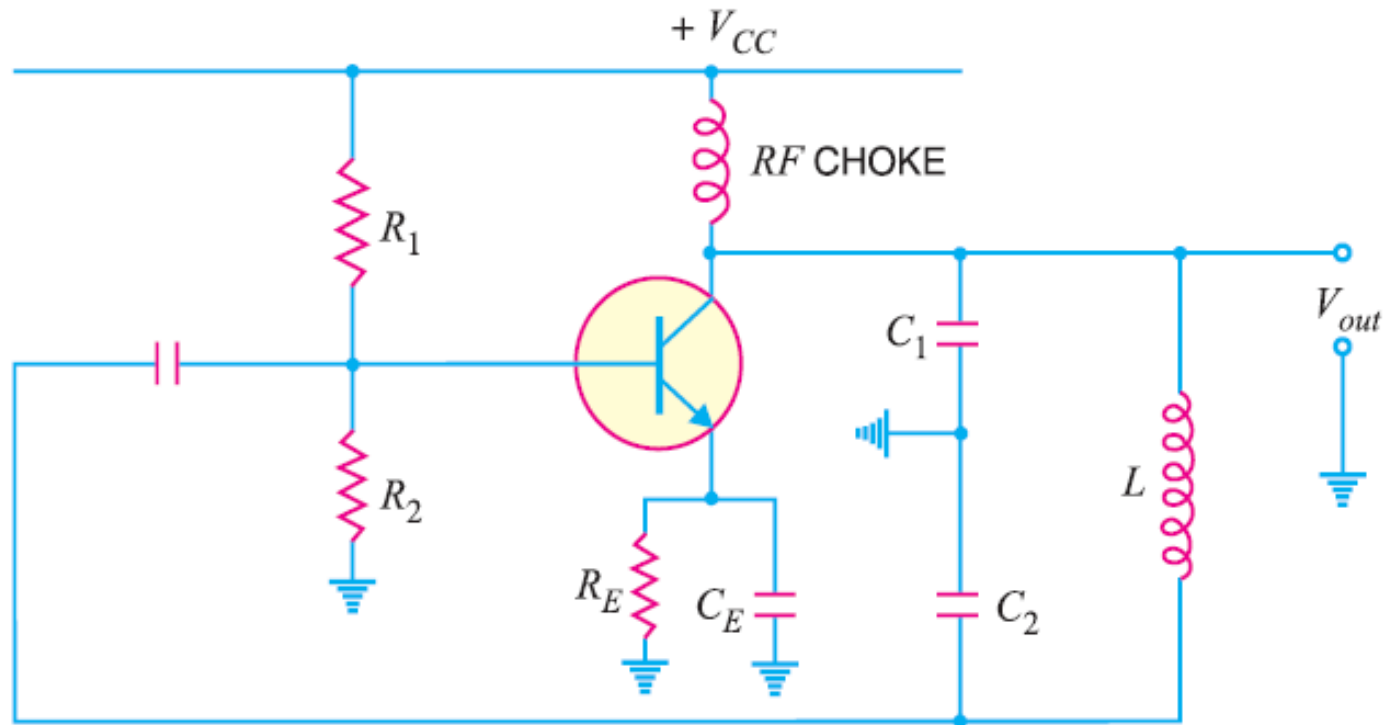


$$\omega = \frac{1}{\sqrt{LC_T}}$$

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

# Hartley Oscillator

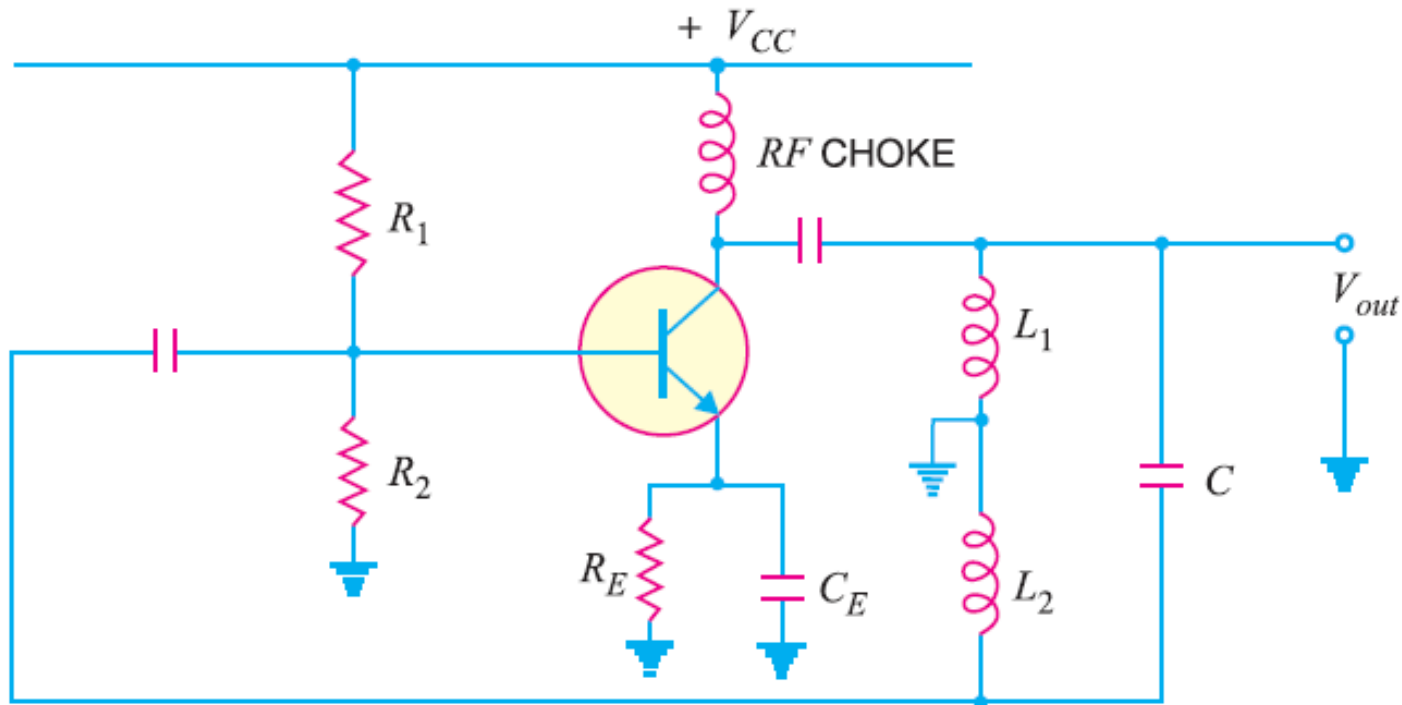


# Hartley Oscillator

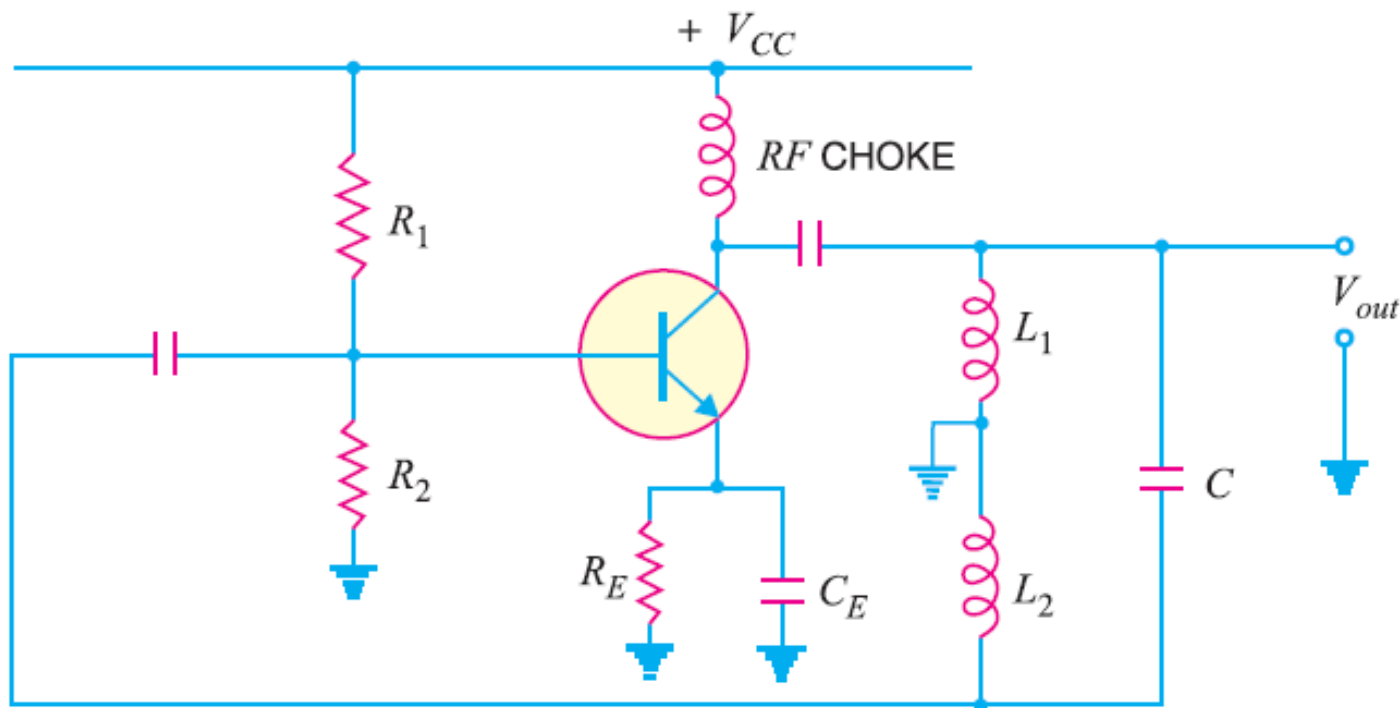

$$\omega = \frac{1}{\sqrt{L_T C}}$$

# Hartley Oscillator

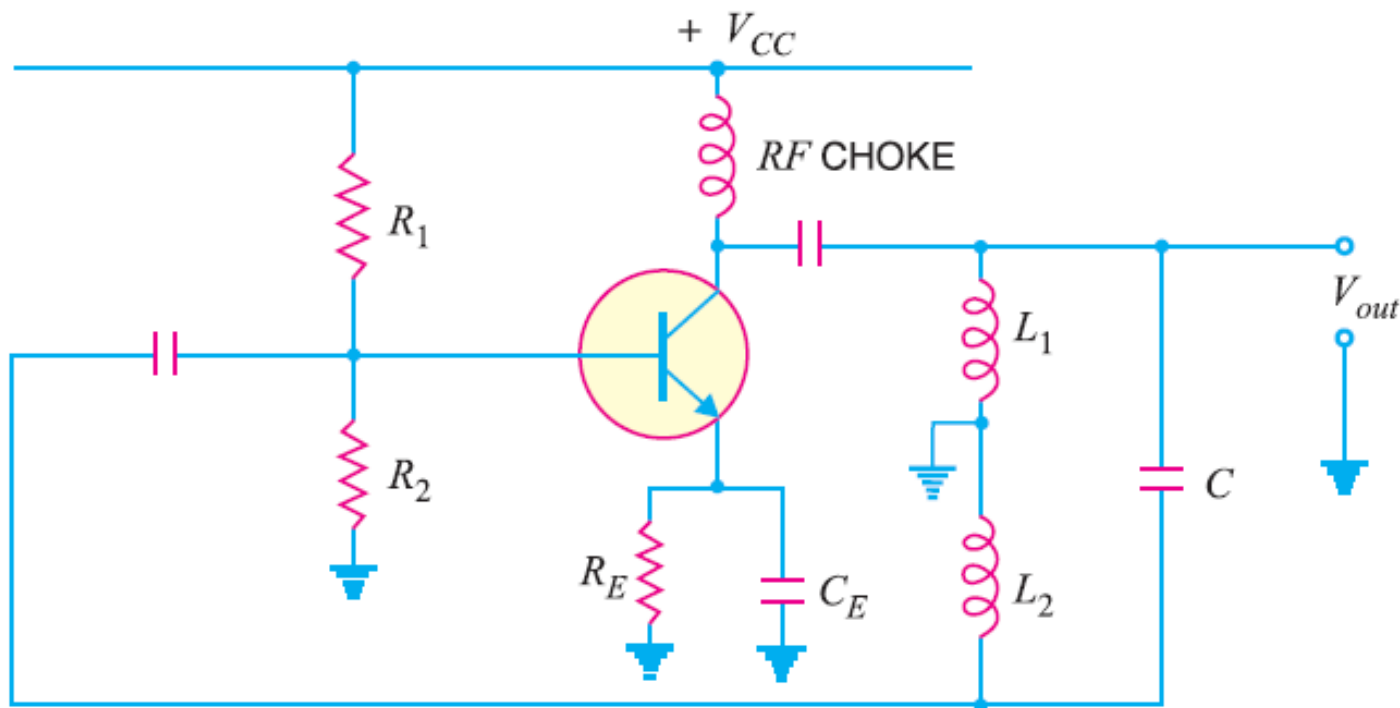


$$\omega = \frac{1}{\sqrt{L_T C}}$$


$$L_T = L_1 + L_2$$



# Clapp Oscillator

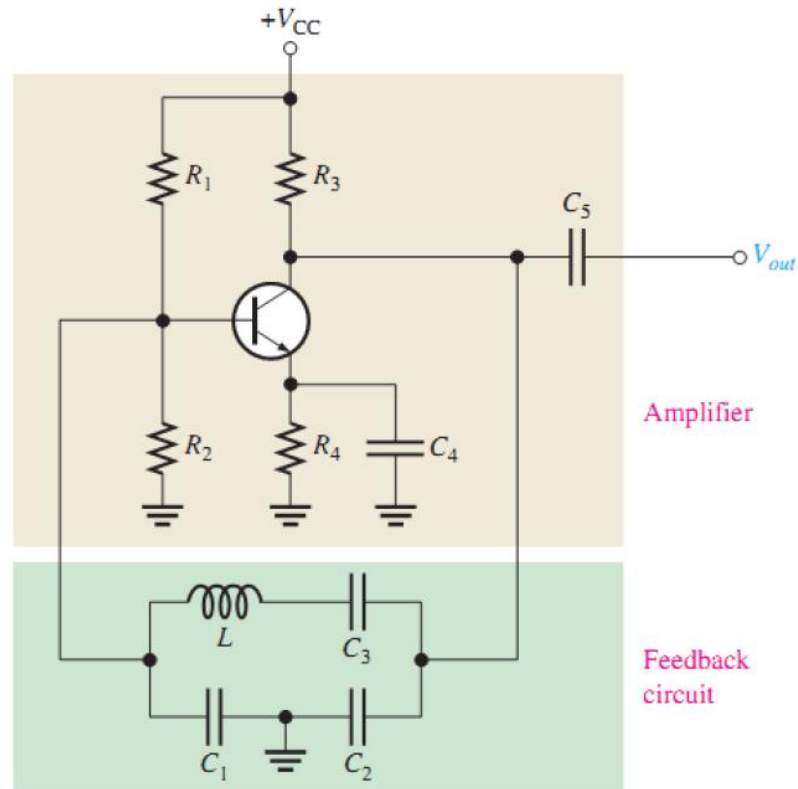


# Clapp Oscillator

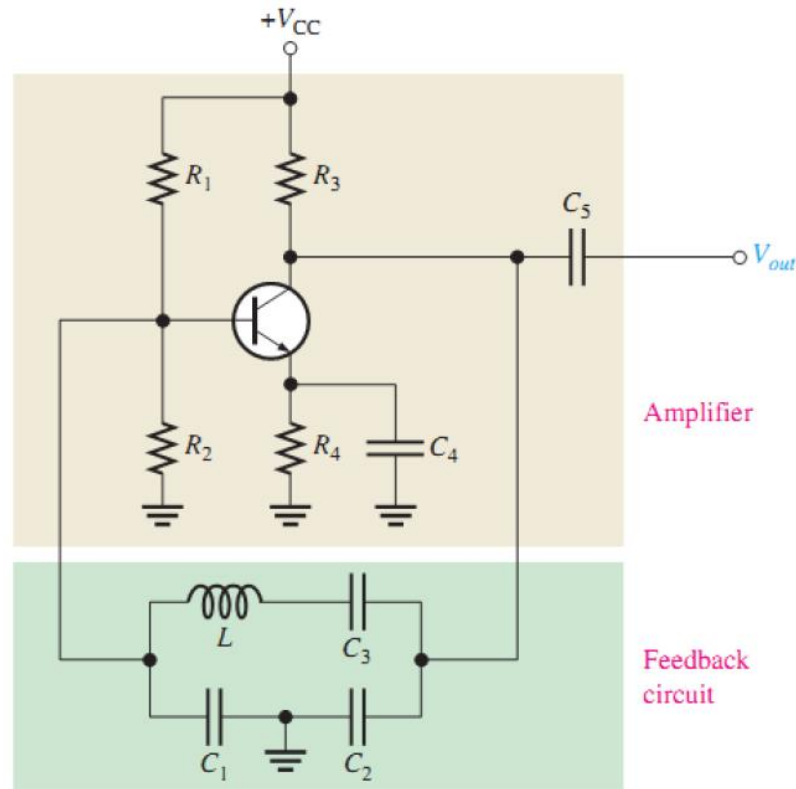

$$\omega = \frac{1}{\sqrt{LC_T}}$$

# Clapp Oscillator

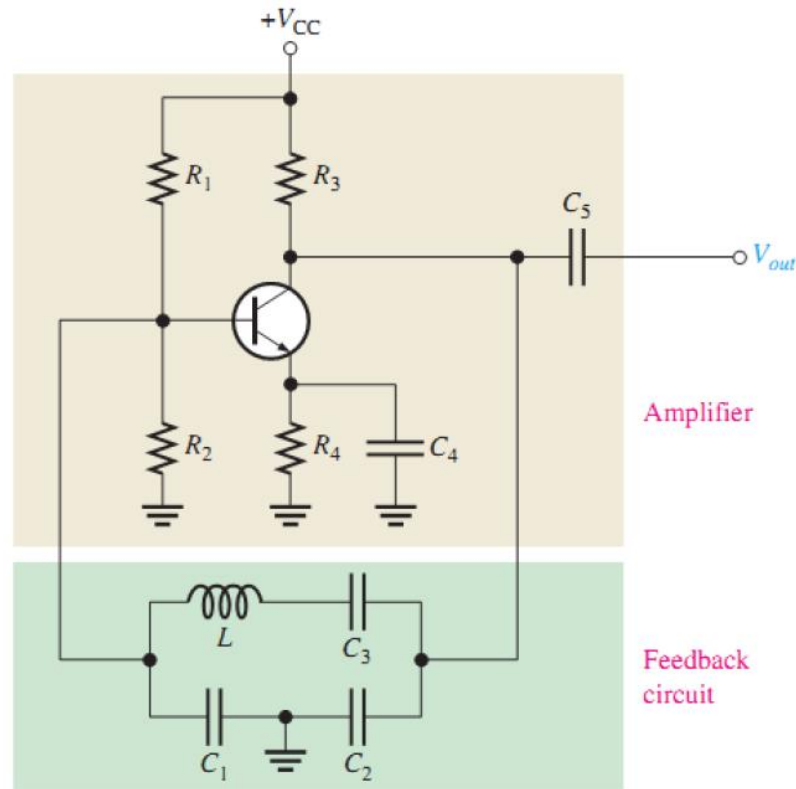

$$\omega = \frac{1}{\sqrt{LC_T}}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$