

Basic Electronic Circuits

(IEC-103)


Lecture-20

Multistage Amplifiers

Cascade Connection

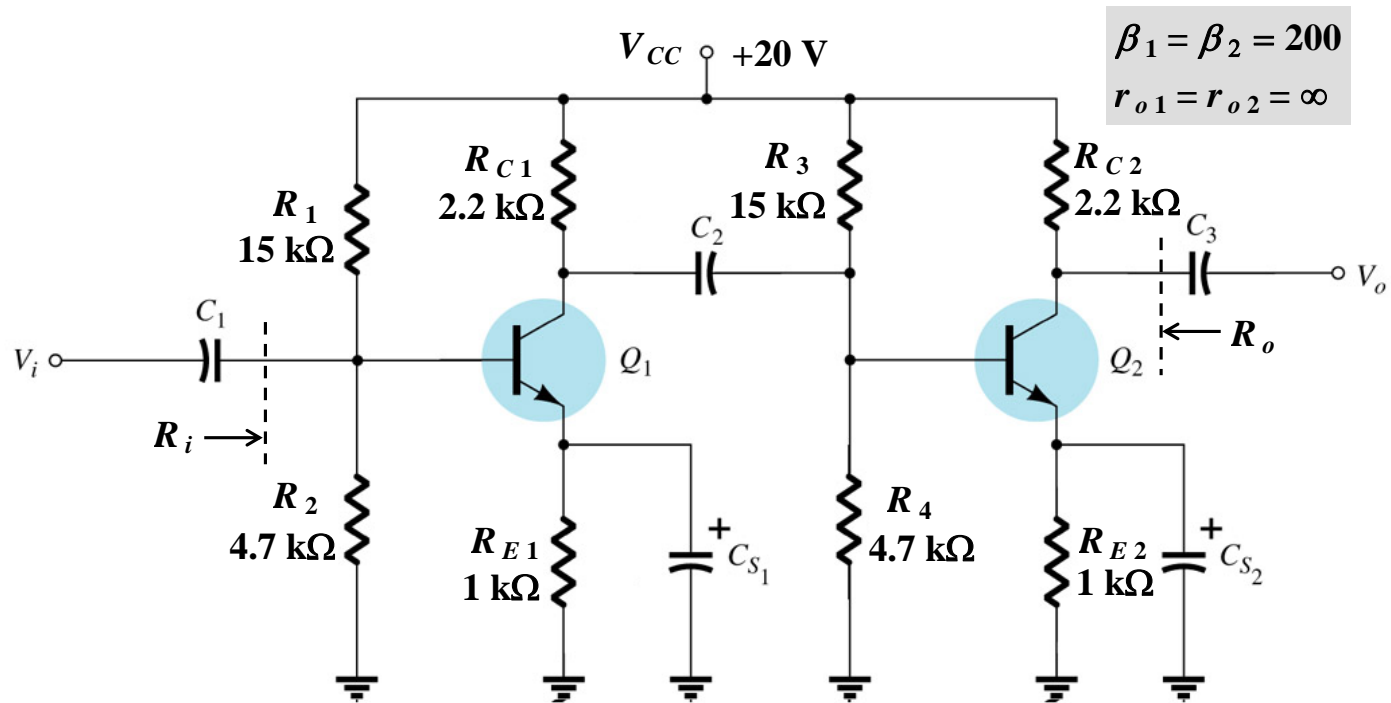
Example

Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



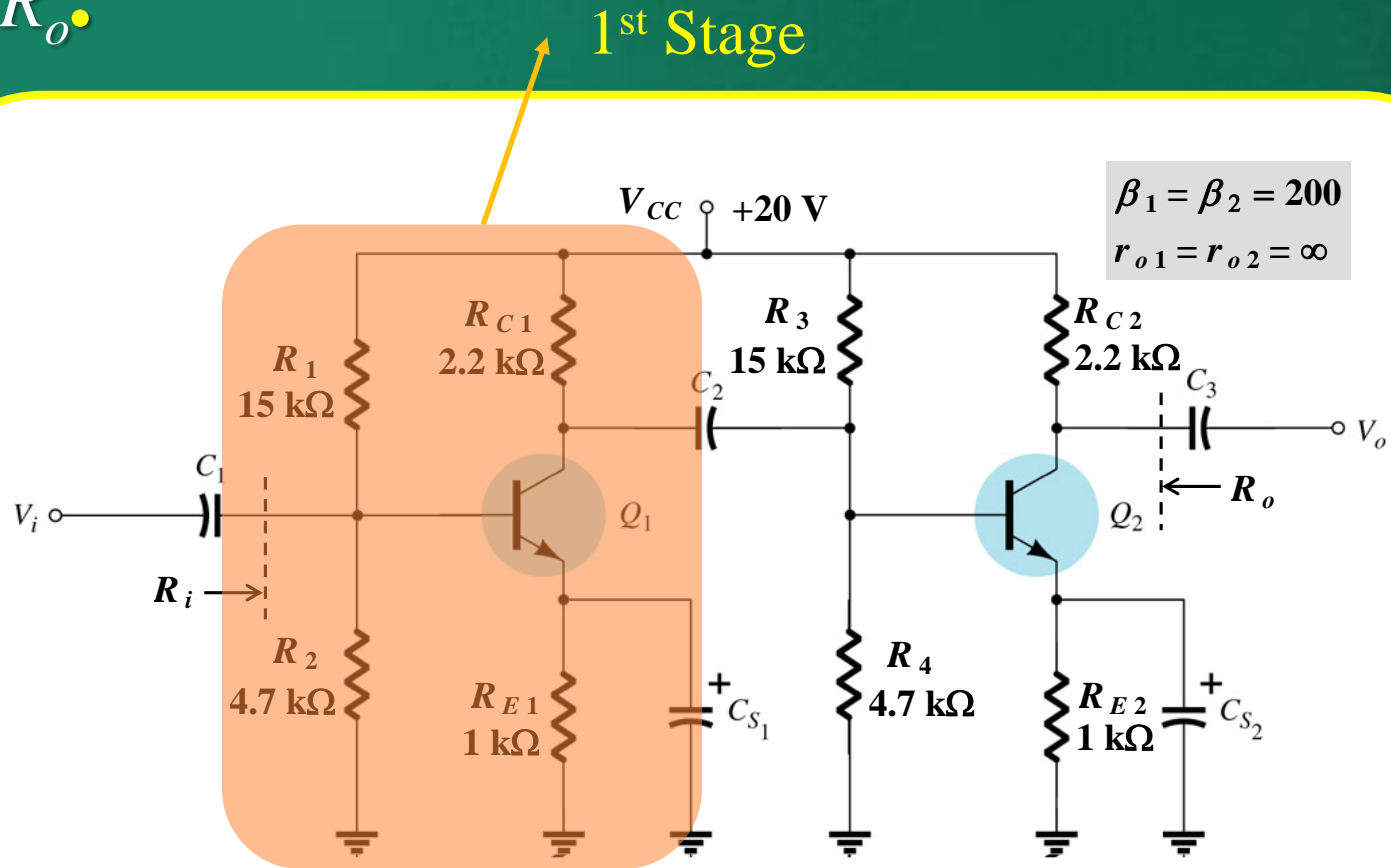
Example

Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



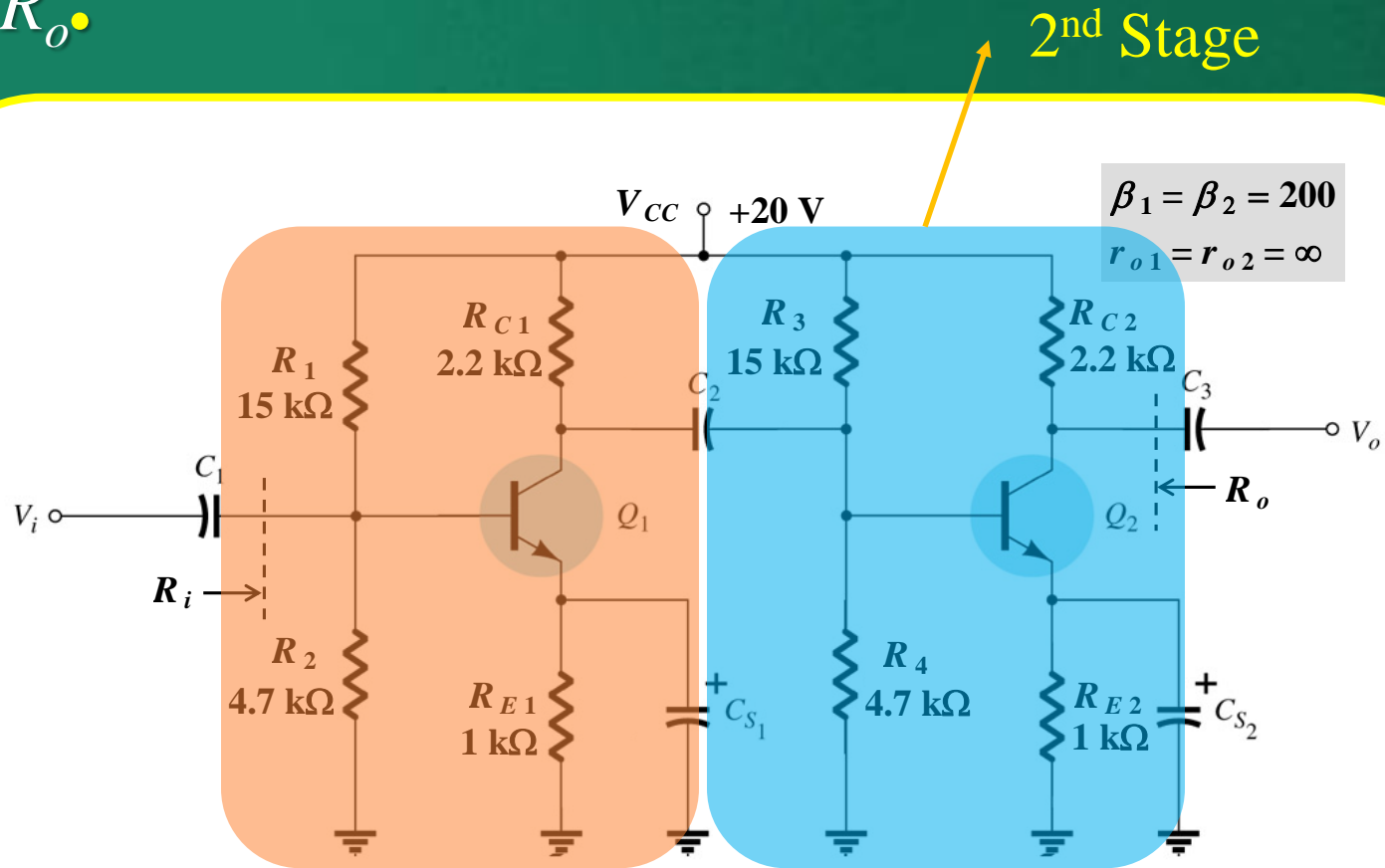Example


Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



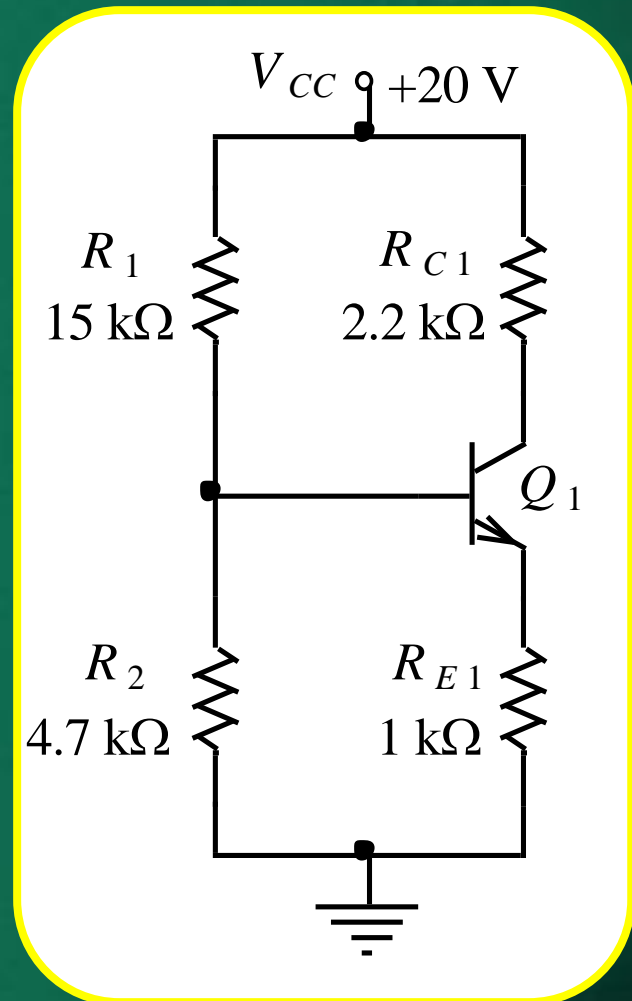Example (continued)


DC analysis

The circuit under DC condition (stage 1 and 2 are identical)



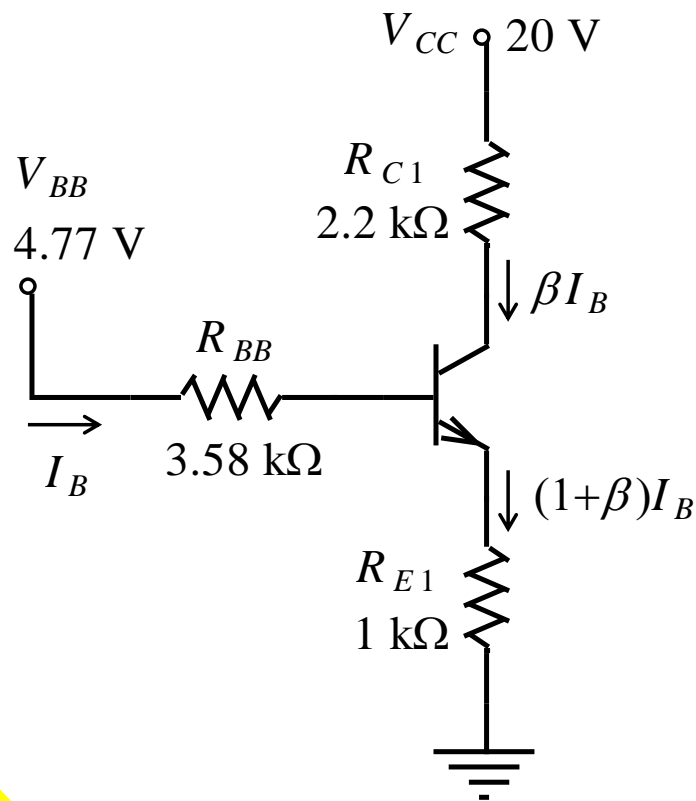Example (continued)

Applying Thévenin's theorem, the circuit becomes



$$I_{BQ1} = I_{BQ2} = 19.89\text{ }\mu\text{A}$$

$$I_{CQ1} = I_{CQ2} = 3.979\text{ mA}$$


$$r_{\pi 1} = r_{\pi 2} = 1.307\text{ k}\Omega$$

$$g_{m1} = g_{m2} = 0.153\text{ A/V}$$

Example (continued)

AC analysis


The small-signal equivalent circuit

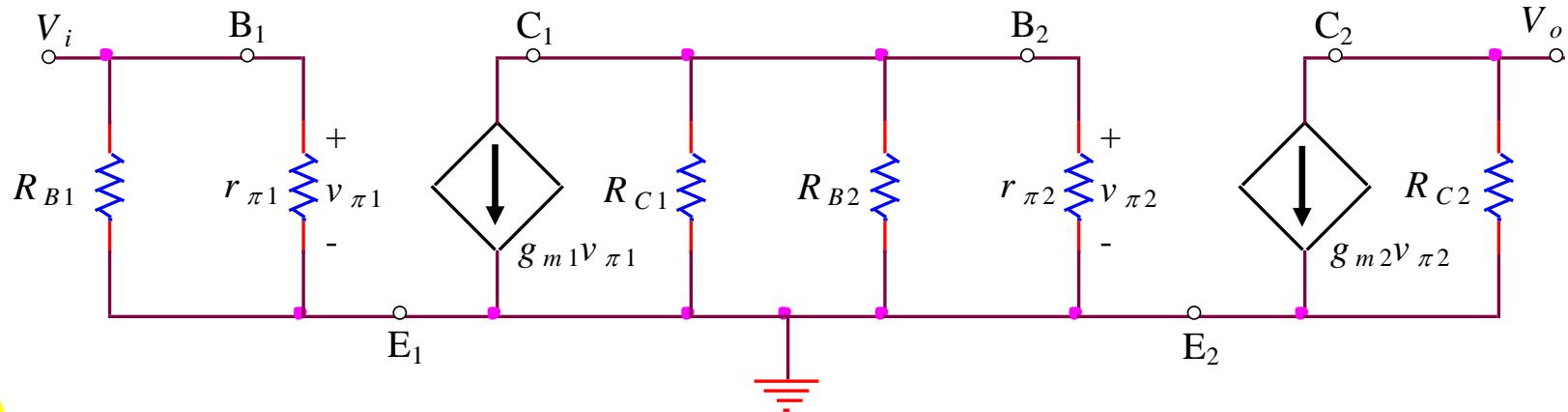

Example (continued)

AC analysis


The small-signal equivalent circuit

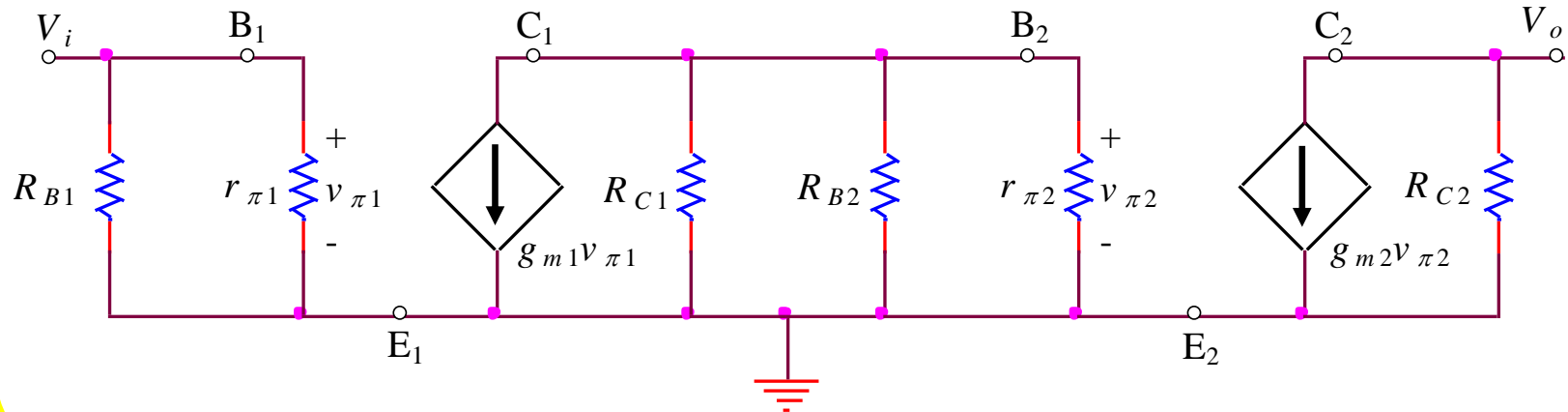

Example (continued)

AC analysis

The small-signal equivalent circuit

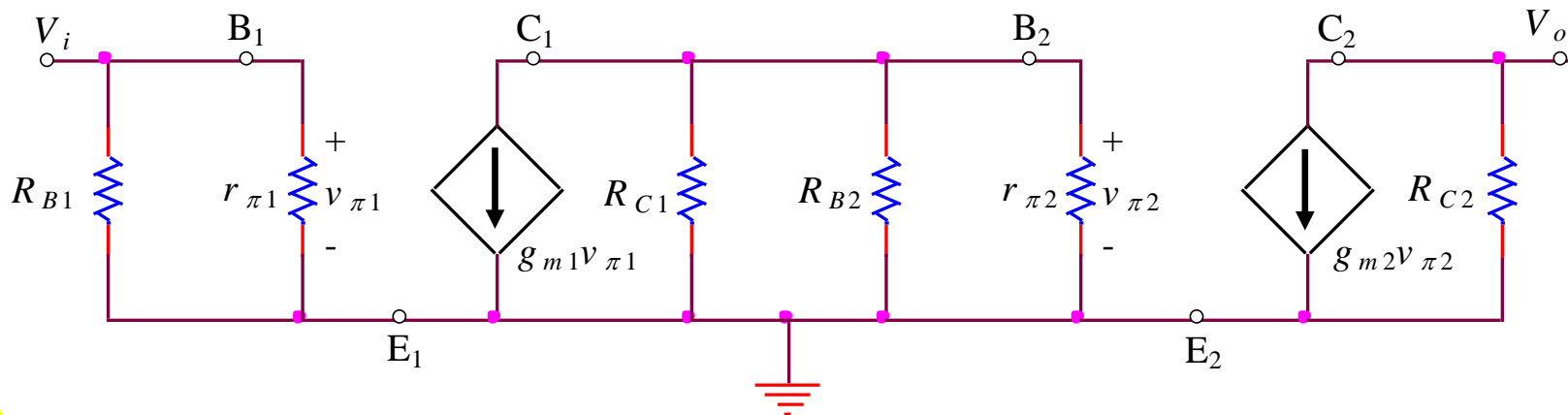

$$R_{B1} = R_1 // R_2$$

$$R_{B2} = R_3 // R_4$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

$$v_{\pi2} = -g_{m1}v_{\pi1}(R_{C1} // R_{B2} // r_{\pi2})$$

Example (continued)

$$V_o = -g_{m2} v_{\pi 2} R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi 2}} = -g_{m2} R_{C2}$$

$$v_{\pi 2} = -g_{m1} v_{\pi 1} (R_{C1} // R_{B2} // r_{\pi 2})$$

$$= -g_{m1} V_i (R_{C1} // R_{B2} // r_{\pi 2})$$

$$[v_{\pi 1} = V_i]$$

Example (continued)

$$V_o = -g_{m2} v_{\pi 2} R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi 2}} = -g_{m2} R_{C2}$$

$$v_{\pi 2} = -g_{m1} v_{\pi 1} (R_{C1} // R_{B2} // r_{\pi 2})$$

$$= -g_{m1} V_i (R_{C1} // R_{B2} // r_{\pi 2})$$

$$[v_{\pi 1} = V_i]$$

$$A_1 = \frac{v_{\pi 2}}{V_i} = -g_{m2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Example (continued)

The small-signal voltage gain

$$A = A_1 A_2 = g_{m1} g_{m2} R_{C2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Example (continued)

The small-signal voltage gain

$$A = A_1 A_2 = g_{m1} g_{m2} R_{C2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Substituting values

$$R_{B1} = R_{B2} = R_3 // R_4 = 15 // 4.7 = 3.579 \text{ k}\Omega$$

$$R_{C1} // R_{B2} // r_{\pi 2} = 2.2 // 3.579 // 1.307 = 667 \text{ }\Omega$$

$$A = 0.153 \times 0.153 \times 2200 \times 667 = 34350 \text{ V/V}$$

Example (continued)

The input resistance

$$R_{in} = R_{B1} // r_{\pi 1} = 3.579 // 1.307 = 0.957 \text{ k}\Omega$$

Example (continued)

The input resistance

$$R_{in} = R_{B1} // r_{\pi 1} = 3.579 // 1.307 = 0.957 \text{ k}\Omega$$

The output resistance

$$R_o = R_{C2} = 2.2 \text{ k}\Omega$$

Cascode Connection

Cascode Connection

- ❑ A cascode connection has one transistor in series with another.

Cascode Connection

- ❑ A cascode connection has one transistor in series with another.
- ❑ The i/p applied to a C-E amplifier (Q_1) whose output is used to drive a C-B amplifier. (Q_2)


Cascode Connection

- ❑ A cascode connection has one transistor in series with another.
- ❑ The i/p applied to a C-E amplifier (Q_1) whose output is used to drive a C-B amplifier. (Q_2)
- ❑ The o/p signal current of Q_1 is the i/p signal of Q_2 .

Cascode Connection


- ❑ A cascode connection has one transistor in series with another.
- ❑ The i/p applied to a C-E amplifier (Q_1) whose output is used to drive a C-B amplifier. (Q_2)
- ❑ The o/p signal current of Q_1 is the i/p signal of Q_2 .
- ❑ The advantage: provides a high i/p impedance. The C-B stage providing good high frequency operation

Cascode Amplifier

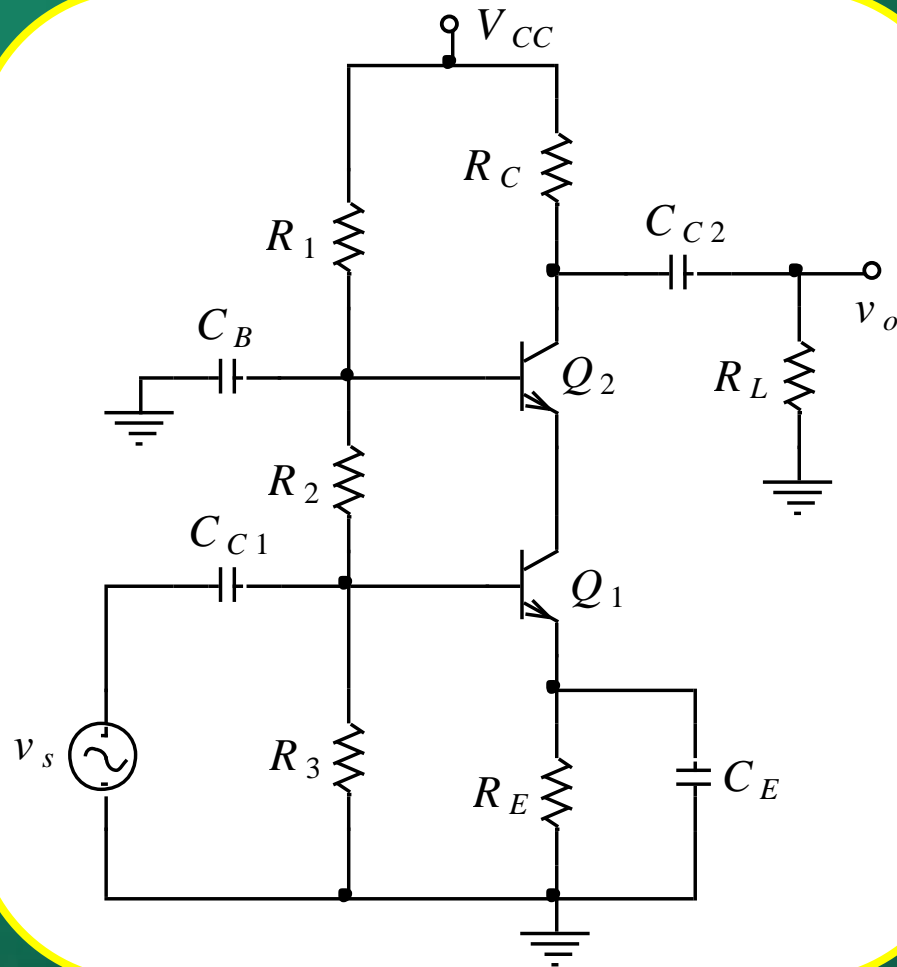


Cascode Amplifier

DC analysis

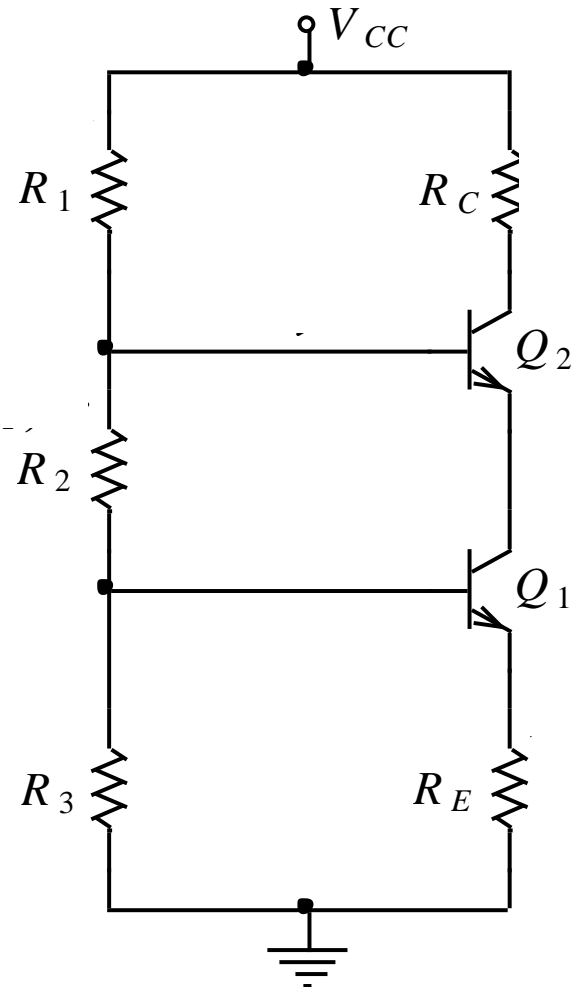


Cascode Amplifier

DC analysis

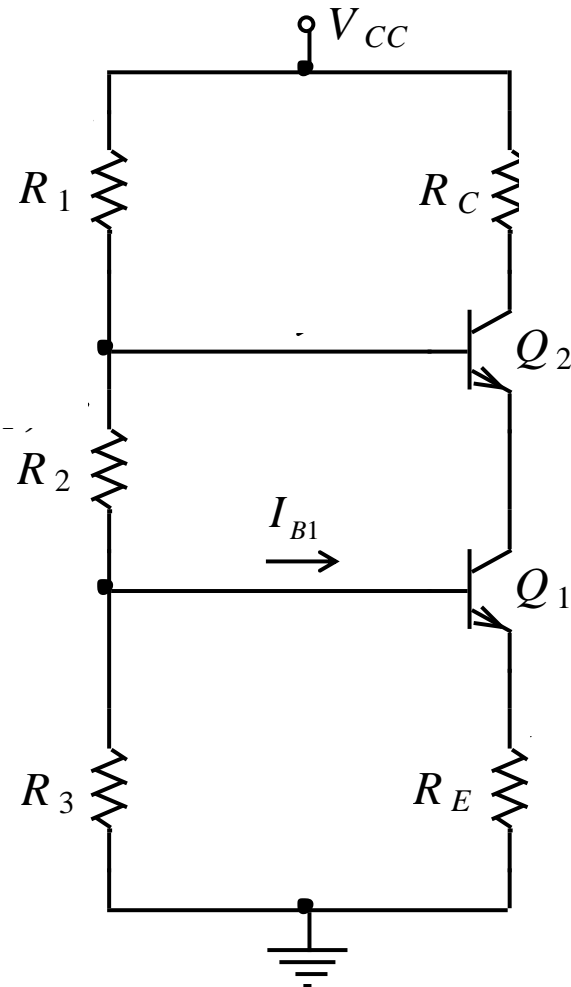


Cascode Amplifier

DC analysis

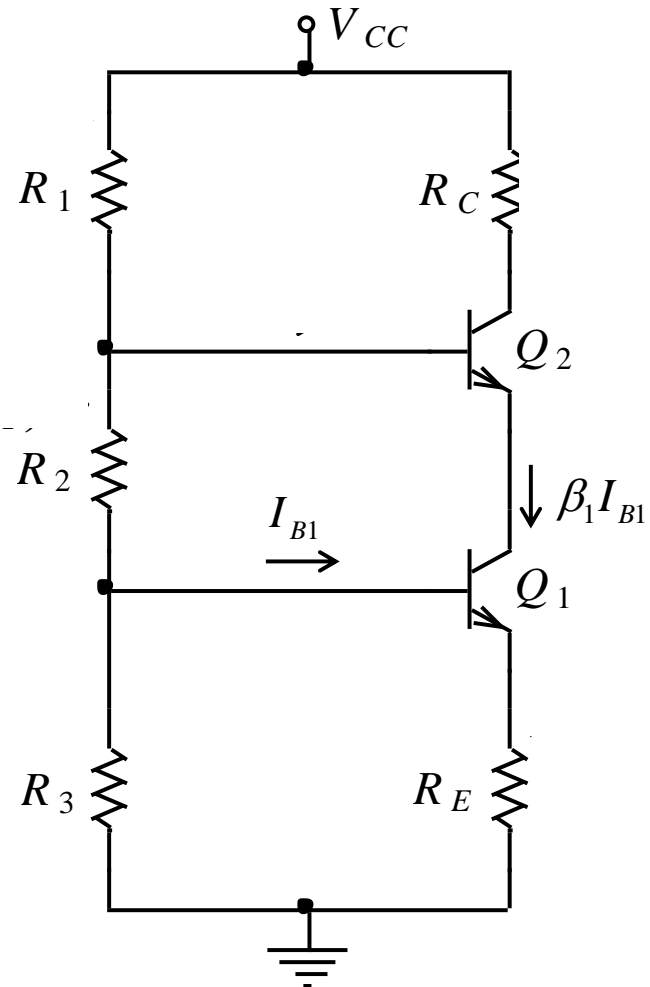


Cascode Amplifier

DC analysis

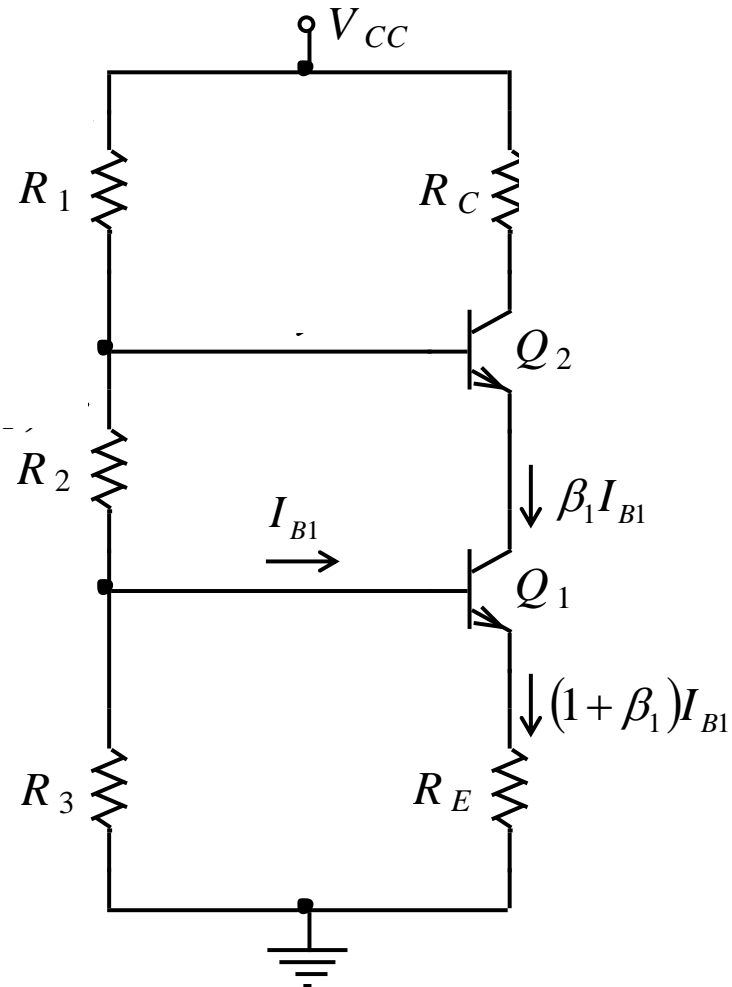


Cascode Amplifier

DC analysis

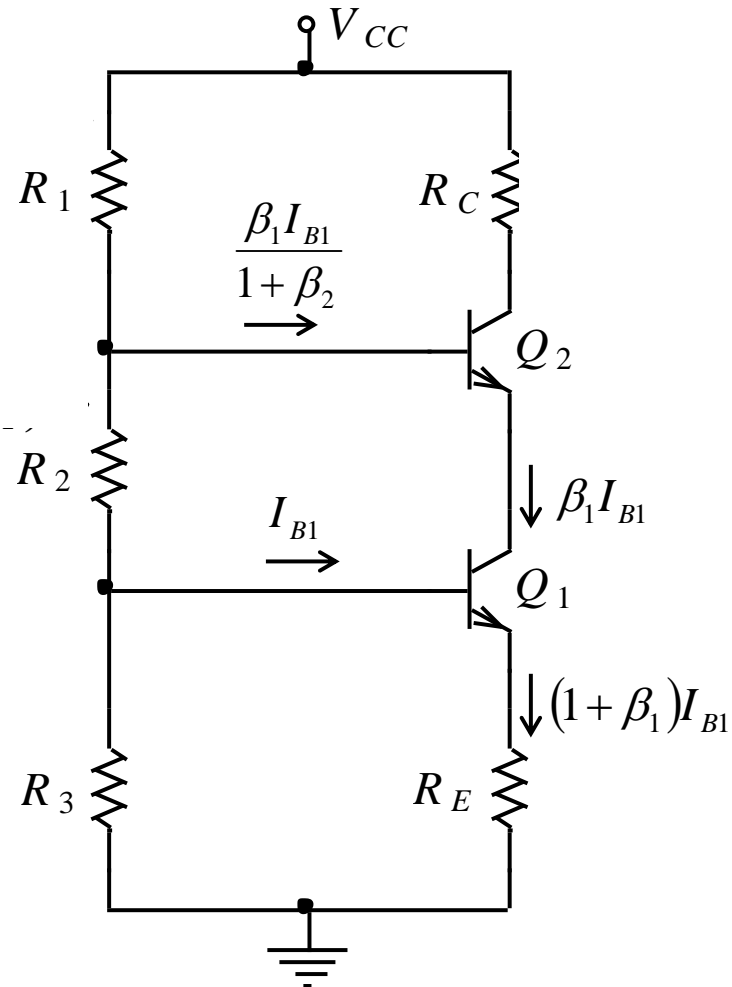


Cascode Amplifier

DC analysis

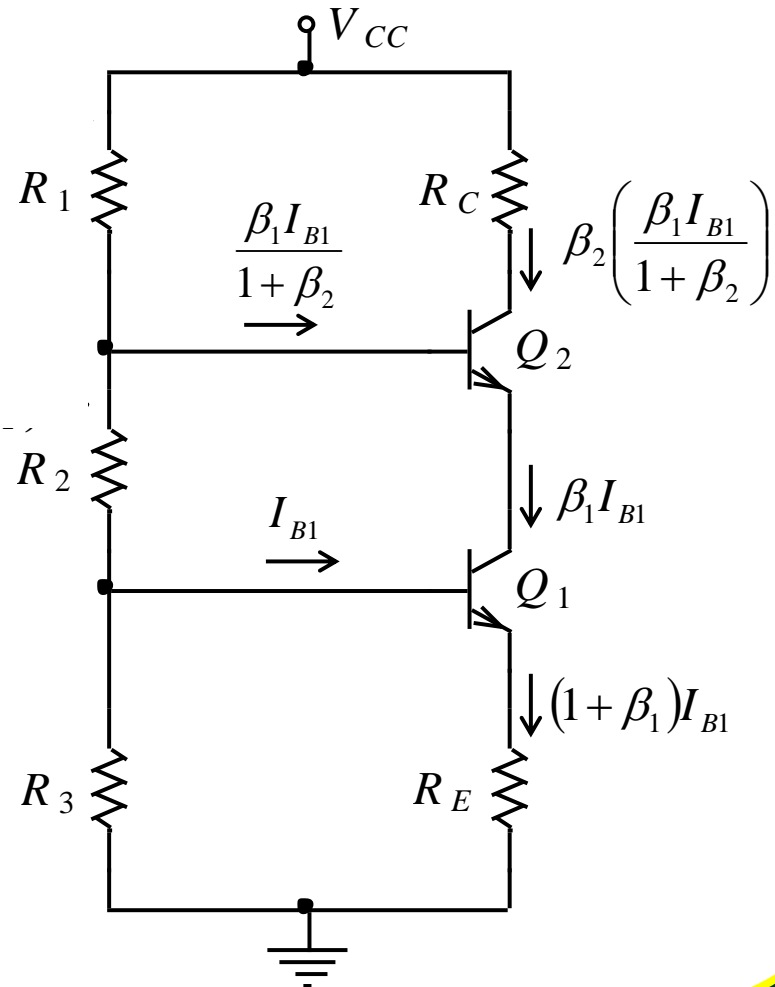


Cascode Amplifier

DC analysis

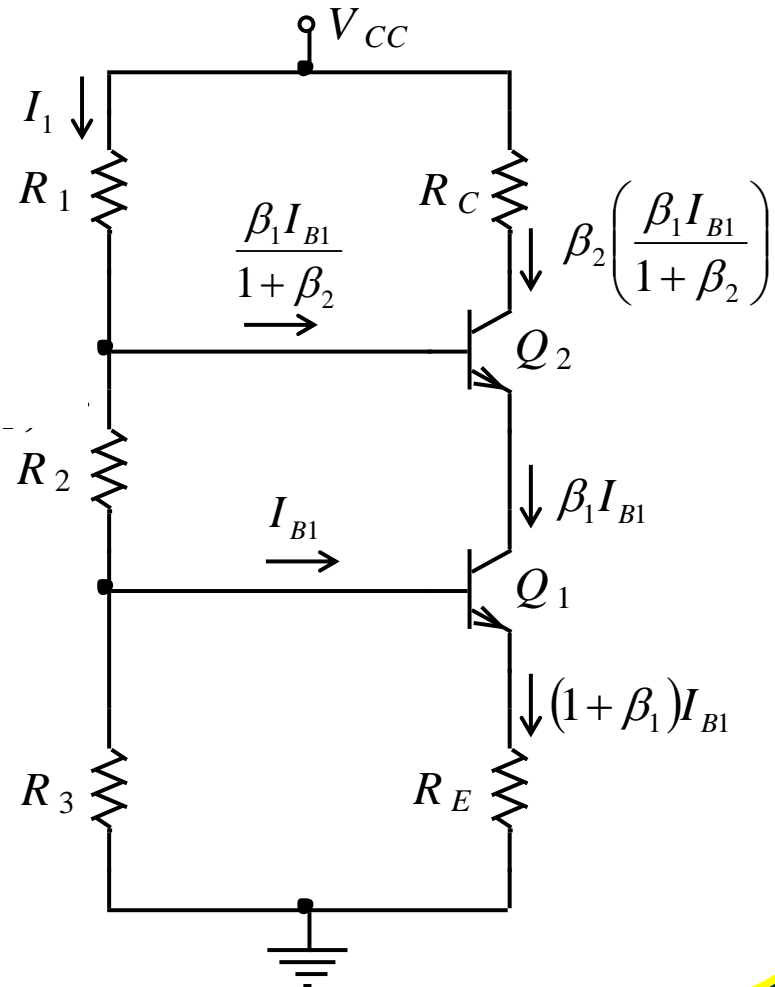


Cascode Amplifier

DC analysis

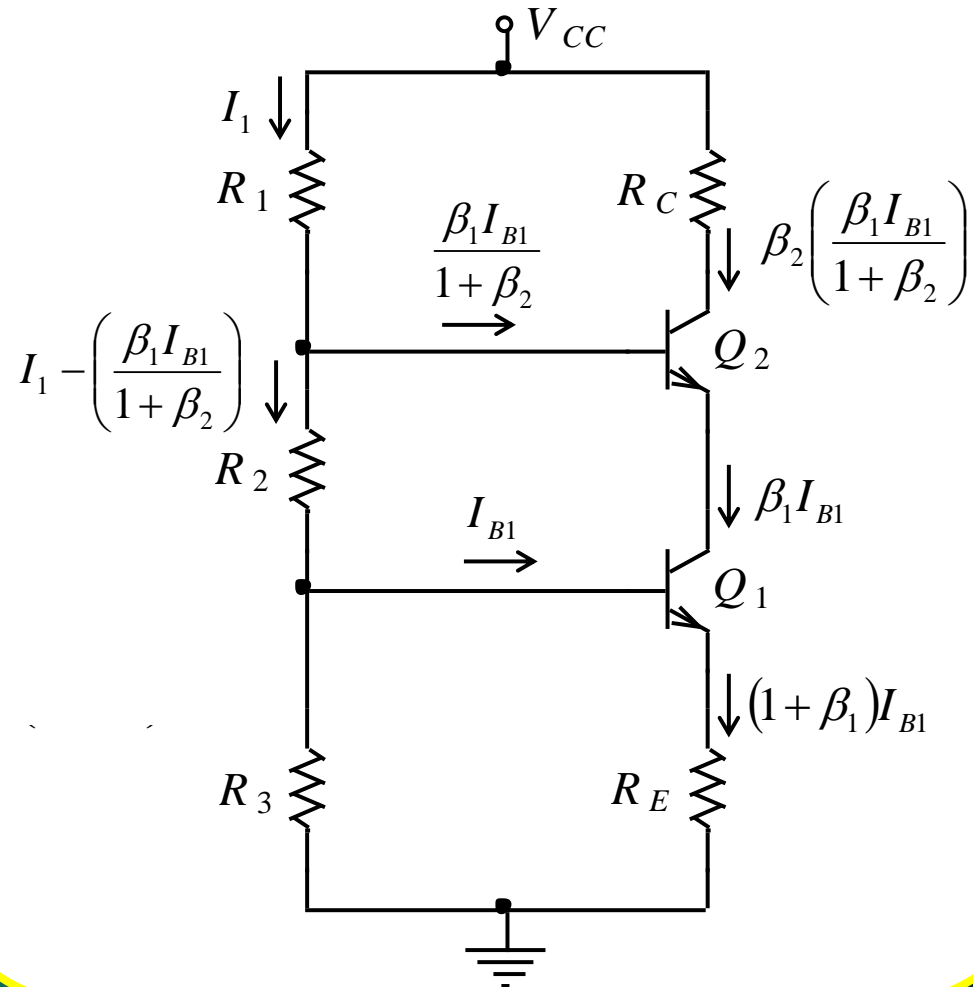

Cascode Amplifier

DC analysis

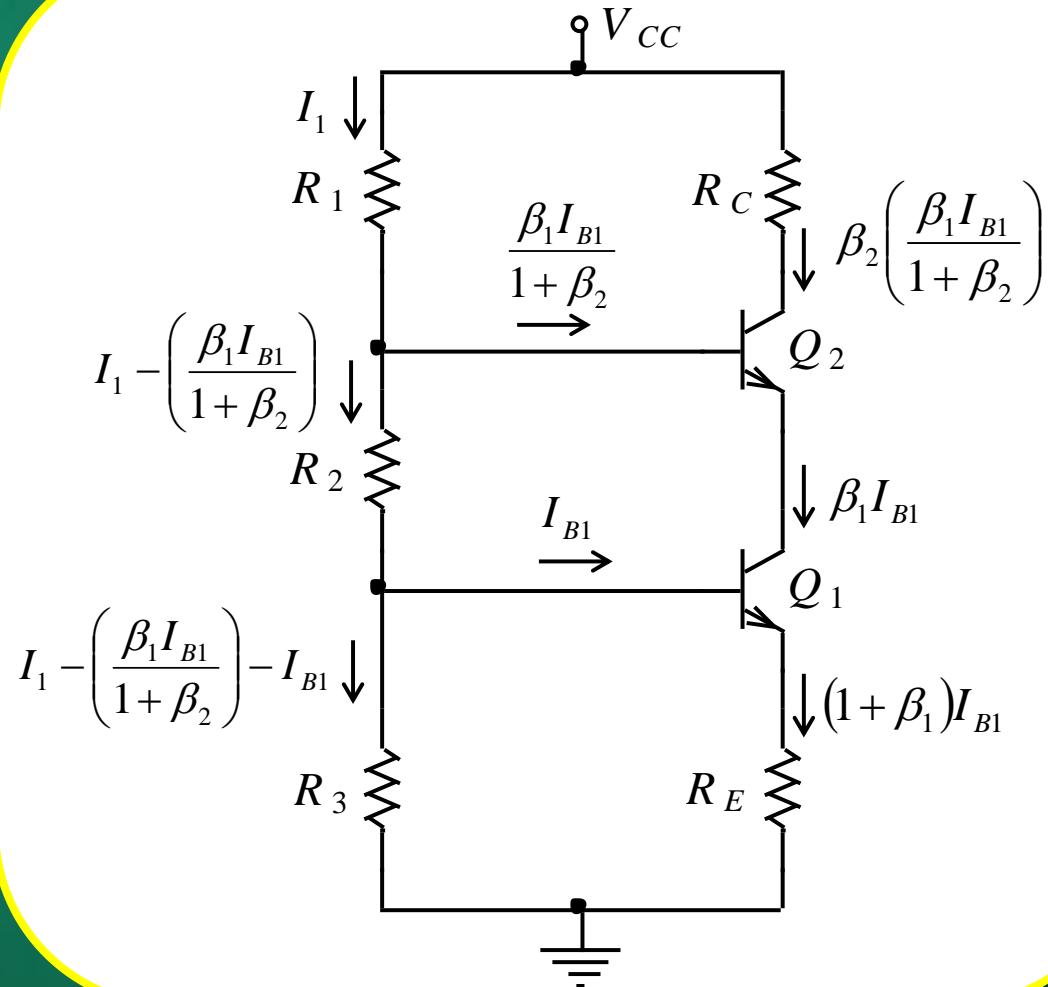

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ for both BJT's

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ **for both BJT's**

$$R_1 I_1 + R_2 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} \right) + R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = V_{CC}$$

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ **for both BJT's**

$$R_1 I_1 + R_2 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} \right) + R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = V_{CC}$$

$$R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = 0.7 + R_E (\beta_1 + 1) I_{B1}$$

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ for both BJT's

$$R_1 I_1 + R_2 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} \right) + R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = V_{CC}$$


$$R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = 0.7 + R_E (\beta_1 + 1) I_{B1}$$

The above equations may solved for the two unknown currents namely I_1 and I_{B1} .

Cascode Amplifier

AC analysis

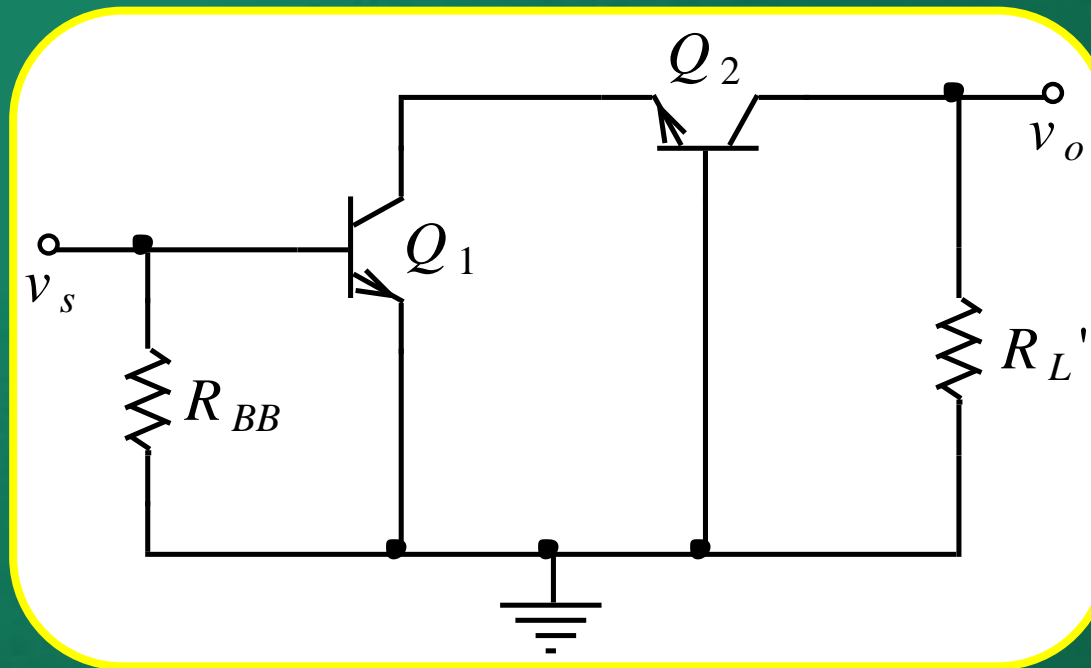
The equivalent circuit under AC condition



Cascode Amplifier

AC analysis

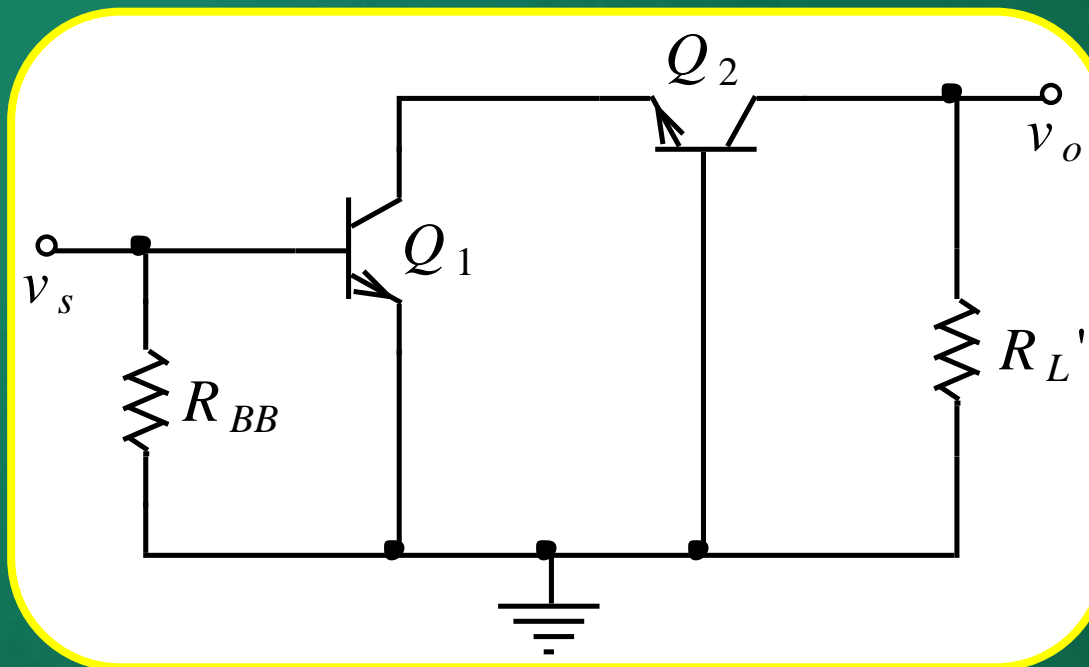The equivalent circuit under AC condition




$$R_{BB} = R_2 // R_3$$

$$R_L' = R_C // R_L$$


Cascode Amplifier

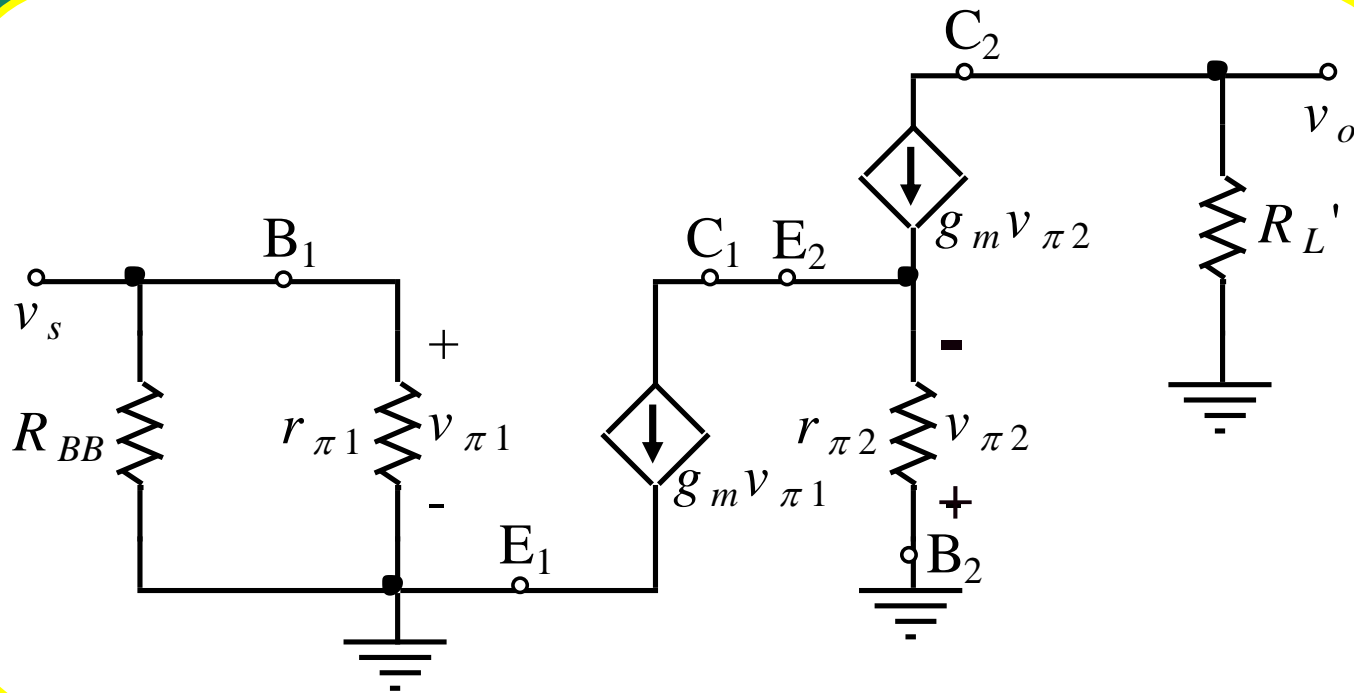The ac equivalent circuit using hybrid- π model



Cascode Amplifier

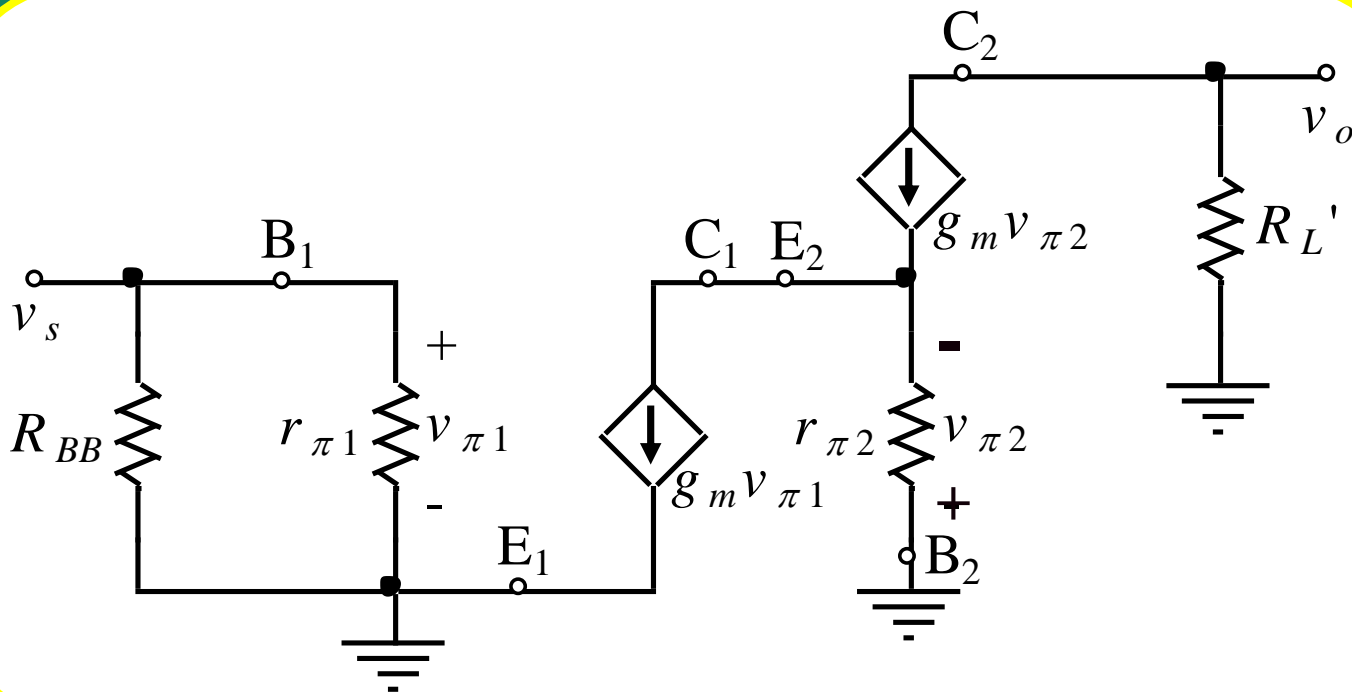The ac equivalent circuit using hybrid- π model



$$R_{BB} = R_2 // R_3$$

$$R_L' = R_C // R_L$$

Cascode Amplifier

$$v_o = -g_{m2}v_{\pi2}R_L' \quad (1)$$

Cascode Amplifier

$$v_o = -g_{m2}v_{\pi2}R_L' \quad (1)$$

At node E_2

$$g_{m1}v_{\pi1} = \frac{v_{\pi2}}{r_{\pi2}} + g_{m2}v_{\pi2}$$

Or

$$v_{\pi2} = \frac{g_{m1}r_{\pi2}v_{\pi1}}{1 + g_{m2}r_{\pi2}}$$

Cascode Amplifier

$$v_o = -g_{m2} v_{\pi 2} R_L' \quad (1)$$

At node E_2

$$g_{m1} v_{\pi 1} = \frac{v_{\pi 2}}{r_{\pi 2}} + g_{m2} v_{\pi 2}$$

Or

$$v_{\pi 2} = \frac{g_{m1} r_{\pi 2} v_{\pi 1}}{1 + g_{m2} r_{\pi 2}}$$

Substituting in (1);

$$v_o = -\left(\frac{g_{m1} g_{m2} r_{\pi 2}}{1 + g_{m2} r_{\pi 2}} \right) R_L' v_{\pi 1} = -g_{m1} \left(\frac{\beta_2}{1 + \beta_2} \right) R_L' v_s$$

Cascode Amplifier

The small-signal voltage gain

$$A_v = \frac{v_o}{v_s} = -g_{m1} \left(\frac{\beta_2}{1 + \beta_2} \right) R_L'$$

Cascode Amplifier

The small-signal voltage gain

$$A_v = \frac{v_o}{v_s} = -g_{m1} \left(\frac{\beta_2}{1 + \beta_2} \right) R_L'$$

When $\beta_2 \gg 1$


$$A_v \cong -g_{m1} R_L'$$

Darlington Connection

Darlington pair

Internal connection;

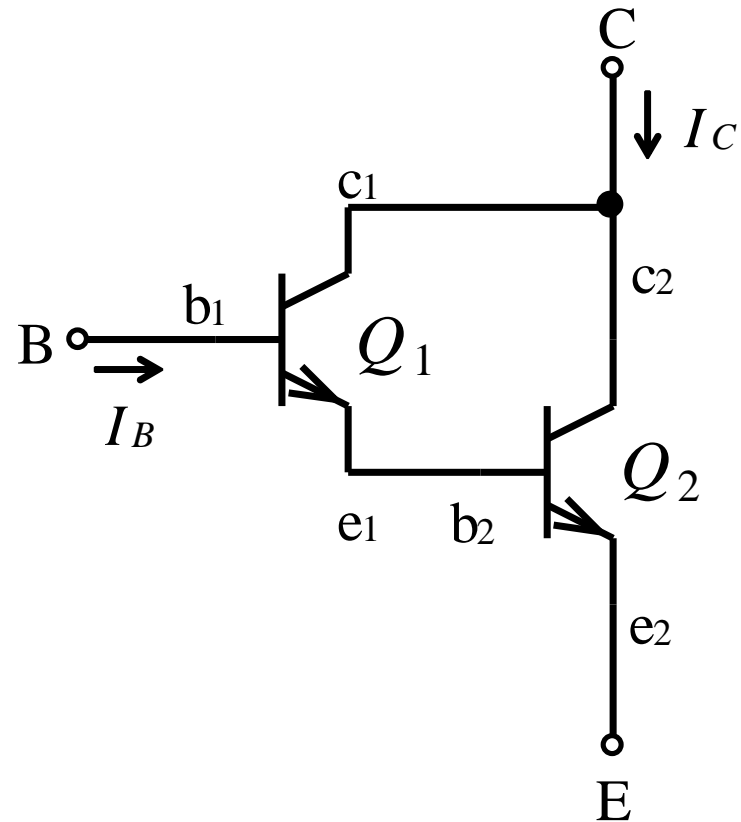
- **Collectors of Q_1 and Q_2**
- **Emitter of Q_1 and base of Q_2**



Provides high current gain : $I_C \cong \beta^2 I_B$


Darlington Connection

Currents in darlington pair

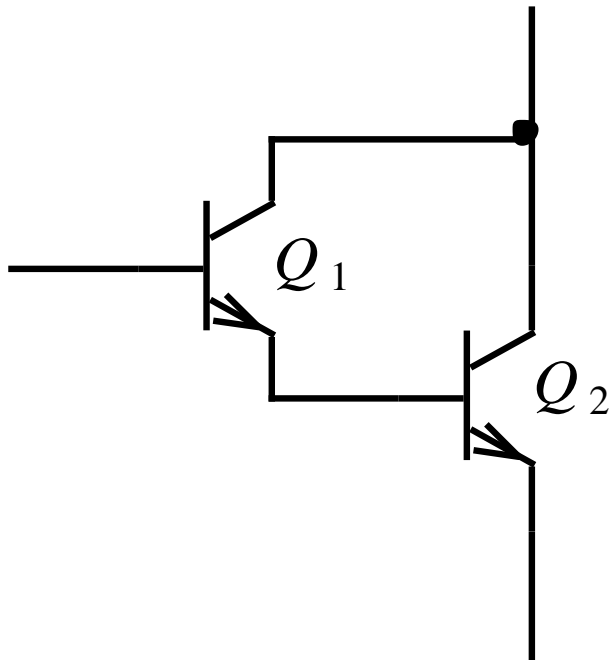


Darlington Connection

Currents in darlington pair

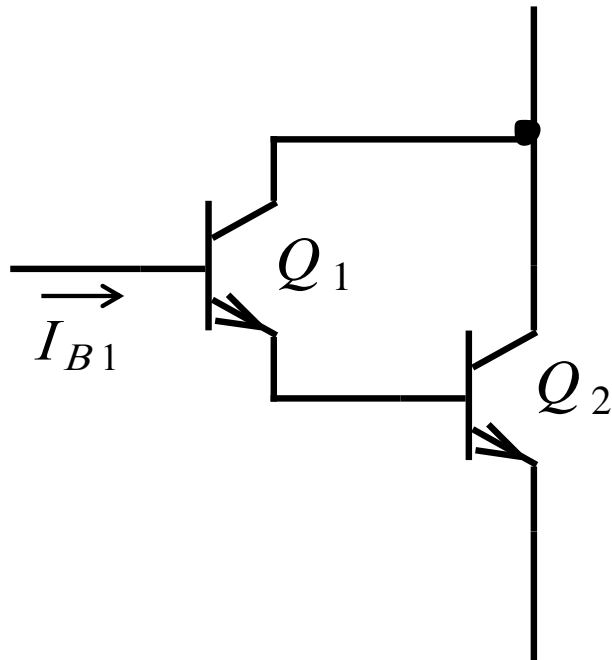


Darlington Connection

Currents in darlington pair

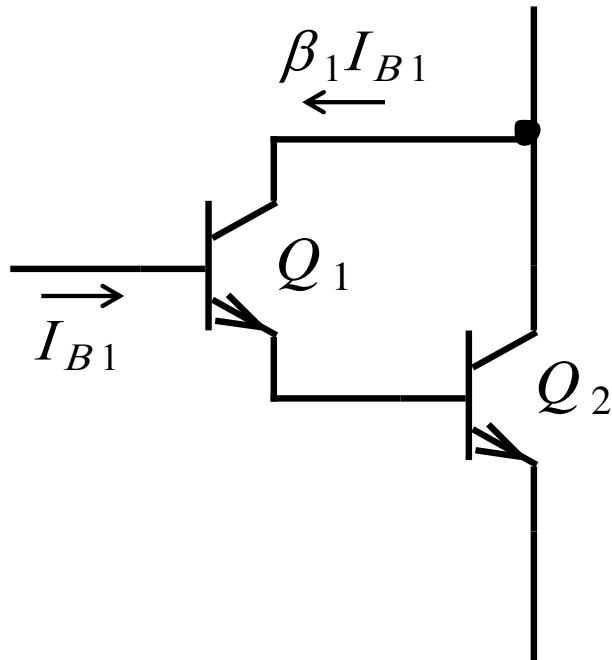


Darlington Connection

Currents in darlington pair

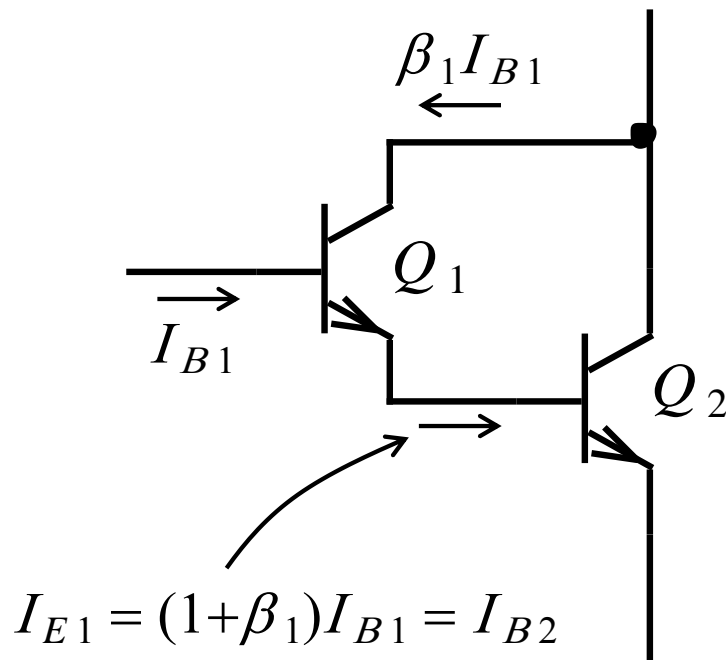


Darlington Connection

Currents in darlington pair

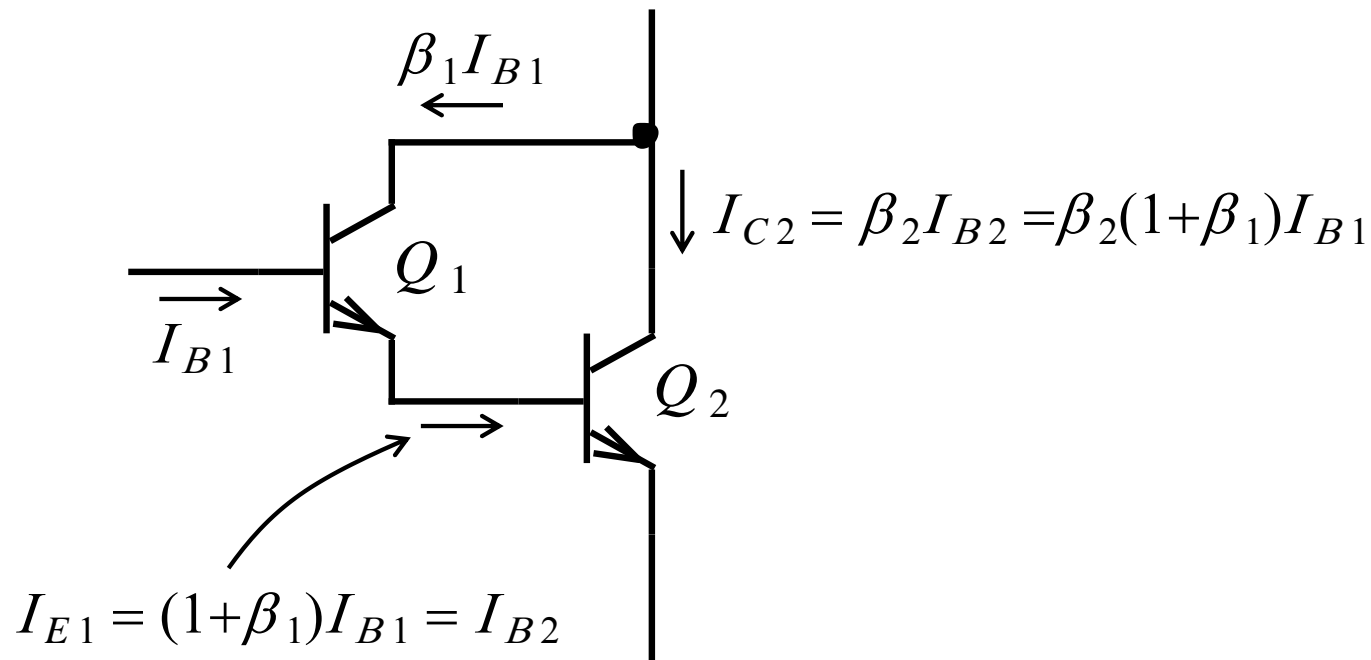


Darlington Connection

Currents in darlington pair

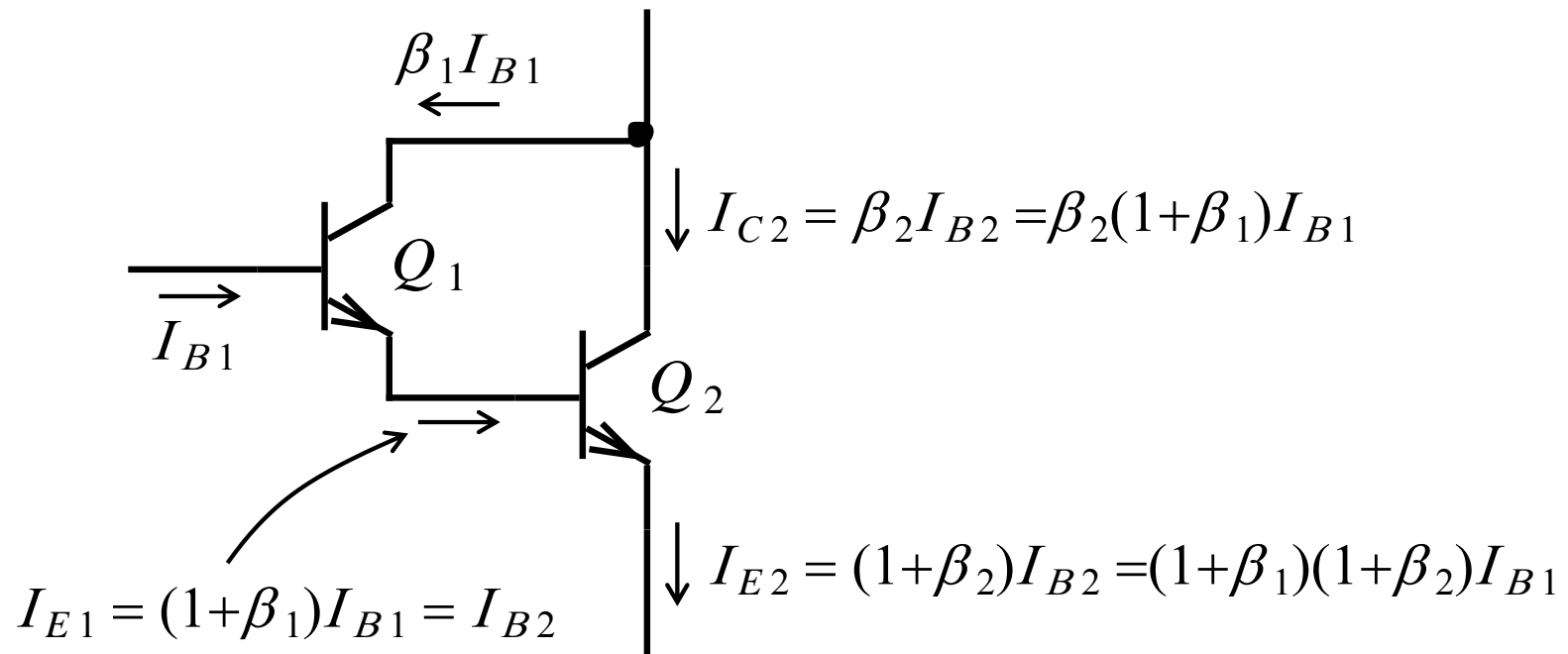


Darlington Connection

Currents in darlington pair

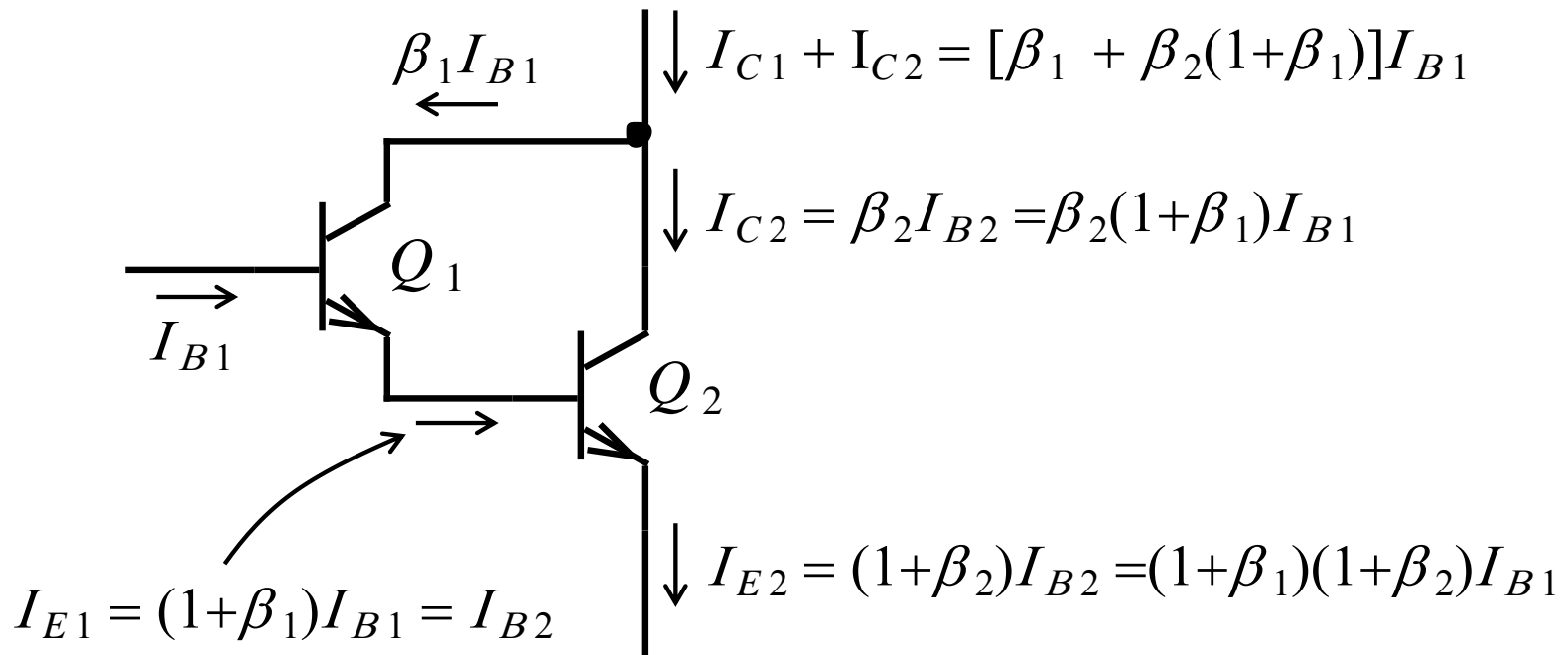


Darlington Connection

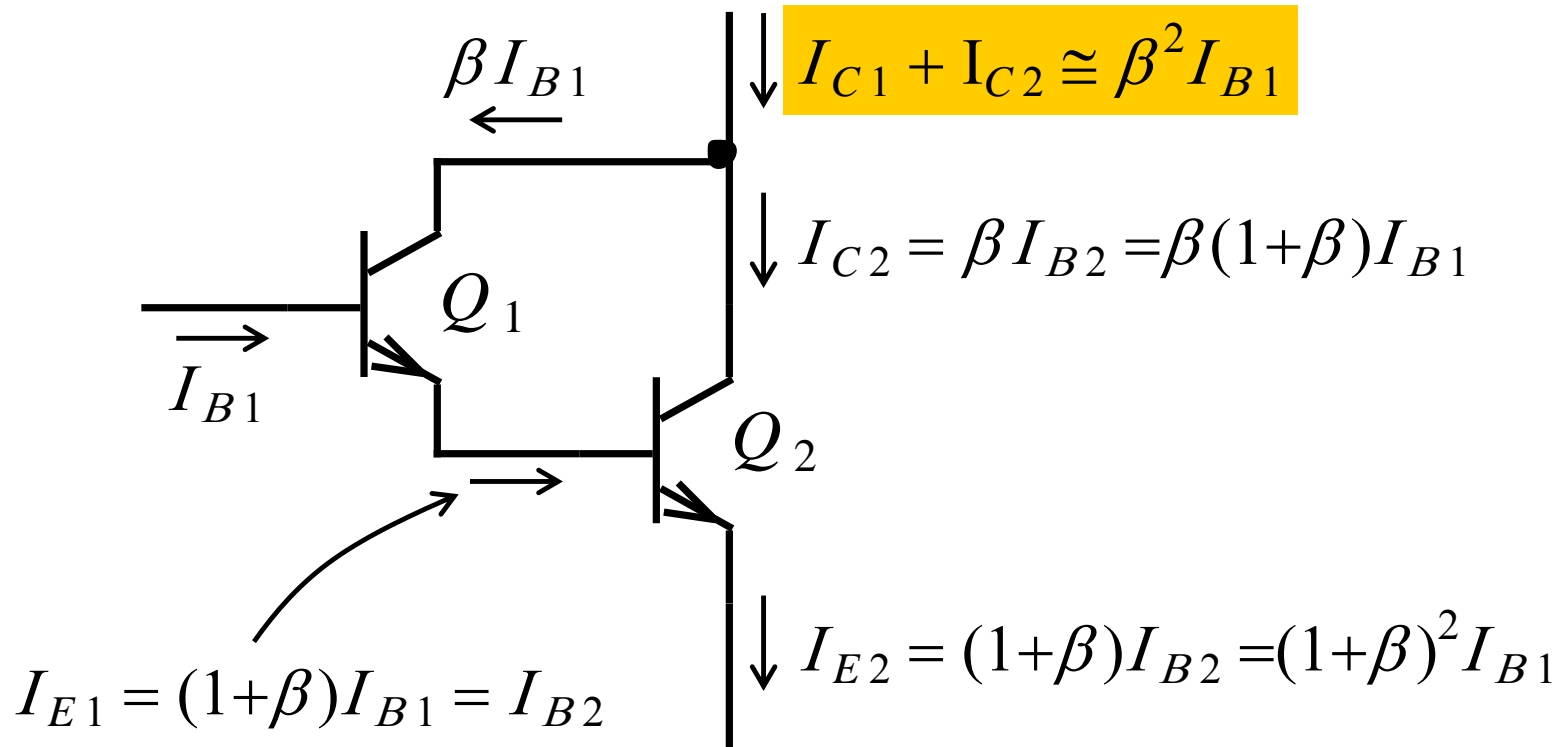If $\beta_1 = \beta_2 = \beta$ and assuming β is large




Darlington Connection

Hybrid- π model

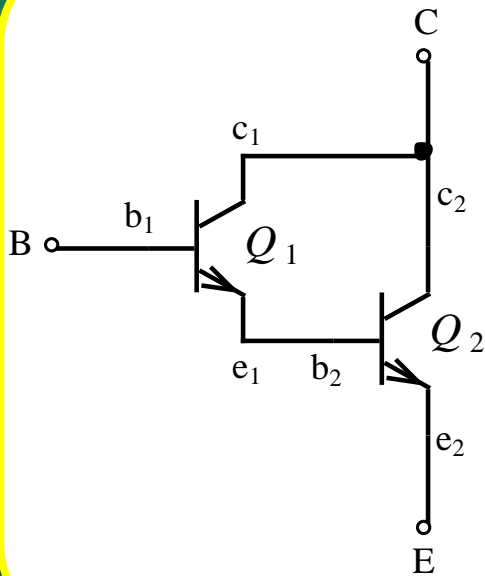


Darlington Connection

Hybrid- π model

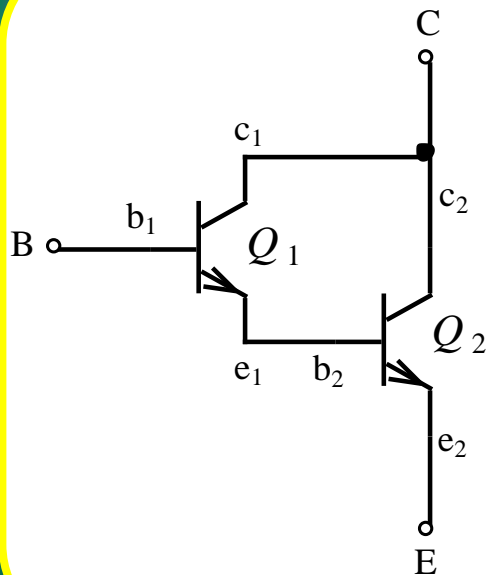


\equiv

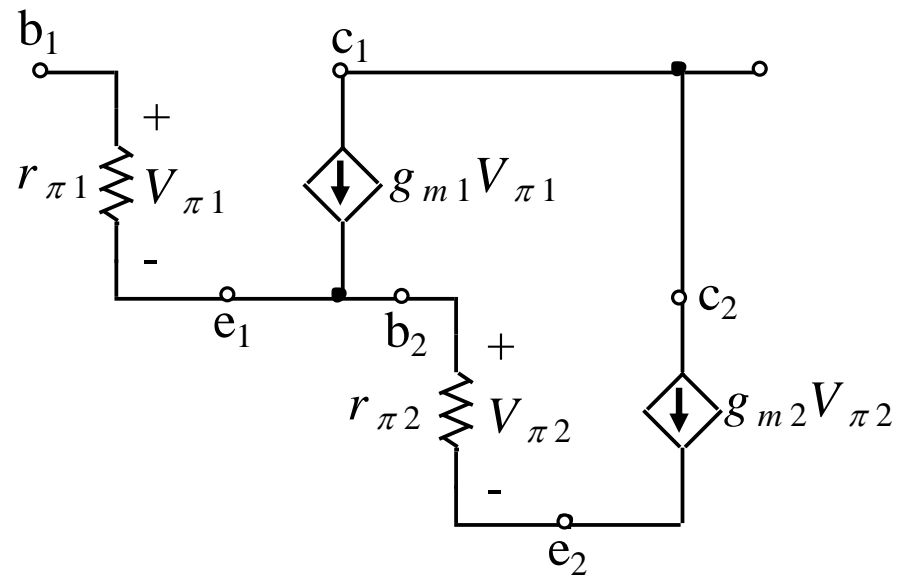

Darlington Connection


Darlington configuration provides

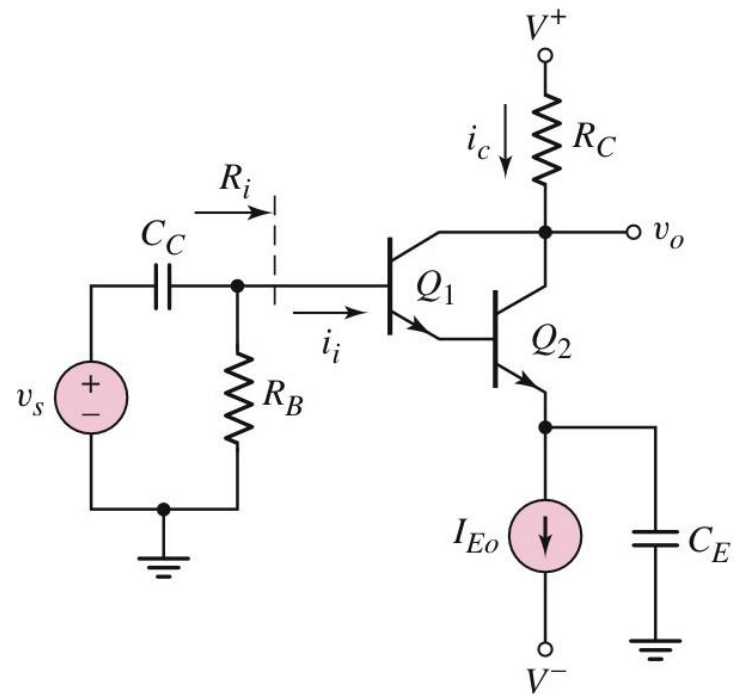- Increased current
- High input resistance




Darlington Connection

Small-signal equivalent circuit

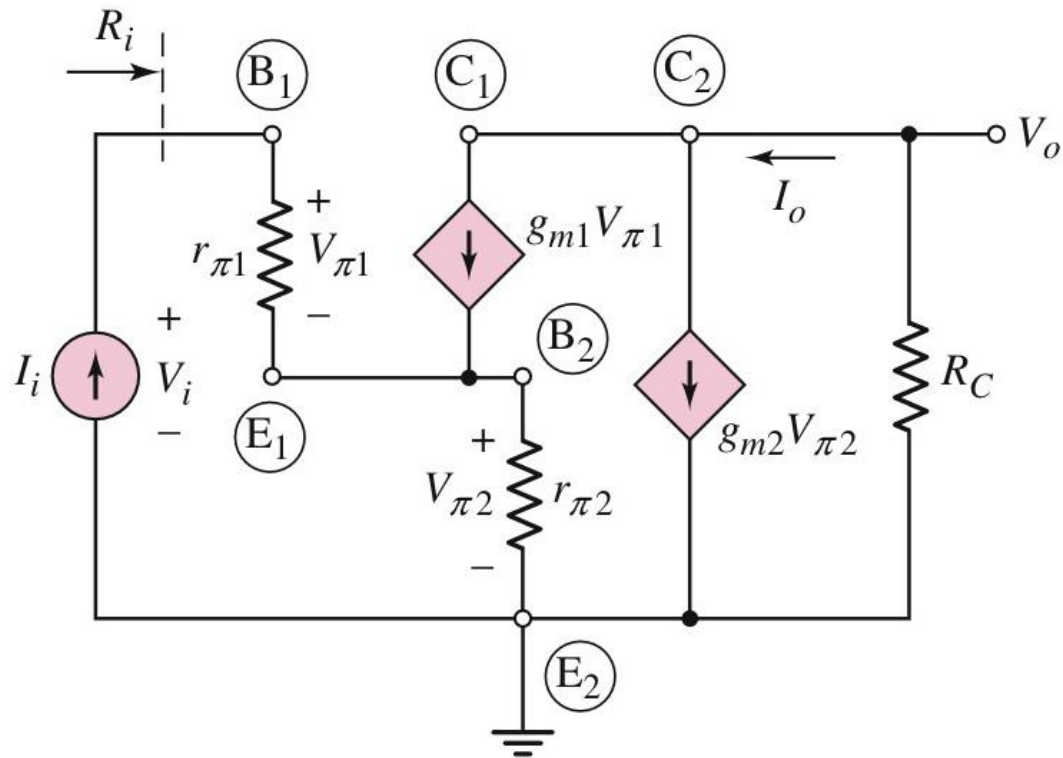


Darlington Connection

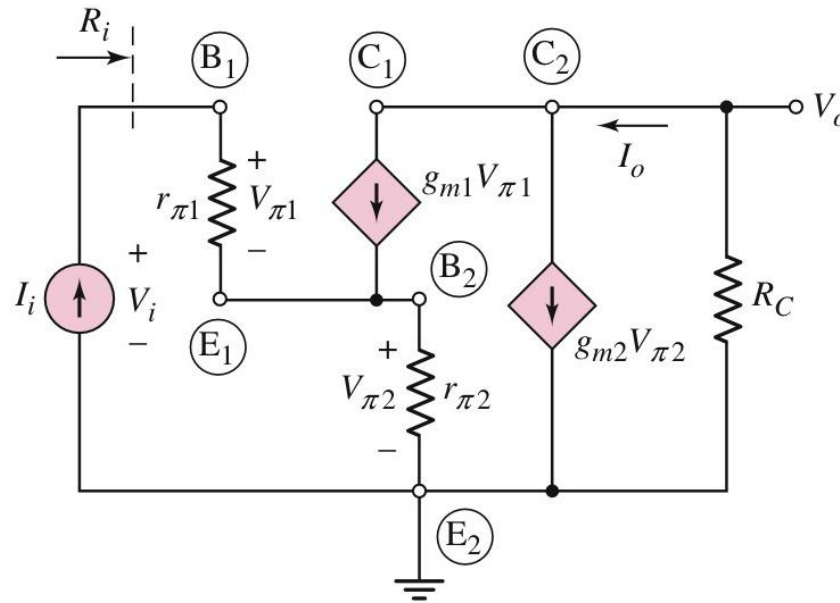

Darlington Connection

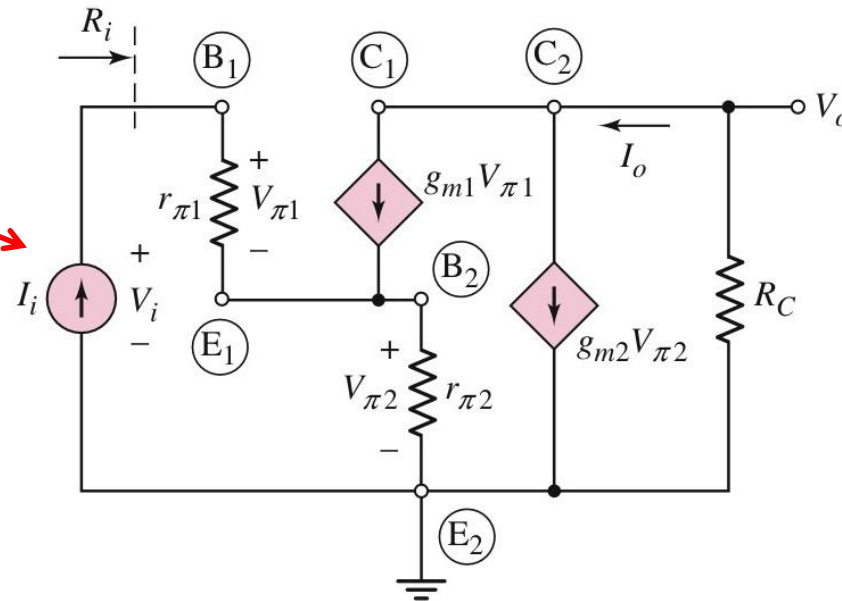
Input voltage source is transformed into current source



Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

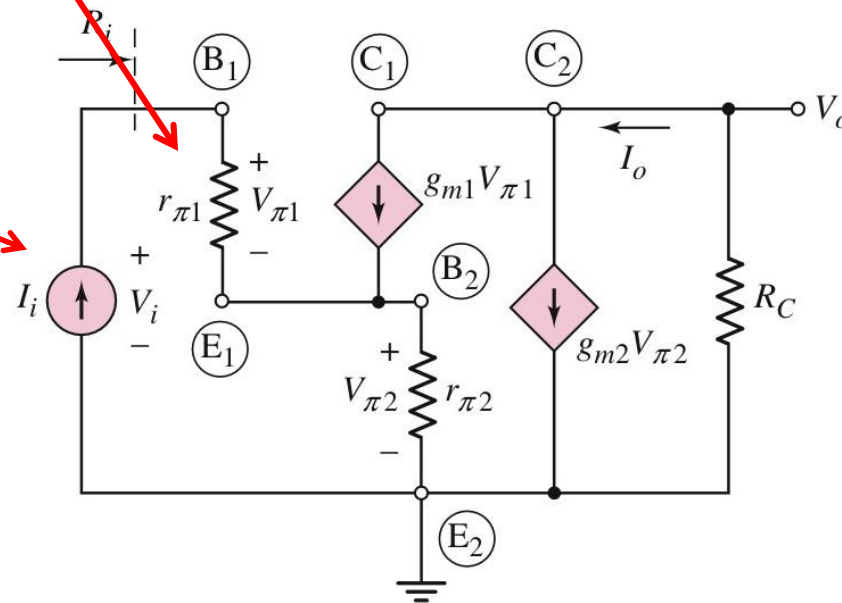Input voltage source is transformed into current source




Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

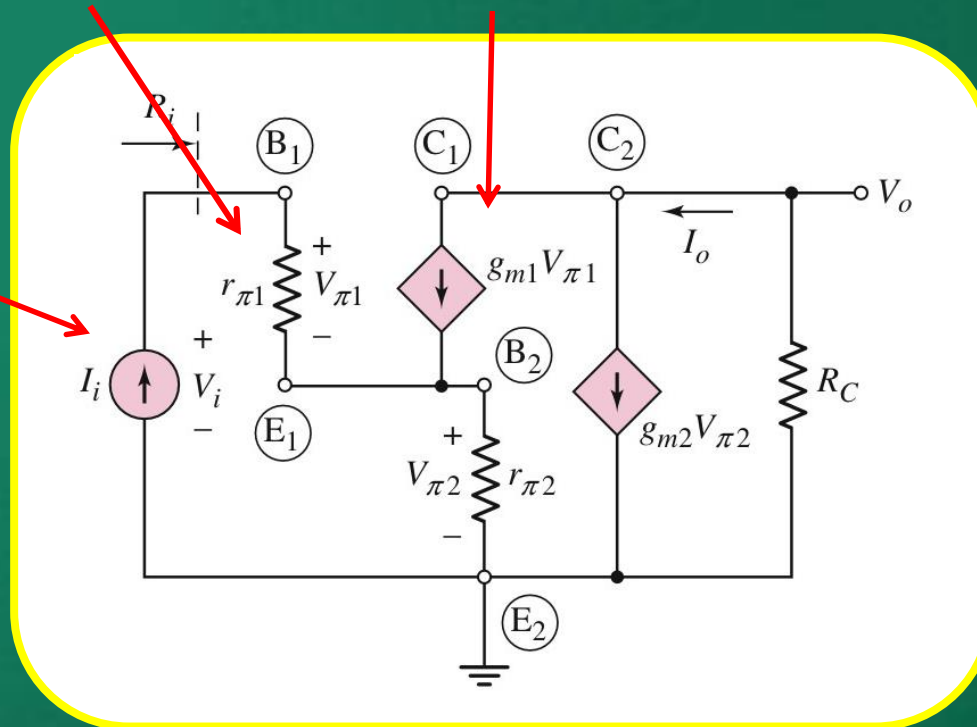Input voltage source is transformed into current source




Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

Input voltage source is transformed into current source

$$V_i = V_{\pi 1} + V_{\pi 2}$$

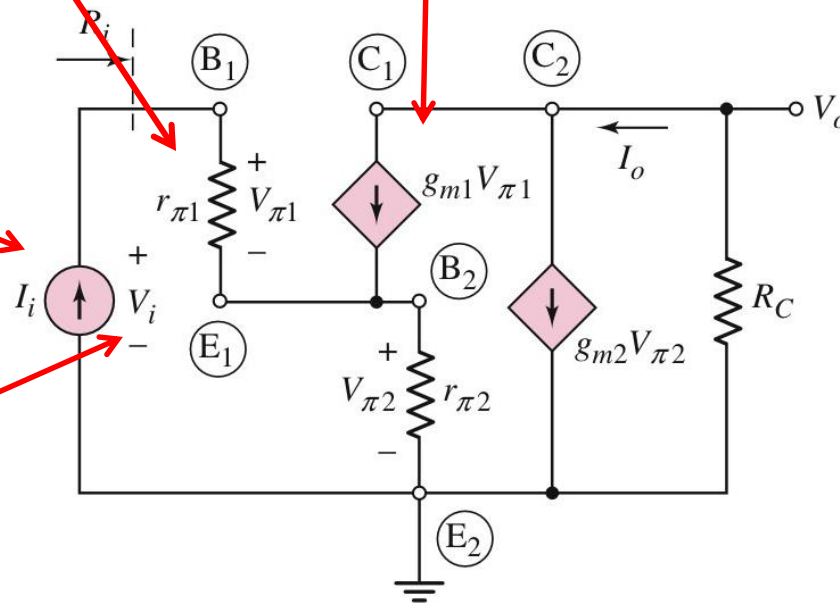


Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

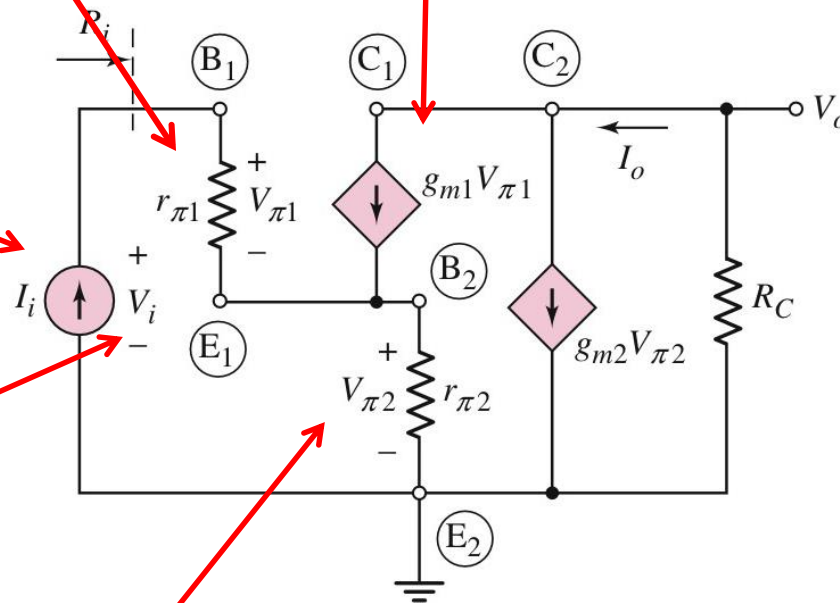Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$


$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

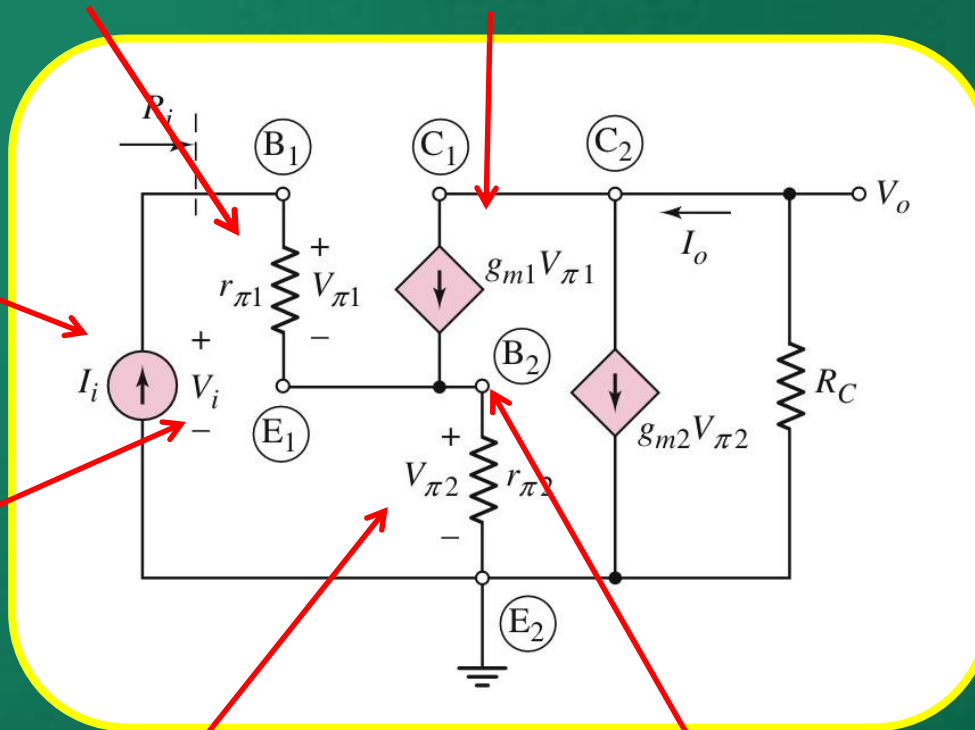Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$


$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

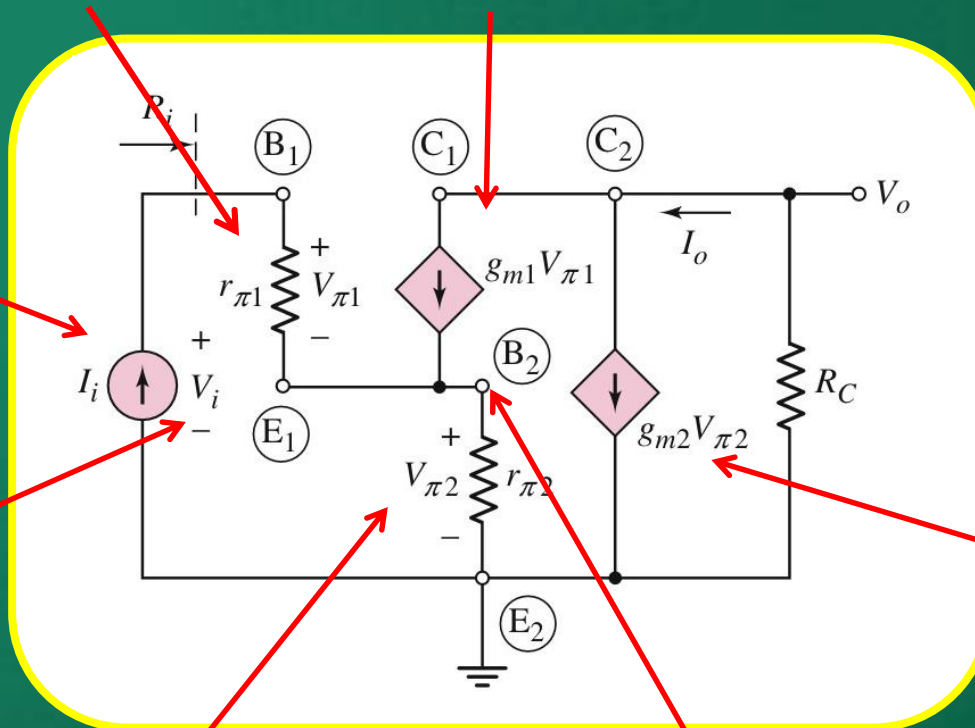Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$\begin{aligned} g_{m2} V_{\pi 2} &= g_{m2} (1 + \beta_1) I_i r_{\pi 2} \\ &= \beta_2 (1 + \beta_1) I_i \end{aligned}$$

$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$


Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$\begin{aligned} I_o &= g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} \\ &= \beta_1 I_i + \beta_2 (1 + \beta_1) I_i \end{aligned}$$

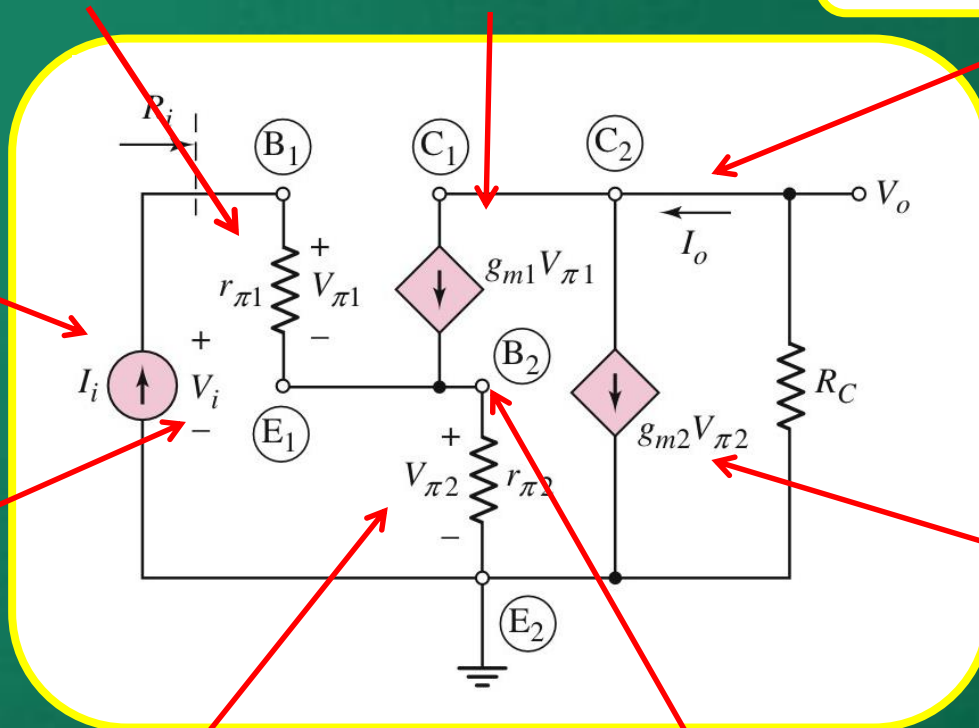Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$\begin{aligned} g_{m2} V_{\pi 2} &= g_{m2} (1 + \beta_1) I_i r_{\pi 2} \\ &= \beta_2 (1 + \beta_1) I_i \end{aligned}$$

$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$g_{m2} V_{\pi 2} = g_{m2} (1 + \beta_1) I_i r_{\pi 2} = \beta_2 (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$g_{m2} V_{\pi 2} = g_{m2} (1 + \beta_1) I_i r_{\pi 2} = \beta_2 (1 + \beta_1) I_i$$

$$I_o = g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} = \beta_1 I_i + \beta_2 (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$g_{m2} V_{\pi 2} = g_{m2} (1 + \beta_1) I_i r_{\pi 2} = \beta_2 (1 + \beta_1) I_i$$

$$I_o = g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} = \beta_1 I_i + \beta_2 (1 + \beta_1) I_i$$

The current gain is

$$A_i = \frac{I_o}{I_i} = \beta_1 + \beta_2 (1 + \beta_1) \cong \beta_1 \beta_2$$

Darlington Connection

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + (1 + \beta_1) I_i r_{\pi 2}$$

Darlington Connection

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + (1 + \beta_1) I_i r_{\pi 2}$$

The input resistance is

$$R_i = \frac{V_i}{I_i} = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

Darlington Connection

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + (1 + \beta_1) I_i r_{\pi 2}$$

The input resistance is

$$R_i = \frac{V_i}{I_i} = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

Approximate expression for the input resistance of the darlington configuration above is

$$R_i \cong 2\beta_1 r_{\pi 2}$$

since

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}}$$

&

$$I_{CQ1} \cong \frac{I_{CQ2}}{\beta_2}$$