

Tutorial Sheet - 4

IEC103

(Q1). Find the output voltage  $V_o$  of the amplifier circuit shown in Fig. Q1. Assume that all op-amps are ideal and none of the op-amps saturate.

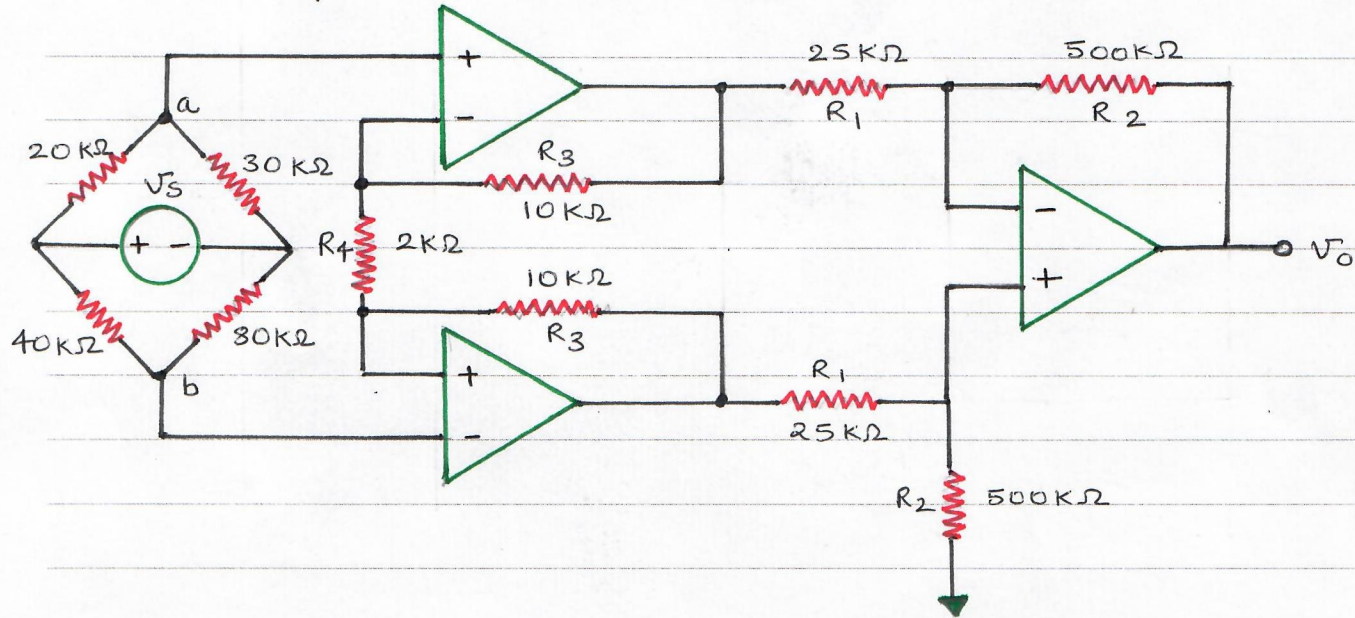


Fig. Q1

(Q2) The opamp circuit shown in Fig. Q2 is designed to amplify a voltage signal and current signal from two transducers. Applying superposition, find the output voltage  $V_o(t)$  in terms of inputs  $V_{IN}(t)$  and  $i_{IN}(t)$ . You may find it convenient to first find the values of intermediate variables  $V_1(t)$  and  $V_2(t)$  shown in the Fig. 2 and then find  $V_o(t)$ . Assume that op amps are ideal.

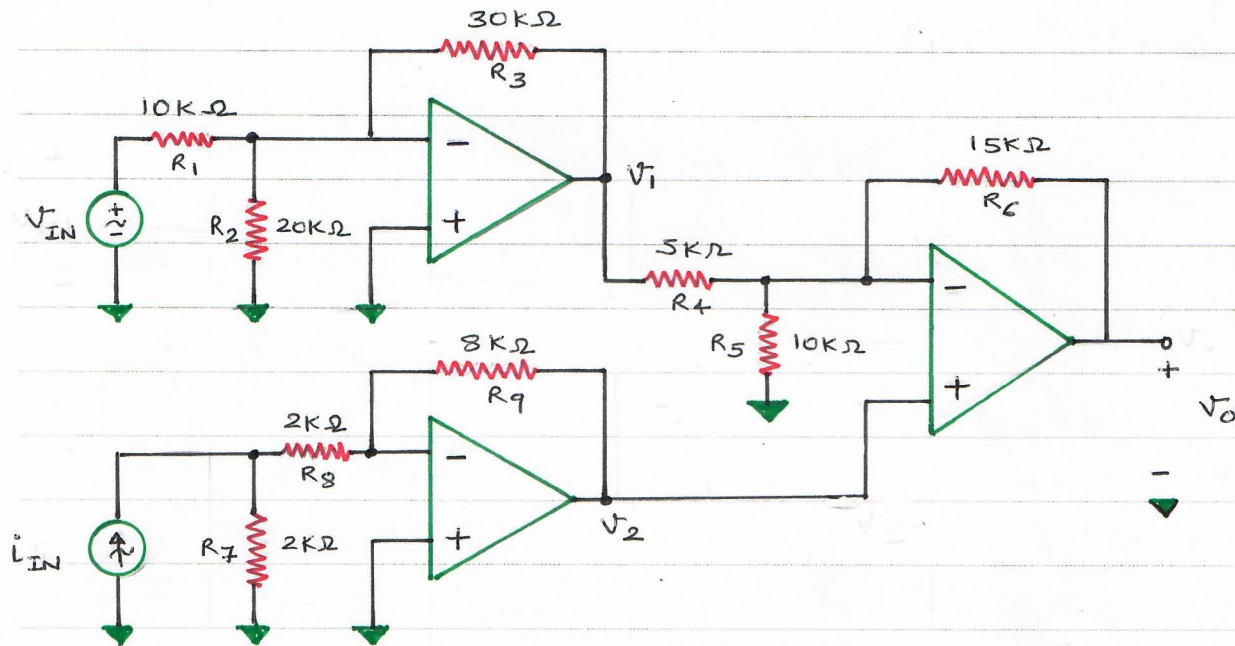


Fig. Q2

Q3. i) What type of feedback is incorporated in Q.3a, Q.3b, Q.3c, and Q.3d.

ii) Assuming ideal op amp, find  $\beta$  and  $A_f$  relevant to each circuit.

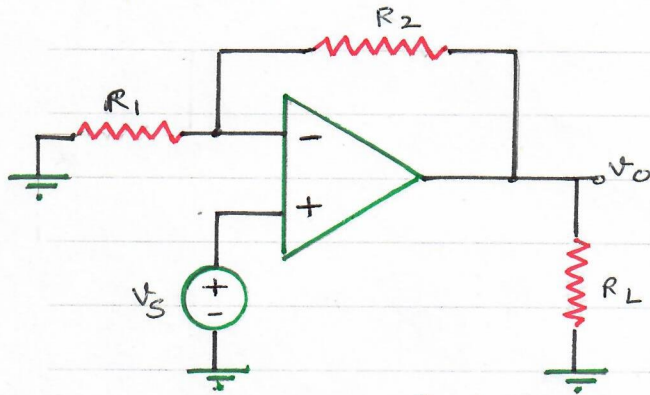


Fig. Q3a

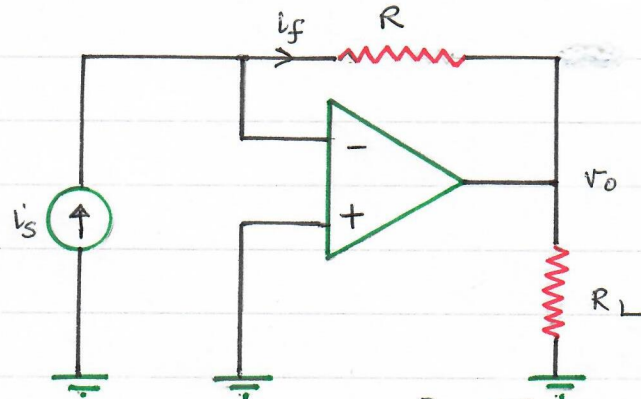


Fig. Q3b

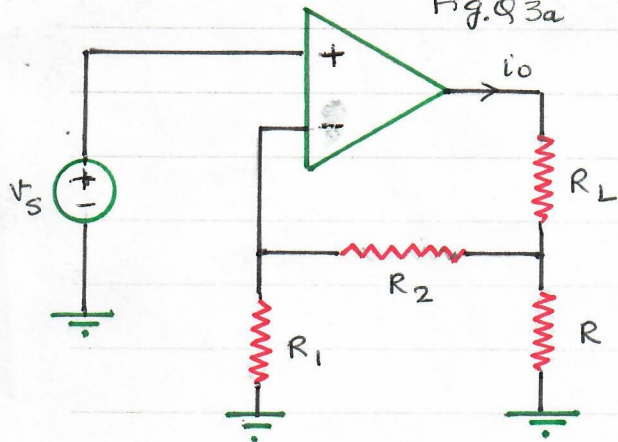


Fig. Q3c

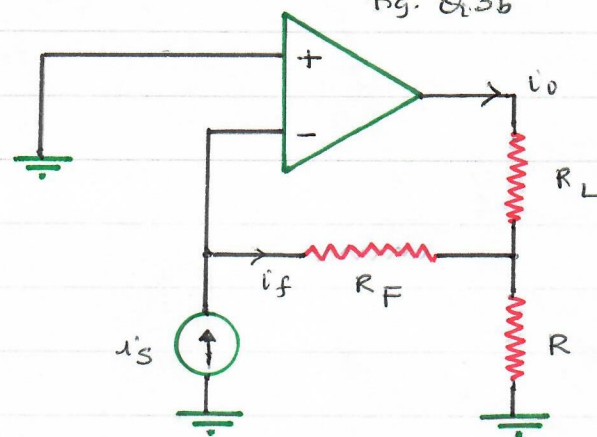


Fig. Q3d

Q4 For the amplifier circuit shown in Fig. Q4, find the expression for  $i_L$  in terms of  $V_S$ , if  $R_2 = R_4$  and  $R_1 = R_3$ . What type of amplifier is it? Assume that the op-amp is ideal and operates in linear region.

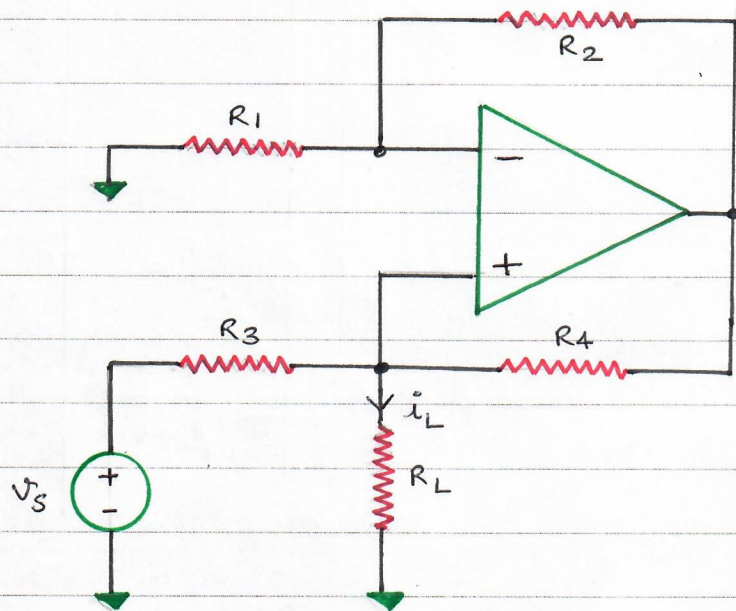


Fig. Q4



Q5 Fig. Q5 shows a feedback transconductance amplifier implemented using an op amp with open-loop gain  $\mu$ , a very large input resistance<sup>( $\infty$ )</sup>, and an output resistance  $r_o$ . The output current  $I_o$  that is delivered to the load resistance  $R_L$  is sensed by the feedback network composed of three resistances  $R_M$ ,  $R_1$ , and  $R_2$ , and a proportional voltage  $V_f$  is fed back to the negative-input terminal of the op amp. Find the expressions for  $A = I_o/V$ ,  $\beta = V_f/I_o$ , and  $A_f = I_o/V_s$ . If the loop gain is large, find the approximate expression for  $A_f$  (closed-loop gain)

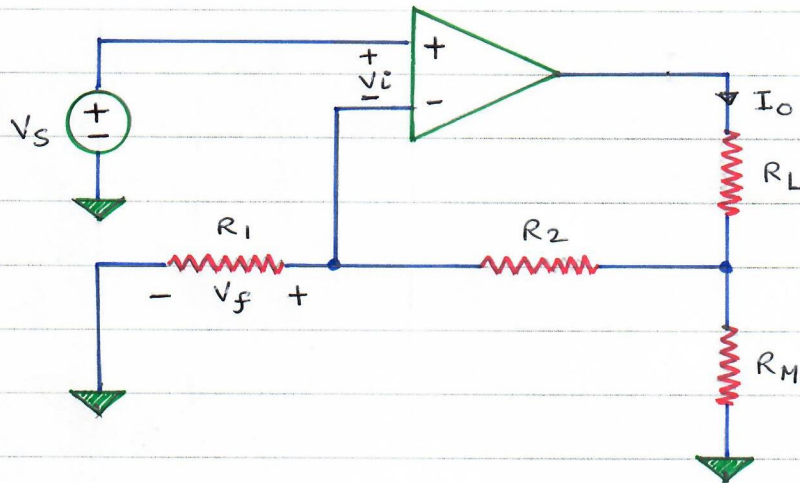


Fig. Q5