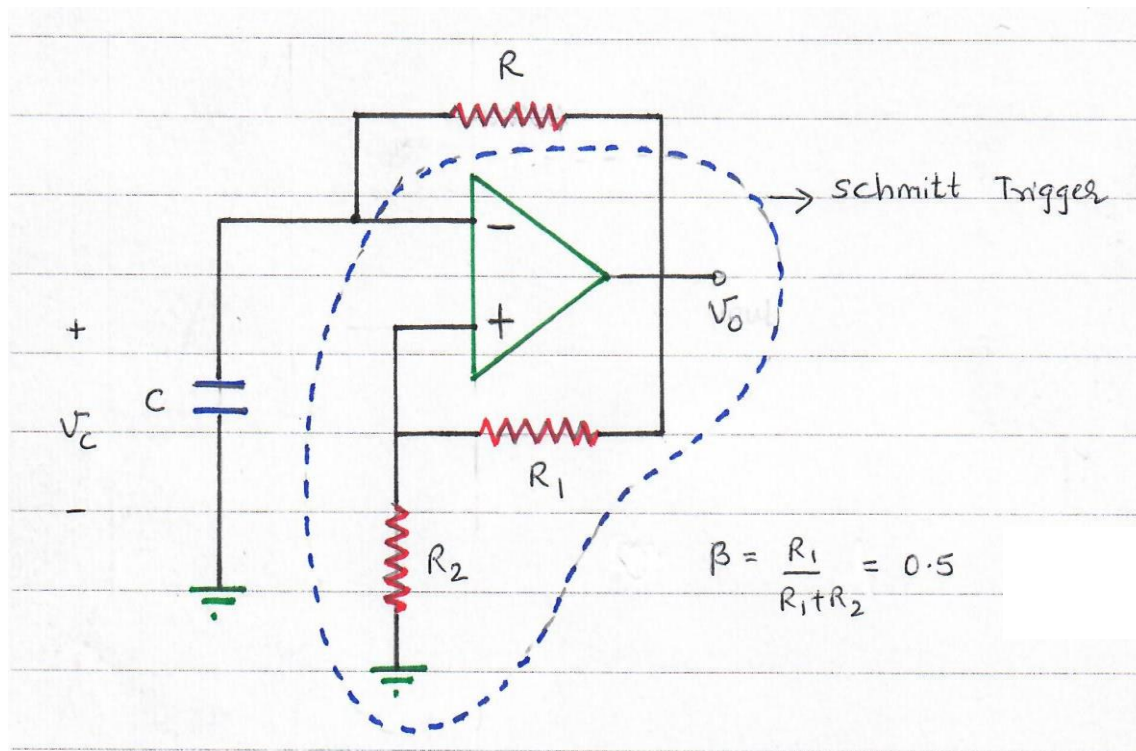


Basic Electronic Circuits (IEC-103)


Lecture-09

Square Wave Generator


Square Wave Generation




Square Wave Generator

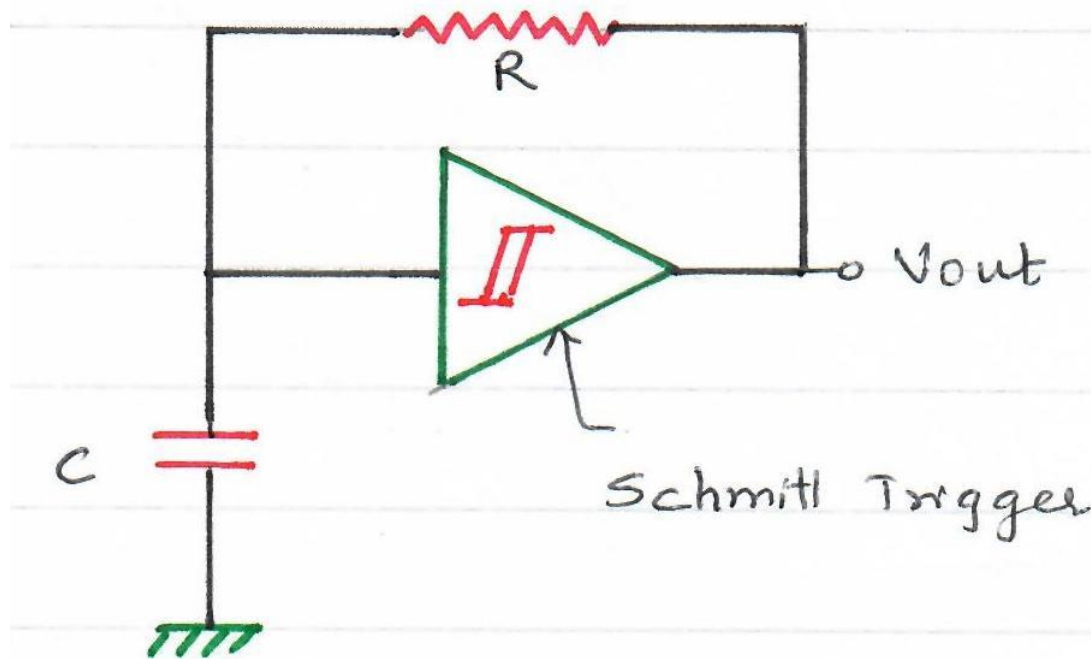


Transfer Characteristics

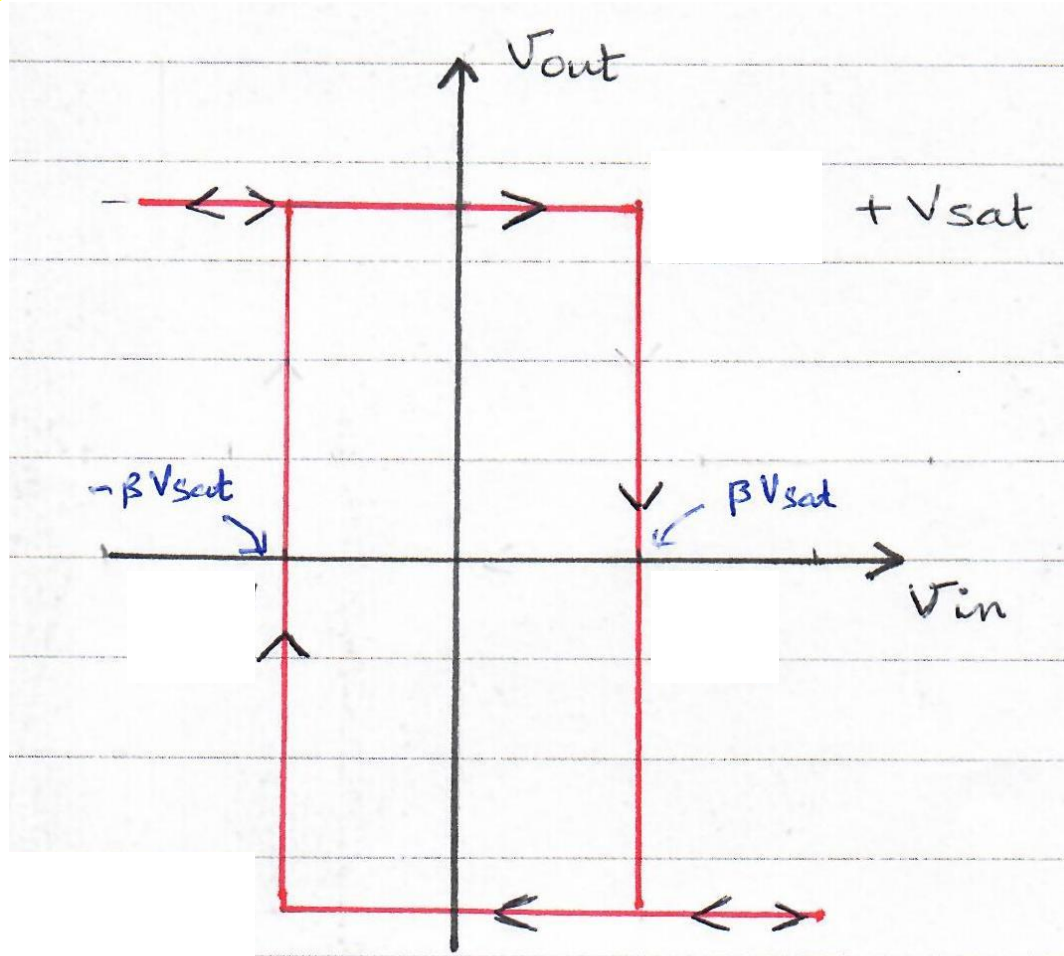

Output and Capacitor Voltage

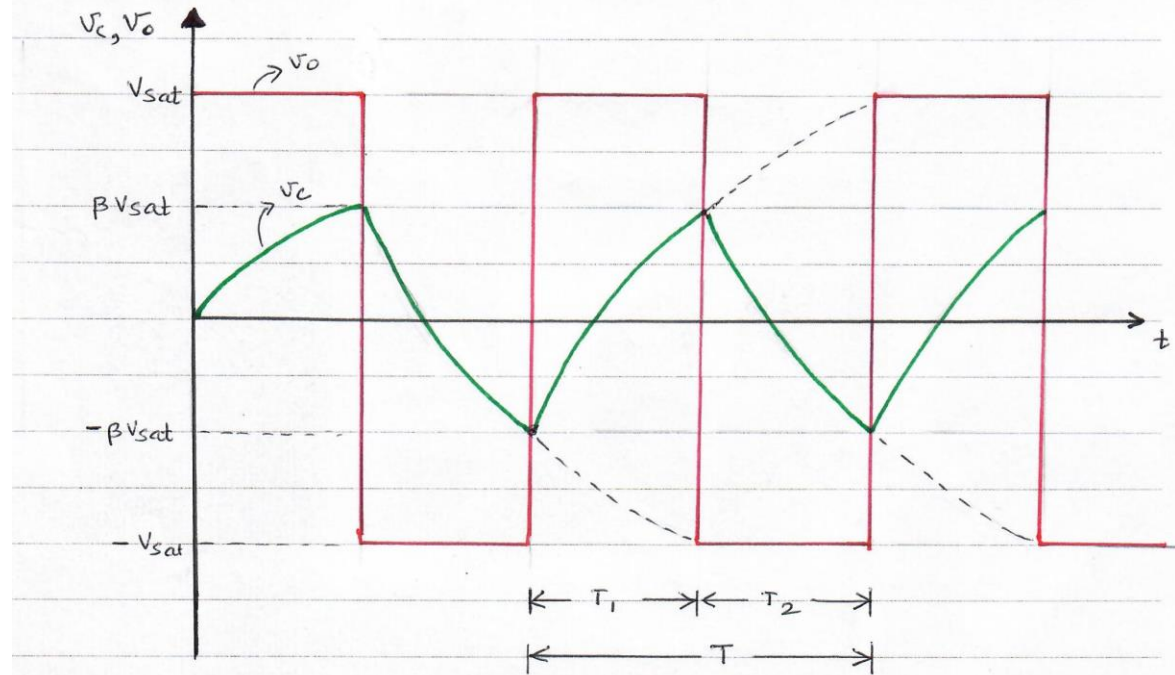


Output and Capacitor Voltage

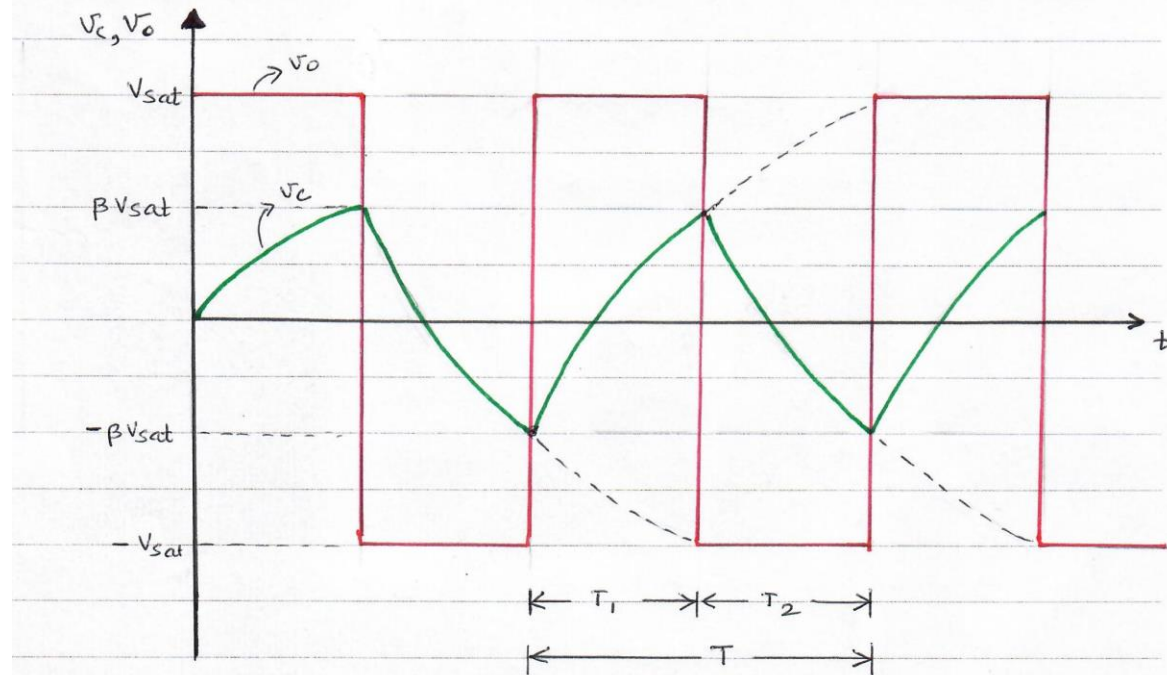

$$\Rightarrow T = 2RC \ln\left(\frac{1+0.5}{1-0.5}\right) = 2RC \ln(3) = 2.197RC$$

Log and Antilog Amplifier

Logarithmic Amplifier

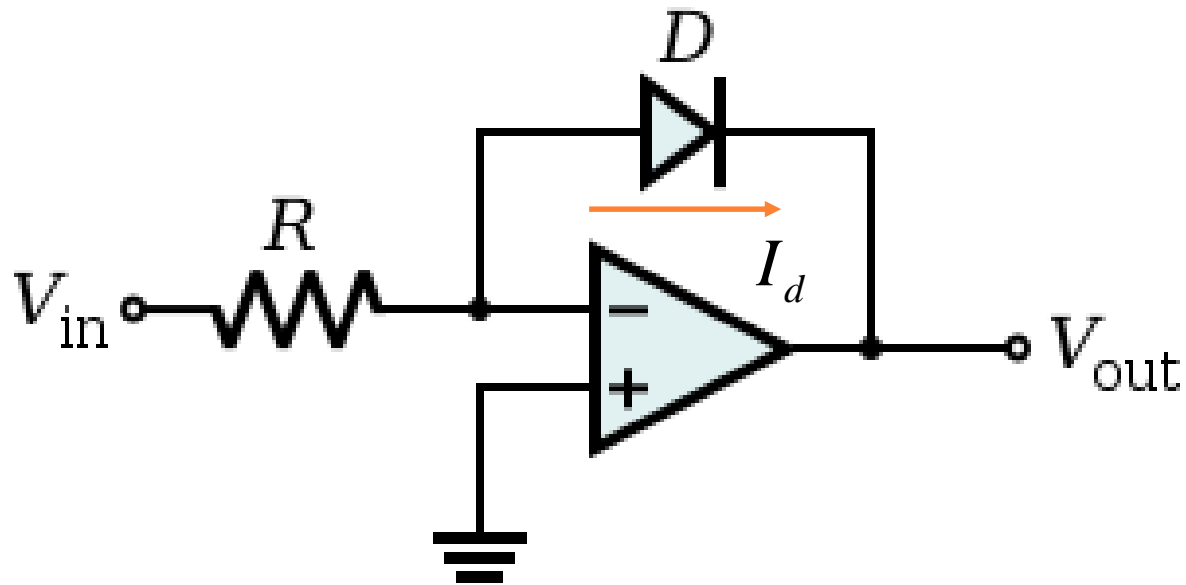

Diode Equation

$$i_D = I_0 \left(e^{\frac{qv_D}{nKT}} - 1 \right)$$

Diode Equation

$$i_D = I_0 \left(e^{\frac{qv_D}{nKT}} - 1 \right)$$

i_D = the net current flowing through the diode;

I_0 = "dark saturation current", the diode leakage current in the absence of light;

v_D = applied voltage across the terminals of the diode;

q = absolute value of electron charge (1.6×10^{-19} C);

k = Boltzmann's constant (1.38×10^{-23} J/K);

T = absolute temperature in Kelvin (K); and

n = empirical constant, 1 for Ge and 2 for Si diode.

Diode Equation

$$i_D = I_0 \left(e^{\frac{qv_D}{nKT}} - 1 \right)$$

i_D = the net current flowing through the diode;

I_0 = "dark saturation current", the diode leakage current in the absence of light;

v_D = applied voltage across the terminals of the diode;

q = absolute value of electron charge (1.6×10^{-19} C);

k = Boltzmann's constant (1.38×10^{-23} J/K);

T = absolute temperature in Kelvin (K); and

n = empirical constant, 1 for Ge and 2 for Si diode.

At 300 K, $kT/q = 26$ mV, the thermal voltage.

Diode Equation

$$i_D = I_0 \left(e^{\left(\frac{v_D}{0.026} \right)} - 1 \right)$$

where v_D is the voltage applied across diode in volts.

If diode is forward biased

$$i_D \cong I_0 e^{\left(\frac{v_D}{0.026} \right)}$$

Analysis

Applying KCL at inverting input

Analysis

Applying KCL at inverting input

$$\frac{0 - V_{\text{in}}}{R} + I_d = 0 \Rightarrow I_d = \frac{V_{\text{in}}}{R}$$

Analysis

Applying KCL at inverting input

$$\frac{0 - V_{\text{in}}}{R} + I_d = 0 \Rightarrow I_d = \frac{V_{\text{in}}}{R}$$

But

$$I_d = I_0 (e^{(v_d / v_T)} - 1)$$

Analysis

Applying KCL at inverting input

$$\frac{0 - V_{\text{in}}}{R} + I_d = 0 \Rightarrow I_d = \frac{V_{\text{in}}}{R}$$

But

$$I_d = I_0 (e^{(v_d / v_T)} - 1)$$

When diode is forward biased

$$I_d \cong I_0 (e^{(v_d / v_T)})$$

Analysis

Analysis

Here $V_d = -V_{out}$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

$$e^{(-V_{out} / V_T)} = \frac{V_{in}}{I_0 R}$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out} / V_T)}$$

$$I_0 e^{(-V_{out} / V_T)} = \frac{V_{in}}{R}$$

$$e^{(-V_{out} / V_T)} = \frac{V_{in}}{I_0 R}$$

$$V_{out} = -V_T \ln\left(\frac{V_{in}}{I_0 R}\right) = k_1 \ln\left(\frac{V_{in}}{k_2}\right)$$

Analysis

Here $V_d = -V_{out}$

$$\therefore I_d = I_0 e^{(-V_{out}/V_T)}$$

$$I_0 e^{(-V_{out}/V_T)} = \frac{V_{in}}{R}$$


$$e^{(-V_{out}/V_T)} = \frac{V_{in}}{I_0 R}$$

$$V_{out} = -V_T \ln\left(\frac{V_{in}}{I_0 R}\right) = k_1 \ln\left(\frac{V_{in}}{k_2}\right)$$

where

$$k_1 = -V_T \text{ and } k_2 = I_0 R$$

Antilog Amplifier

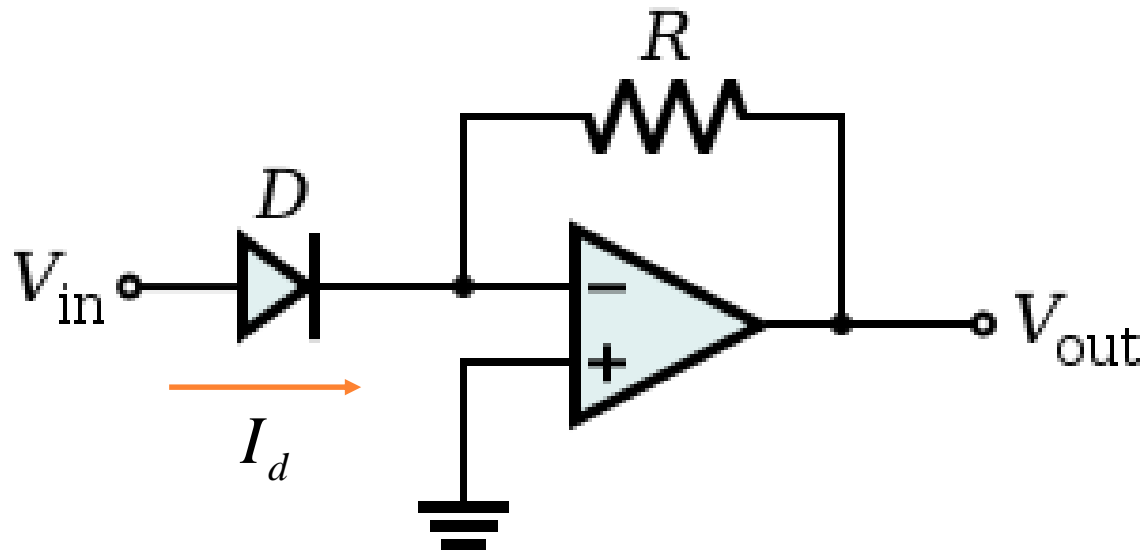

Analysis

$$I_d = -\frac{V_{\text{out}}}{R} \Rightarrow V_{\text{out}} = -RI_d$$

Analysis

$$I_d = -\frac{V_{\text{out}}}{R} \Rightarrow V_{\text{out}} = -RI_d$$

and

$$I_d \cong I_0 e^{(v_{\text{in}} / v_T)}$$

Analysis

$$I_d = -\frac{V_{\text{out}}}{R} \Rightarrow V_{\text{out}} = -RI_d$$

and

$$I_d \cong I_0 e^{(v_{\text{in}} / v_T)}$$

$$V_{\text{out}} = -RI_0 e^{(v_{\text{in}} / v_T)} = k_3 e^{v_{\text{in}}}$$

Analysis

$$I_d = -\frac{V_{\text{out}}}{R} \Rightarrow V_{\text{out}} = -RI_d$$

and

$$I_d \cong I_0 e^{(v_{\text{in}} / v_T)}$$


$$V_{\text{out}} = -RI_0 e^{(v_{\text{in}} / v_T)} = k_3 e^{v_{\text{in}}}$$

This amplifier is called exponential amplifier.


Other Nonlinear Amplifiers

Build a multiplying and squaring amplifier using op-amp.


Analog Multiplier

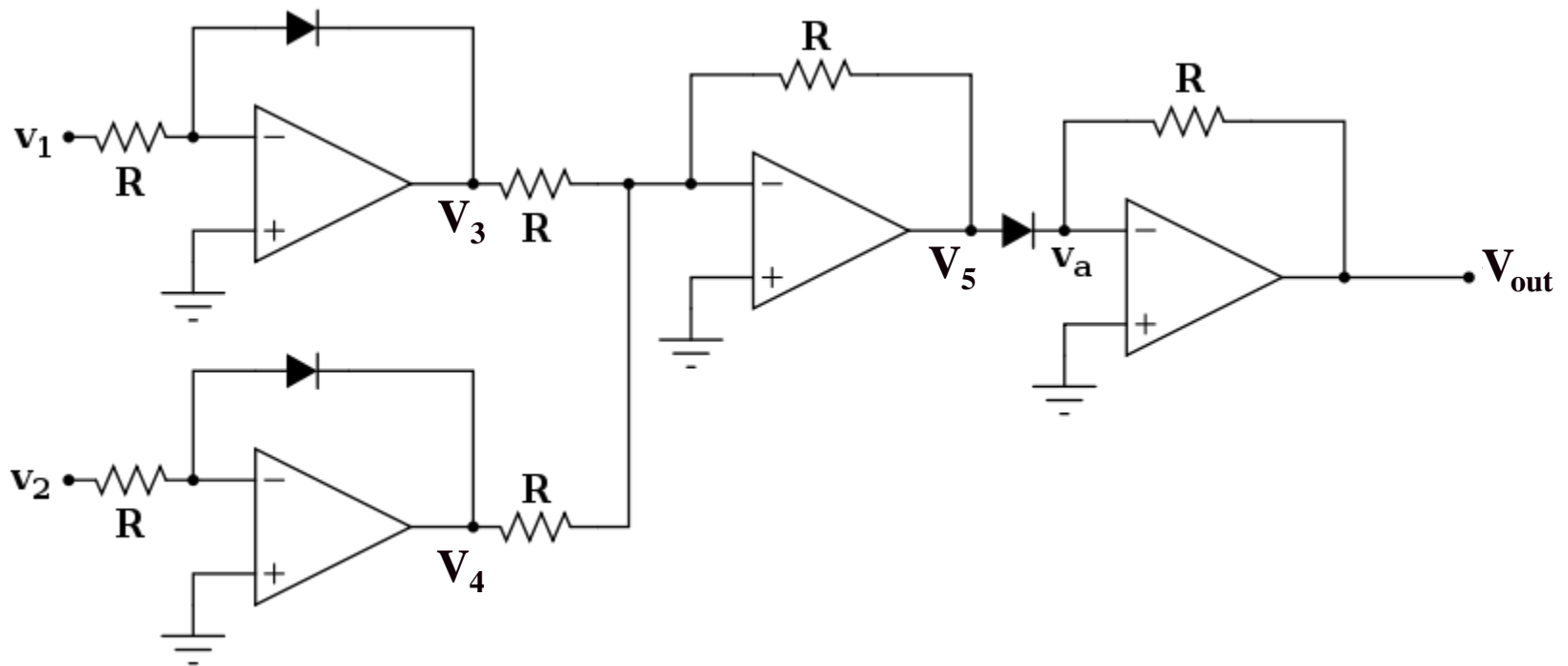


Analog Multiplier

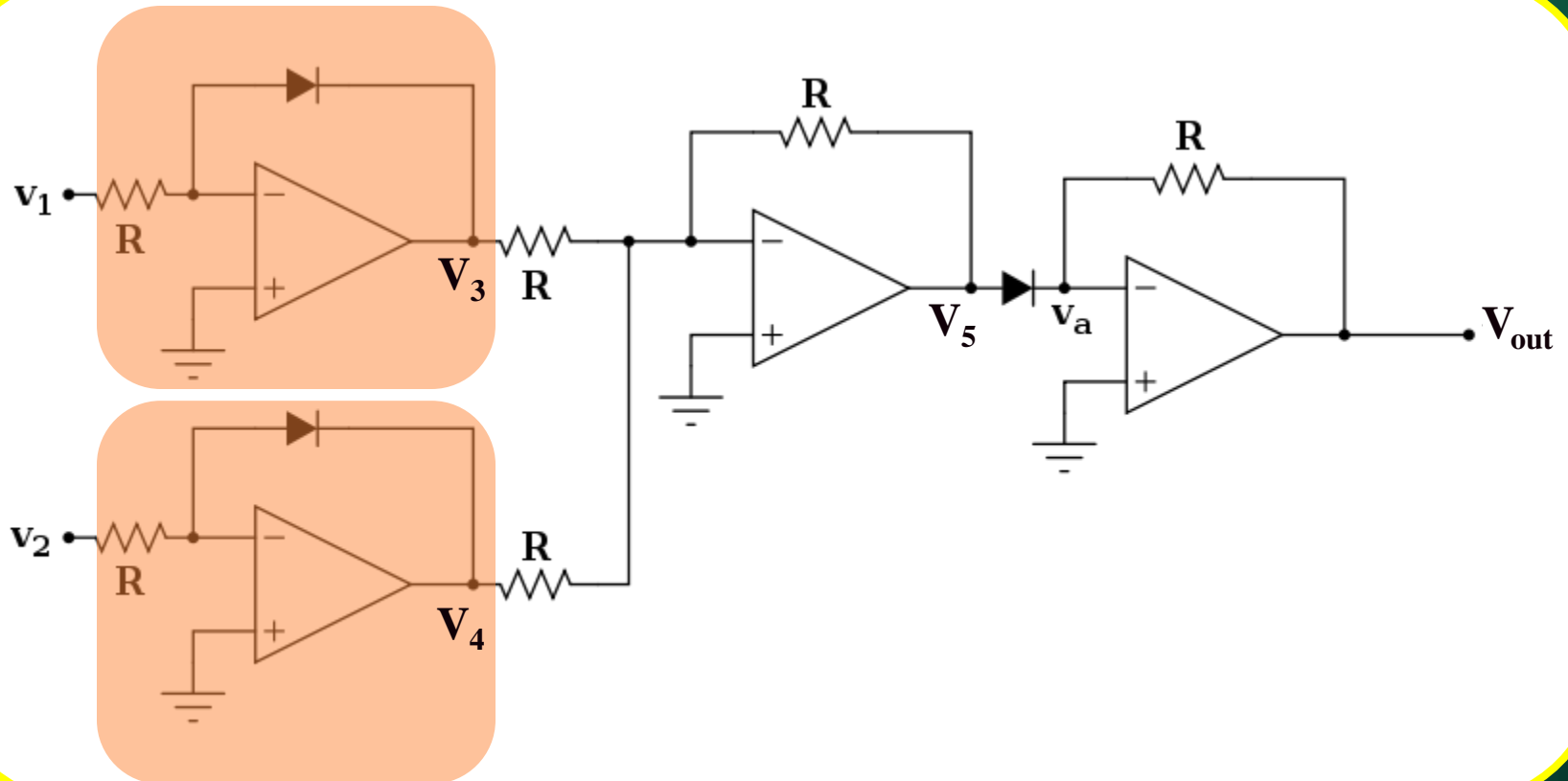

Analog Multiplier

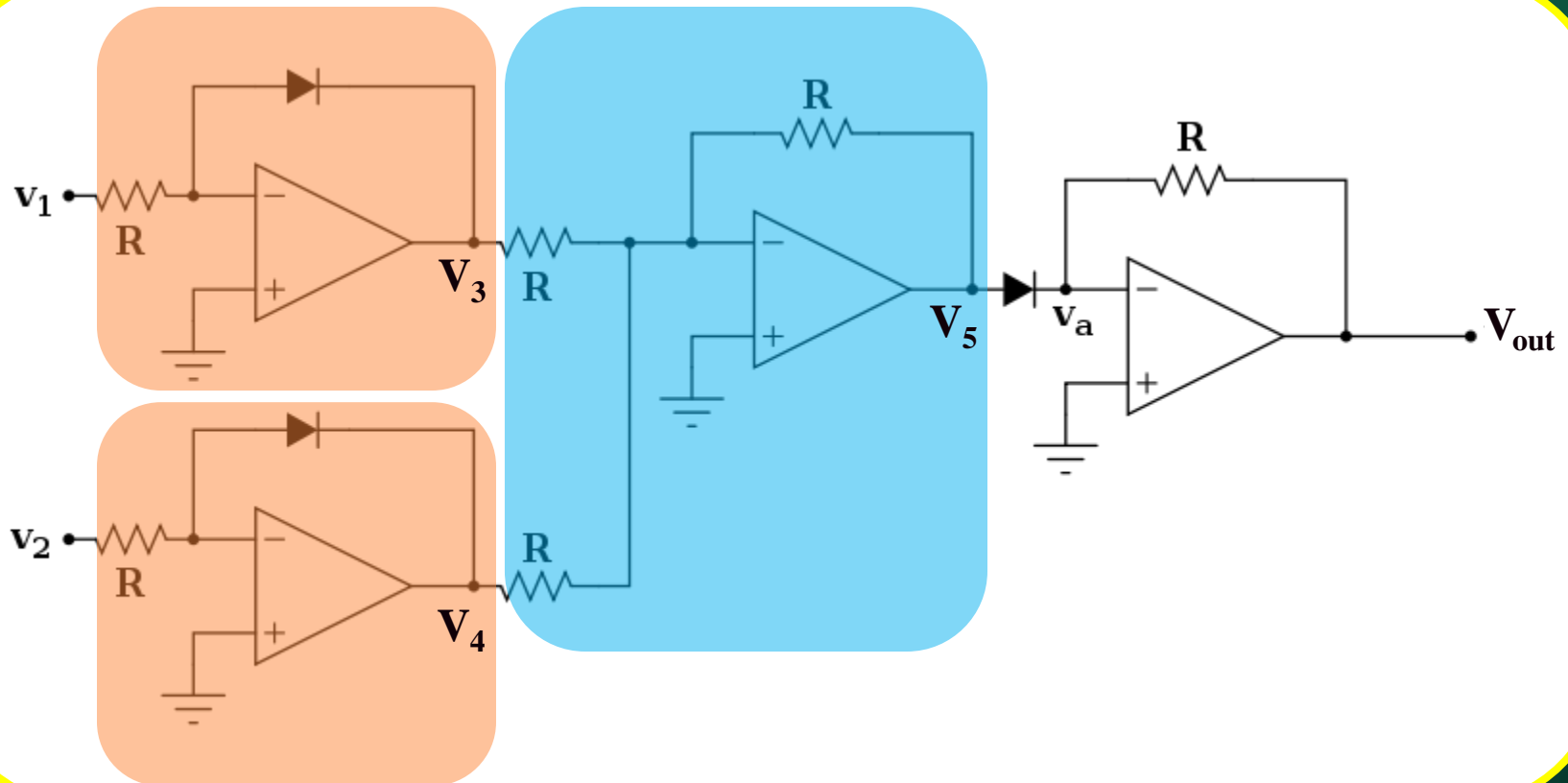

Analog Multiplier

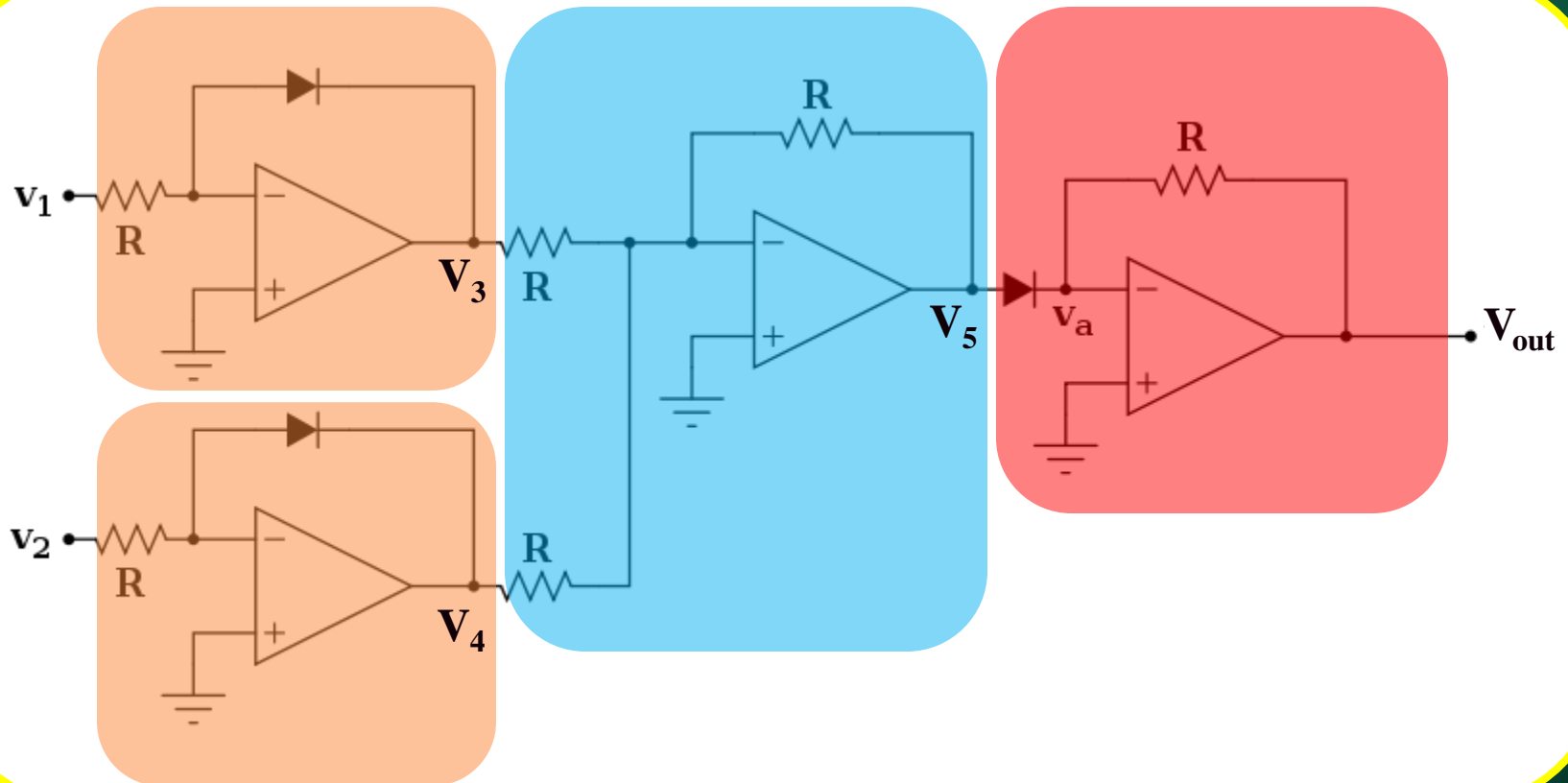


Analog Multiplier

$$V_{\text{out}} \propto V_1 V_2$$

Sinusoidal Oscillators

LC Tank Circuit


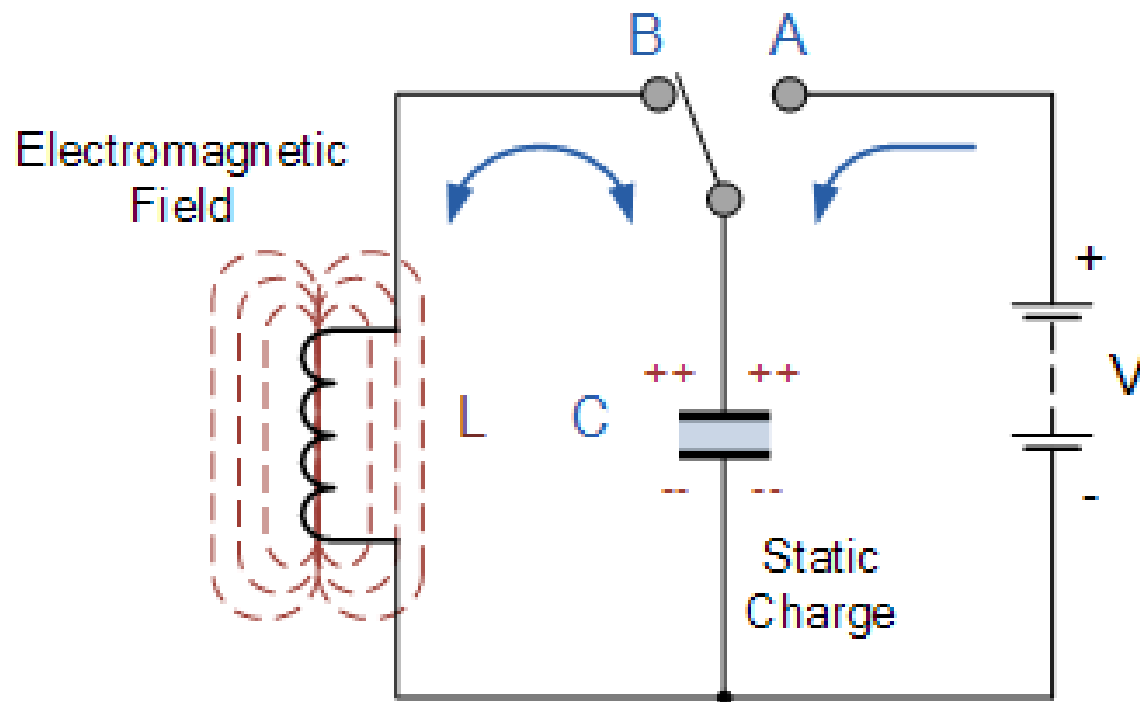


LC Tank Circuit

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

LC Tank Circuit

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

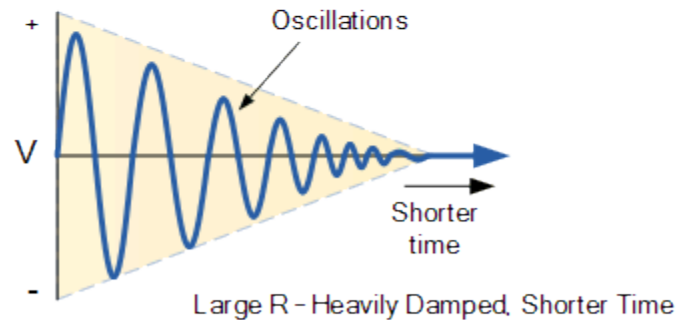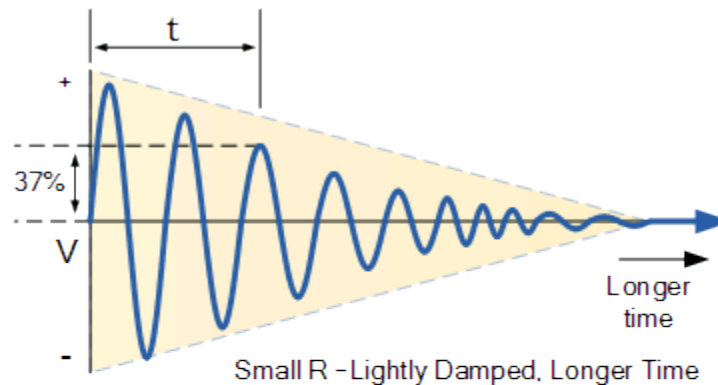

Oscillators

- ❑ **Oscillators are electronic circuits that generate an output signal without the necessity of an input signal.**

Oscillators

- ❑ **Oscillators are electronic circuits that generate an output signal without the necessity of an input signal.**
- ❑ **It produces a periodic waveform on its output with only the DC supply voltage as an input.**

Oscillators

- ☐ **Oscillators are electronic circuits that generate an output signal without the necessity of an input signal.**
- ☐ **It produces a periodic waveform on its output with only the DC supply voltage as an input.**
- ☐ **The output voltage can be either sinusoidal or non-sinusoidal, depending on the type of oscillator.**

Oscillators

- Different types of oscillators can produce various types of outputs including sine, square, saw tooth, and triangular waveforms.

Oscillators

For a circuit to operate as an oscillator following three basic factors must be provided in the circuit

Oscillators

For a circuit to operate as an oscillator following three basic factors must be provided in the circuit

- **Amplification**

Oscillators

For a circuit to operate as an oscillator following three basic factors must be provided in the circuit

- **Amplification**
- **Positive feedback**


Oscillators

For a circuit to operate as an oscillator following three basic factors must be provided in the circuit

- **Amplification**
- **Positive feedback**
- **Frequency determining network**

Oscillators

Oscillators

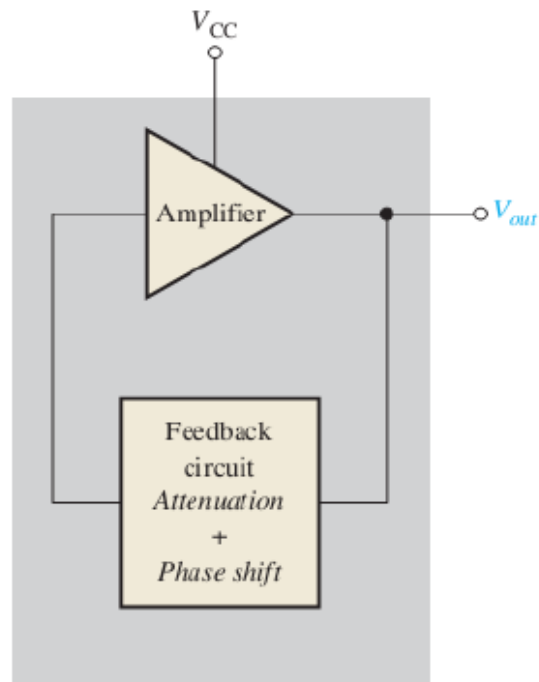

Oscillator

Types of Oscillators

- 1. Feedback Oscillator**
- 2. Relaxation Oscillators**

Types of Oscillators

1. **Feedback Oscillator**
2. **Relaxation Oscillators**

☐ **Feedback Oscillators**

Types of Oscillators

1. **Feedback Oscillator**
2. **Relaxation Oscillators**

☐ **Feedback Oscillators**

- **A fraction of output is feedback to the input with no net phase shift.**

Types of Oscillators

1. **Feedback Oscillator**
2. **Relaxation Oscillators**

☐ **Feedback Oscillators**

- **A fraction of output is feedback to the input with no net phase shift.**
- **The loop gain must be maintained at 1 to maintain oscillations**

Types of Oscillators

1. **Feedback Oscillator**
2. **Relaxation Oscillators**

☐ **Feedback Oscillators**

- **A fraction of output is feedback to the input with no net phase shift.**
- **The loop gain must be maintained at 1 to maintain oscillations**
- **Amplifier can be made of either discrete transistor or an op-amp.**

Types of Oscillators

☐ Relaxation Oscillators

Types of Oscillators

□ Relaxation Oscillators

- An RC timing circuit is used to generate oscillations.

Types of Oscillators

□ Relaxation Oscillators

- An RC timing circuit is used to generate oscillations.
- The circuit operates in nonlinear region.

Types of Oscillators


□ Relaxation Oscillators

- **An RC timing circuit is used to generate oscillations.**
- **The circuit operates in nonlinear region.**
- **Example: Schmitt trigger based square wave oscillator.**


Positive Feedback

A portion of the output is fed back to the input with no net phase shift, resulting in strengthening of the output signal.

Positive Feedback

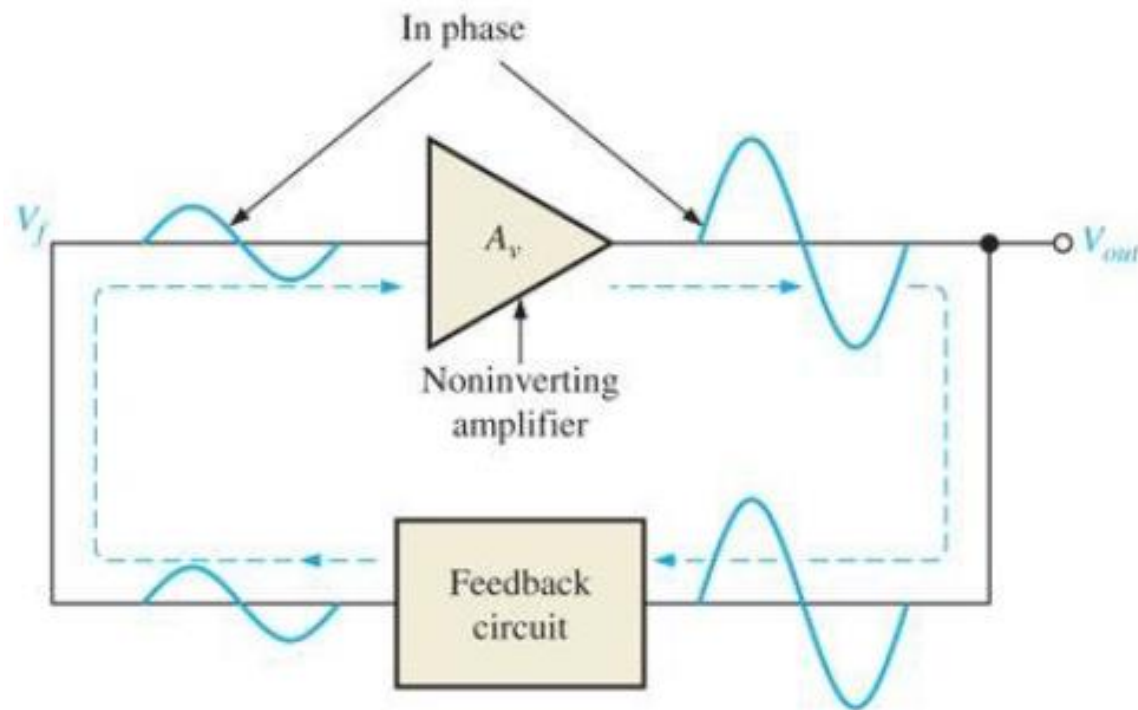

Positive Feedback

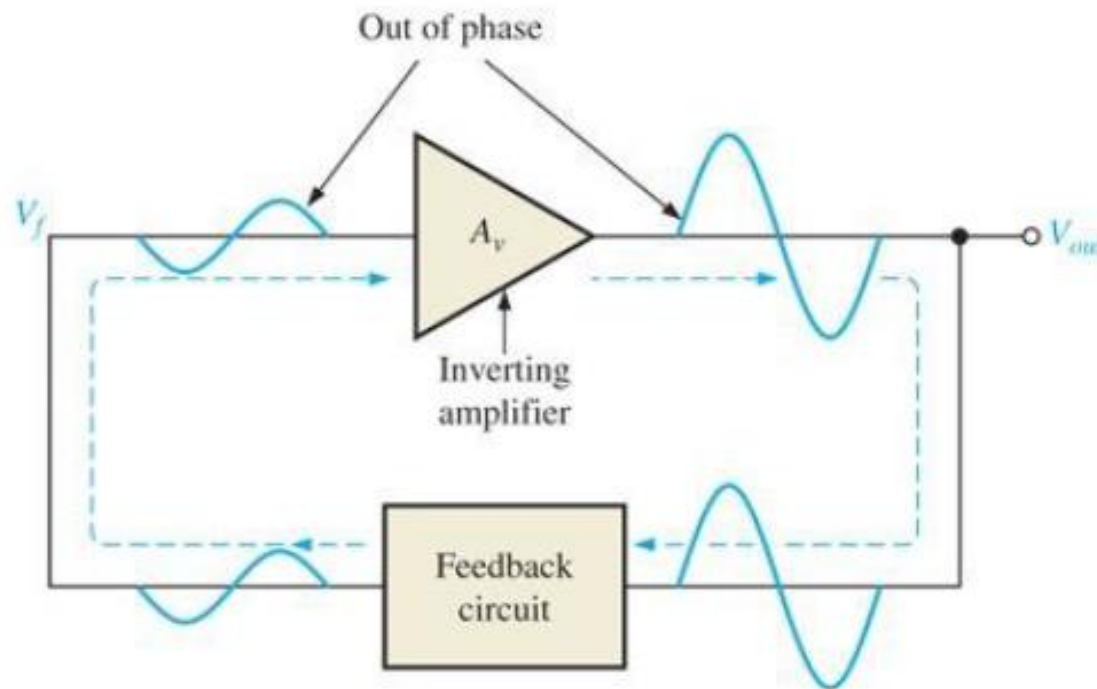

Conditions for Oscillations

Two conditions must be satisfied for sustained oscillations

Conditions for Oscillations

Two conditions must be satisfied for sustained oscillations


- 1. The phase shift around the feedback loop must be effectively 0° .**

Conditions for Oscillations


Two conditions must be satisfied for sustained oscillations

- 1. The phase shift around the feedback loop must be effectively 0° .**
- 2. The voltage gain $A\beta$ around the closed feedback loop (loop gain) must be equal to 1.**

Conditions for Oscillations

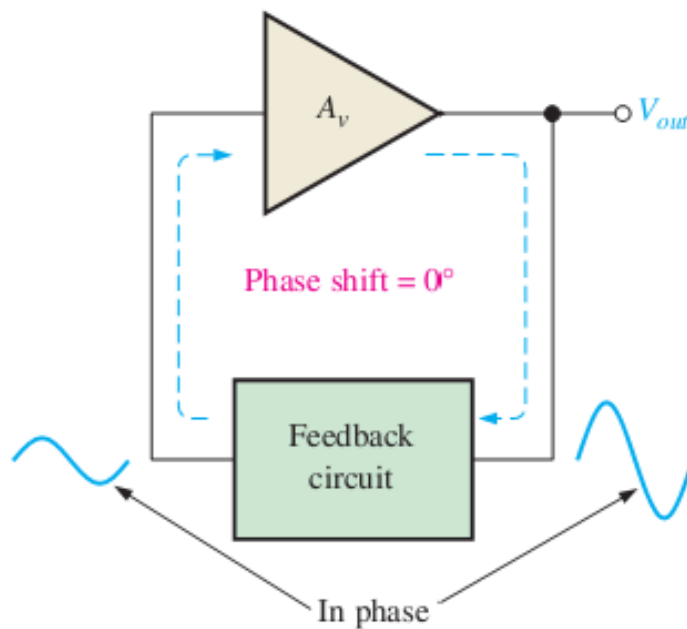

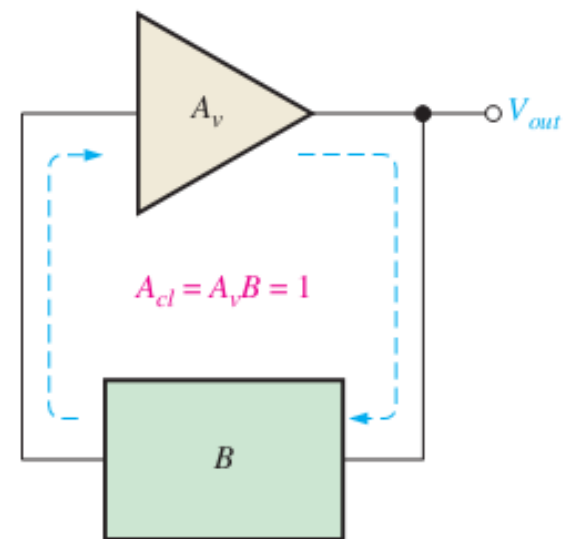(a) The phase shift around the loop is 0° .



(b) The closed loop gain is 1.

RC and LC Oscillators

RC Oscillators: The frequency determining network contains only resistive and capacitive elements.

- Wein bridge oscillator
- Phase-shift oscillator
- Twin-T oscillator


RC and LC Oscillators

LC Oscillators: The frequency determining network contains inductive and capacitive elements.


- **Hartly**
- **Colpitts**
- **Capp**
- **Pierce**

RC Oscillators


Wein Bridge Oscillator

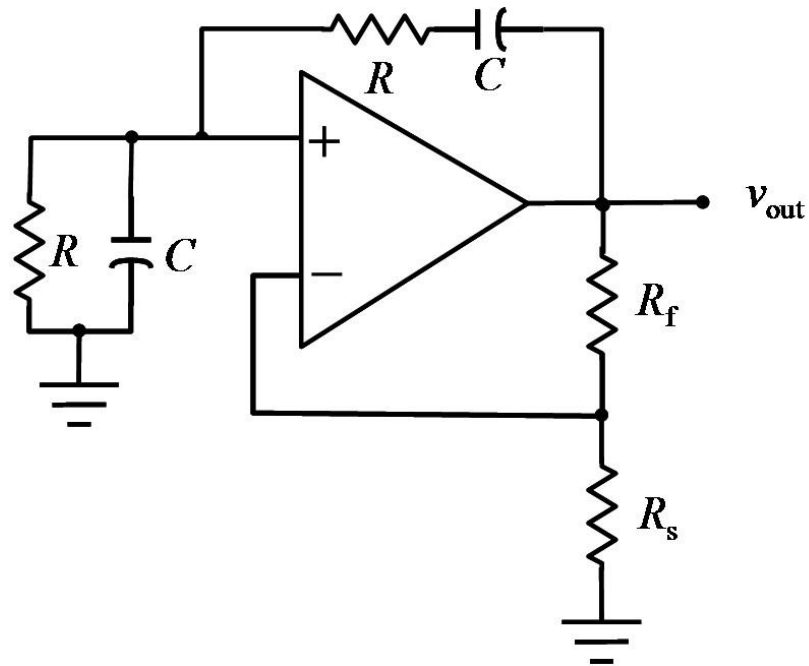

Wein Bridge Oscillator

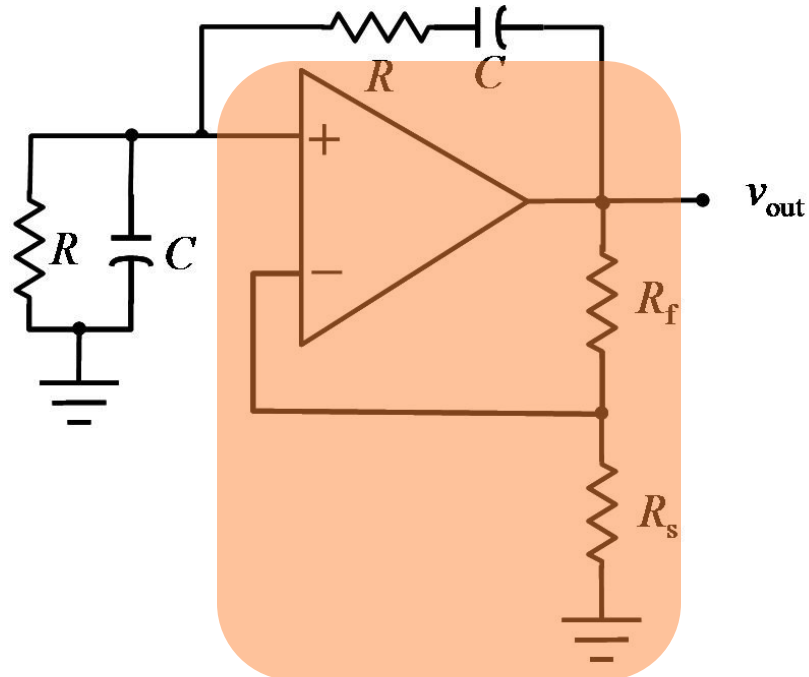


Wein Bridge Oscillator

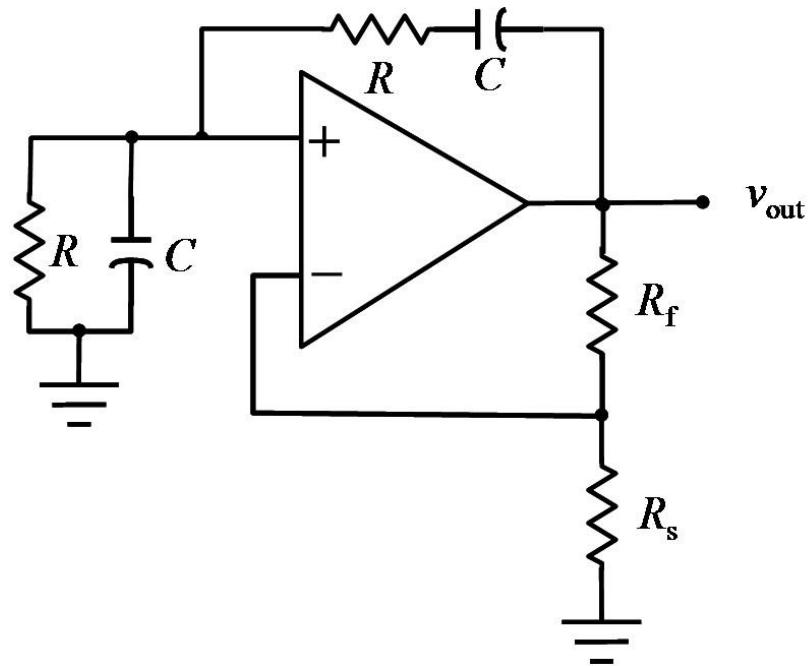

$$R_F = 2R_s$$

Wein Bridge Oscillator

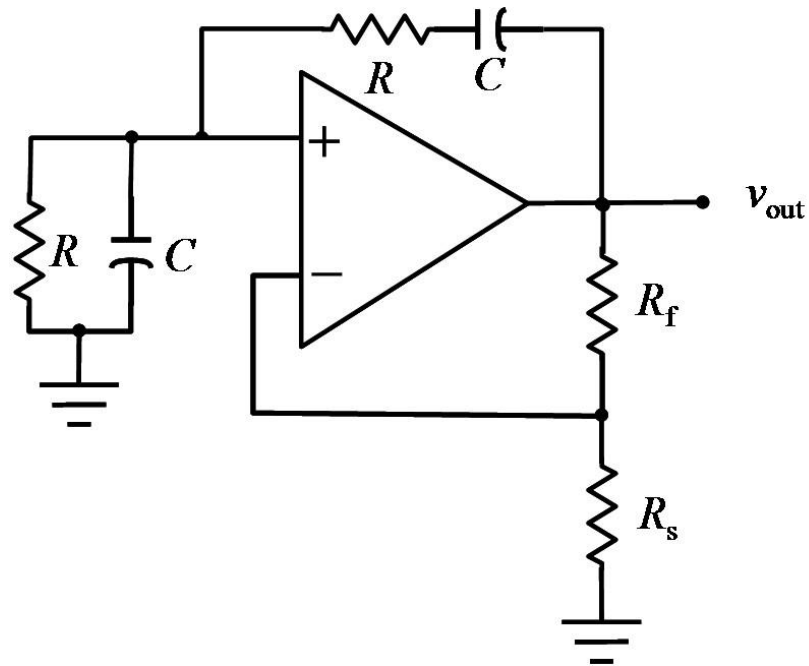

$$R_F = 2R_s$$

$$\omega = \frac{1}{RC}$$

RC Phase Shift Oscillator

