


# **Basic Electronic Circuits**

## **(IEC-103)**


### **Lecture-15**

# **Bipolar Junction Transistors**


# Transistor DC Model

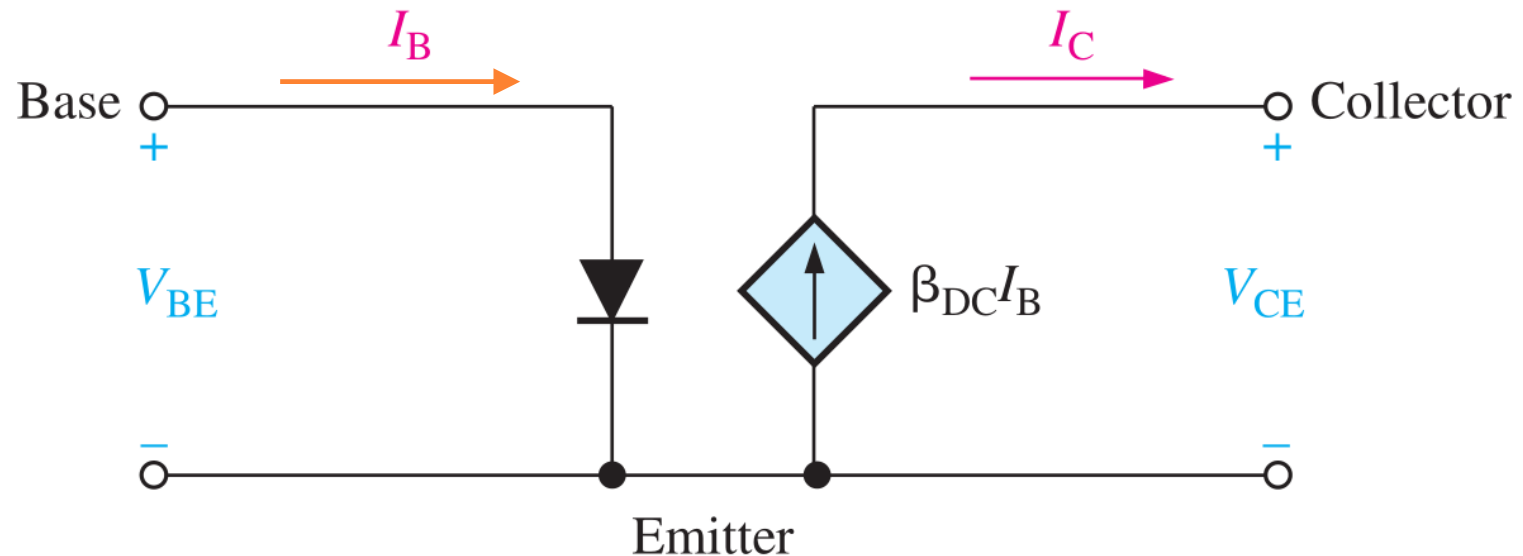

# Transistor Circuit

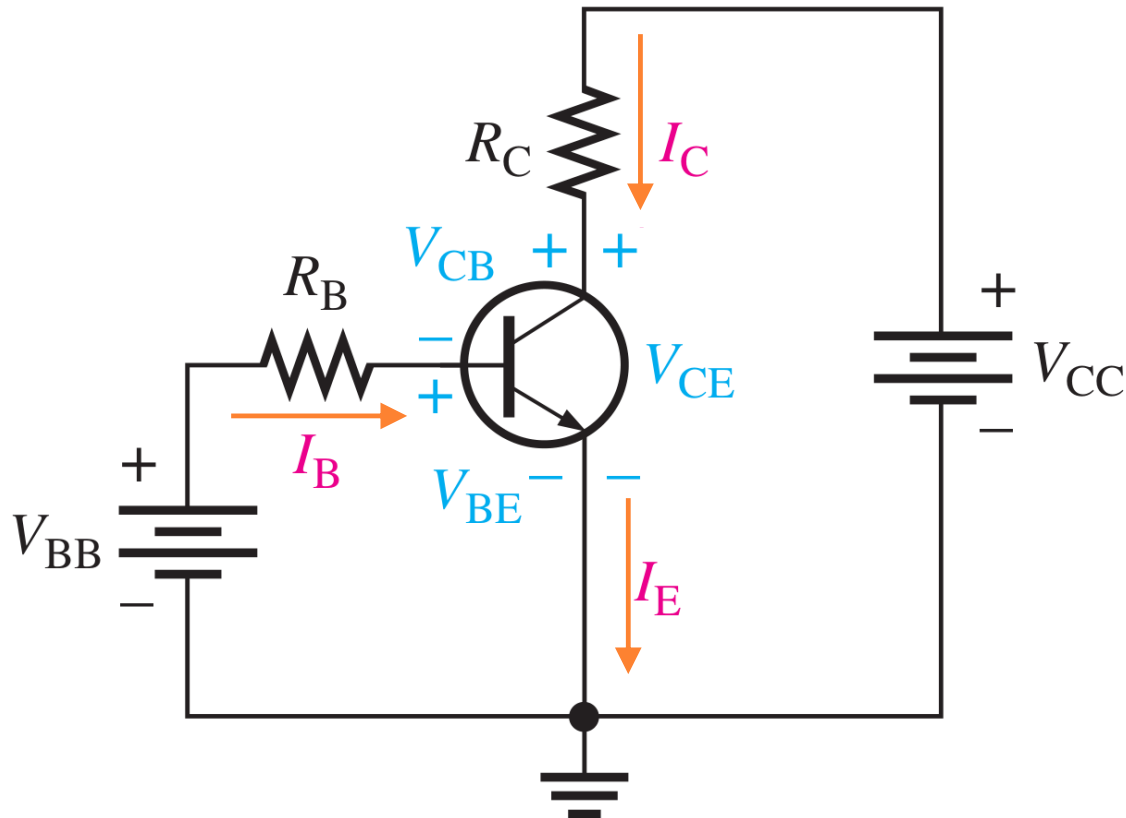

# Transistor Circuit as an Amplifier

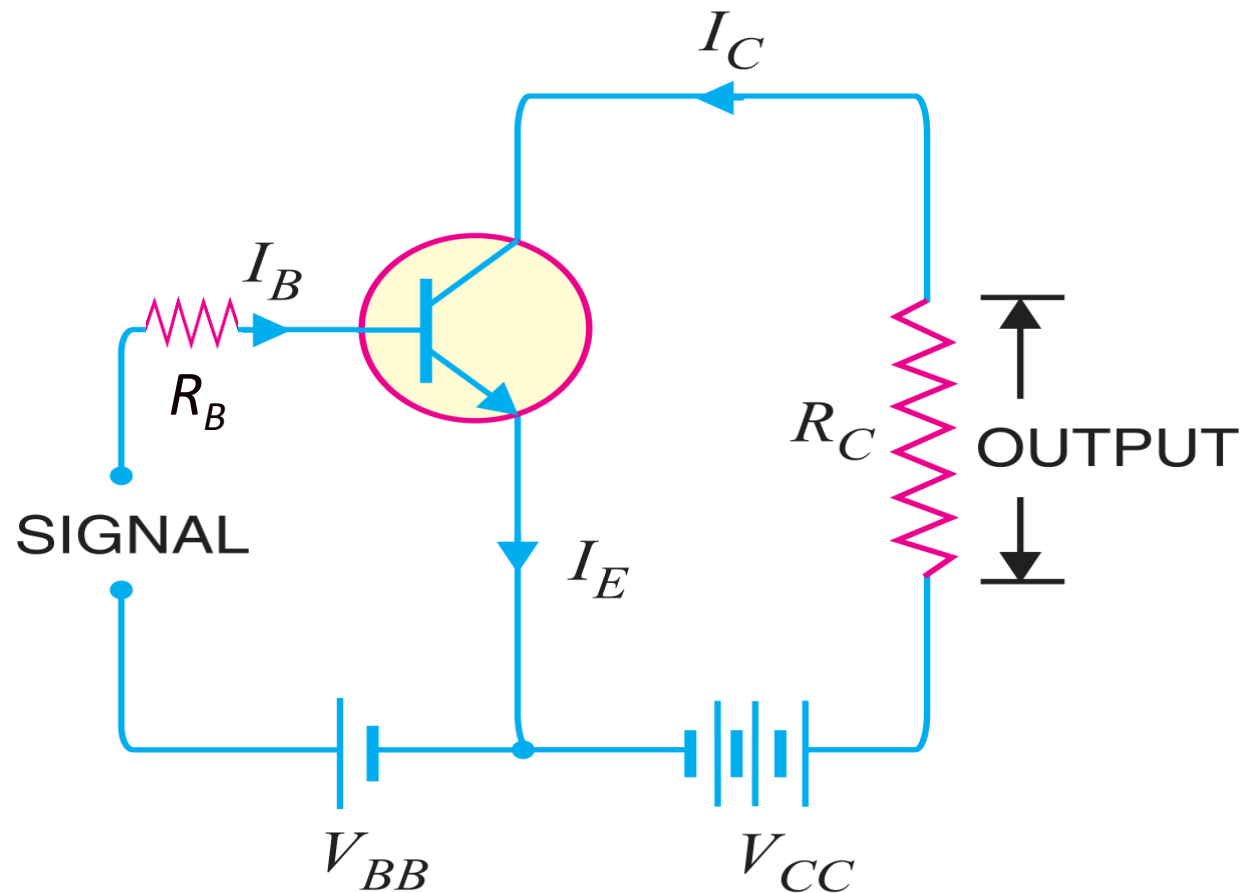

# **Transistor Connections**



# Transistor Connections

- ❑ Transistor can be connected in a circuit in 3 ways
  - Common base connection
  - Common emitter connection
  - Common collector connection

# Transistor Connections



- ❑ Transistor can be connected in a circuit in 3 ways
  - Common base connection
  - Common emitter connection
  - Common collector connection
- ❑ Each connection has their own advantages and disadvantages.





# Transistor Connections

- ❑ Transistor can be connected in a circuit in 3 ways
  - Common base connection
  - Common emitter connection
  - Common collector connection
- ❑ Each connection has their own advantages and disadvantages.
- ❑ In all cases, the emitter-base junction is forward biased and collector-base junction is reverse biased (amplifier application).

# Common Base Connection

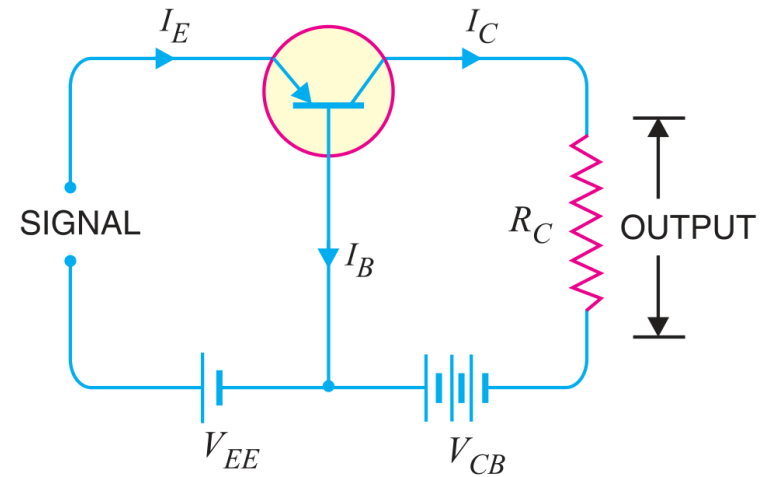
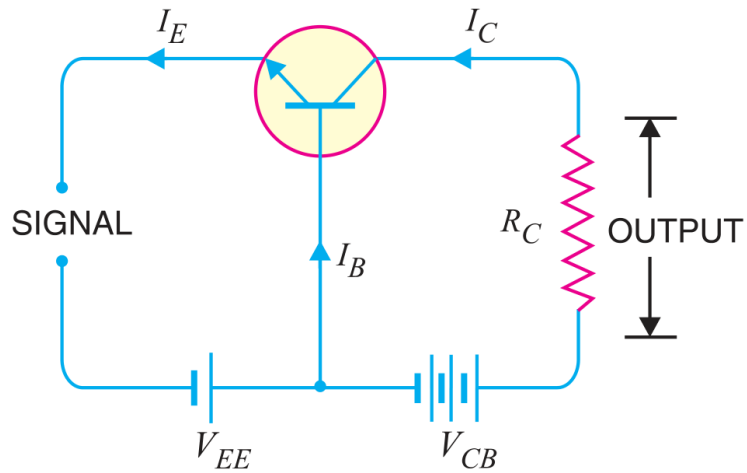


# Common Base Connection

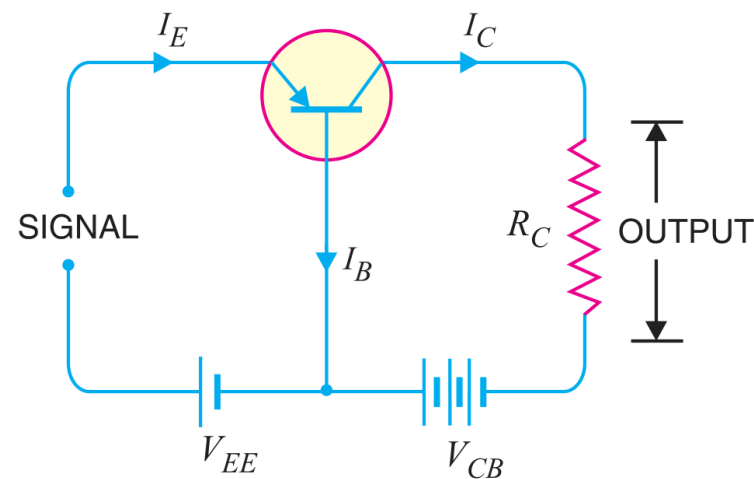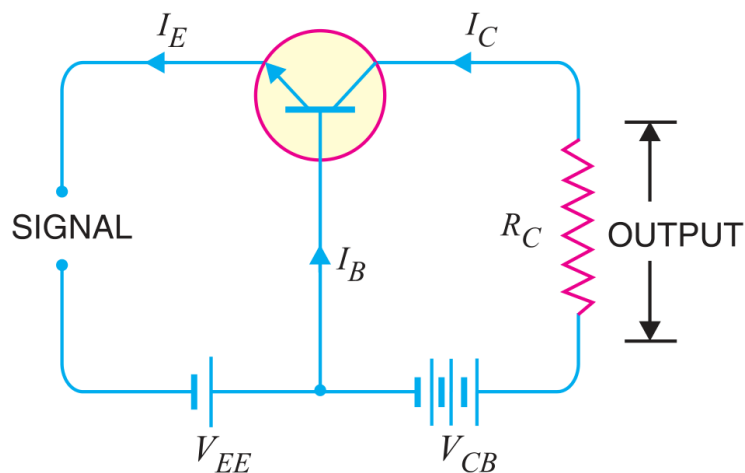

- ❑ **Current amplification factor ( $\alpha$ ):** The ratio of change in collector current to change in emitter current at constant collector base voltage ( $V_{CB}$ )

# Common Base Connection

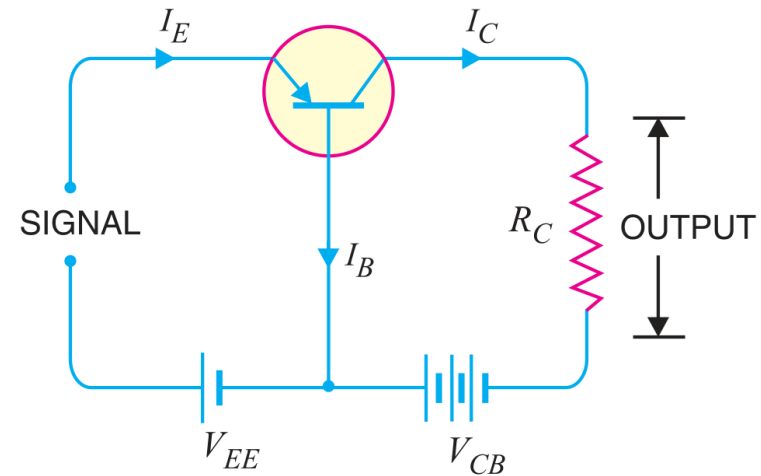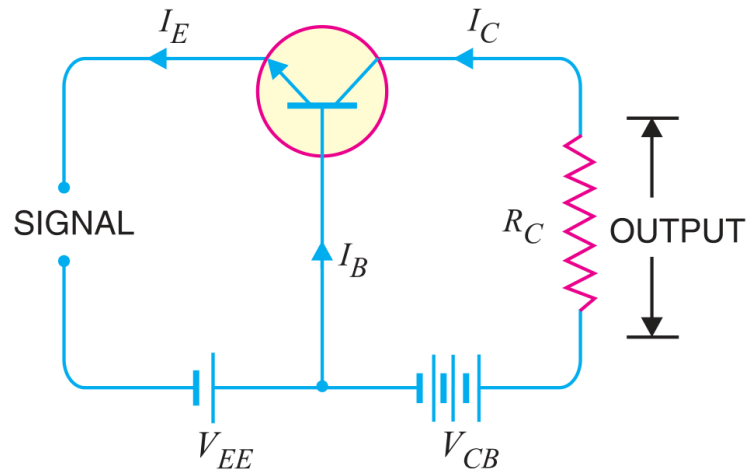

- ❑ **Current amplification factor ( $\alpha$ ):** The ratio of change in collector current to change in emitter current at constant collector base voltage ( $V_{CB}$ )

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \text{at constant } V_{CB}$$

# Common Base Connection



# Common Base Connection

- The amplification factor is less than unity and its value can be increased (but not more than 1) by decreasing base current (can be achieved by making base thin and doping it lightly).



# Common Base Connection

- ❑ The amplification factor is less than unity and its value can be increased (but not more than 1) by decreasing base current (can be achieved by making base thin and doping it lightly).
- ❑ Collector current:

# Common Base Connection


- ❑ The amplification factor is less than unity and its value can be increased (but not more than 1) by decreasing base current (can be achieved by making base thin and doping it lightly).
- ❑ Collector current:

$$I_C = \alpha I_E + I_{leakage}$$

# Common Base Connection

- ❑ The amplification factor is less than unity and its value can be increased (but not more than 1) by decreasing base current (can be achieved by making base thin and doping it lightly).
- ❑ Collector current:


$$I_C = \alpha I_E + I_{leakage}$$

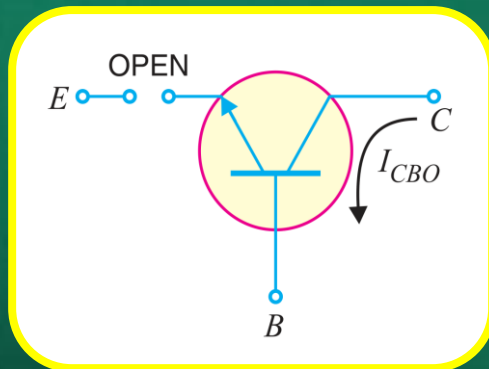

# Common Base Connection

- ❑ The amplification factor is less than unity and its value can be increased (but not more than 1) by decreasing base current (can be achieved by making base thin and doping it lightly).
- ❑ Collector current:

$$I_C = \alpha I_E + I_{leakage}$$

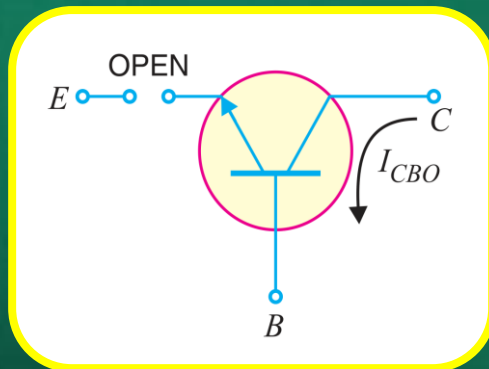


$$I_{leakage} = I_{CBO}$$



# Common Base Connection

- ❑ The amplification factor is less than unity and its value can be increased (but not more than 1) by decreasing base current (can be achieved by making base thin and doping it lightly).
- ❑ Collector current:

$$I_C = \alpha I_E + I_{leakage}$$

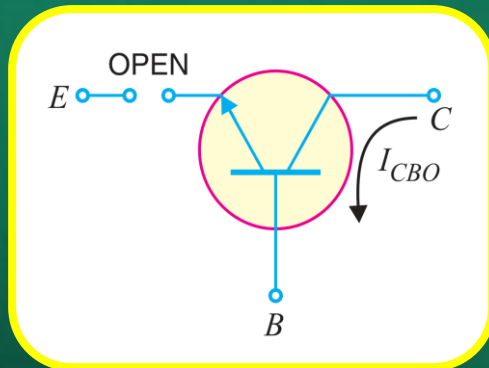

$$I_{leakage} = I_{CBO}$$

$$\therefore I_C = \alpha I_E + I_{CBO}$$

# Common Base Connection

$$I_C = \alpha I_E + I_{CBO}$$



# Common Base Connection

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

# Common Base Connection

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$\therefore I_C = \alpha(I_C + I_B) + I_{CBO}$$

# Common Base Connection

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$\therefore I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$\Rightarrow (1 - \alpha)I_C = \alpha I_B + I_{CBO}$$

# Common Base Connection

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$\therefore I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$\Rightarrow (1 - \alpha)I_C = \alpha I_B + I_{CBO}$$


$$\Rightarrow I_C = \frac{\alpha}{(1 - \alpha)} I_B + \frac{I_{CBO}}{(1 - \alpha)}$$

# Common Base Connection

- Generally  $I_{CBO}$  is very small for general purpose and low powered transistors and may be neglected in calculations.
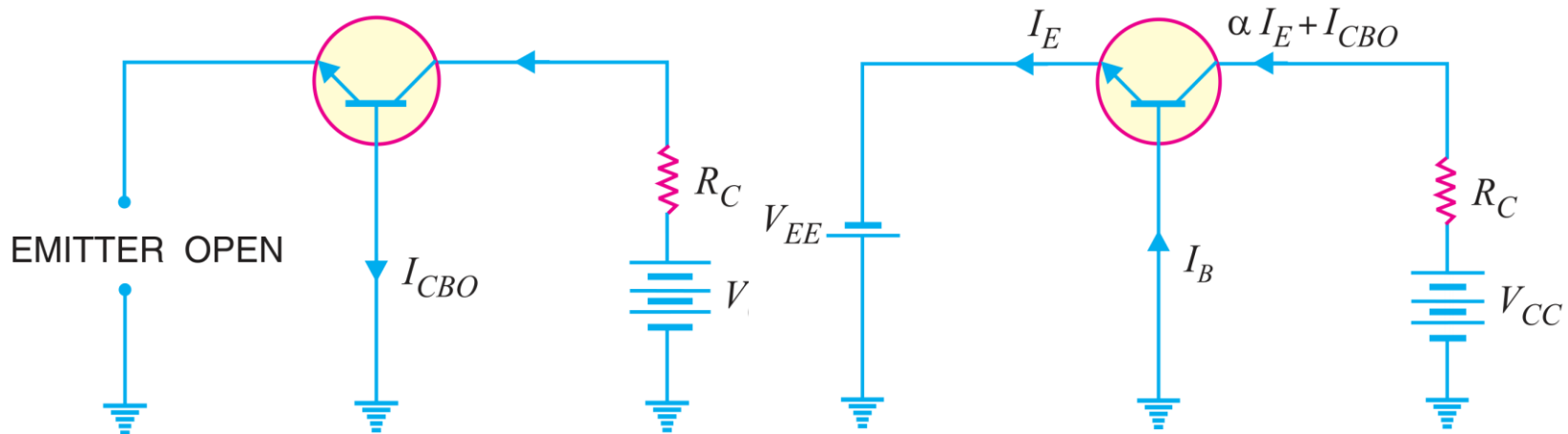
# Common Base Connection

- Generally  $I_{CBO}$  is very small for general purpose and low powered transistors and may be neglected in calculations.






# Common Base Characteristics

- Important characteristics of a common base connection
  - Input characteristics ( $I_E$  vs  $V_{EB}$ )
  - Output characteristics ( $I_C$  vs  $V_{CB}$ )

# Input Characteristics (CB)

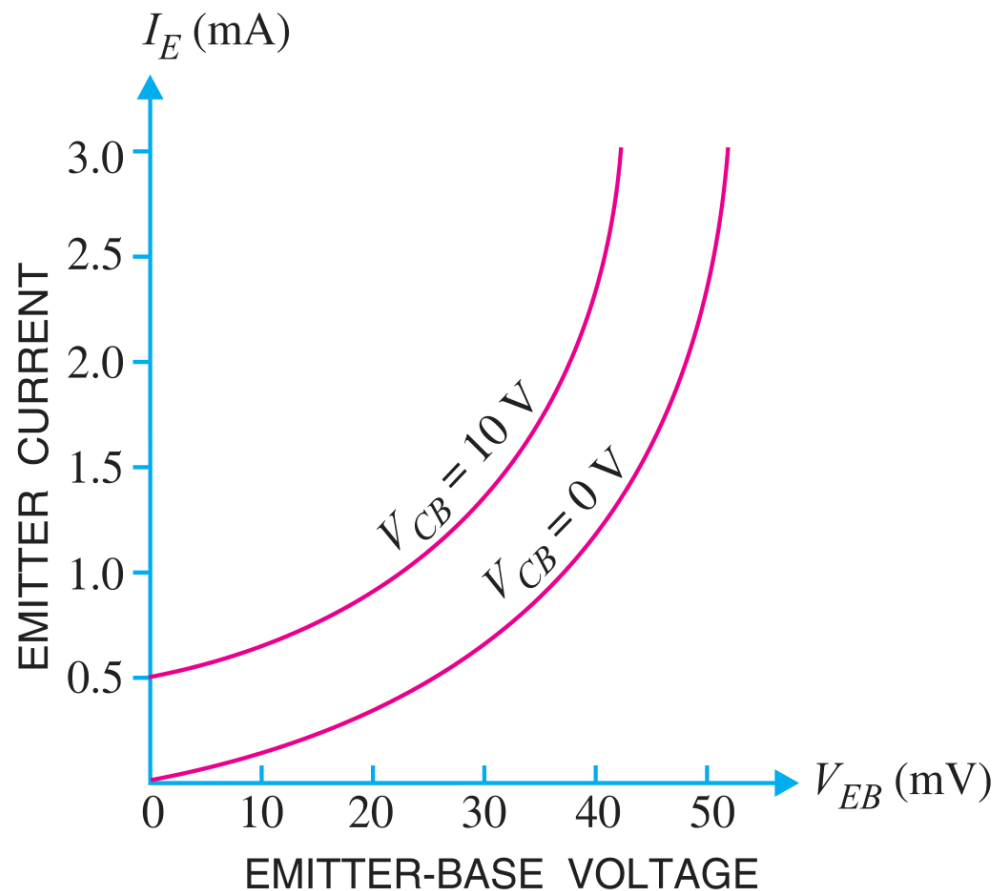

# Input Characteristics (CB)

# Input Characteristics (CB)

- The emitter current increases rapidly with small increase in emitter base voltage (i.e., input resistance is very small).

# Input Characteristics (CB)

- ❑ The emitter current increases rapidly with small increase in emitter base voltage (i.e., input resistance is very small).
- ❑ The emitter current is almost independent of collector-base voltage.



# Input Characteristics (CB)

- ❑ The emitter current increases rapidly with small increase in emitter base voltage (i.e., input resistance is very small).
- ❑ The emitter current is almost independent of collector-base voltage.

$$\text{Input resistance } r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CB}$$




# Input Characteristics (CB)

- ❑ The emitter current increases rapidly with small increase in emitter base voltage (i.e., input resistance is very small).
- ❑ The emitter current is almost independent of collector-base voltage.

$$\text{Input resistance } r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CB}$$

- ❑ Input resistance is very small and is of the order of few ohms.

# Output Characteristics (CB)

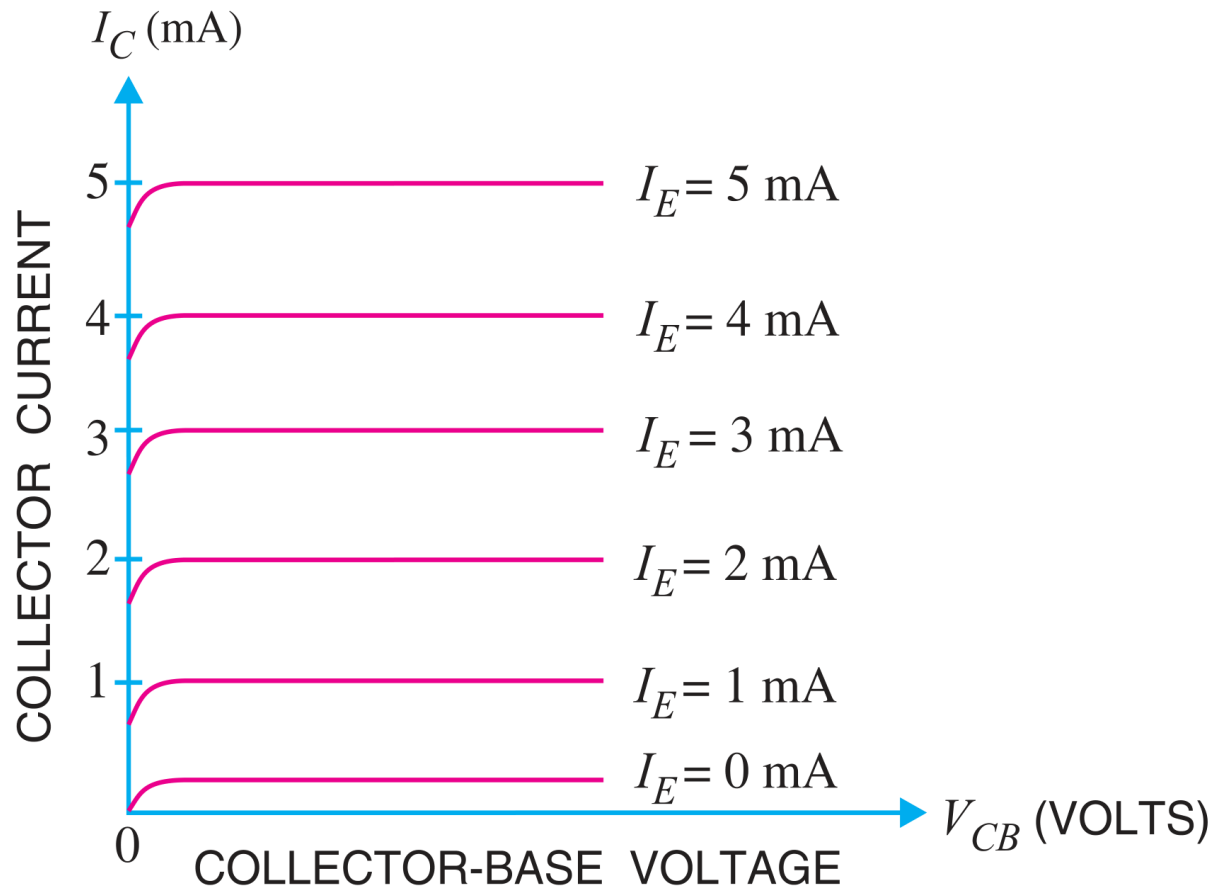

# Output Characteristics (CB)

# Output Characteristics (CB)

- ❑ The collector current varies with  $V_{CB}$  at very low voltages ( $< 1V$ ). Transistor is never operated in this region.

# Output Characteristics (CB)

- ❑ The collector current varies with  $V_{CB}$  at very low voltages ( $< 1V$ ). Transistor is never operated in this region.
- ❑ The collector current is almost constant even if  $V_{CB}$  is varied (after  $V_{CB} > 1V$ ). Transistor is always operated in this region.



# Output Characteristics (CB)

- ❑ The collector current varies with  $V_{CB}$  at very low voltages ( $< 1V$ ). Transistor is never operated in this region.
- ❑ The collector current is almost constant even if  $V_{CB}$  is varied (after  $V_{CB} > 1V$ ). Transistor is always operated in this region.

$$\text{Output resistance } r_o = \frac{\Delta V_{CB}}{\Delta I_C} \text{ at constant } I_E$$



# Output Characteristics (CB)

- ❑ The collector current varies with  $V_{CB}$  at very low voltages ( $< 1V$ ). Transistor is never operated in this region.
- ❑ The collector current is almost constant even if  $V_{CB}$  is varied (after  $V_{CB} > 1V$ ). Transistor is always operated in this region.

$$\text{Output resistance } r_o = \frac{\Delta V_{CB}}{\Delta I_C} \text{ at constant } I_E$$

- ❑ Output resistance is very high and is of the order of tens of kilo ohms.

# Example



**In a common base connection  $\alpha = 0.95$ . The voltage drop across  $2\text{ k}\Omega$  resistance connected in collector circuit is  $2\text{V}$ . Find the base current  $I_B$ .**

# Example


**In a common base connection  $\alpha = 0.95$ . The voltage drop across  $2\text{ k}\Omega$  resistance connected in collector circuit is  $2\text{ V}$ . Find the base current  $I_B$ .**

**Answer:**  $I_B = 0.05\text{ mA}$

# Common Emitter Connection

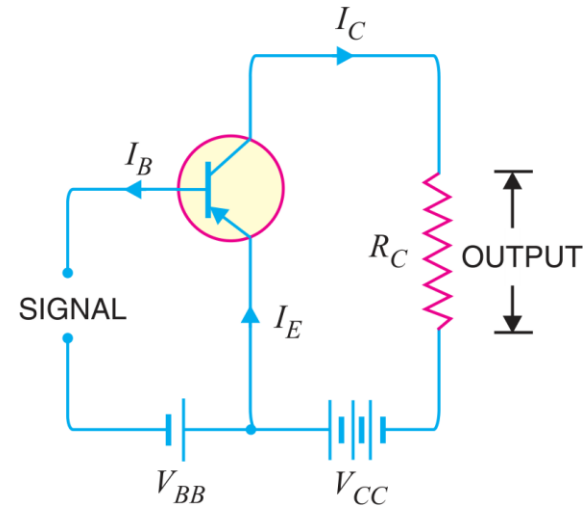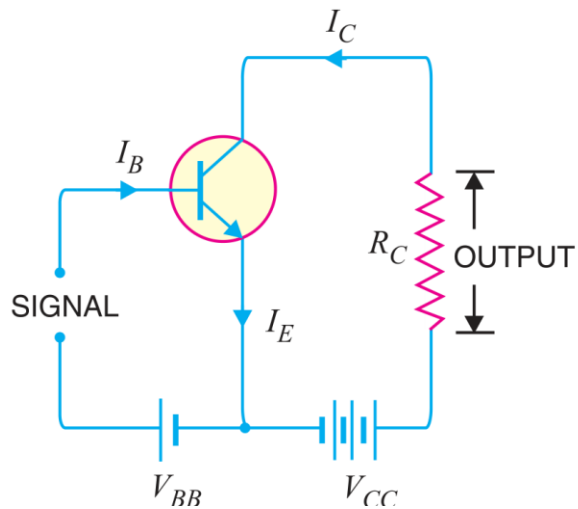


# Common Emitter Connection

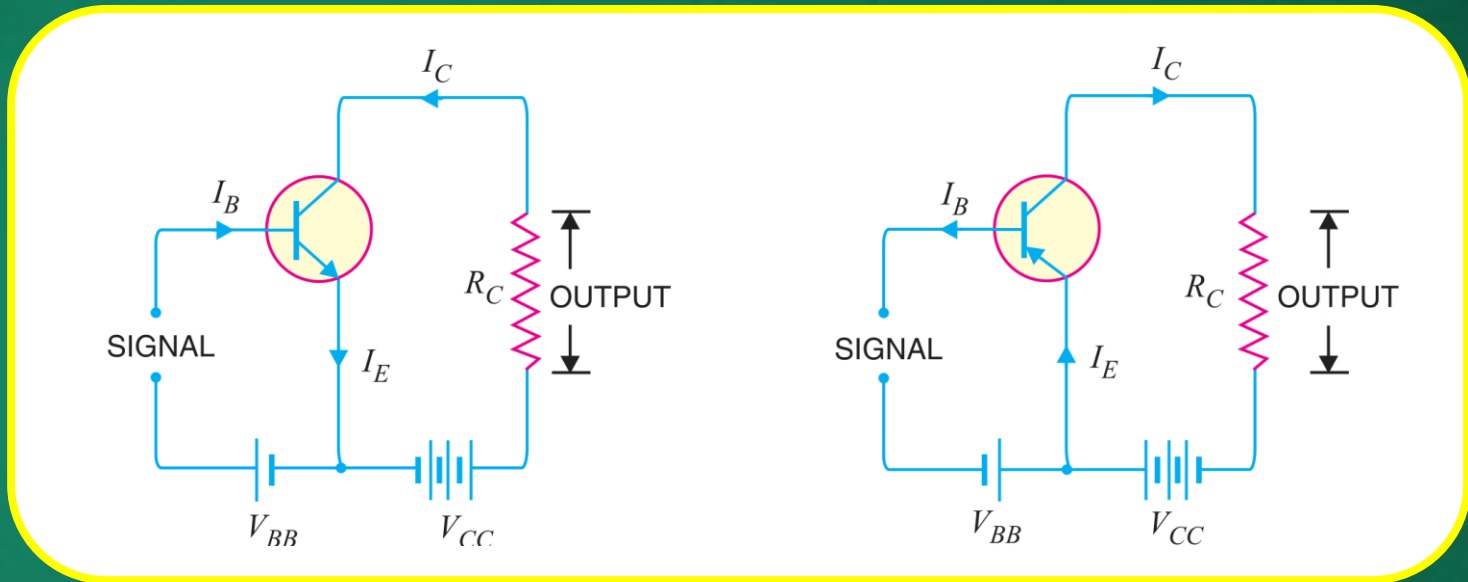

- ❑ **Current amplification factor ( $\beta$ ):** The ratio of change in collector current to change in base current at constant collector emitter voltage ( $V_{CE}$ )



# Common Emitter Connection

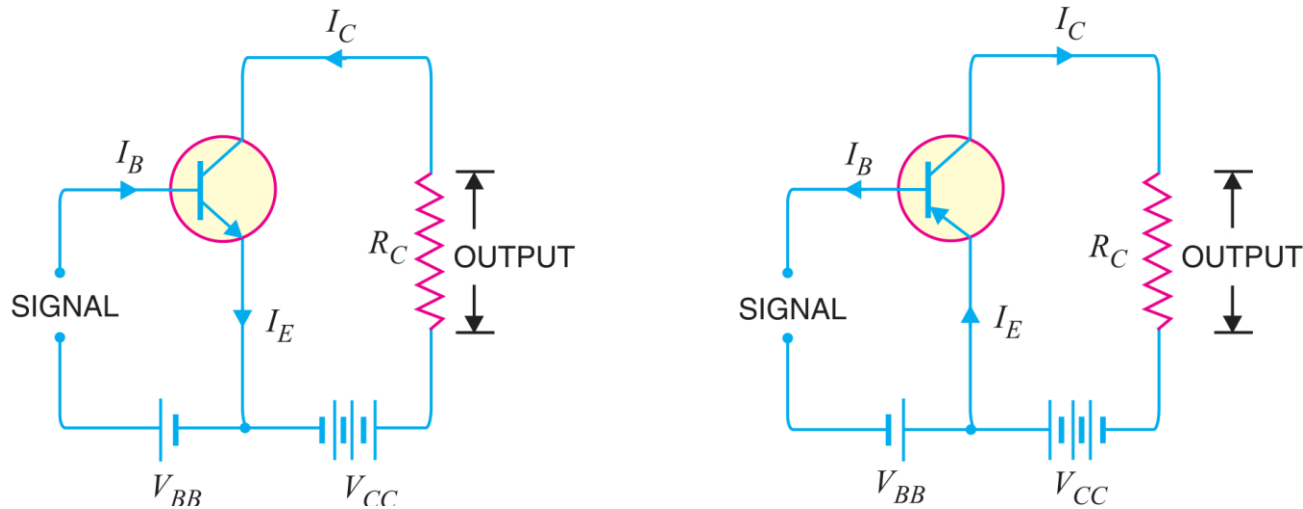

- ❑ **Current amplification factor ( $\beta$ ):** The ratio of change in collector current to change in base current at constant collector emitter voltage ( $V_{CE}$ )

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \text{at constant } V_{CE}$$

# Common Emitter Connection

- The amplification factor  $\beta$  is greater than 20 and can vary between 20 to 500. This type of connection is frequently used as it gives fair current & voltage gain.

# Common Emitter Connection

- ❑ The amplification factor  $\beta$  is greater than 20 and can vary between 20 to 500. This type of connection is frequently used as it gives fair current & voltage gain.
- ❑ Relation between  $\alpha$  and  $\beta$

# Common Emitter Connection

- ❑ The amplification factor  $\beta$  is greater than 20 and can vary between 20 to 500. This type of connection is frequently used as it gives fair current & voltage gain.
- ❑ Relation between  $\alpha$  and  $\beta$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

# Common Emitter Connection

- ❑ The amplification factor  $\beta$  is greater than 20 and can vary between 20 to 500. This type of connection is frequently used as it gives fair current & voltage gain.
- ❑ Relation between  $\alpha$  and  $\beta$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$



# Common Emitter Connection

# Common Emitter Connection

$$I_E = I_C + I_B$$

# Common Emitter Connection

$$I_E = I_C + I_B$$

$$\Rightarrow \Delta I_E = \Delta I_C + \Delta I_B$$

# Common Emitter Connection

$$I_E = I_C + I_B$$

$$\Rightarrow \Delta I_E = \Delta I_C + \Delta I_B$$

$$\Rightarrow \Delta I_C = \Delta I_E - \Delta I_B$$

# Common Emitter Connection

$$I_E = I_C + I_B$$

$$\Rightarrow \Delta I_E = \Delta I_C + \Delta I_B$$

$$\Rightarrow \Delta I_C = \Delta I_E - \Delta I_B$$

$$\Rightarrow \frac{\Delta I_C}{\Delta I_B} = \beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} = \frac{\Delta I_C / \Delta I_E}{\Delta I_E / \Delta I_E - \Delta I_C / \Delta I_E}$$



# Common Emitter Connection

$$I_E = I_C + I_B$$

$$\Rightarrow \Delta I_E = \Delta I_C + \Delta I_B$$

$$\Rightarrow \Delta I_C = \Delta I_E - \Delta I_B$$

$$\Rightarrow \frac{\Delta I_C}{\Delta I_B} = \beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} = \frac{\Delta I_C / \Delta I_E}{\Delta I_E / \Delta I_E - \Delta I_C / \Delta I_E}$$

$$\Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$

# Common Emitter Connection

□ **Collector current:**

# Common Emitter Connection

□ Collector current:

$$I_E = I_C + I_B$$

# Common Emitter Connection

□ Collector current:

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

# Common Emitter Connection

□ Collector current:

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$



# Common Emitter Connection

□ **Collector current:**

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$(1 - \alpha)I_C = \alpha I_B + I_{CBO}$$

# Common Emitter Connection

## □ Collector current:

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$(1 - \alpha)I_C = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{(1 - \alpha)} I_B + \frac{I_{CBO}}{(1 - \alpha)}$$

# Common Emitter Connection

$$I_C = \frac{\alpha}{(1 - \alpha)} I_B + \frac{I_{CBO}}{(1 - \alpha)}$$

# Common Emitter Connection

$$I_C = \frac{\alpha}{(1 - \alpha)} I_B + \frac{I_{CBO}}{(1 - \alpha)}$$

$$\Rightarrow I_C = \beta I_B + I_{CEO}$$

# Common Emitter Connection

$$I_C = \frac{\alpha}{(1 - \alpha)} I_B + \frac{I_{CBO}}{(1 - \alpha)}$$

$$\Rightarrow I_C = \beta I_B + I_{CEO}$$

$I_{CEO}$  is the collector to emitter current with base open.





# Common Emitter Connection


$$I_C = \frac{\alpha}{(1-\alpha)} I_B + \frac{I_{CBO}}{(1-\alpha)}$$

$$\Rightarrow I_C = \beta I_B + I_{CEO}$$

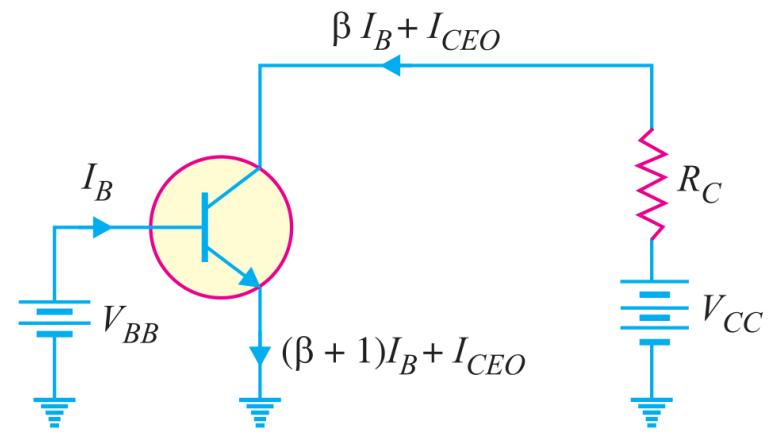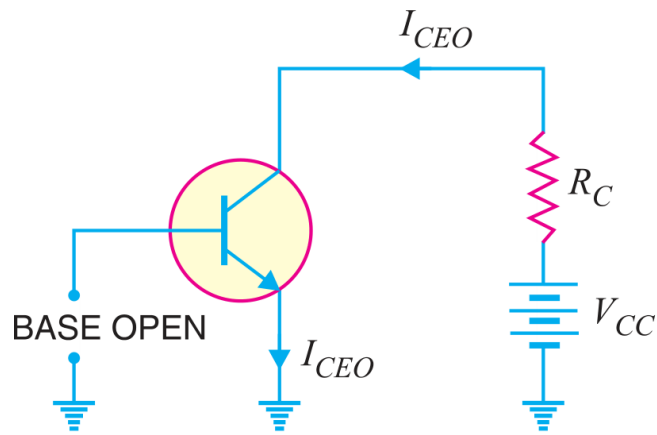$I_{CEO}$  is the collector to emitter current with base open.



# Measurement of Leakage Current

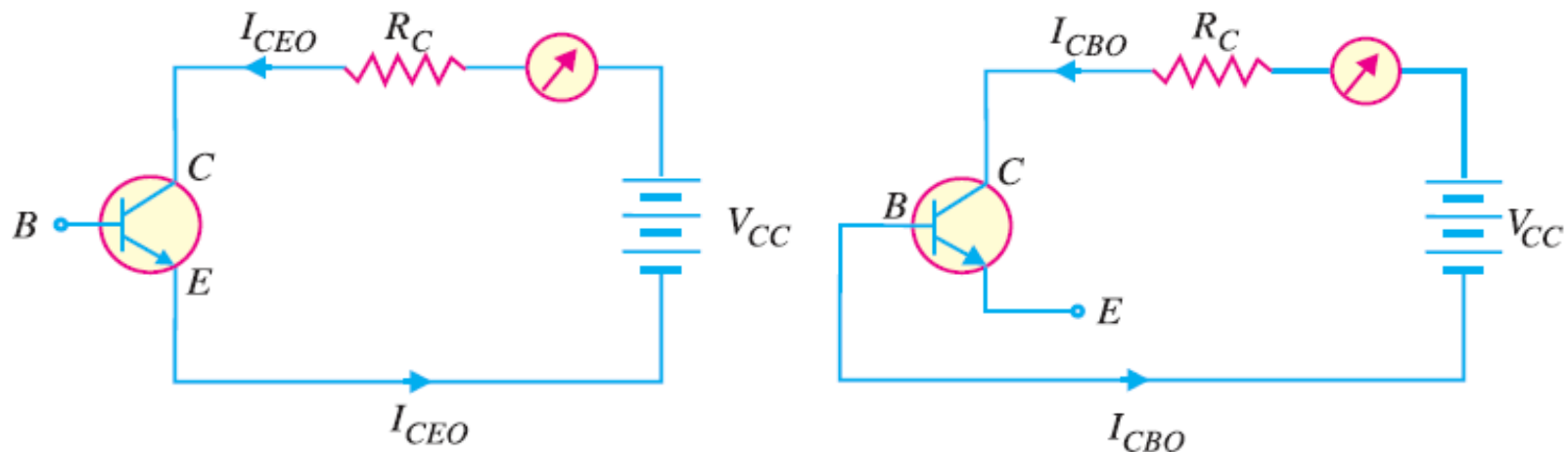


# Common Emitter Characteristics

- ❑ Important characteristics of a common emitter connection
  - Input characteristics ( $I_B$  vs  $V_{BE}$ )
  - Output characteristics ( $I_C$  vs  $V_{CE}$ )


# Common Emitter Characteristics
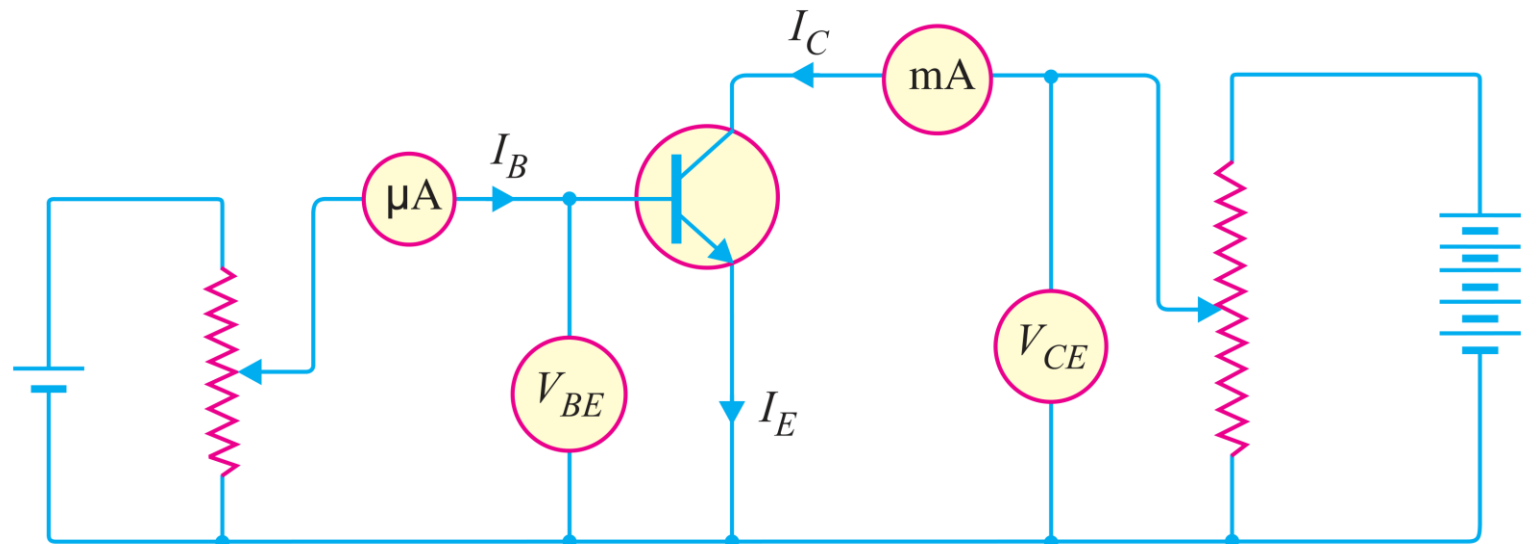
## □ Important characteristics of a common emitter connection

- **Input characteristics ( $I_B$  vs  $V_{BE}$ )**
- **Output characteristics ( $I_C$  vs  $V_{CE}$ )**



# Input Characteristics (CE)

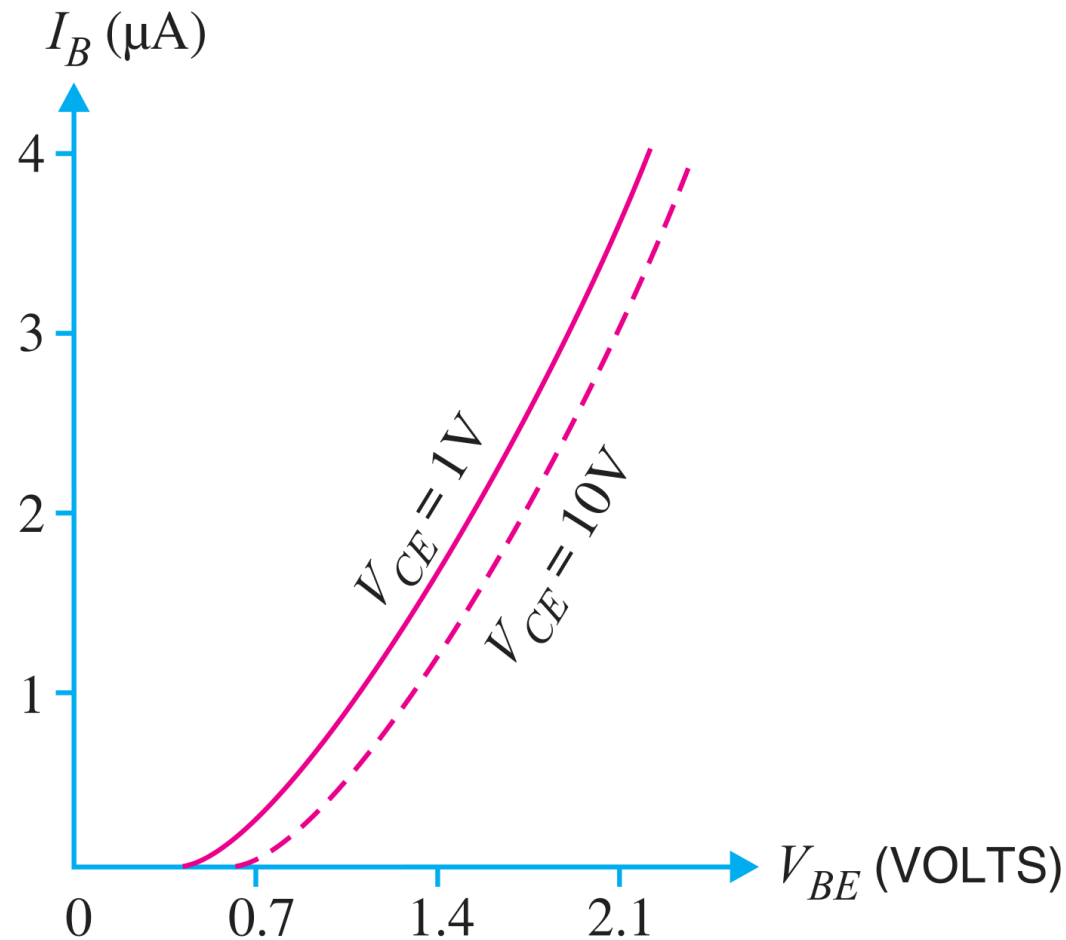



# Input Characteristics (CE)

- The emitter current increases less rapidly with  $V_{BE}$  compared to CB connection, hence input resistance is higher compared to CB connection.

# Input Characteristics (CE)

- ❑ The emitter current increases less rapidly with  $V_{BE}$  compared to CB connection, hence input resistance is higher compared to CB connection.
- ❑ The emitter current is almost independent of collector-base voltage.

# Input Characteristics (CE)

- The emitter current increases less rapidly with  $V_{BE}$  compared to CB connection, hence input resistance is higher compared to CB connection.
- The emitter current is almost independent of collector-base voltage.

$$\text{Input resistance } r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CE}$$


# Input Characteristics (CE)

- ❑ The emitter current increases less rapidly with  $V_{BE}$  compared to CB connection, hence input resistance is higher compared to CB connection.
- ❑ The emitter current is almost independent of collector-base voltage.

$$\text{Input resistance } r_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CE}$$


- ❑ Input resistance is very small and is of the order of few hundred ohms.

# Output Characteristics (CE)



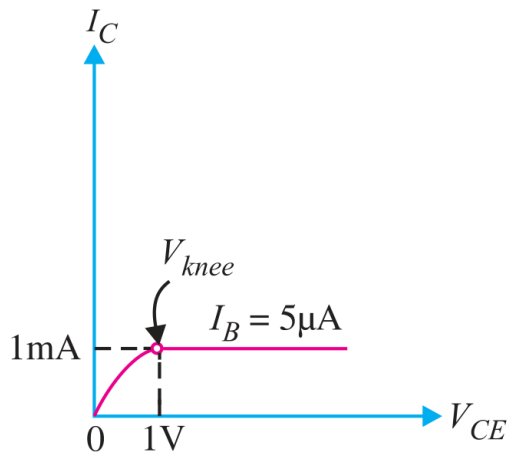





# Output Characteristics (CE)

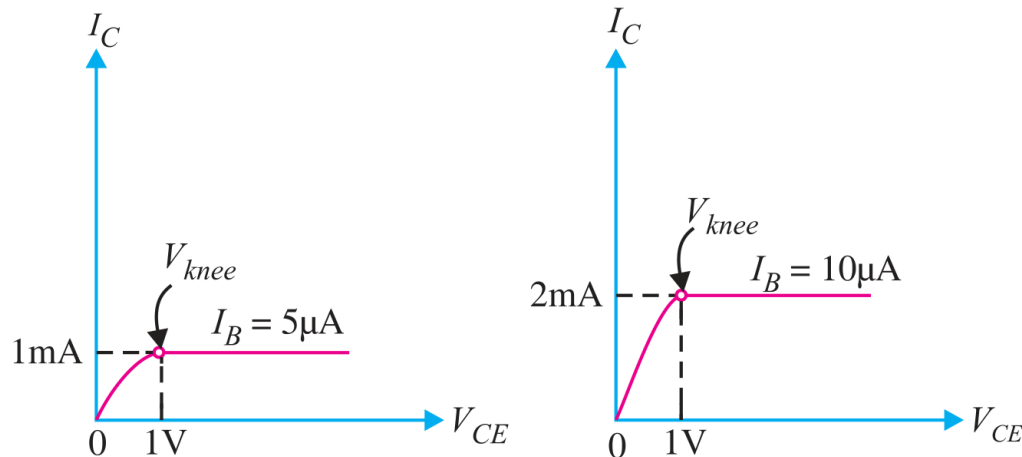


# Output Characteristics (CE)

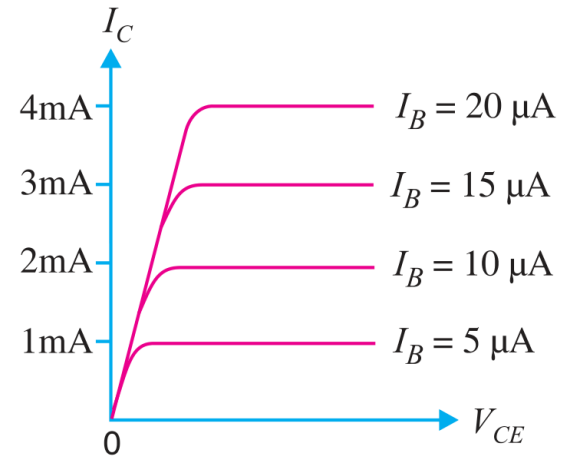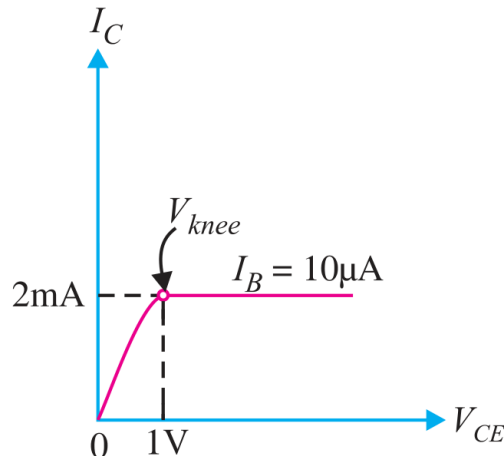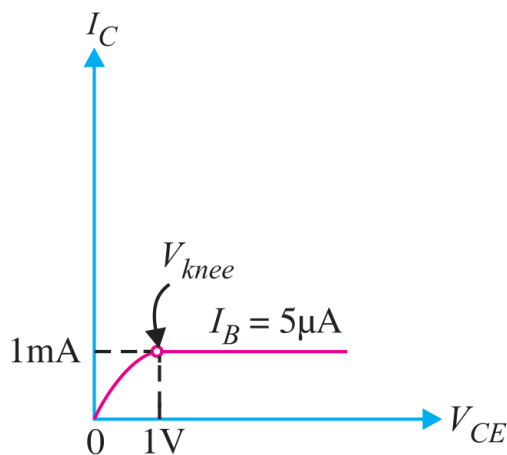


# Output Characteristics (CE)

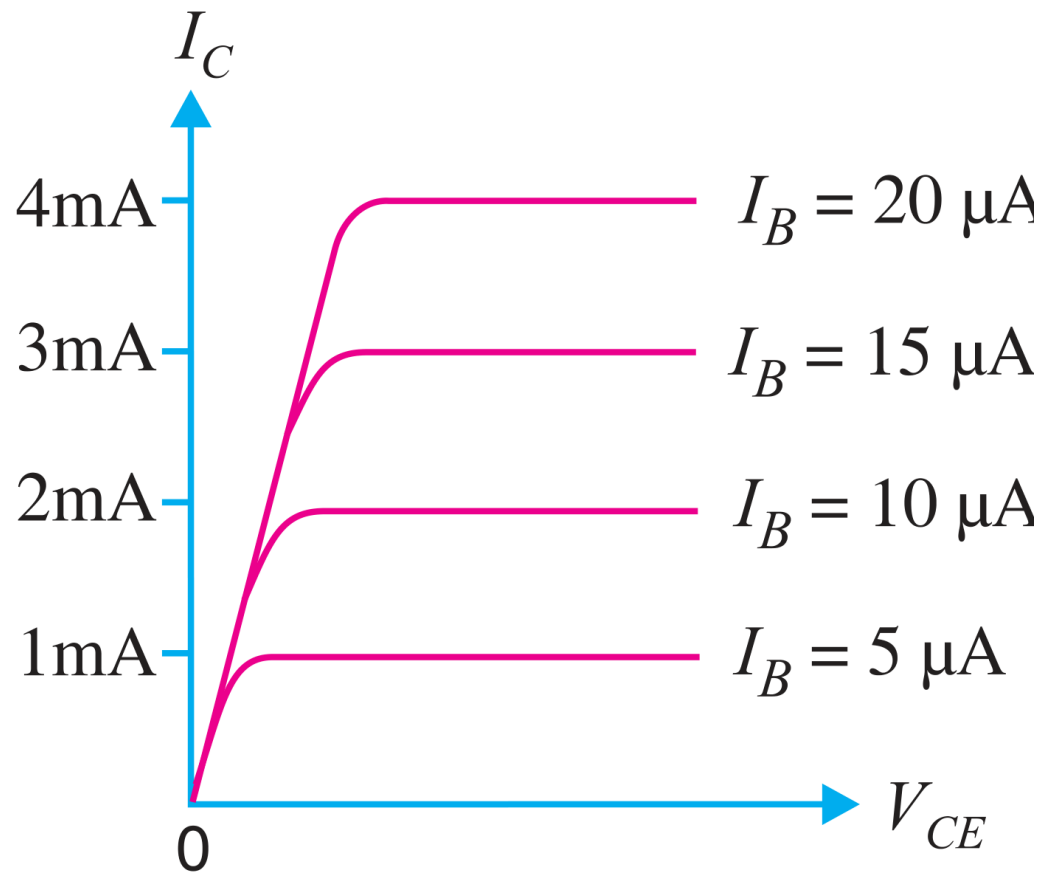

# Output Characteristics (CE)

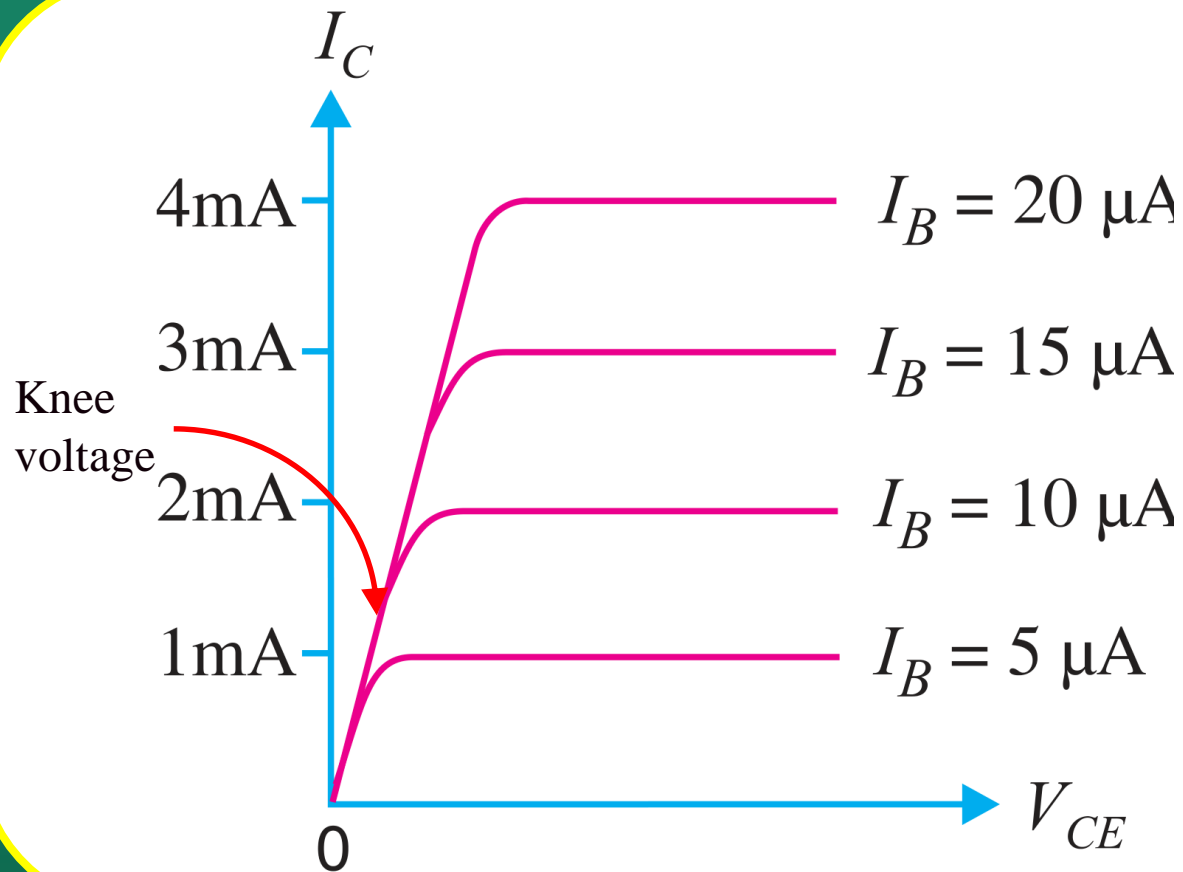

# Output Characteristics (CE)

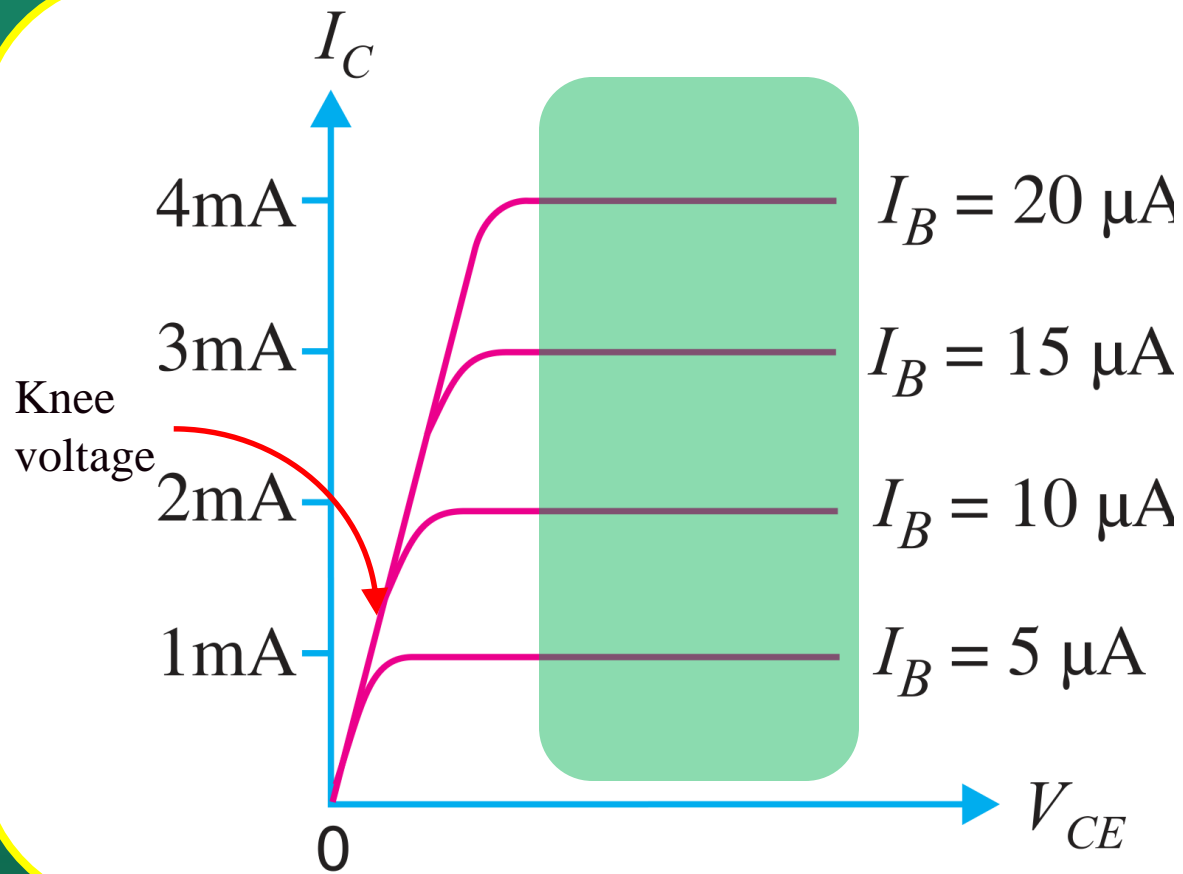



# Output Characteristics (CE)

- The collector current varies with  $V_{CE}$  up to 1V and after that it remains constant and independent of  $V_{CE}$ .

# Output Characteristics (CE)

- ❑ The collector current varies with  $V_{CE}$  up to 1V and after that it remains constant and independent of  $V_{CE}$ .
- ❑ The collector current is almost constant even if  $V_{CB}$  is varied (after  $V_{CB} > 1V$ ). Transistor is always operated in this region.

# Output Characteristics (CE)

- ❑ The collector current varies with  $V_{CE}$  up to 1V and after that it remains constant and independent of  $V_{CE}$ .
- ❑ The collector current is almost constant even if  $V_{CB}$  is varied (after  $V_{CB} > 1V$ ). Transistor is always operated in this region.

$$\text{Output resistance } r_o = \frac{\Delta V_{CE}}{\Delta I_C} \text{ at constant } I_B$$

# Output Characteristics (CE)

- ❑ The collector current varies with  $V_{CE}$  up to 1V and after that it remains constant and independent of  $V_{CE}$ .
- ❑ The collector current is almost constant even if  $V_{CB}$  is varied (after  $V_{CB} > 1V$ ). Transistor is always operated in this region.

$$\text{Output resistance } r_o = \frac{\Delta V_{CE}}{\Delta I_C} \text{ at constant } I_B$$

- ❑ Output resistance is very high but less than that of CB connection and is of the order of 50 K $\Omega$ .



# Example

**A transistor is connected in CE configuration in which the collector supply is 8 V and voltage drop across  $R_C$  connected in the collector circuit is 0.5 V. The value of  $R_C = 800 \Omega$ . If  $\alpha = 0.96$ , determine**

**a) collector-emitter voltage**

**b) Base current**



# Example

**A transistor is connected in CE configuration in which the collector supply is 8 V and voltage drop across  $R_C$  connected in the collector circuit is 0.5 V. The value of  $R_C = 800 \Omega$ . If  $\alpha = 0.96$ , determine**


**a) collector-emitter voltage**

**b) Base current**

**Answer:**  $V_{CE} = 7.5 \text{ V}$ ,  $I_B = 26 \mu\text{A}$

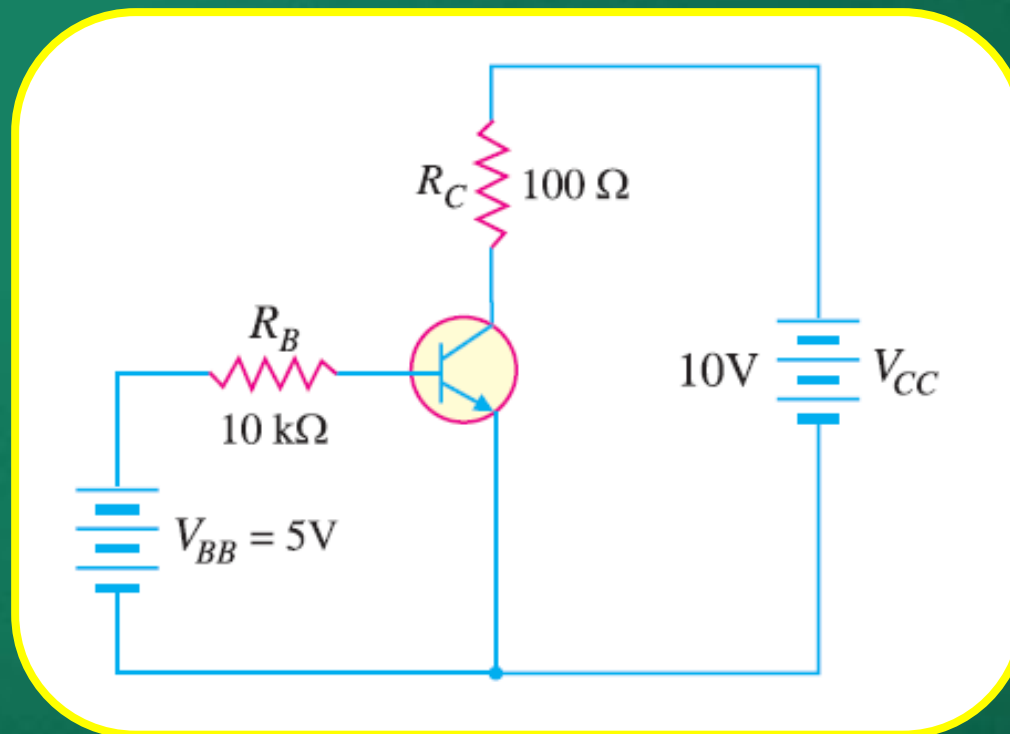
# Example

Determine  $V_{CB}$  in the transistor circuit shown in Fig. below. The transistor is of silicon and has  $\beta = 150$ .


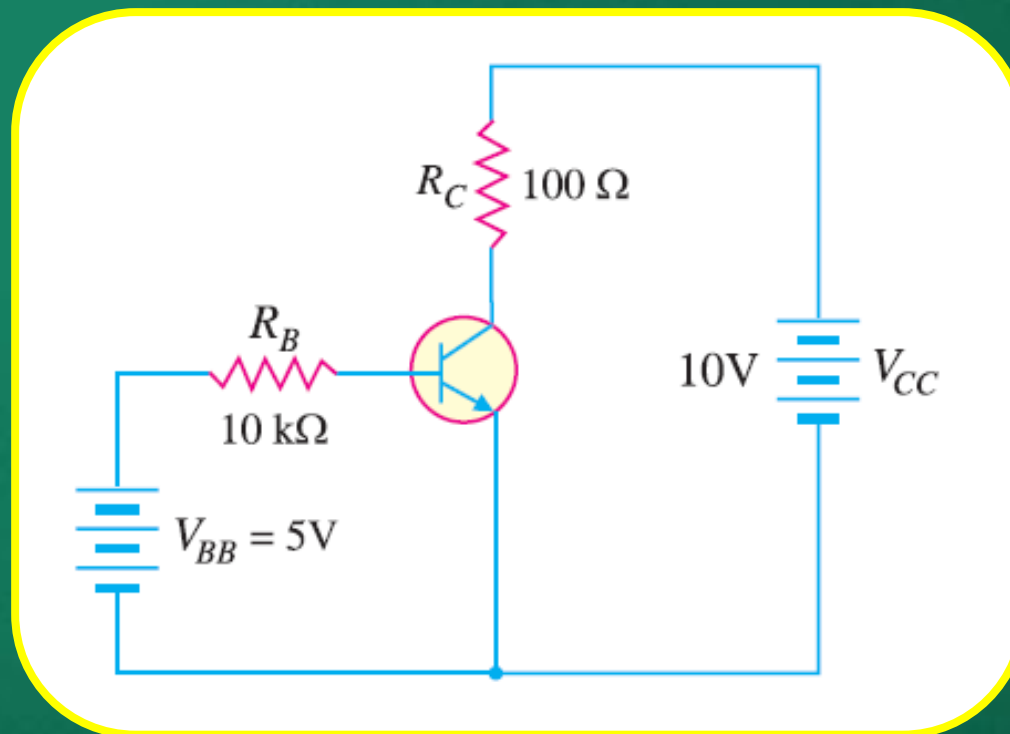
# Example

Determine  $V_{CB}$  in the transistor circuit shown in Fig. below. The transistor is of silicon and has  $\beta = 150$ .



Answer:  $V_{CB} = V_{CE} - V_{BE} = 2.85\text{ V}$