

Solutions to Tutorial Sheet - 11

IEC103

Q1 Find the Q points ( $V_{CE1}, I_{C1}$ ) and ( $V_{CE2}, I_{C2}$ ) of transistors  $Q_1$  and  $Q_2$  respectively in the amplifier circuit shown in Fig. Q1

Take  $I_C \approx I_E$ ,  $|V_{BE}| = 0.7V$

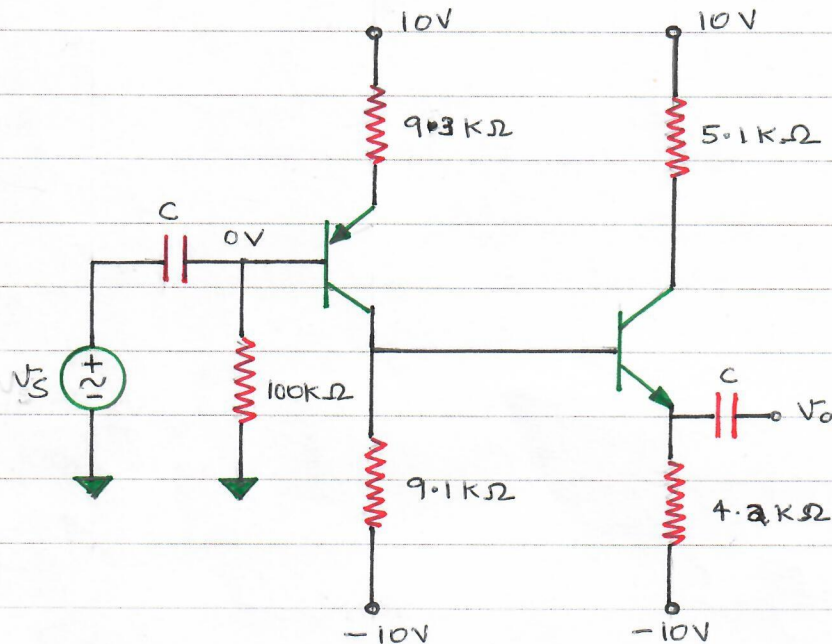


Fig. Q1

Sol.

$$i) \quad I_{C1} = \frac{10 - 0.7}{9.3K} = \frac{9.3}{9.3K} = 1mA \approx I_{E1}$$

$$V_{E1} = 10 - 1 \times 10^{-3} \times 9.3 \times 10^3 = 10 - 9.3 = 0.7V$$

$$V_{C1} = -10 + 9.1 \times 10^3 \times 1 \times 10^{-3} = -10 + 9.1 = -0.9V$$

$$V_{CE1} = V_{C1} - V_{E1} = -0.9 - 0.7 = -1.6V$$

Q point of transistor  $Q_1$  is  $(-1.6V, 1mA)$

$$ii) \quad V_{E2} = V_{C1} - V_{BE} = -0.9 - 0.7 = -1.6V$$

$$I_{E2} = \frac{V_{E2} - (-10)}{4.2K} = \frac{-1.6 + 10}{4.2K} = \frac{8.4}{4.2K} = 2mA \approx I_{C2}$$

$$V_{C2} = 10 - I_{C2} \times 5.1K = 10 - 2 \times 10^{-3} \times 5.1 \times 10^3 = -0.2$$

$$V_{CE2} = V_{C2} - V_{E2} = -0.2 - (-1.6) = 1.4V$$

Q point of transistor  $Q_2$  is  $(1.4V, 2mA)$

(Q2) Calculate the quiescent points of transistors  $Q_1$  and  $Q_2$  shown in Fig. Q2. Assume that the base currents are negligible and take  $V_{BE} = 0.7V$  for both  $Q_1$  and  $Q_2$ .


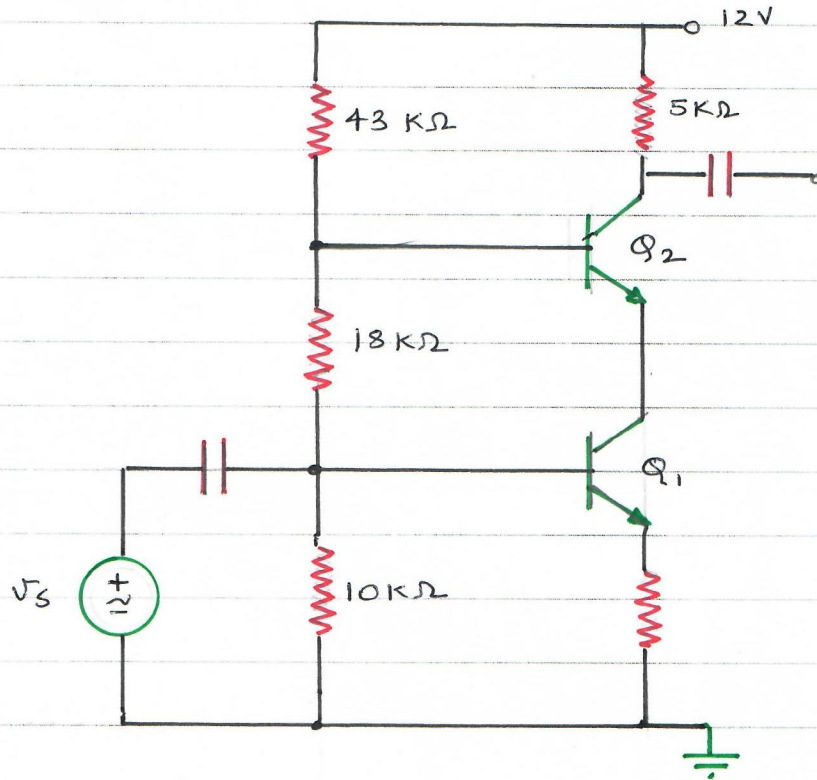


Fig. Q2

Sol. DC equivalent circuit

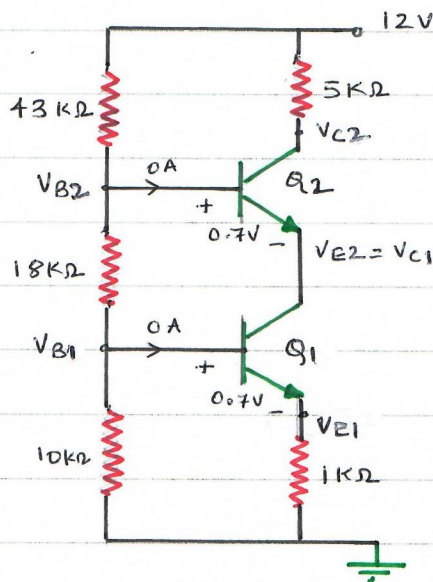

$$I_{B1} = I_{B2} = 0A$$

$$V_{BE1} = V_{BE2} = 0.7V$$

$$V_{B1} = \frac{10}{10+18+43} \times 12 \approx 1.7V$$

$$V_{B2} = \frac{10+18}{10+18+43} \approx 4.7V$$

$$V_{E1} = V_{B1} - 0.7 = 1.7 - 0.7 = 1V$$

$$V_{E2} = V_{B2} - 0.7 = 4.7 - 0.7 = 4V$$

$$I_{E1} = \frac{V_{E1}}{1K} A = \dots = 1mA \approx I_{C1}$$

$$I_{C1} \approx I_{E2} = 1mA = I_{C2}$$

$$V_{C2} = 12 - I_{C2} \times 5K$$

$$= 12 - 1 \times 5 = 7V$$

$$V_{CE1} = V_{C1} - V_{E1} = V_{E2} - V_{E1} \\ = 4 - 1 = 3V$$

$$V_{CE2} = V_{C2} - V_{E2} =$$

$$= 7 - 4 = 3V$$

∴ Q point for  $Q_1$  and  $Q_2$  are

$$V_{CE1} = 3V, I_{C1} = 1mA \quad \text{and}$$

$$V_{CE2} = 3V, I_{C2} = 1mA$$



Q3 For the amplifier circuit shown below, calculate the voltage gain  $A_v \left( \frac{v_o}{v_s} \right)$ , current gain  $(i_o/i_s)$ , input resistance ( $R_{in}$ ), and output resistance ( $R_o$ ). Given that the transistor is of silicon and  $\beta = 100$ .


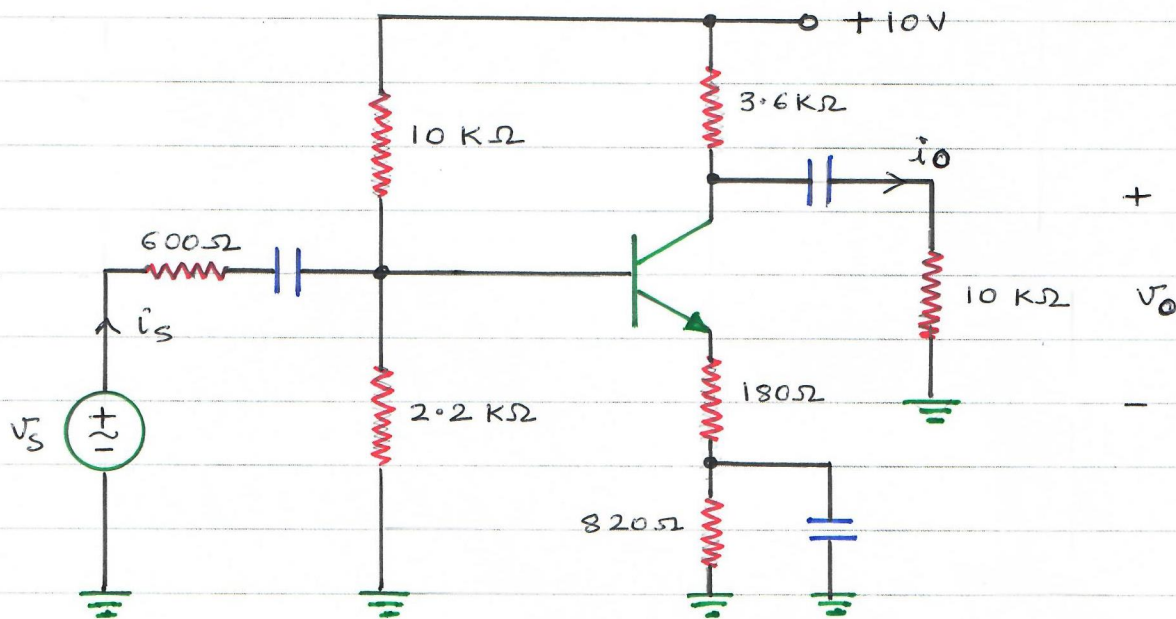


Fig. Q3

Sol.

Capacitors act as open circuit to DC and short circuit to AC.

DC equivalent circuit

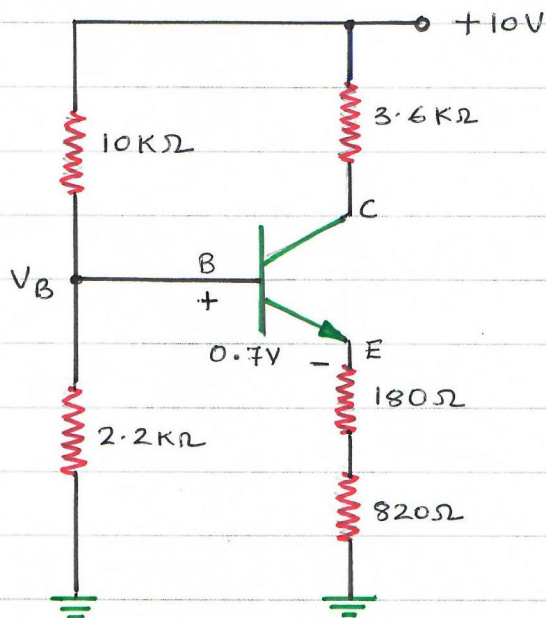

$$V_B \approx \frac{10 \times 2.2}{2.2 + 10} = 1.803 \text{ V}$$

$$V_E = V_B - 0.7 = 1.103 \text{ V}$$

$$I_E = \frac{1.103}{180 + 820} = \frac{1.103}{1000} = 1.103 \text{ mA}$$



$$I_C \approx I_E = 1.103 \text{ mA}$$

$$\begin{aligned} V_C &= 10 - I_C \times 3.6 \text{ K} \\ &= 10 - 3.6 \times 10^3 \times 1.103 \times 10^{-3} \\ &= 10 - 3.6 \times 1.103 \\ &= 6.03 \text{ V} \end{aligned}$$


$$V_{CB} = V_C - V_B = 6.03 - 1.803 = 4.227 \text{ V}$$

So, collector base junction is reverse biased. So, the transistor is in active region.

AC equivalent circuit

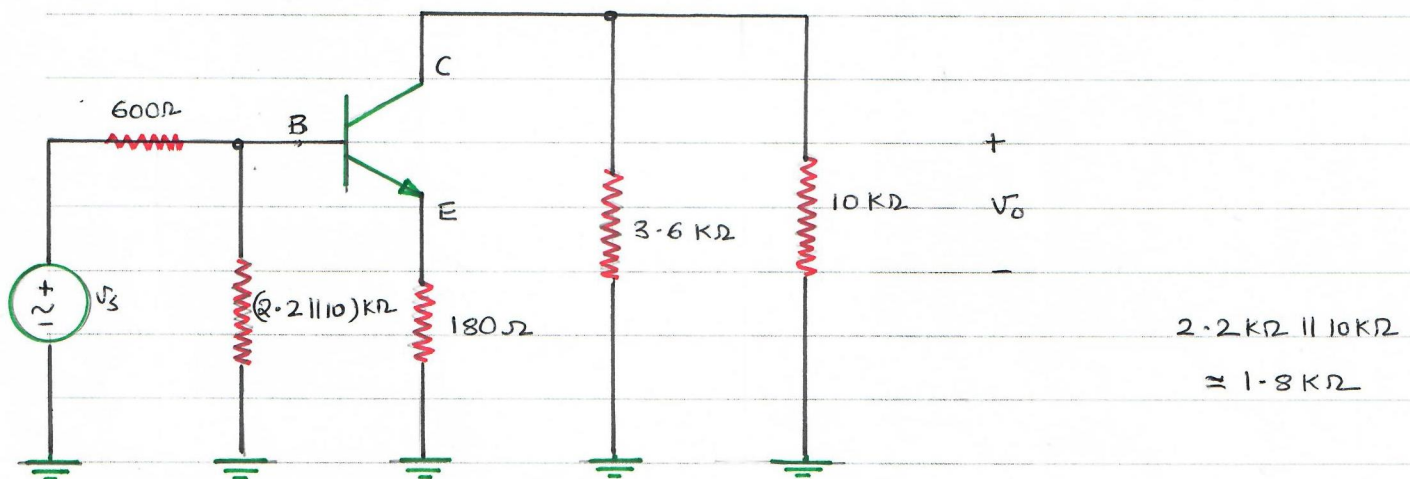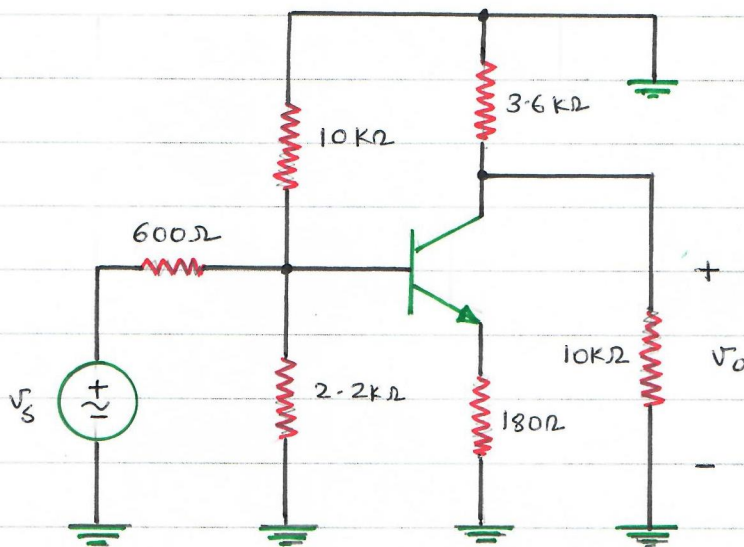

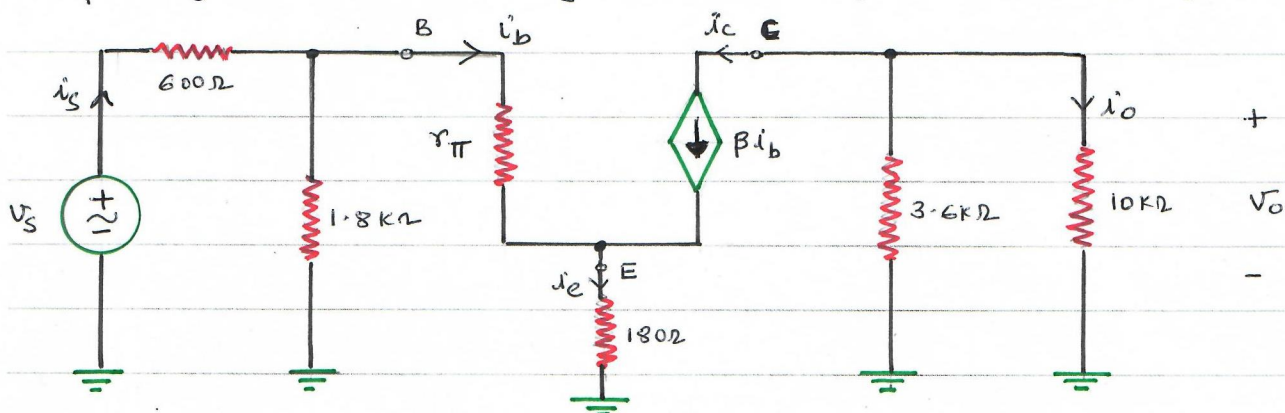Replacing the transistor by its small-signal model (or hybrid- $\pi$  model)



$$r_{\pi} = \frac{25 \times 10^{-3}}{I_B} = \frac{25 \times 10^{-3}}{(I_C/\beta)} = \frac{25 \times 10^{-3} \times 100}{I_C}$$

$$= \frac{2.5}{1.103 \times 10^{-3}} = 2.27 \text{ K}\Omega$$

Voltage gain

$$\begin{aligned} V_b &= r_{\pi} i_b + V_e \\ &= r_{\pi} i_b + 180 i_e \\ &= r_{\pi} i_b + 180(1+\beta) i_b \\ &\approx r_{\pi} i_b + 180\beta i_b \\ &= (r_{\pi} + 180\beta) i_b \\ &= (2.27 \text{ K} + 18 \text{ K}) i_b \\ &= 20.27 \text{ K} i_b \end{aligned}$$

$$i_s = i_b + \frac{V_b}{1.8 \text{ K}}$$

$$= i_b + \frac{20.27 \text{ K} i_b}{1.8 \text{ K}} = i_b + \frac{20.27}{1.8} i_b$$

$$\Rightarrow i_s = 11.26 i_b + i_b = 12.26 i_b$$

$$\begin{aligned} V_s &= V_b + i_s \times 600 \\ &= 600 \times 12.26 i_b + V_b \\ &= 7356 i_b + 20270 i_b \\ &= 27626 i_b \end{aligned}$$

$$\begin{aligned} V_o &= -i_c \times 3.6 \text{ K} \parallel 10 \text{ K} \\ &= -2.65 \text{ K} i_c \\ &= -2.65 \text{ K} \times \beta i_b \\ &= -2.65 \text{ K} \times 100 i_b = -265000 i_b \end{aligned}$$

$$\begin{aligned} \text{Voltage gain} &= \frac{V_o}{V_s} = \frac{-265000}{27626} \\ &= -9.5924 \end{aligned}$$



current gain

$$\hat{i}_o = -\hat{i}_c \times \frac{3.6}{10+3.6}$$

$$= -0.265 \hat{i}_c$$

$$= -0.265 \times \beta \hat{i}_b$$

$$= -26.5 \hat{i}_b$$

Already we know that  $\hat{i}_s = 12.26 \hat{i}_b$

$$\text{current gain} = \frac{\hat{i}_o}{\hat{i}_s} = \frac{-26.5 \hat{i}_b}{12.26 \hat{i}_b} = -2.16 = A_i$$

Input resistance

$$R_{in} = \frac{V_s}{\hat{i}_s} = \frac{27626 \hat{i}_b}{12.26 \hat{i}_b} = 2253.3 = 2.253 \text{ K}\Omega$$

or

$$R_{in} = 600 + 1.8 \text{ K} \parallel [r_{\pi} + (\beta+1) \times 180]$$

$$\approx 600 + 1.8 \text{ K} \parallel [r_{\pi} + \beta \times 180]$$

$$= 600 + 1.8 \text{ K} \parallel [2.27 \text{ K} + 18 \text{ K}]$$

$$= 600 + 1.8 \text{ K} \parallel 20.27 \text{ K}$$

$$= 600 + 1.6532 \text{ K}$$

$$= 0.6 \text{ K} + 1.6532 \text{ K} = 2.2532 \text{ K}\Omega$$


output resistance

$$R_o = 3.6 \text{ K}\Omega \parallel 10 \text{ K}\Omega$$

$$= 2.647 \text{ K}\Omega$$



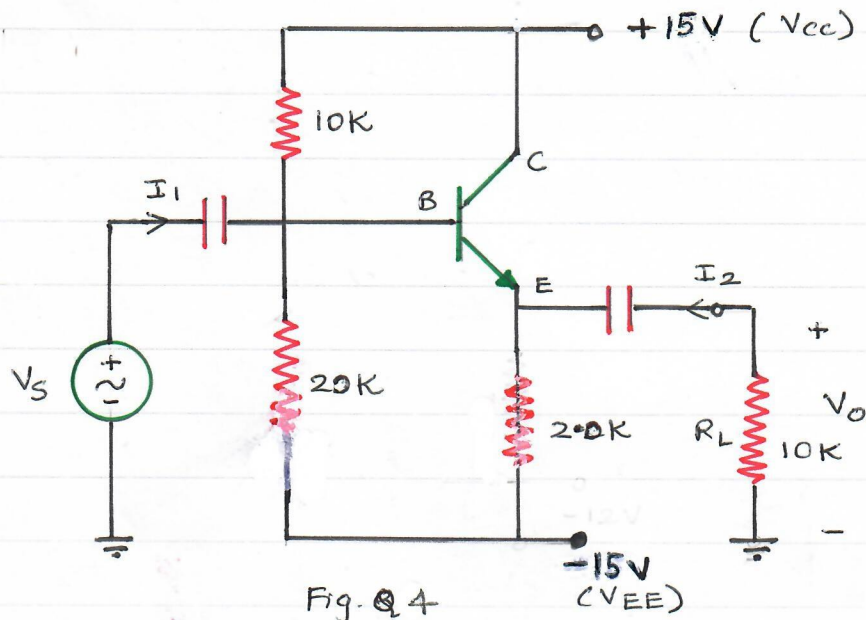(Q4) For the CC amplifier shown in Fig. Q4 shown below draw the small signal equivalent of the circuit and compute the voltage gain  $= A_V = \frac{V_o}{V_s}$  of the circuit



Assume that capacitors act as short circuit in the frequency range of interest. Take  $\beta = 100$ ,  $V_{BE} = 0.7V$

Sol.

Calculating the Q-point values

$$V_B = \frac{15 \times 20}{20 + 10} - \frac{15 \times 10}{20 + 10} = 5V$$

$$V_E = V_B - V_{BE} = 5 - 0.7 = 4.3V$$


$$I_E = \frac{V_E}{2K} = \frac{4.3}{2K} = 2.15mA$$

$$I_C = \frac{\beta}{\beta + 1} I_E = \frac{100}{101} I_E \approx I_E = 2.15mA$$

$$V_{CE} = V_C - V_E = 15 - 4.3 = 11.7V$$

$$r_e = \frac{25}{I_C (\text{in mA})} = \frac{25}{2.15} = 11.6\Omega$$

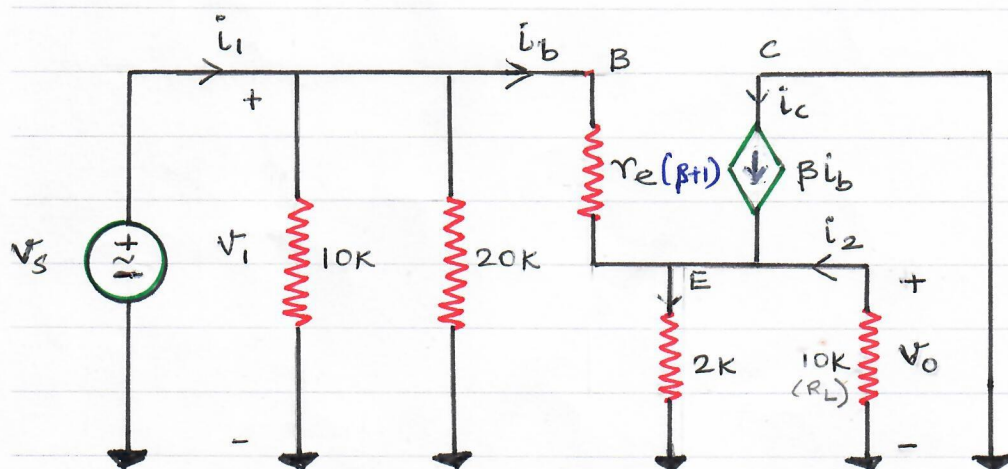Small signal equivalent of the circuit is as given below.



i)  $A_v = \frac{v_o}{v_s}$

$$v_o = 10K \times -i_2 = 2K \times i_e$$

$$= 2K \times (\beta+1) i_b$$

$$v_o = -i_2 \times 10K$$

$$A_v = \frac{v_o}{v_s} =$$

ii)  $A_v =$

$$v_1 = v_s = (\beta+1)r_e i_b + (\beta+1) \times 2K \times i_b$$

$$= (\beta+1) \times (r_e + 2K) i_b$$

$$A_v = \frac{v_o}{v_s} = \frac{2K \times (\beta+1) i_b}{(\beta+1) (r_e + 2K) i_b} \approx 1$$

$\because r_e + 2K \approx 2K$