


# **Basic Electronic Circuits**

## **(IEC-103)**

### **Lecture-07**

# Feedback

# Basic Block Diagram

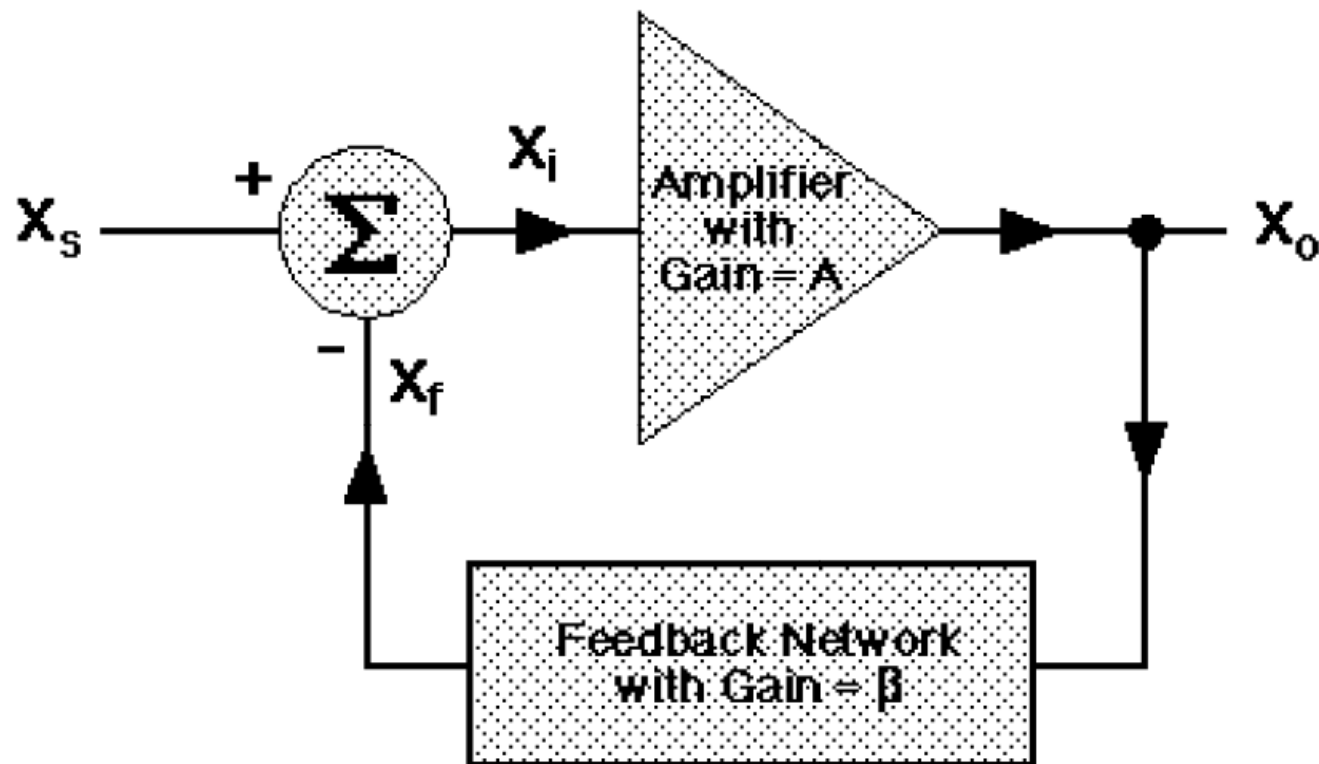

# Closed Loop Gain

$$X_i = X_s - X_f = X_s - \beta X_o$$

# Closed Loop Gain

$$X_i = X_s - X_f = X_s - \beta X_o$$

**But**  $X_o = AX_i$

# Closed Loop Gain

$$X_i = X_s - X_f = X_s - \beta X_o$$

But  $X_o = AX_i$

$$\therefore \frac{X_o}{A} = X_s - \beta X_o$$



# Closed Loop Gain

$$X_i = X_s - X_f = X_s - \beta X_o$$

But  $X_o = AX_i$

$$\therefore \frac{X_o}{A} = X_s - \beta X_o$$

**Rearranging**

# Closed Loop Gain

$$X_i = X_s - X_f = X_s - \beta X_o$$

But  $X_o = AX_i$

$$\therefore \frac{X_o}{A} = X_s - \beta X_o$$

Rearranging

$$\left( \frac{1}{A} + \beta \right) X_o = X_s$$



# Closed Loop Gain

Closed loop gain is  $A_f = \frac{X_o}{X_s}$

# Closed Loop Gain

Closed loop gain is  $A_f = \frac{x_o}{x_s}$

$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} \text{ (for very large } A\text{)}$$

# Closed Loop Bandwidth

Open loop gain

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

# Closed Loop Bandwidth

Open loop gain

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

If we use amplifier with negative feedback

# Closed Loop Bandwidth

Open loop gain

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_H}}$$

If we use amplifier with negative feedback

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)}$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}}$$



# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

**where**

$$\omega_{Hf} = \omega_H(1 + \beta A_0)$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$

where

$$\omega_{Hf} = \omega_H(1 + \beta A_0)$$

$$A_{of} = \frac{A_0}{(1 + \beta A_0)}$$

# Closed Loop Bandwidth

$$A_f(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_H(1 + \beta A_0)}} = \frac{A_{of}}{1 + \frac{s}{\omega_{Hf}}}$$


where

$$\omega_{Hf} = \omega_H(1 + \beta A_0)$$


$$A_{of} = \frac{A_0}{(1 + \beta A_0)}$$

**The cut-off frequency is increased by a factor  $(1 + A_0\beta)$**

# Closed Loop Bandwidth

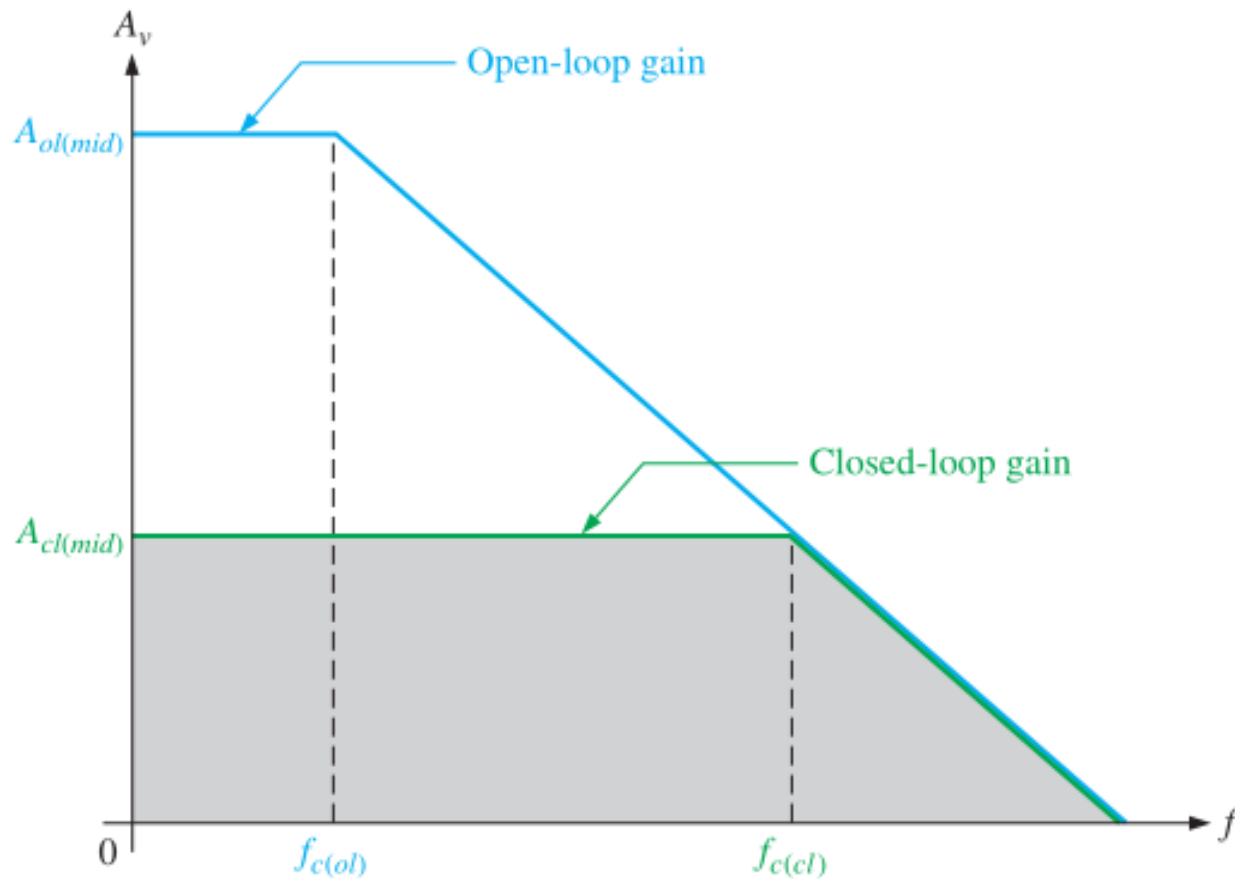


# Closed Loop Bandwidth

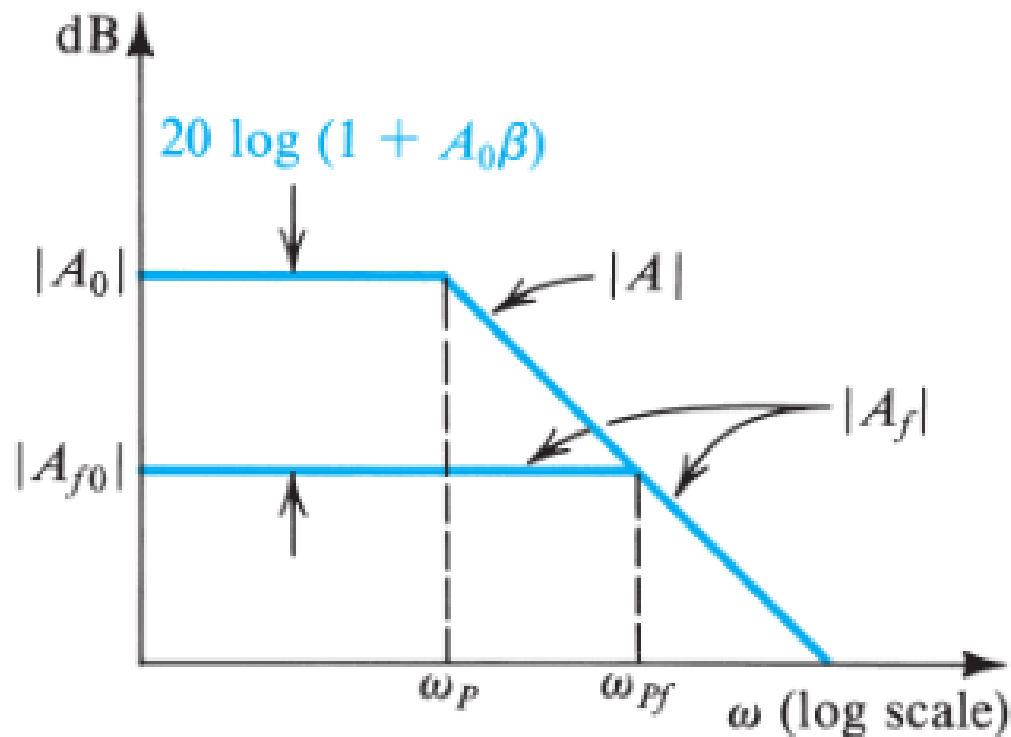



# Closed Loop Bandwidth

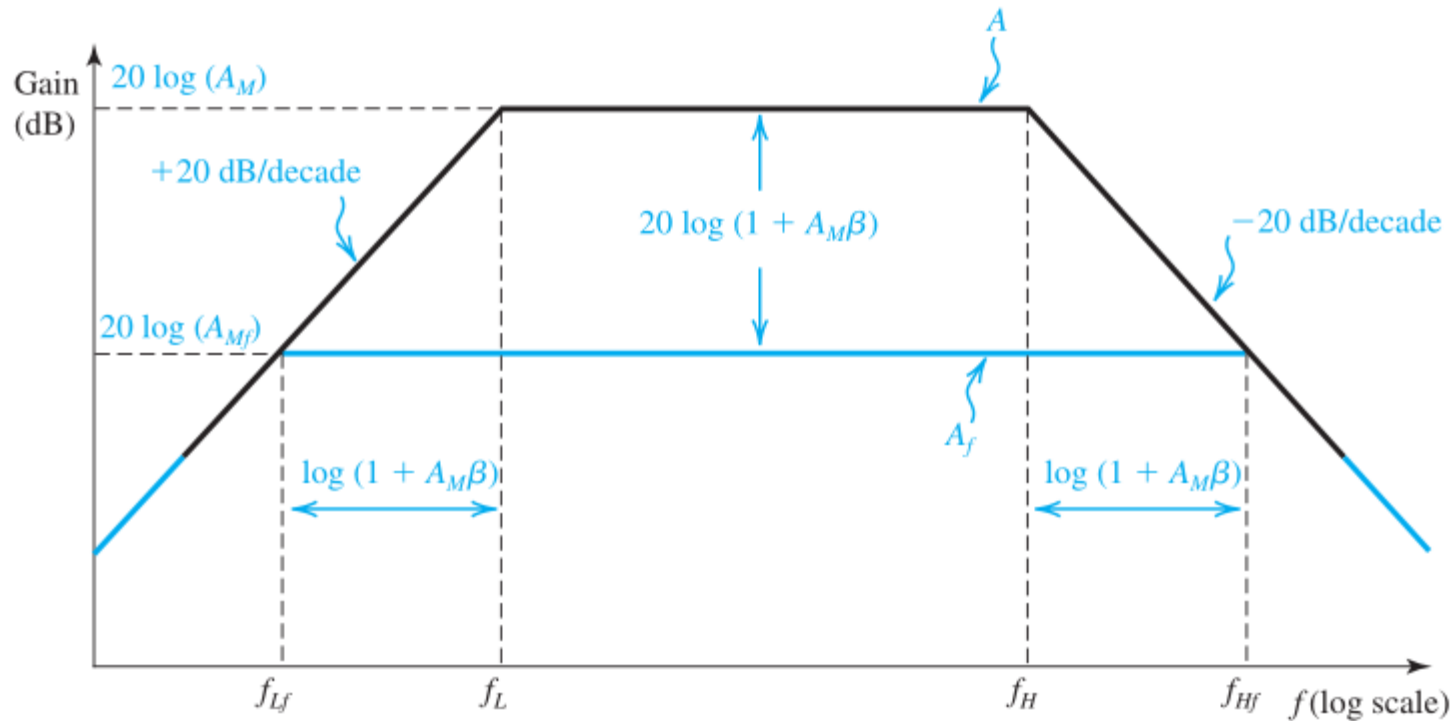

$$f_{Lf} = \frac{f_L}{1 + A_M \beta}$$

$$A_{Mf} = \frac{A_M}{1 + A_M \beta}$$

$$f_{Hf} = f_H (1 + A_M \beta)$$

# Effect of Negative Feedback on Operational Amplifiers

	VOLTAGE GAIN	INPUT $Z$	OUTPUT $Z$	BANDWIDTH
Without negative feedback	$A_{ol}$ is too high for linear amplifier applications	Relatively high	Relatively low	Relatively narrow (because the gain is so high)
With negative feedback	$A_{cl}$ is set to desired value by the feedback circuit	Can be increased or reduced to a desired value depending on type of circuit	Can be reduced to a desired value	Significantly wider

# **Types of Amplifiers**

# **Types of Amplifiers**

**Amplifiers can be classified in to 4 types depending on input and output.**

# Types of Amplifiers

Amplifiers can be classified in to 4 types depending on input and output.

□ **Voltage Amplifier (Voltage-Voltage)**



# Types of Amplifiers

Amplifiers can be classified in to 4 types depending on input and output.

□ Voltage Amplifier (Voltage-Voltage)

□ Transconductance Amplifier (Voltage-Current)



# Types of Amplifiers

Amplifiers can be classified in to 4 types depending on input and output.


- ❑ Voltage Amplifier (Voltage-Voltage)
- ❑ Transconductance Amplifier (Voltage-Current)
- ❑ Transresistance Amplifier (Current-Voltage)

# Types of Amplifiers


Amplifiers can be classified in to 4 types depending on input and output.

- ❑ Voltage Amplifier (Voltage-Voltage)
- ❑ Transconductance Amplifier (Voltage-Current)
- ❑ Transresistance Amplifier (Current-Voltage)
- ❑ Current Amplifier (Current-Current)

# Ideal Voltage Amplifier

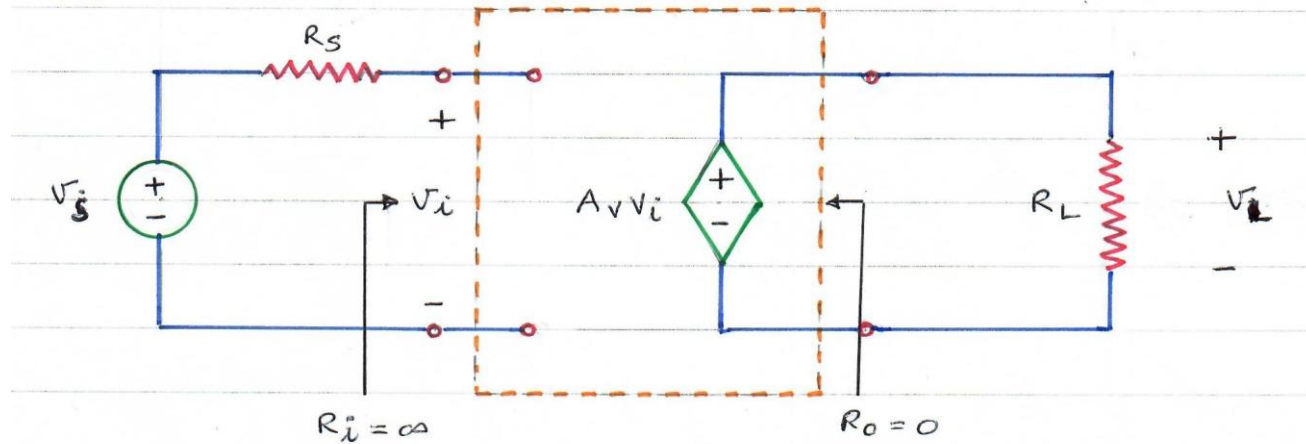

# Ideal Voltage Amplifier

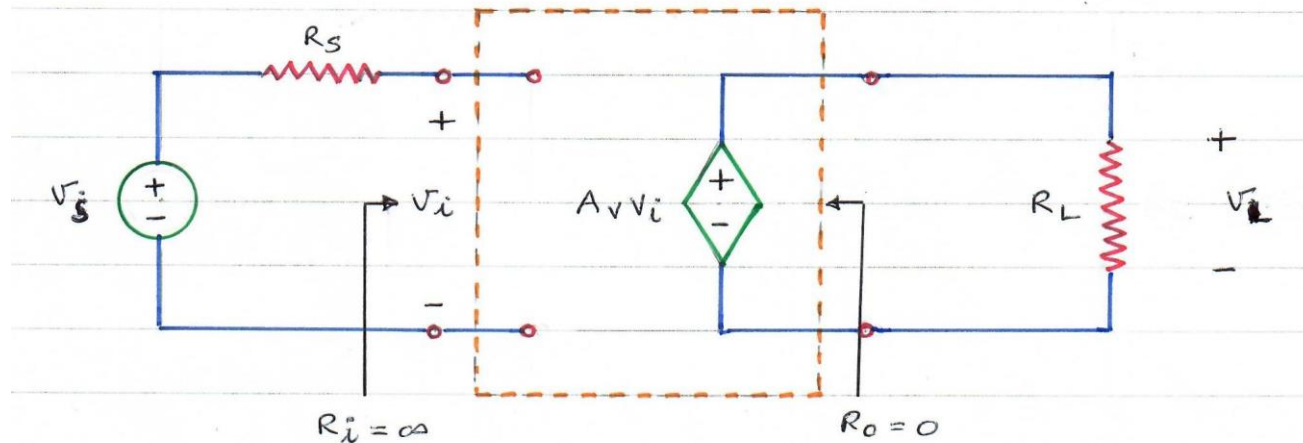

$$\frac{V_L}{V_s} = A_v$$



# Practical Voltage Amplifier


- ❑ Any signal source has finite source resistance  $R_s$ .
- ❑ The amplifier is often asked to drive current in to a load of finite impedance  $R_L$  (Ex:  $8\ \Omega$  speaker).
- ❑ The controlled source is a voltage controlled voltage source (VCVS).
- ❑  $A_v$  = Open Circuit Voltage Gain **can be found by applying a voltage source with  $R_s = 0$  and measuring the open circuit output (no load or  $R_L = \infty$ ).**
- ❑ **Why are input and output impedance important?**

# Practical Voltage Amplifier


- ❑ Only voltage  $V_{in}$  is amplified to  $A_v V_{in}$ .
- ❑ Since  $R_s$  and  $R_{in}$  form a voltage divider that determines  $V_{in}$ ,  $R_{in}$  should be as large as possible for maximum voltage.
- ❑ Since  $R_L$  and  $R_{out}$  form a voltage divider that determines  $V_{out}$ ,  $R_{out}$  should be as small as possible for maximum output voltage.



# Practical Voltage Amplifier

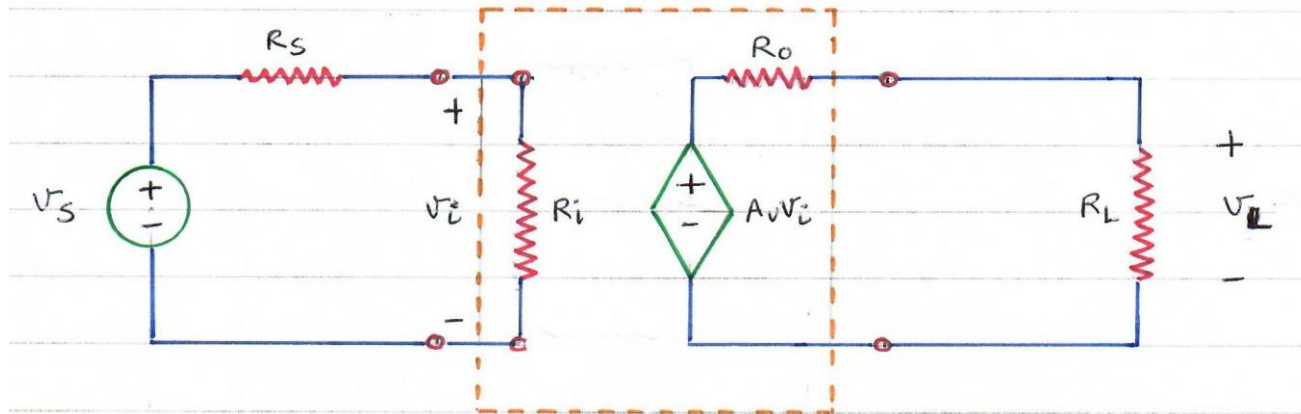


# Practical Voltage Amplifier

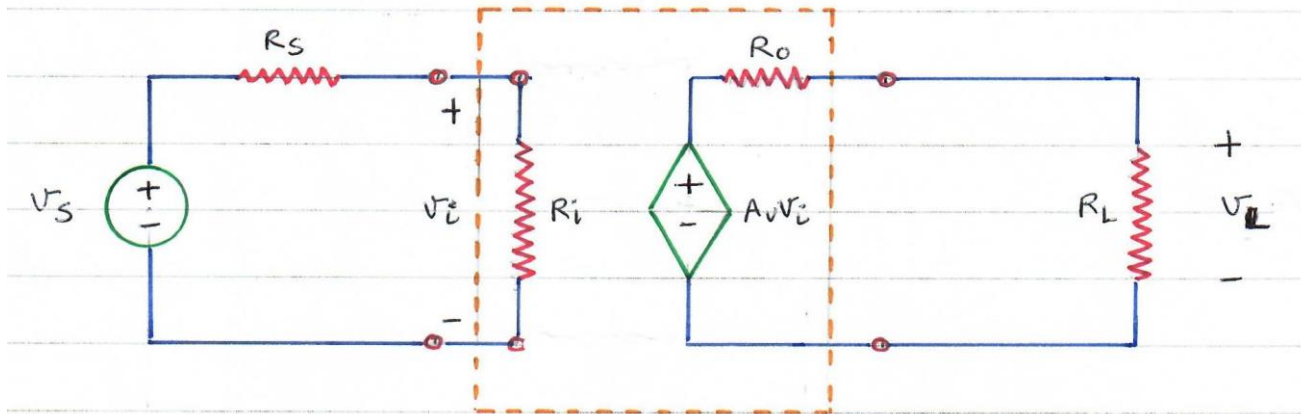

$$\frac{V_L}{V_s} = \frac{A_v R_i R_L}{(R_s + R_i)(R_o + R_L)}$$

# Practical Voltage Amplifier

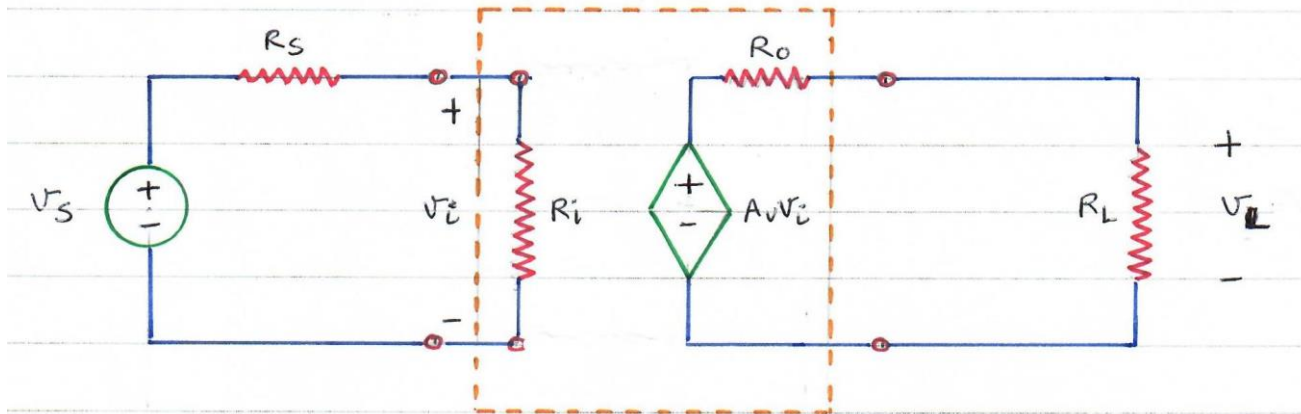


$$\frac{v_L}{v_s} = \frac{A_v R_i R_L}{(R_s + R_i)(R_o + R_L)}$$

$$\frac{v_L}{v_s} = A_v$$


if  $R_i = \infty, R_o = 0$

# Ideal Transconductance Amplifier

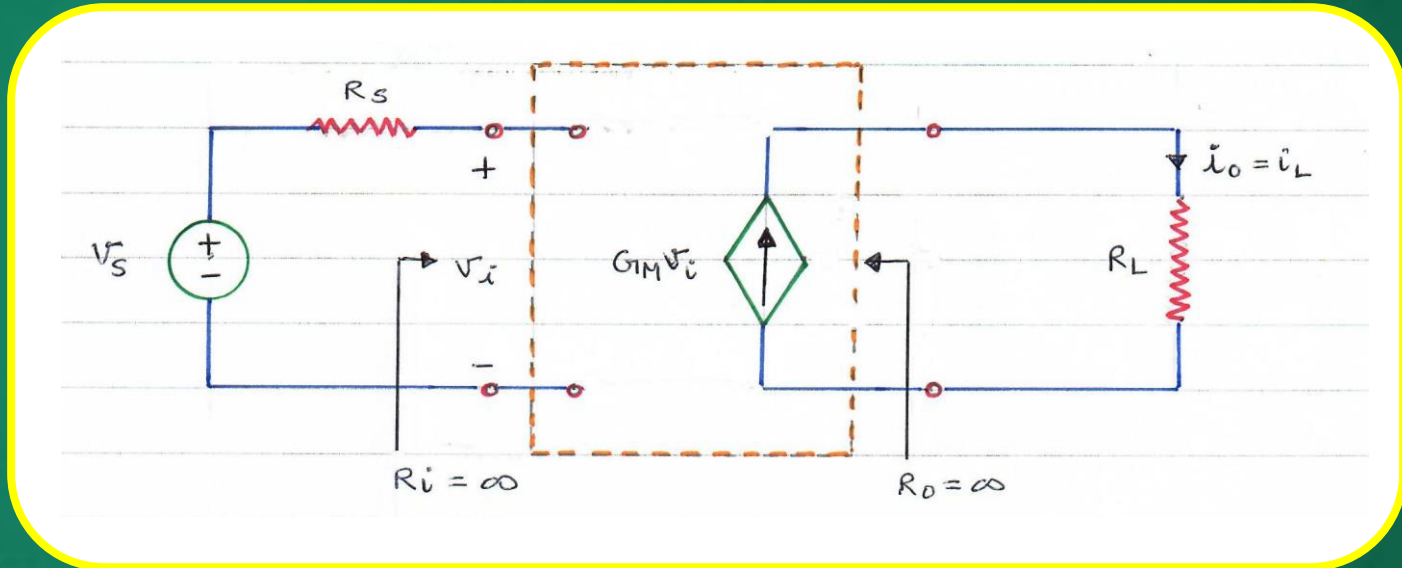




# Ideal Transconductance Amplifier

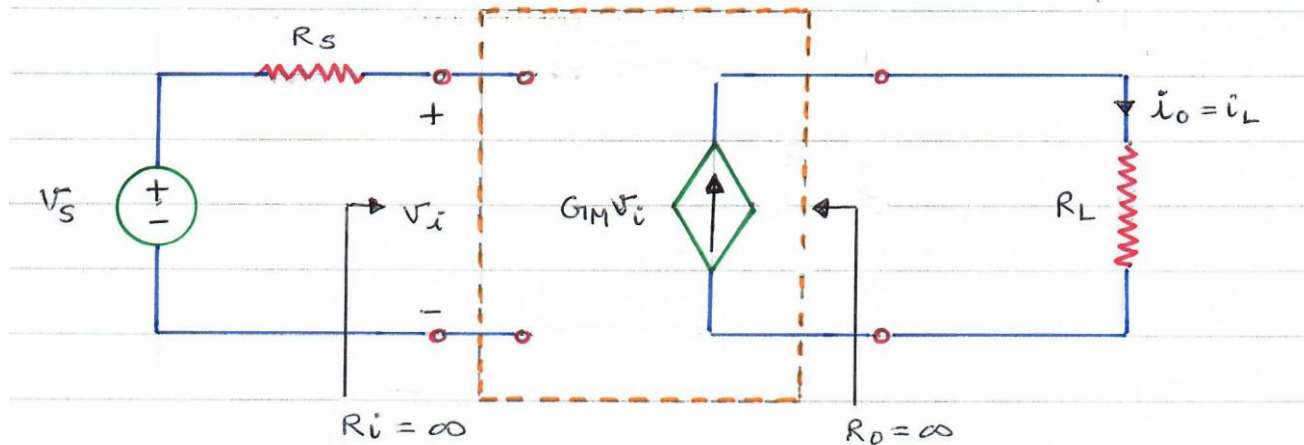


$$\frac{i_L}{V_s} = G_m$$

# Practical Transconductance Amplifier

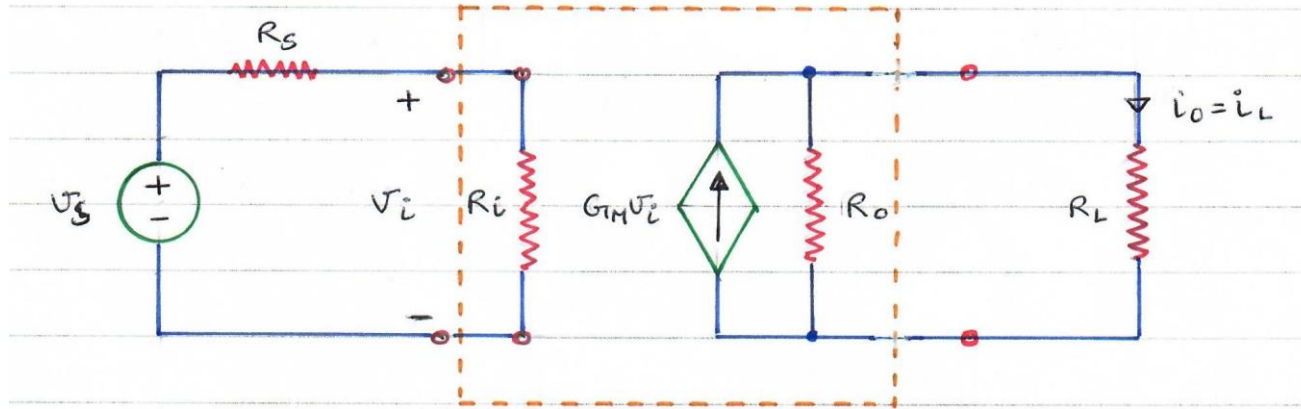




# Practical Transconductance Amplifier

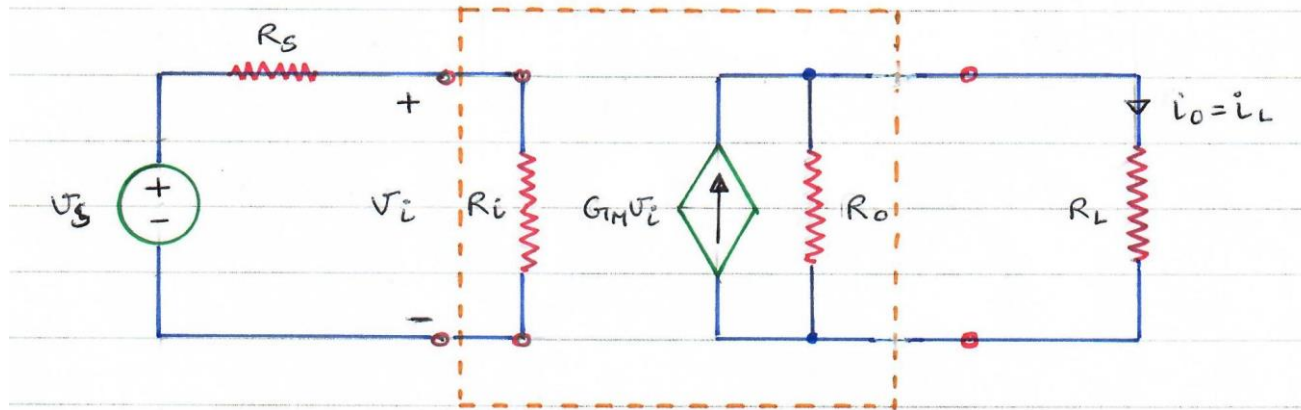

$$\frac{i_L}{v_s} = \frac{G_m R_i R_o}{(R_s + R_i)(R_o + R_L)}$$

# Practical Transconductance Amplifier

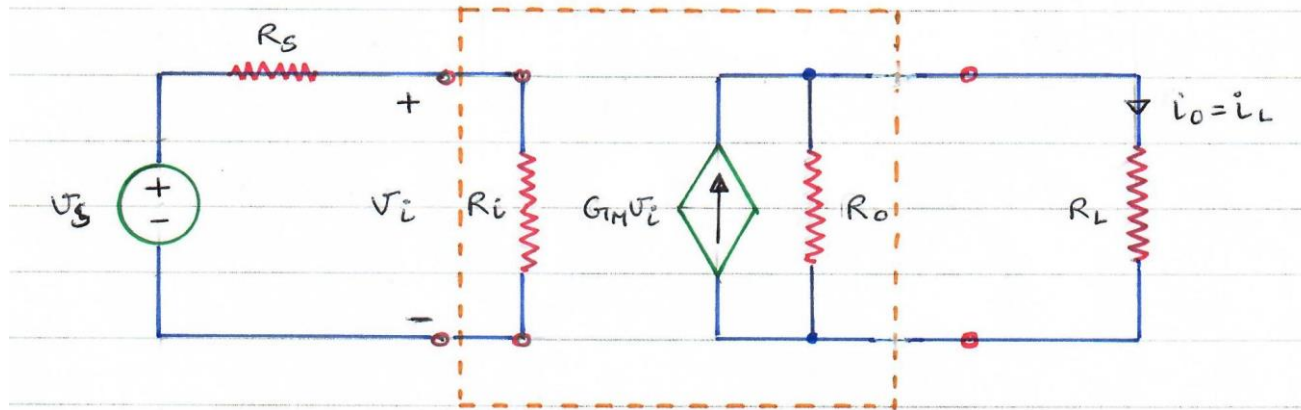


$$\frac{i_L}{v_s} = \frac{G_m R_i R_o}{(R_s + R_i)(R_o + R_L)}$$


$$\frac{i_L}{v_s} = G_m$$

if  $R_i = \infty, R_o = \infty$

# Ideal Transresistance Amplifier

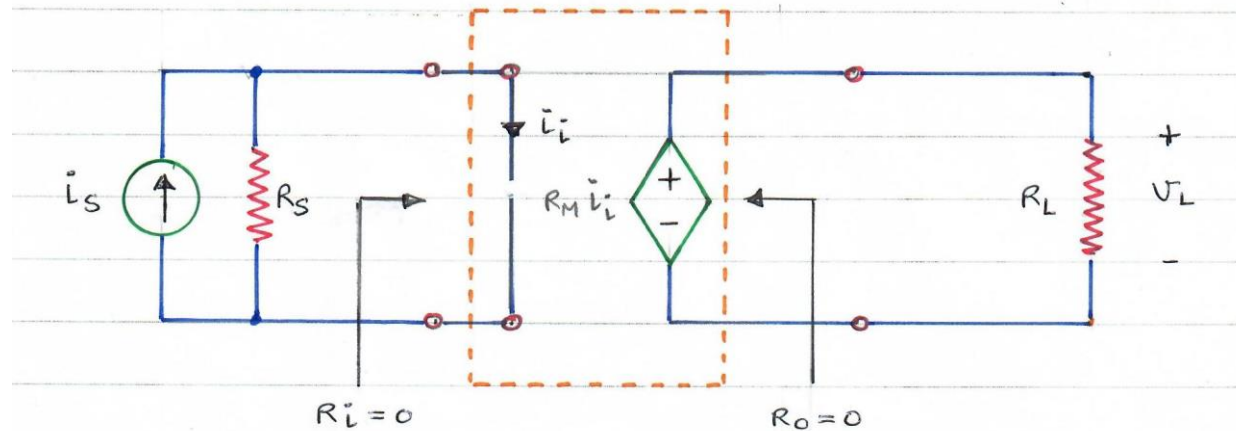


# Ideal Transresistance Amplifier

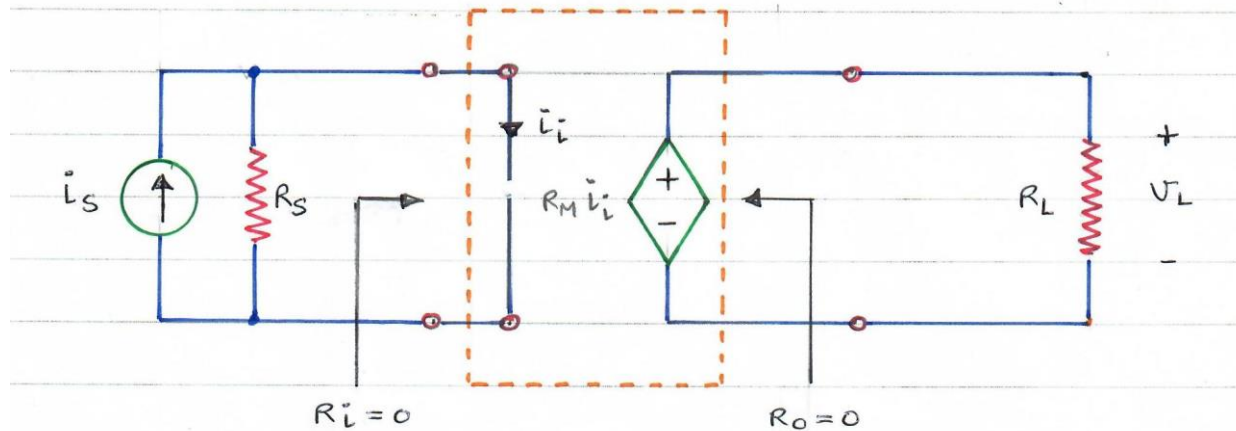


$$\frac{v_L}{\dot{i}_s} = R_m$$



# Practical Transresistance Amplifier

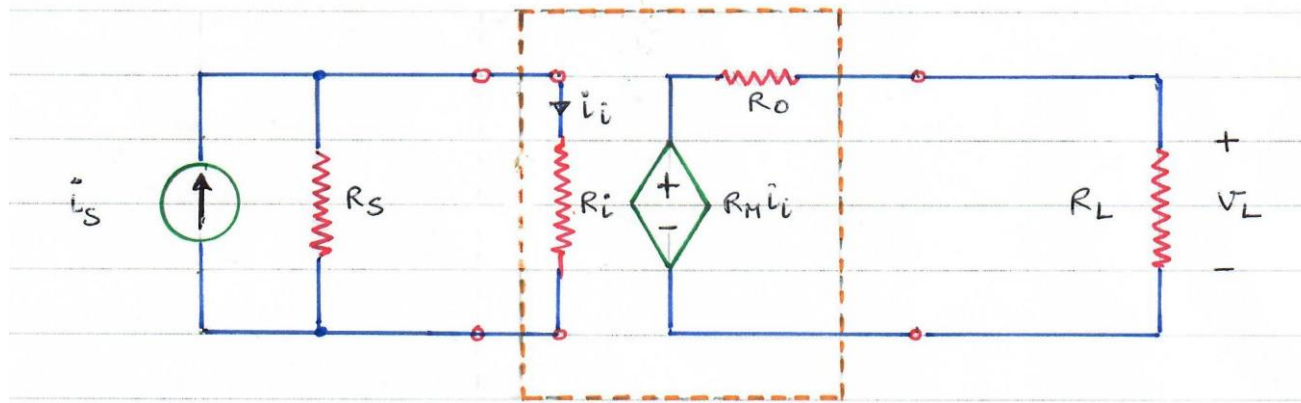


# Practical Transresistance Amplifier

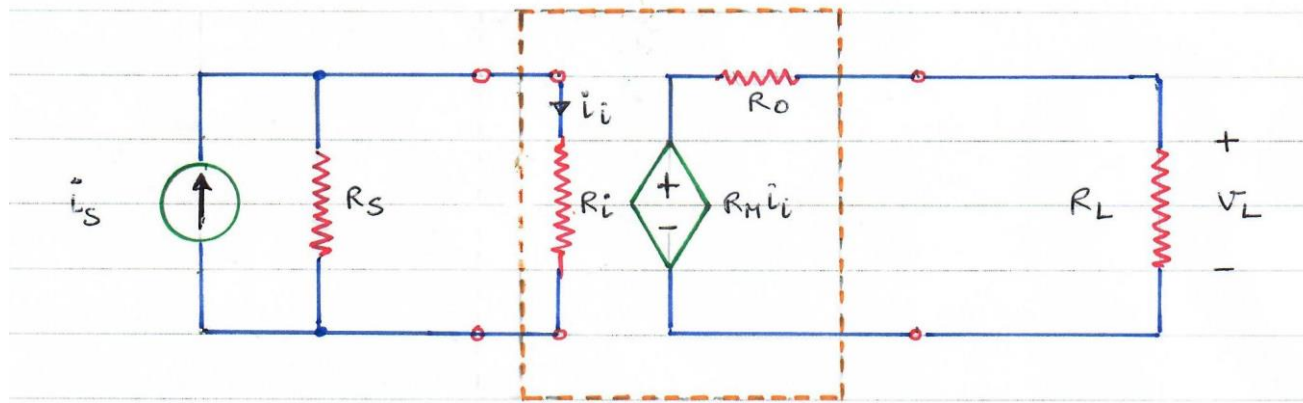

$$\frac{v_L}{i_s} = \frac{R_m R_s R_L}{(R_s + R_i)(R_o + R_L)}$$



# Practical Transresistance Amplifier

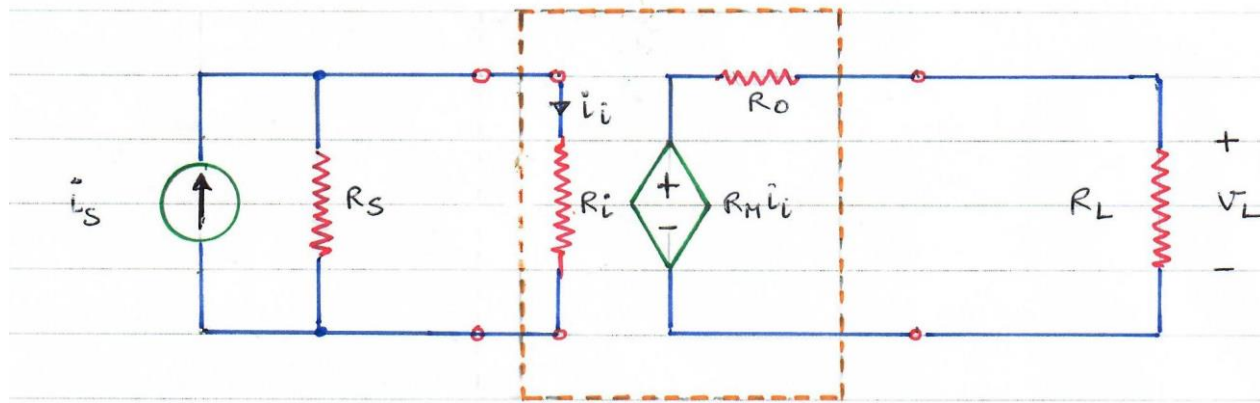


$$\frac{v_L}{i_s} = \frac{R_m R_s R_L}{(R_s + R_i)(R_o + R_L)}$$


$$\frac{v_L}{i_s} = R_m$$

$$\text{if } R_i = 0, R_o = 0$$

# Ideal Current Amplifier

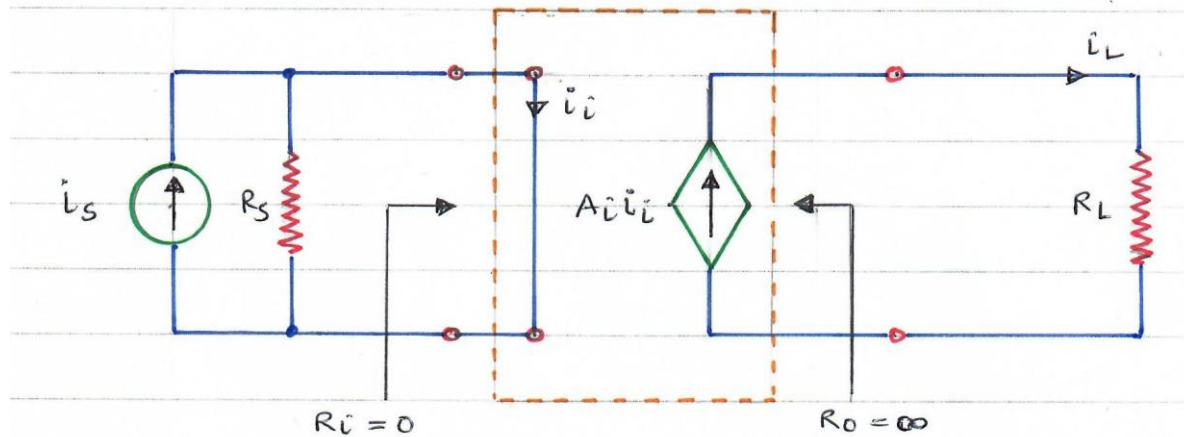


# Ideal Current Amplifier

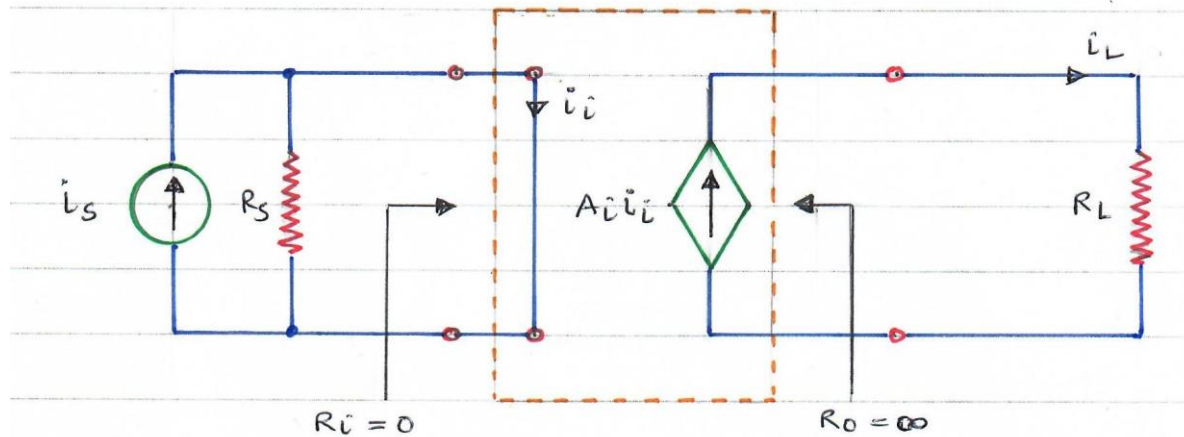


$$\frac{i_L}{i_s} = A_i$$

# Practical Current Amplifier

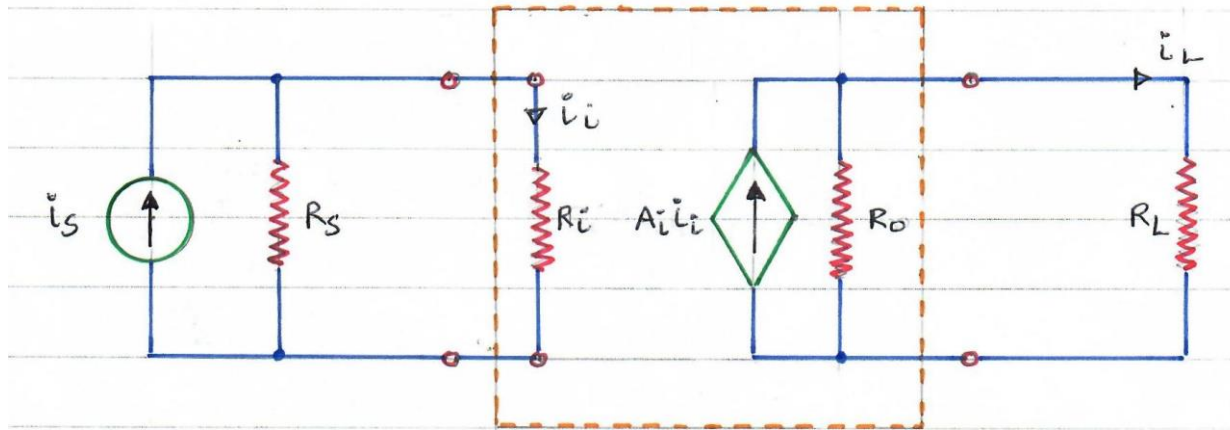




# Practical Current Amplifier

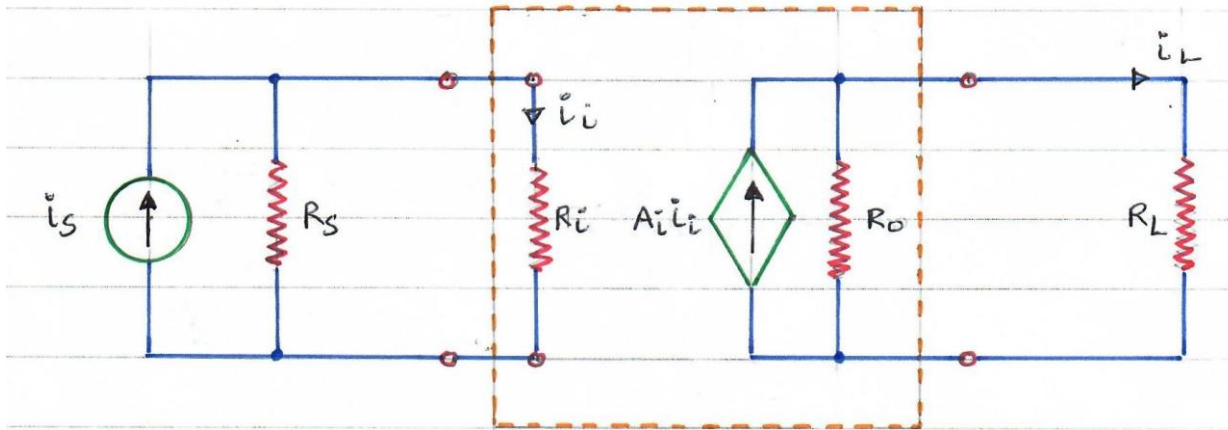

$$\frac{i_L}{i_s} = \frac{A_i R_s R_o}{(R_s + R_i)(R_o + R_L)}$$

# Practical Current Amplifier

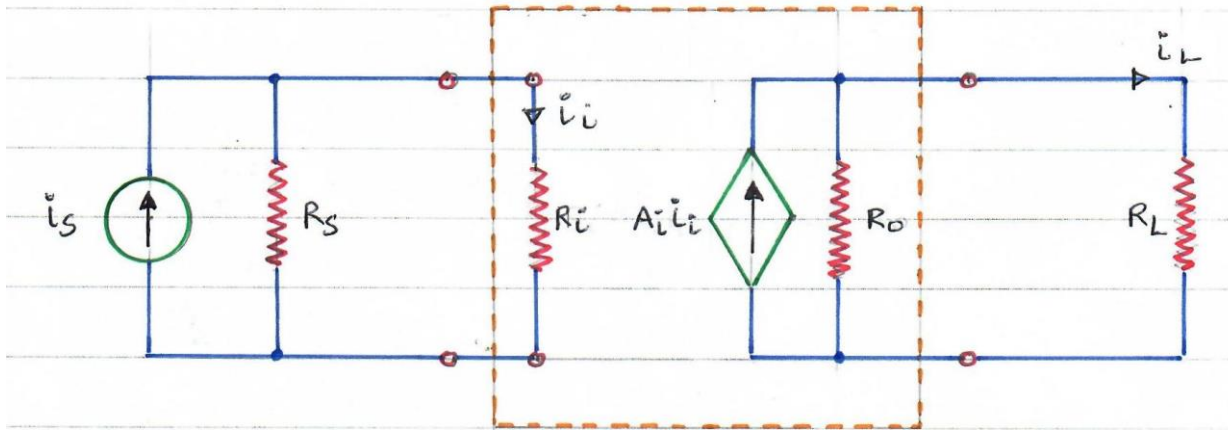

$$\frac{i_L}{i_s} = \frac{A_i R_s R_o}{(R_s + R_i)(R_o + R_L)}$$

$$\frac{i_L}{i_s} = A_i$$

$$\text{if } R_i = 0, R_o = \infty$$



# Practical Current Amplifier


- ❑ Only current  $i_{in}$  is amplified to  $A_i i_{in}$ .
- ❑ Since  $R_s$  and  $R_{in}$  form a current divider that determines  $i_{in}$ ,  $R_{in}$  should be as small as possible for maximum current.
- ❑ Since  $R_L$  and  $R_{out}$  form a current divider that determines  $i_{out}$ ,  $R_{out}$  should be as large as possible for maximum output current.

# Ideal Amplifiers


Type of Amplifier	Gain Expression	Ideal Input Impedance	Ideal Output Impedance
Voltage	$A_v = V_o/V_s$ Voltage Gain (dimensionless)	$Z_i = \infty$	$Z_o = 0$
Transconductance	$G_m = I_o/V_s$ Transconductance (Siemens)	$Z_i = \infty$	$Z_o = \infty$
Transresistance	$R_m = V_o/I_s$ Transresistance (Ohms)	$Z_i = 0$	$Z_o = 0$
Current	$A_i = I_o/I_s$ Current Gain (dimensionless)	$Z_i = 0$	$Z_o = \infty$

# **Feedback Topologies**

# Basic Block Diagram

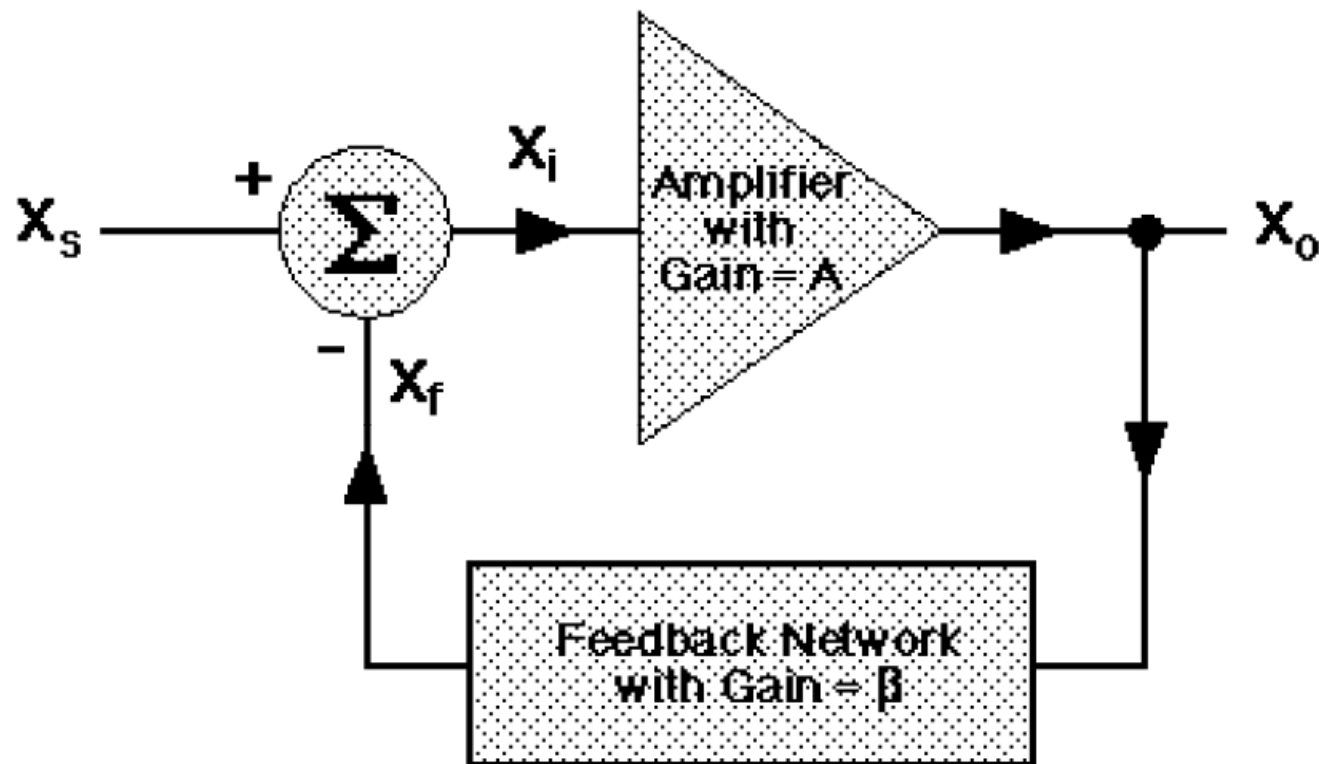


# Basic Block Diagram

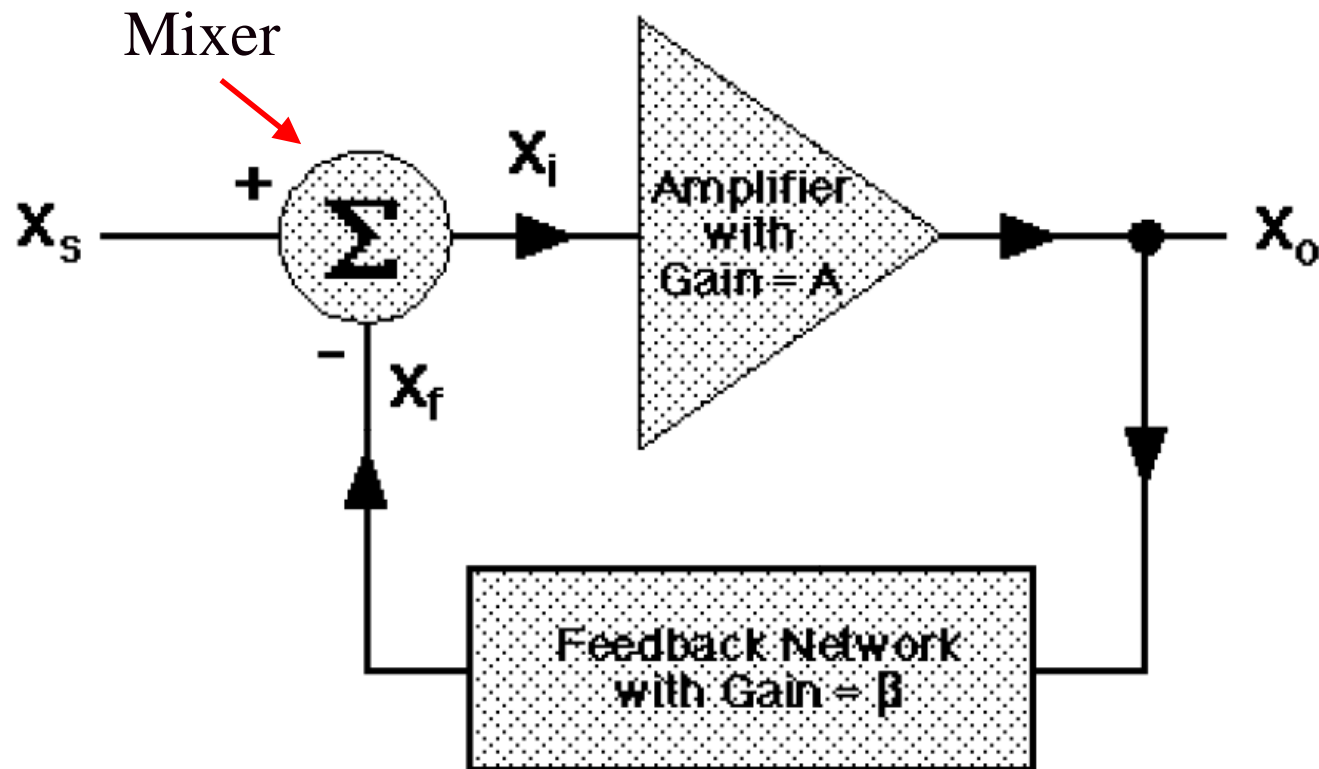




# Basic Block Diagram

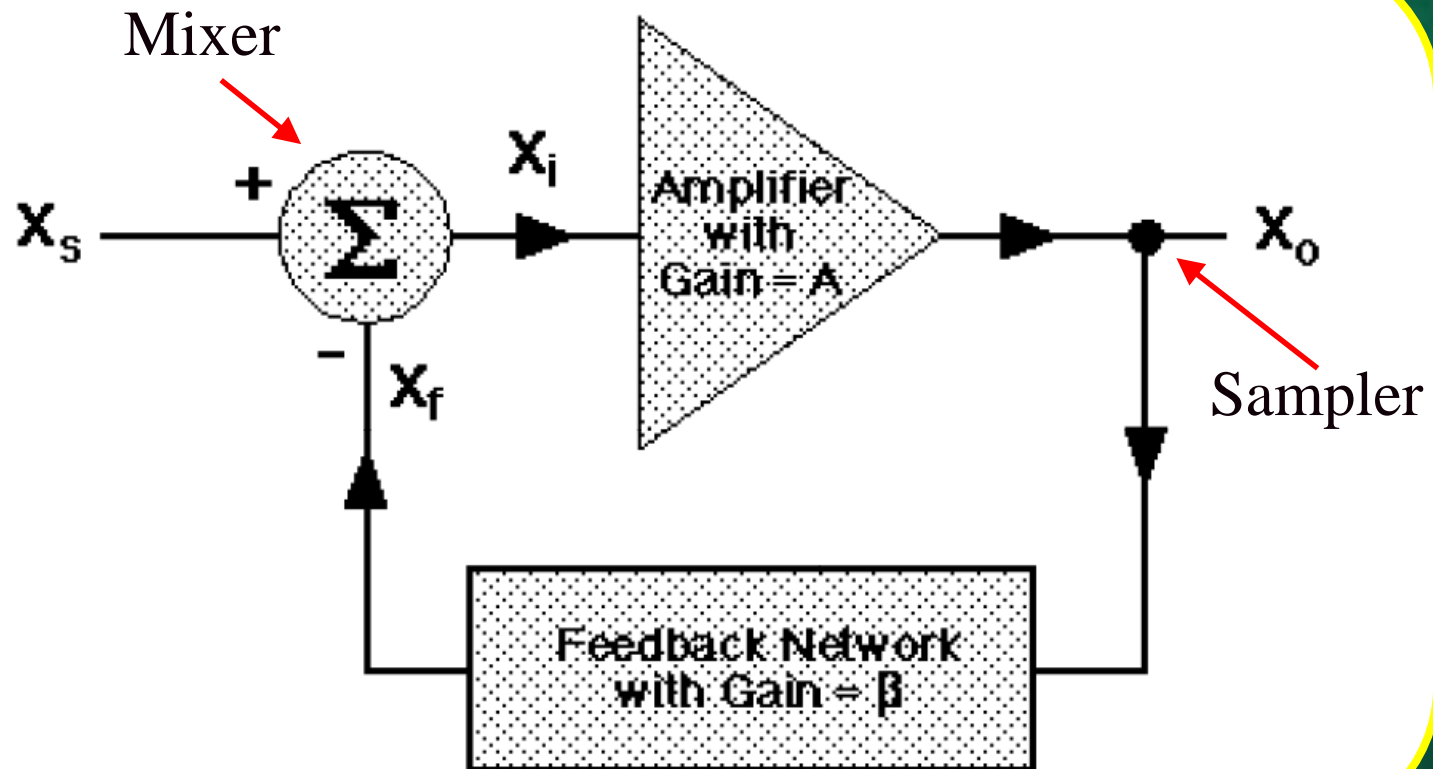


# Types of Mixers

# Series Mixer

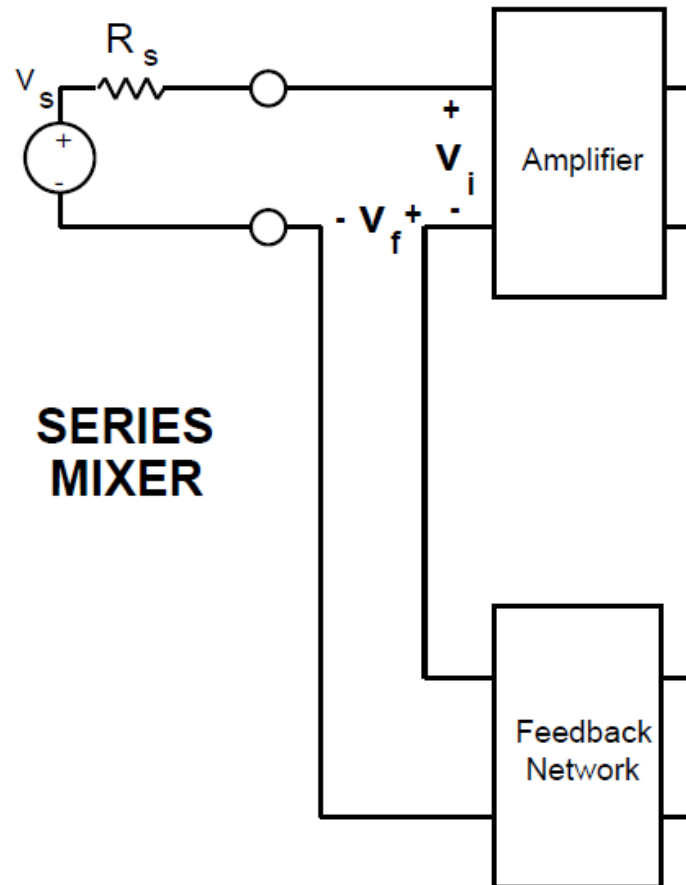


# Shunt Mixer

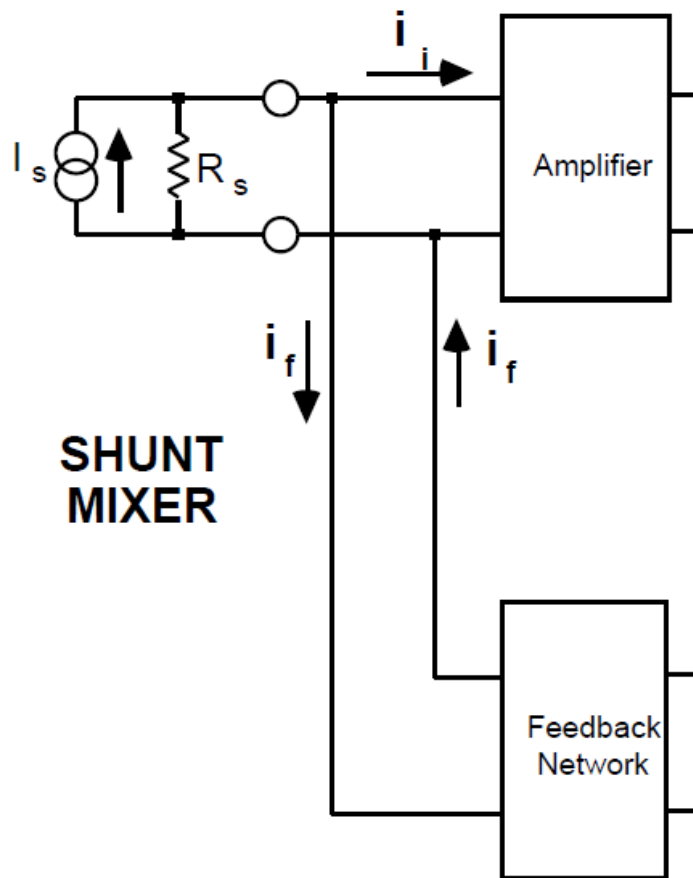


# **Types of Samplers**



# Shunt Sampler

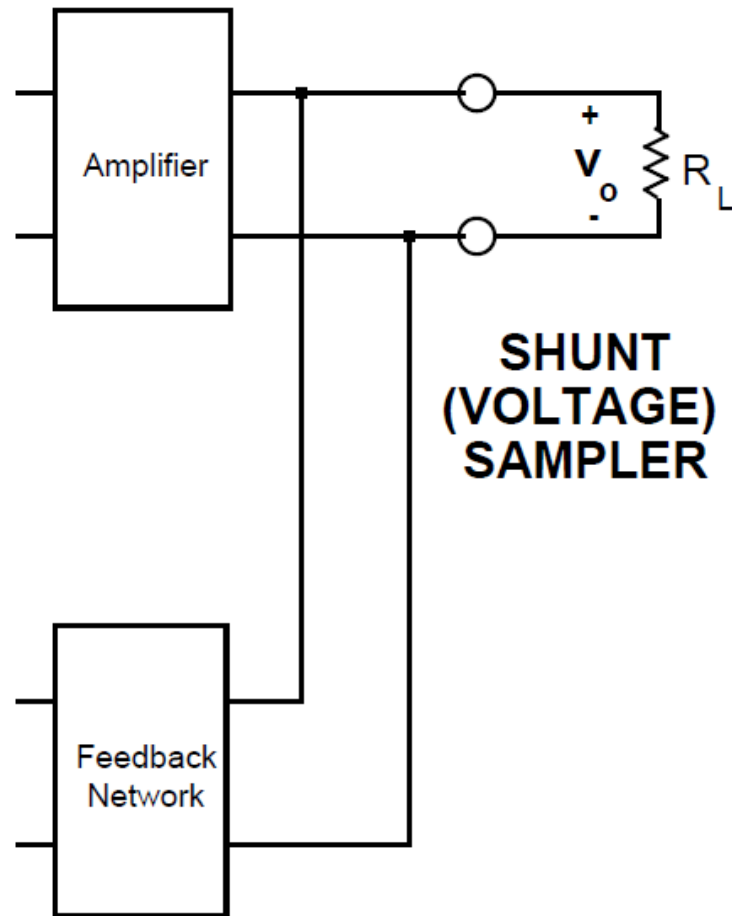


# Series Sampler

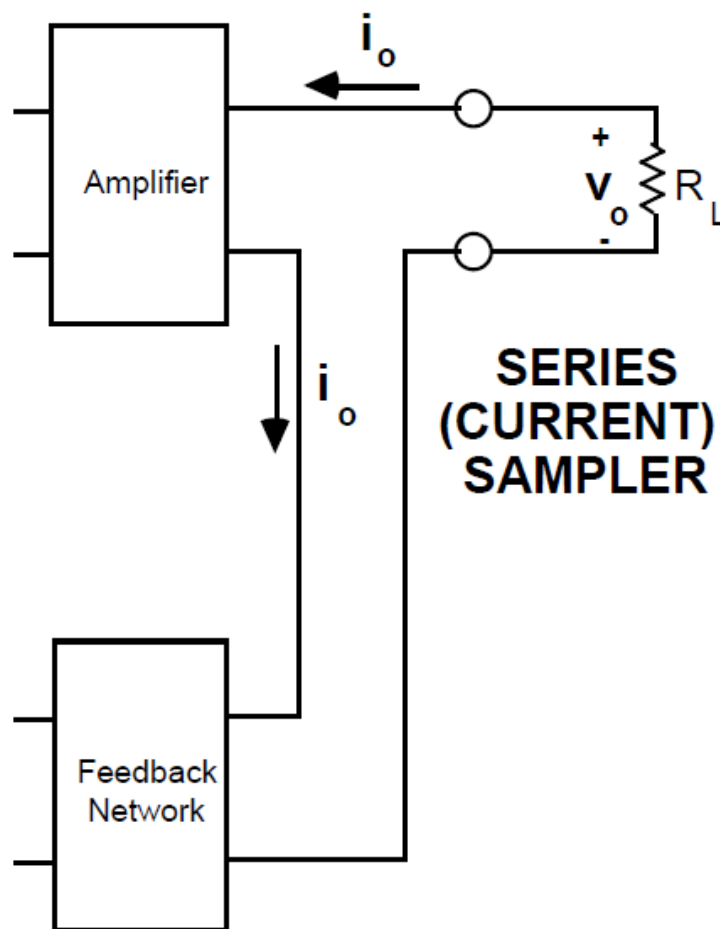


# Types of Amplifiers based on Feedback Topology

Series-Shunt	Series (voltage) mixing, Shunt (voltage) sampling	V-V	Voltage Amplifier
Shunt-Series	Shunt (current) mixing, Series (current) sampling	I-I	Current Amplifier
Series-Series	Series (voltage) mixing, Series (current) sampling	V-I	Transconductance Amplifier
Shunt-Shunt	Shunt (current) mixing, Shunt (voltage) sampling	I-V	Transresistance Amplifier

# Series-Shunt Amplifier

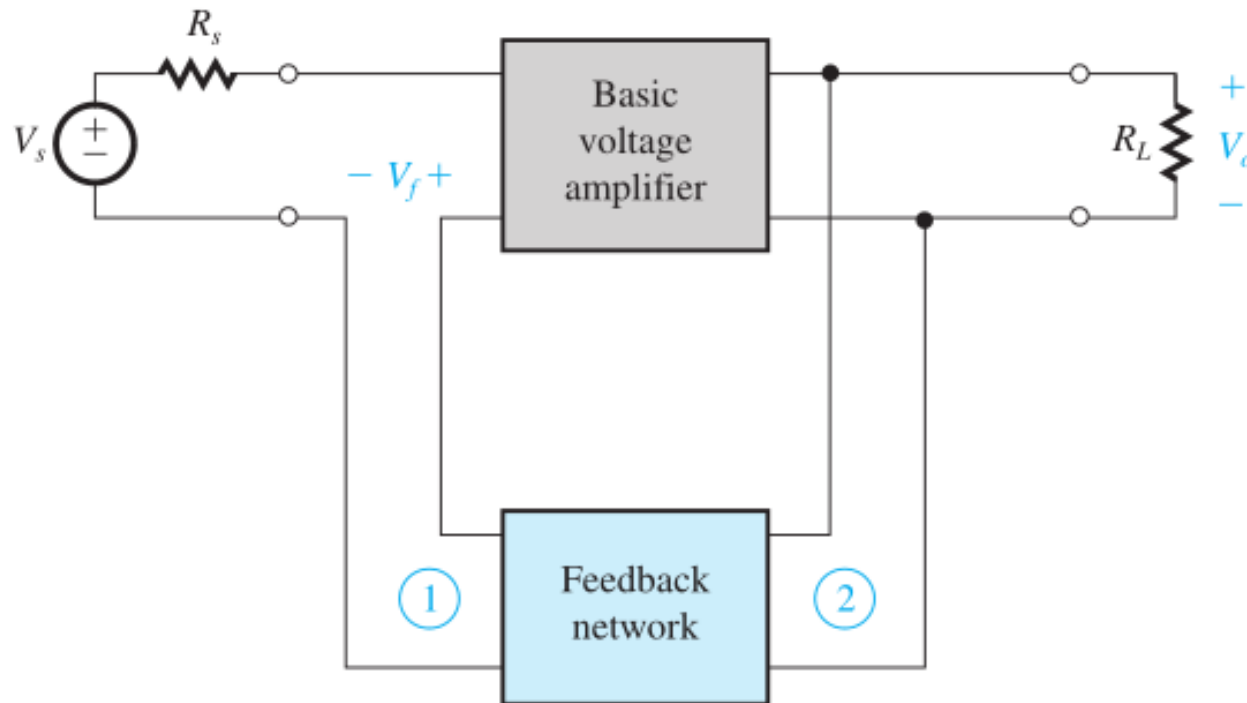


# Series-Shunt Amplifier

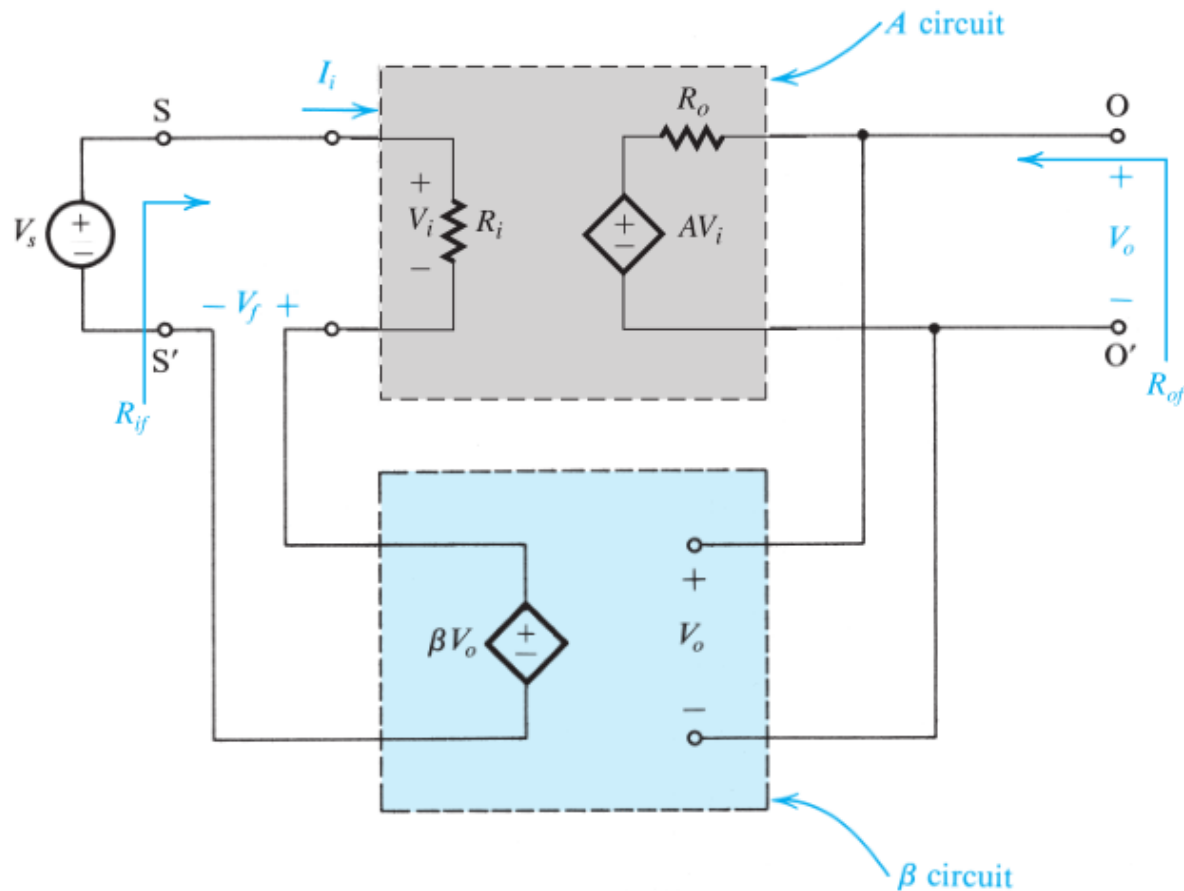



# Series-Shunt Amplifier

## Equivalent Circuit

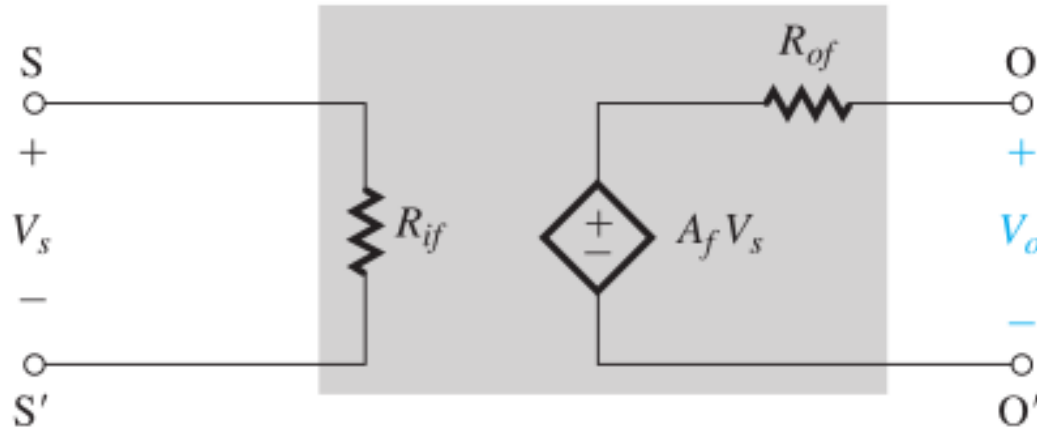

# Series-Shunt Feedback

Input Impedance ( $R_{if}$ )

# Series-Shunt Feedback

## Input Impedance ( $R_{if}$ )

$$R_{if} \equiv \frac{V_s}{I_i} = \frac{V_s}{\left(\frac{V_i}{R_i}\right)} = R_i \left(\frac{V_s}{V_i}\right) = R_i \left(\frac{V_i + V_f}{V_i}\right) = R_i \left(\frac{V_i + \beta A V_i}{V_i}\right)$$

# Series-Shunt Feedback

## Input Impedance ( $R_{if}$ )

$$R_{if} \equiv \frac{V_s}{I_i} = \frac{V_s}{\left(\frac{V_i}{R_i}\right)} = R_i \left(\frac{V_s}{V_i}\right) = R_i \left(\frac{V_i + V_f}{V_i}\right) = R_i \left(\frac{V_i + \beta A V_i}{V_i}\right)$$

$$\Rightarrow R_{if} = R_i (1 + A\beta)$$

# Series-Shunt Feedback

## Input Impedance ( $R_{if}$ )

$$R_{if} \equiv \frac{V_s}{I_i} = \frac{V_s}{\left(\frac{V_i}{R_i}\right)} = R_i \left( \frac{V_s}{V_i} \right) = R_i \left( \frac{V_i + V_f}{V_i} \right) = R_i \left( \frac{V_i + \beta A V_i}{V_i} \right)$$

$$\Rightarrow R_{if} = R_i (1 + A\beta)$$

$$Z_{if}(s) = Z_{if}(s) [1 + A(s)\beta(s)]$$



# Series-Shunt Feedback

## Input Impedance ( $R_{if}$ )

$$R_{if} \equiv \frac{V_s}{I_i} = \frac{V_s}{\left(\frac{V_i}{R_i}\right)} = R_i \left( \frac{V_s}{V_i} \right) = R_i \left( \frac{V_i + V_f}{V_i} \right) = R_i \left( \frac{V_i + \beta A V_i}{V_i} \right)$$

$$\Rightarrow R_{if} = R_i (1 + A\beta)$$

$$Z_{if}(s) = Z_{if}(s) [1 + A(s)\beta(s)]$$

**True for all series mixing cases.**

# Series-Shunt Feedback

Output Impedance ( $R_{of}$ )

# Series-Shunt Feedback

## Output Impedance ( $R_{of}$ )

$$R_{of} \equiv \frac{V_t}{I} \Rightarrow I = \frac{V_t - AV_i}{R_o}$$

# Series-Shunt Feedback

**Output Impedance ( $R_{of}$ )**

$$R_{of} \equiv \frac{V_t}{I} \Rightarrow I = \frac{V_t - AV_i}{R_o}$$

**Disable source input ( $V_s = 0$ )**

# Series-Shunt Feedback

## Output Impedance ( $R_{of}$ )

$$R_{of} \equiv \frac{V_t}{I} \Rightarrow I = \frac{V_t - AV_i}{R_o}$$

## Disable source input ( $V_s = 0$ )

$$V_i = -V_f = -\beta V_o = -\beta V_t$$



# Series-Shunt Feedback

## Output Impedance ( $R_{of}$ )

$$R_{of} \equiv \frac{V_t}{I} \Rightarrow I = \frac{V_t - AV_i}{R_o}$$

## Disable source input ( $V_s = 0$ )

$$V_i = -V_f = -\beta V_o = -\beta V_t$$

$$I = \frac{V_t - AV_i}{R_o} = \frac{V_t + A\beta V_t}{R_o} = \frac{V_t(1 + A\beta)}{R_o}$$

# Series-Shunt Feedback

$$I = \frac{V_t(1 + A\beta)}{R_o} \Rightarrow \frac{V_t}{I} = R_{of} = \frac{R_o}{(1 + A\beta)}$$

# Series-Shunt Feedback

$$I = \frac{V_t(1 + A\beta)}{R_o} \Rightarrow \frac{V_t}{I} = R_{of} = \frac{R_o}{(1 + A\beta)}$$

**Output Impedance ( $R_{of}$ )**

# Series-Shunt Feedback

$$I = \frac{V_t(1 + A\beta)}{R_o} \Rightarrow \frac{V_t}{I} = R_{of} = \frac{R_o}{(1 + A\beta)}$$

## Output Impedance ( $R_{of}$ )

$$R_{of} = \frac{R_o}{1 + A\beta} \text{ or, more generally, } Z_{of}(s) = \frac{Z_o(s)}{1 + A(s)\beta(s)}$$

# Series-Shunt Feedback

$$I = \frac{V_t(1 + A\beta)}{R_o} \Rightarrow \frac{V_t}{I} = R_{of} = \frac{R_o}{(1 + A\beta)}$$

## Output Impedance ( $R_{of}$ )

$$R_{of} = \frac{R_o}{1 + A\beta} \text{ or, more generally, } Z_{of}(s) = \frac{Z_o(s)}{1 + A(s)\beta(s)}$$

**True for all shunt sampling cases.**




# Series-Shunt Feedback


Closed Loop Gain ( $A_f$ )

$$A_f = \frac{A}{1 + A\beta}$$


# Series-Shunt Amplifier

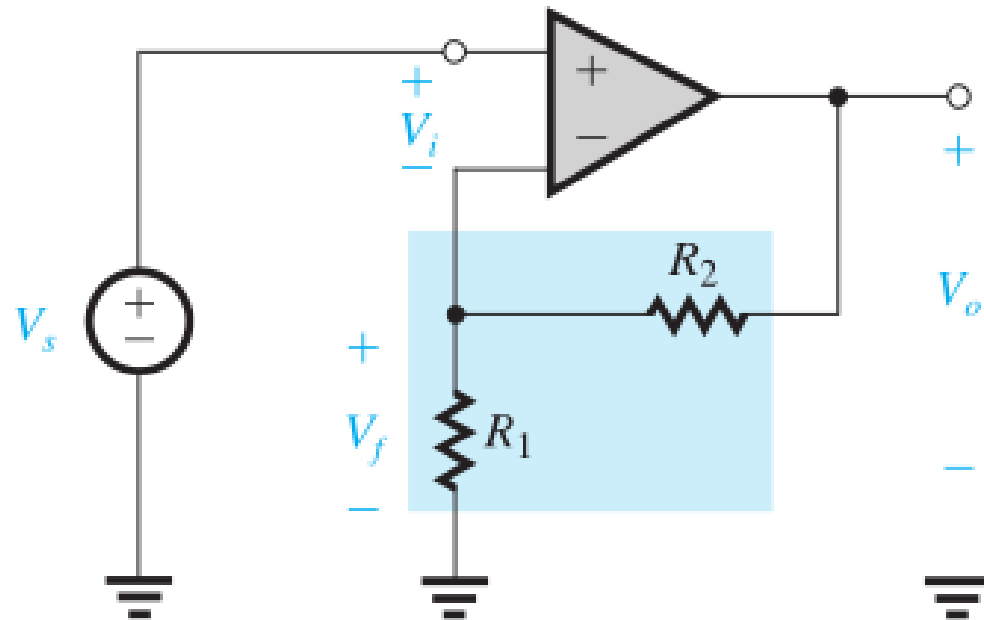


# Shunt-Shunt Amplifier

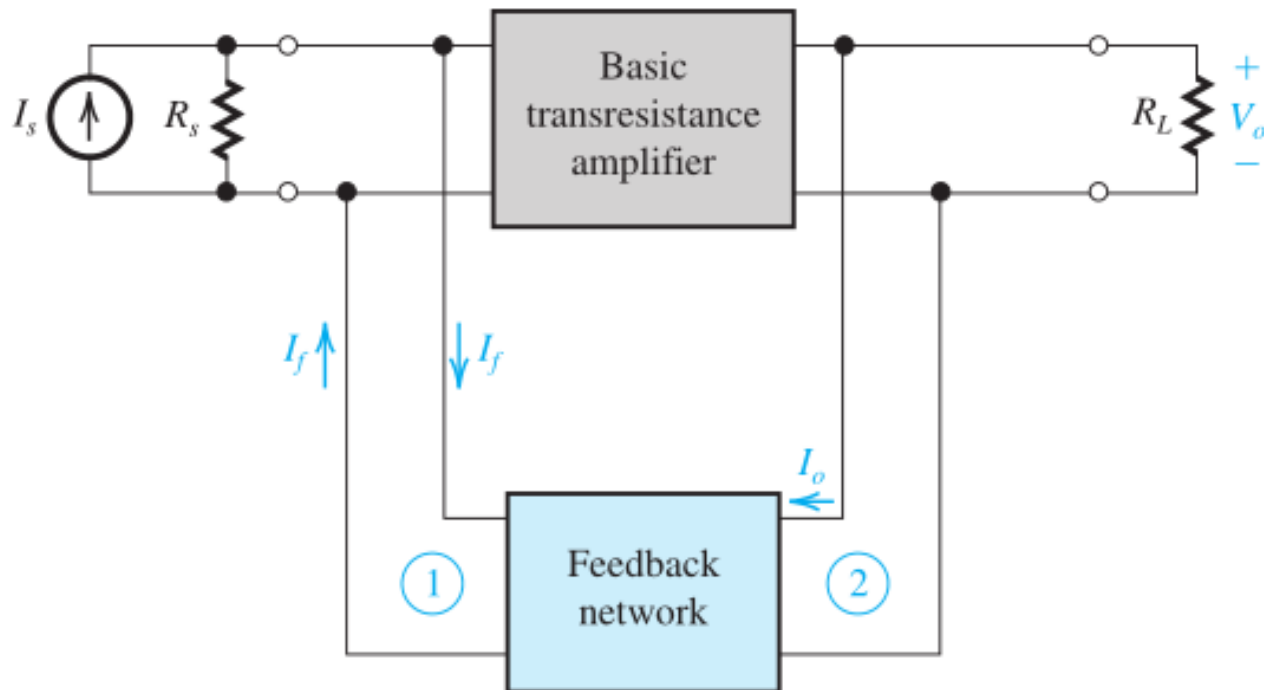

# Shunt-Shunt Amplifier

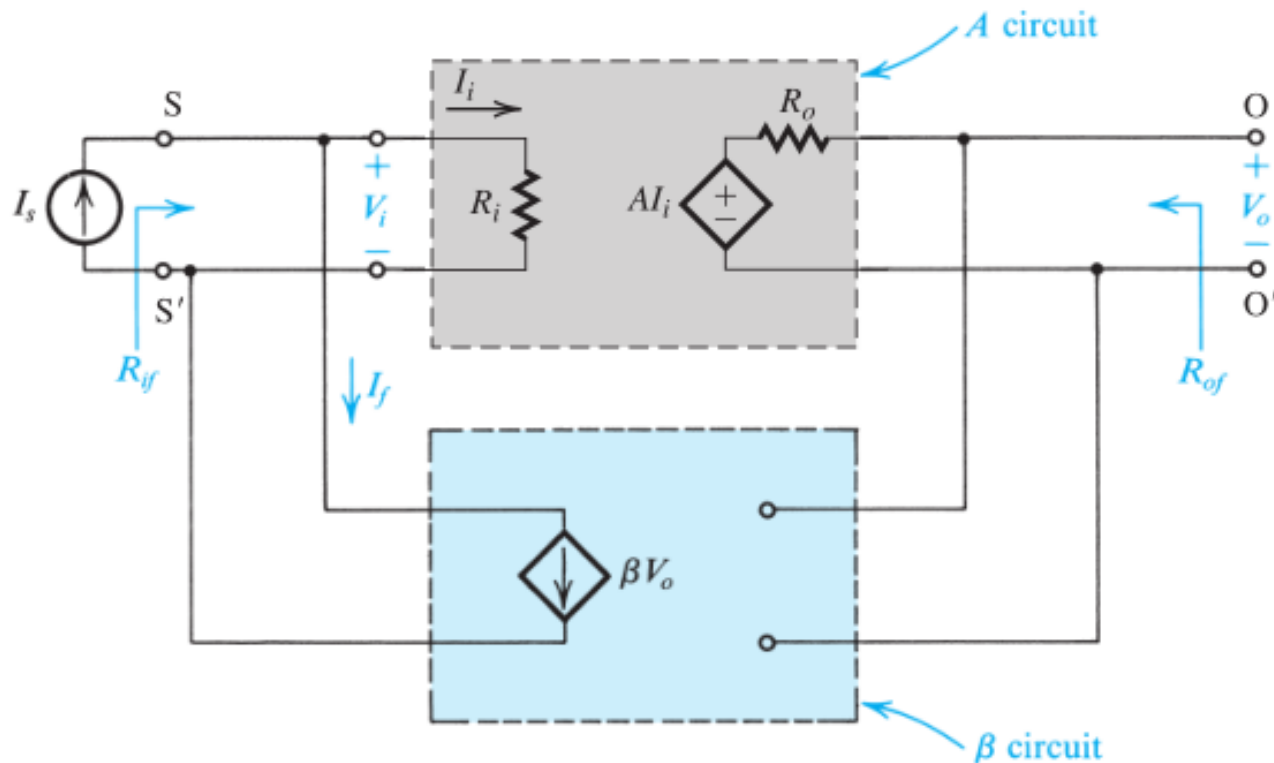


# Shunt-Shunt Amplifier

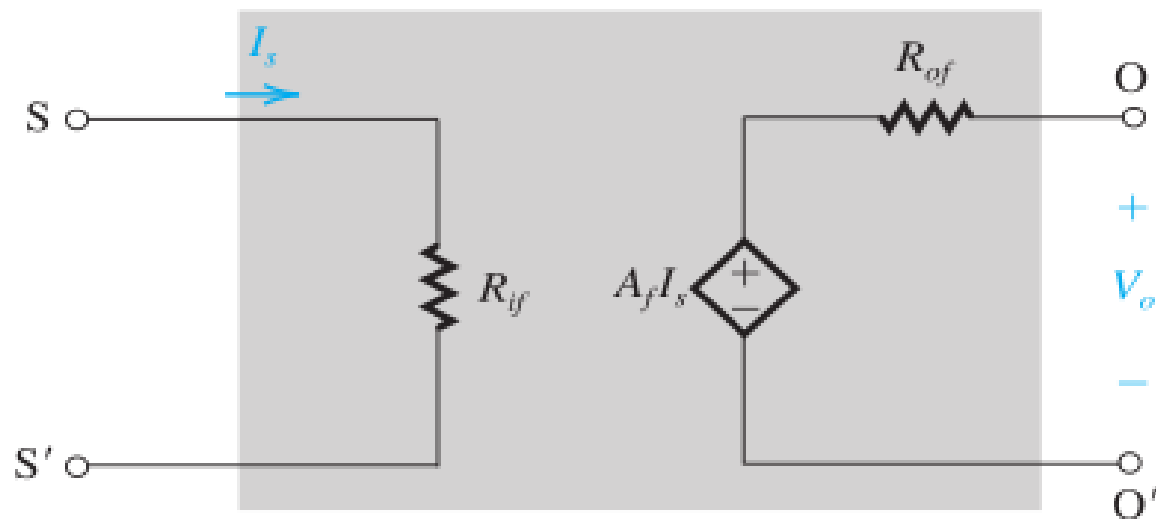





# Shunt-Shunt Amplifier

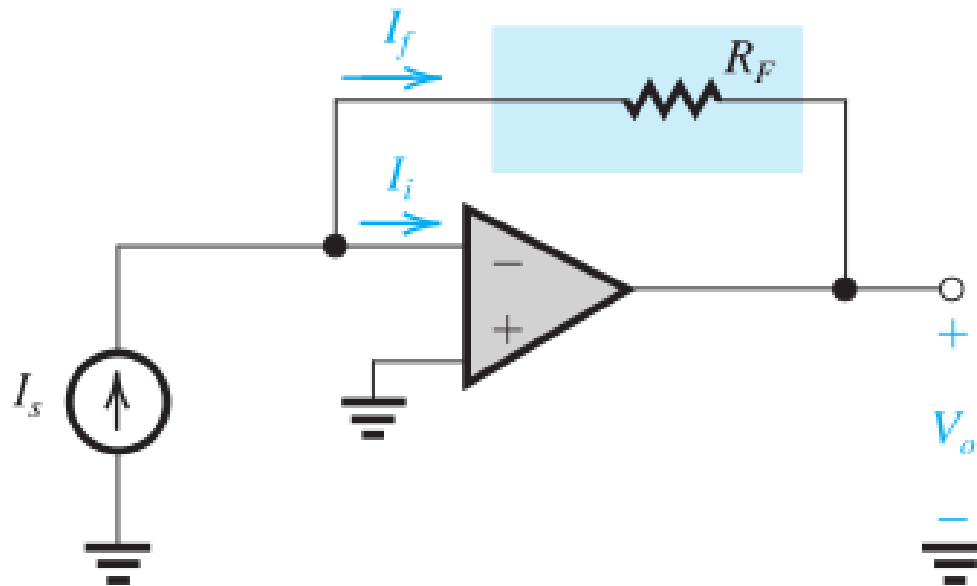


# Shunt-Shunt Amplifier

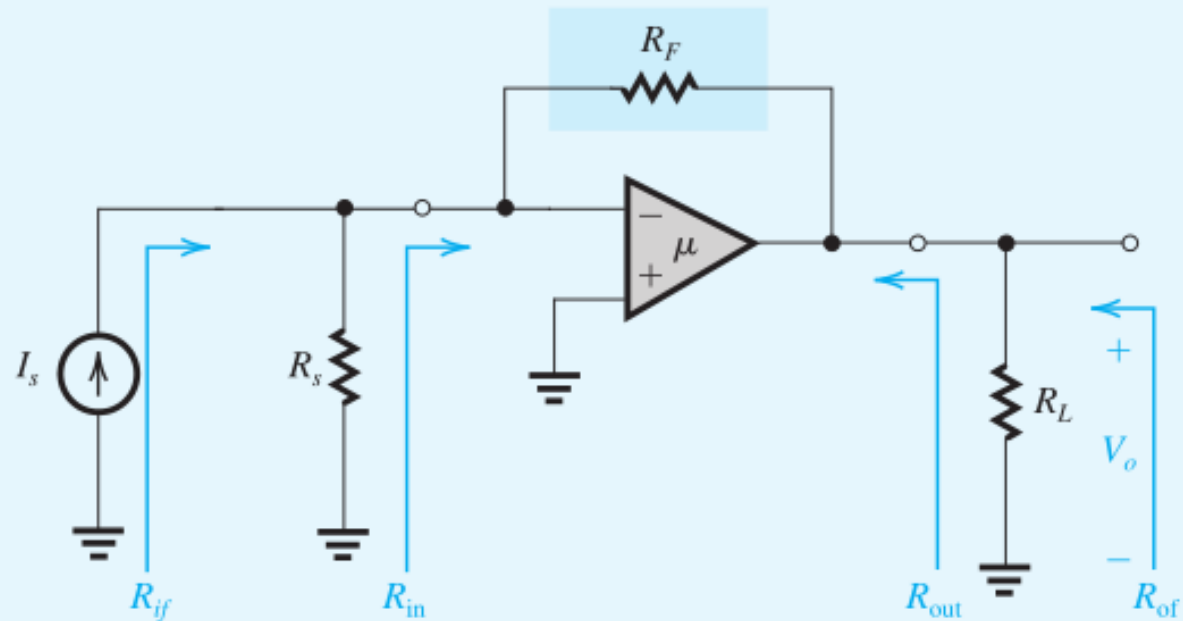


# Series-Series Amplifier

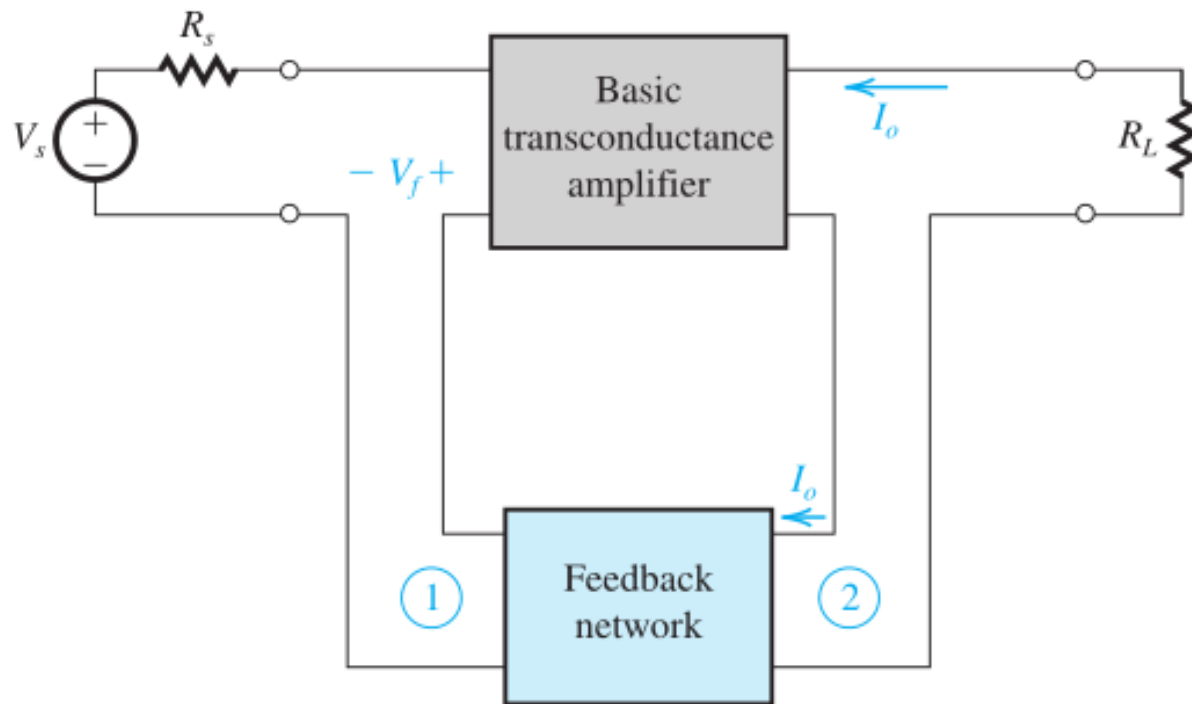

# Series-Series Amplifier

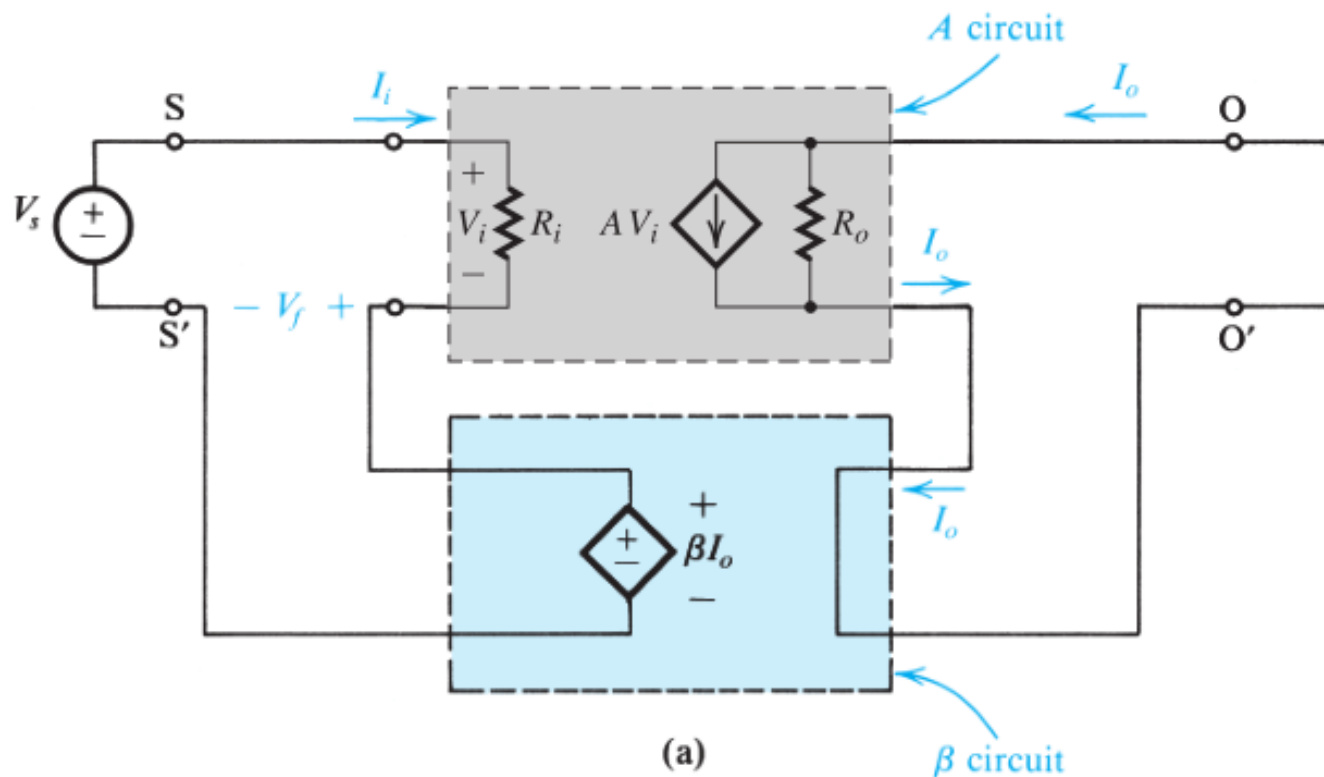


# Series-Series Amplifier

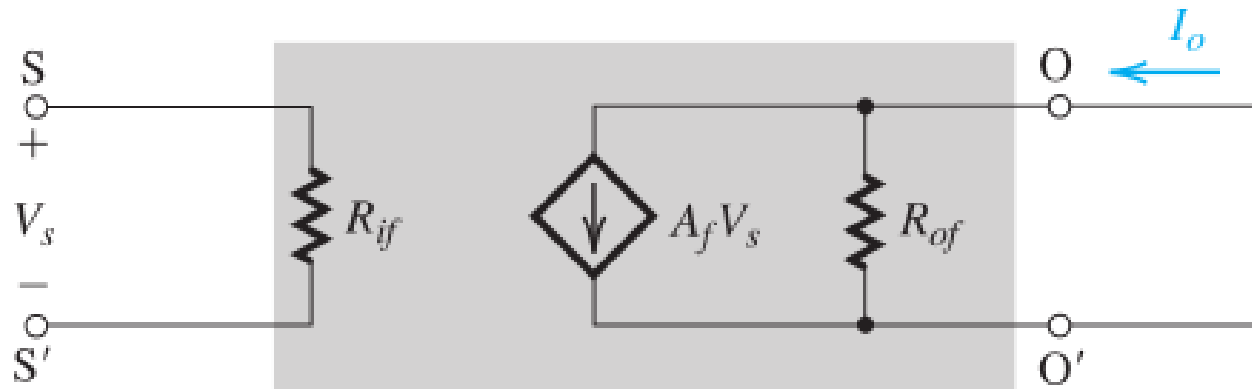





# Shunt-Series Amplifier

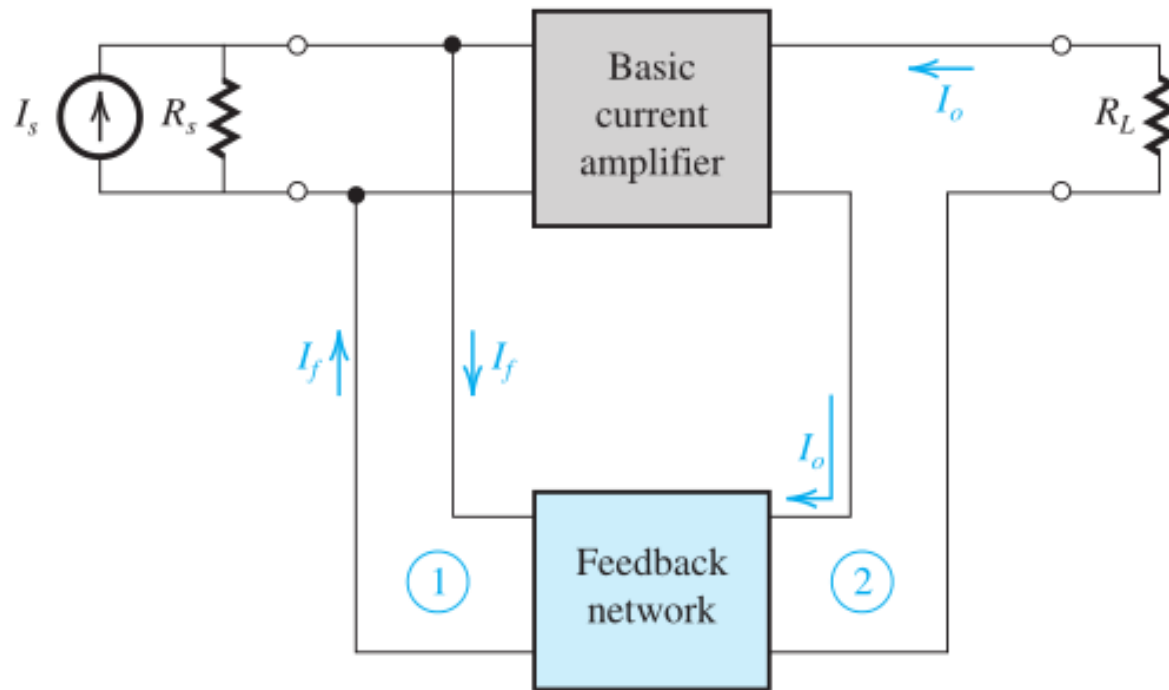

# Shunt-Series Amplifier

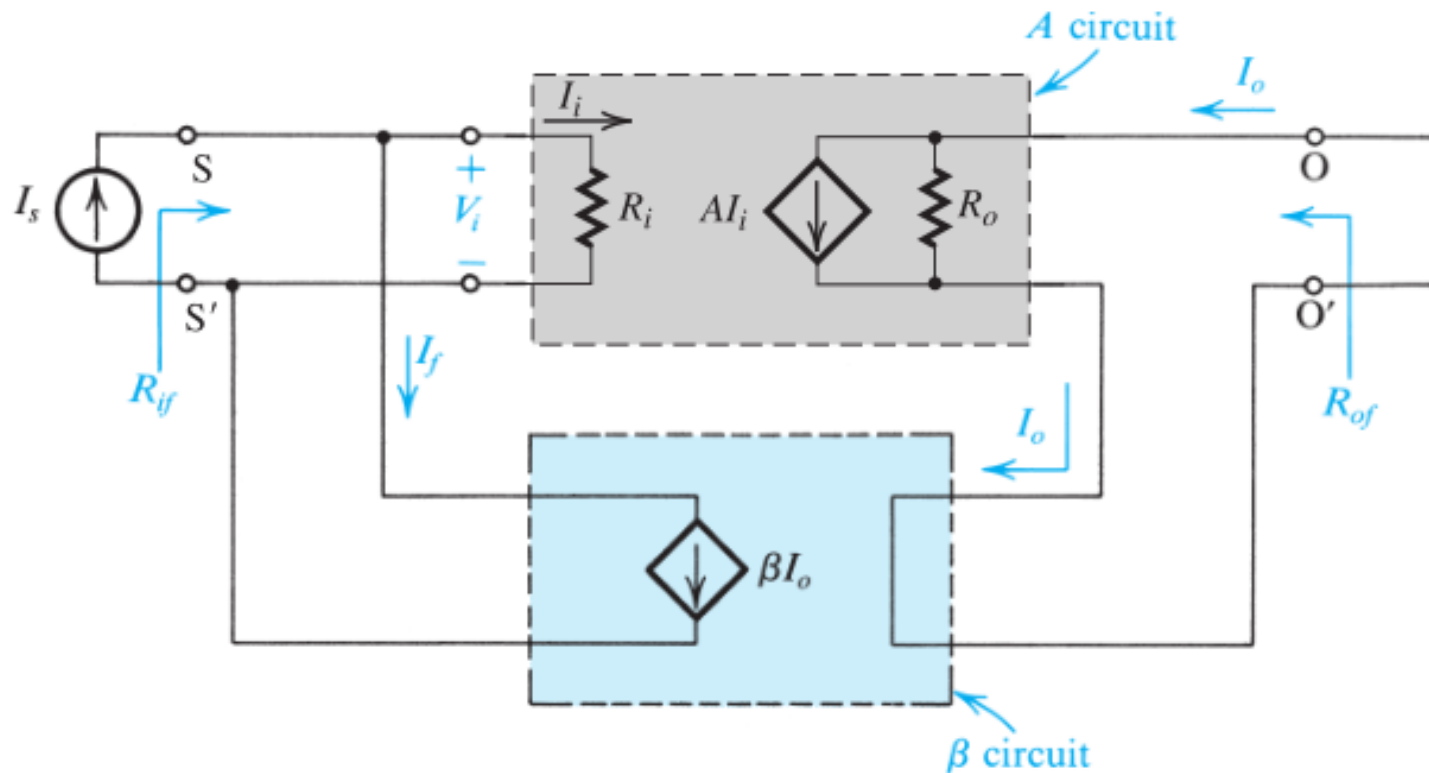

# Shunt-Series Amplifier

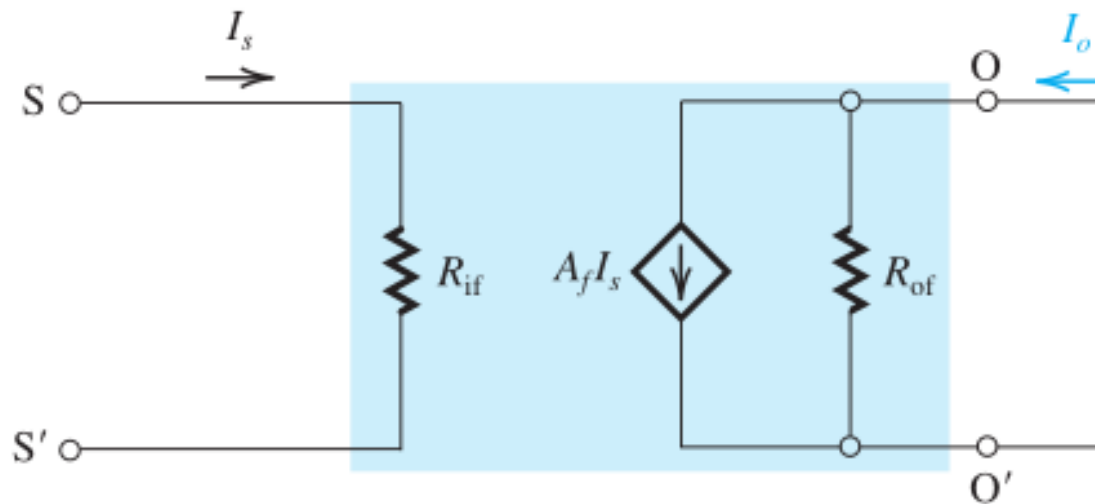


# Feedback Relations

	Gain	Input Resistance	Output Resistance
Without feedback	$A$	$R_i$	$R_o$
Series-shunt $A$ (V/V) $\beta$ (V/V)	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = R_i(1 + \beta A)$	$R_{of} = \frac{R_o}{1 + \beta A}$
Series-series $A$ (A/V or $\mathcal{U}$ ) $\beta$ (V/A or $\Omega$ )	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = R_i(1 + \beta A)$	$R_{of} = R_o(1 + \beta A)$
Shunt-shunt $A$ (V/A or $\Omega$ ) $\beta$ (A/V or $\mathcal{U}$ )	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = \frac{R_o}{1 + \beta A}$
Shunt-series $A$ (A/A) $\beta$ (A/A)	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = R_o(1 + \beta A)$


# Examples




# Identify the Topology

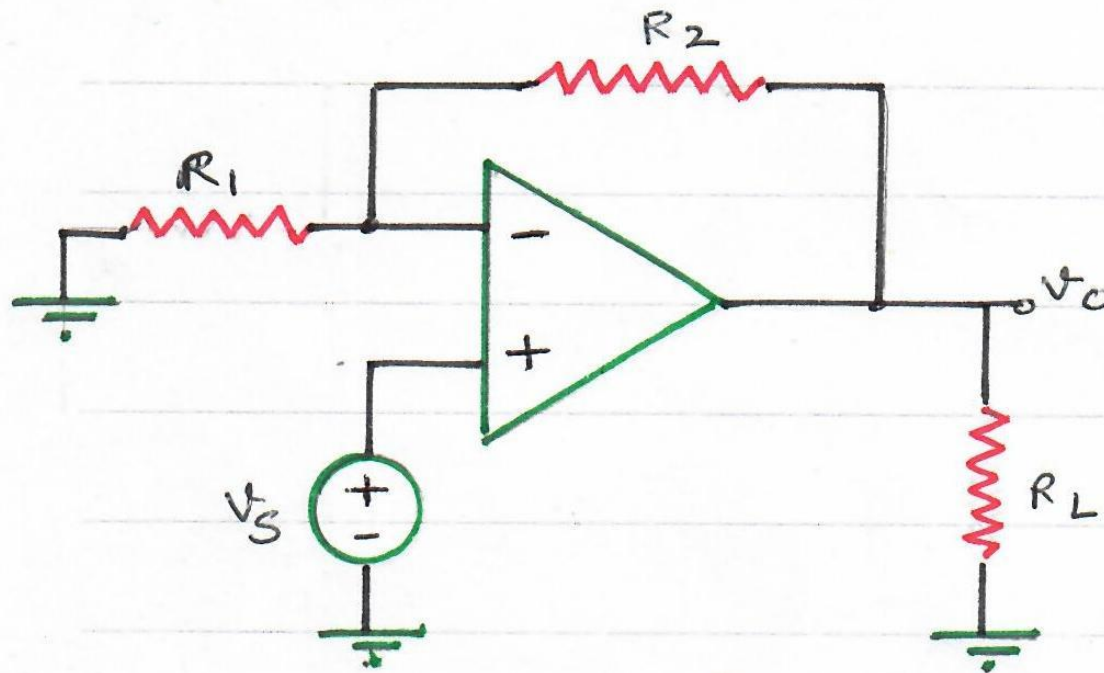

# Identify the Topology

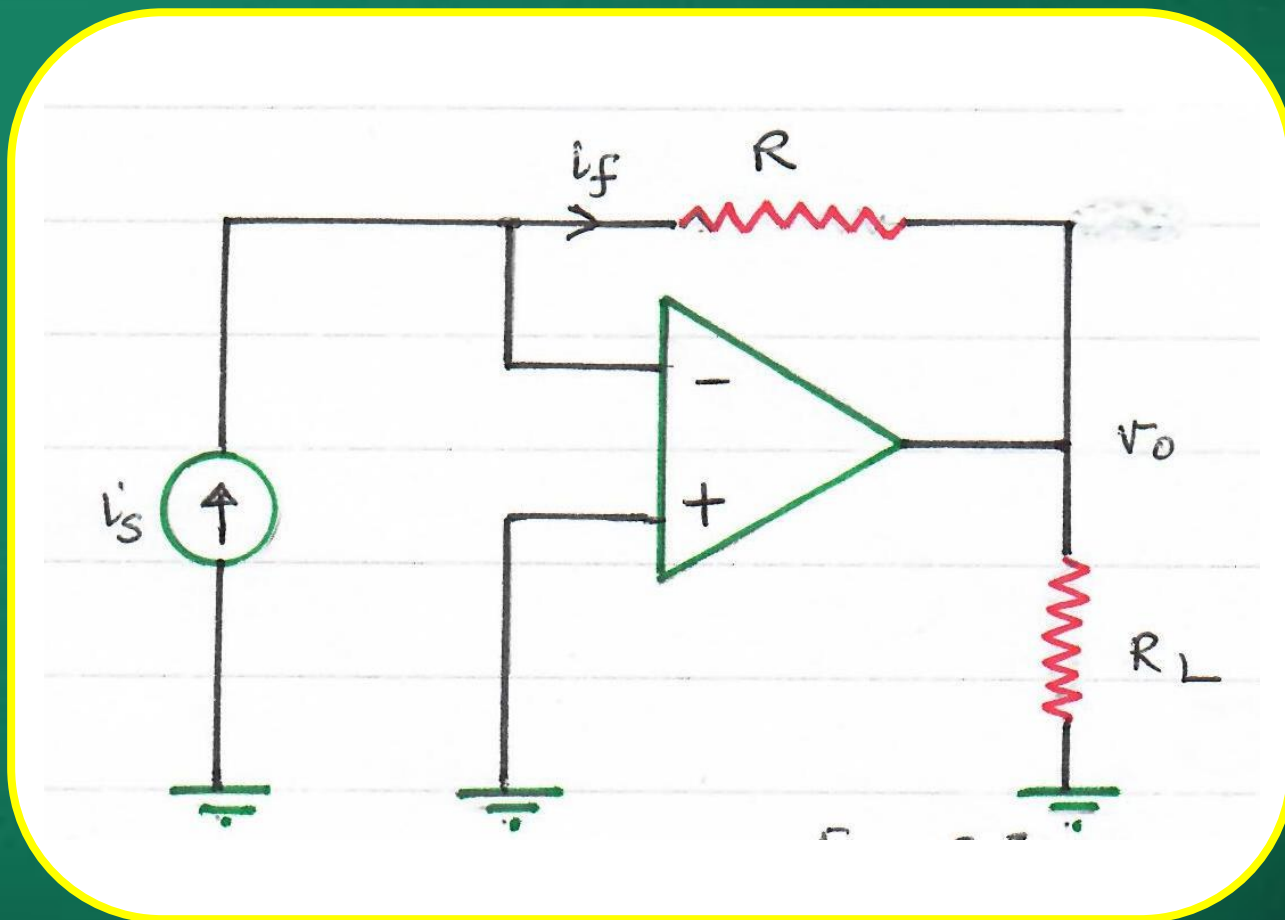

# Identify the Topology

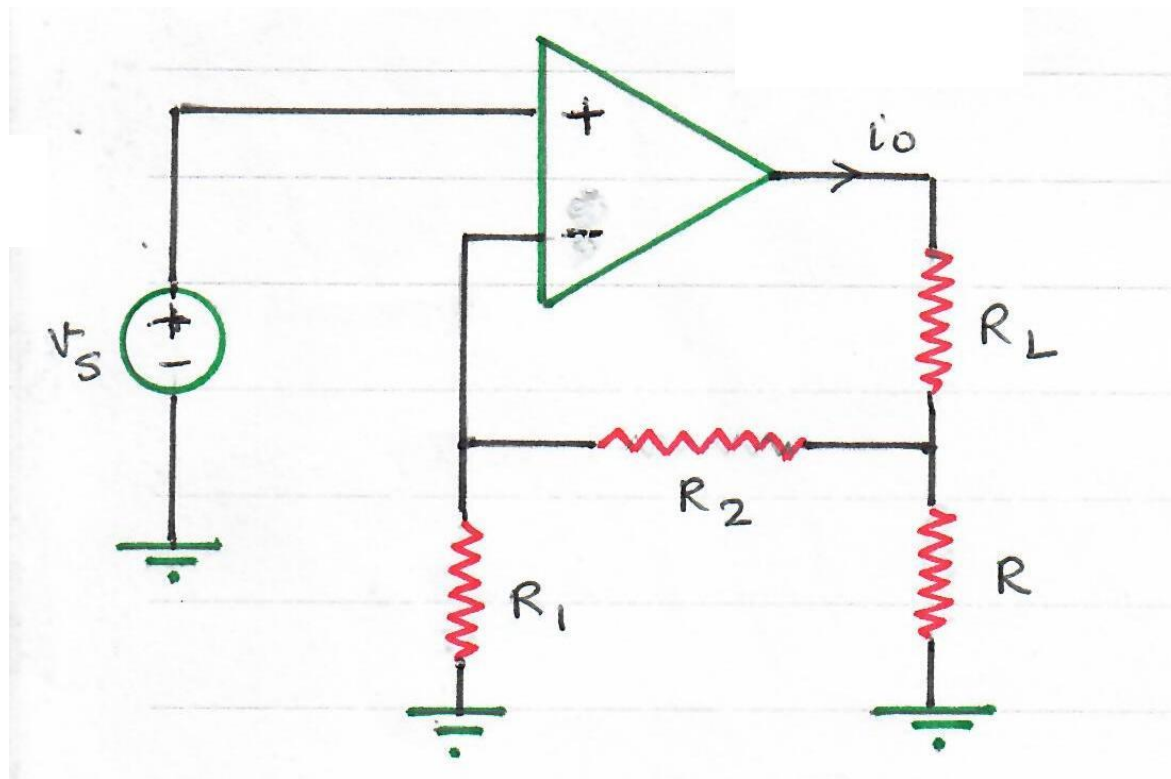

# Identify the Topology

