

Basic Electronic Circuits Lab

(IEC-103)

Experiment-03

Objective

To realize summing, averaging, and difference amplifier using operational amplifier.



Components

- **Op-amp IC (741)**
- **Resistances ($1\text{k}\Omega$, $2.2\text{k}\Omega$ and $4.7\text{k}\Omega$)**
- **Breadboard**
- **Connecting wires**


Equipment

- **Function Generator for generating input signal.**
- **Power supplies ($\pm 12\text{ V}$) to power up op-amp.**
- **CRO for input and output voltage measurements**


741 Op Amp IC

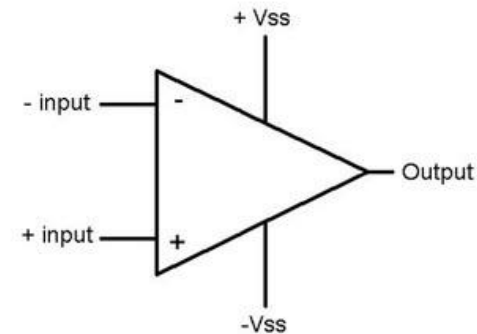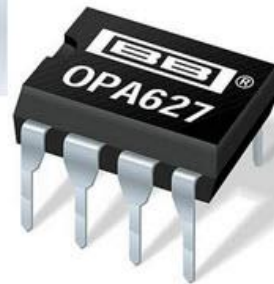

OP-AMP

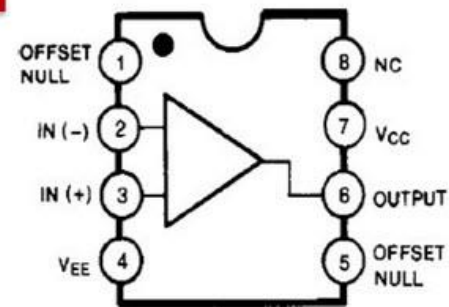


741 Op Amp IC (Pin Diagram)

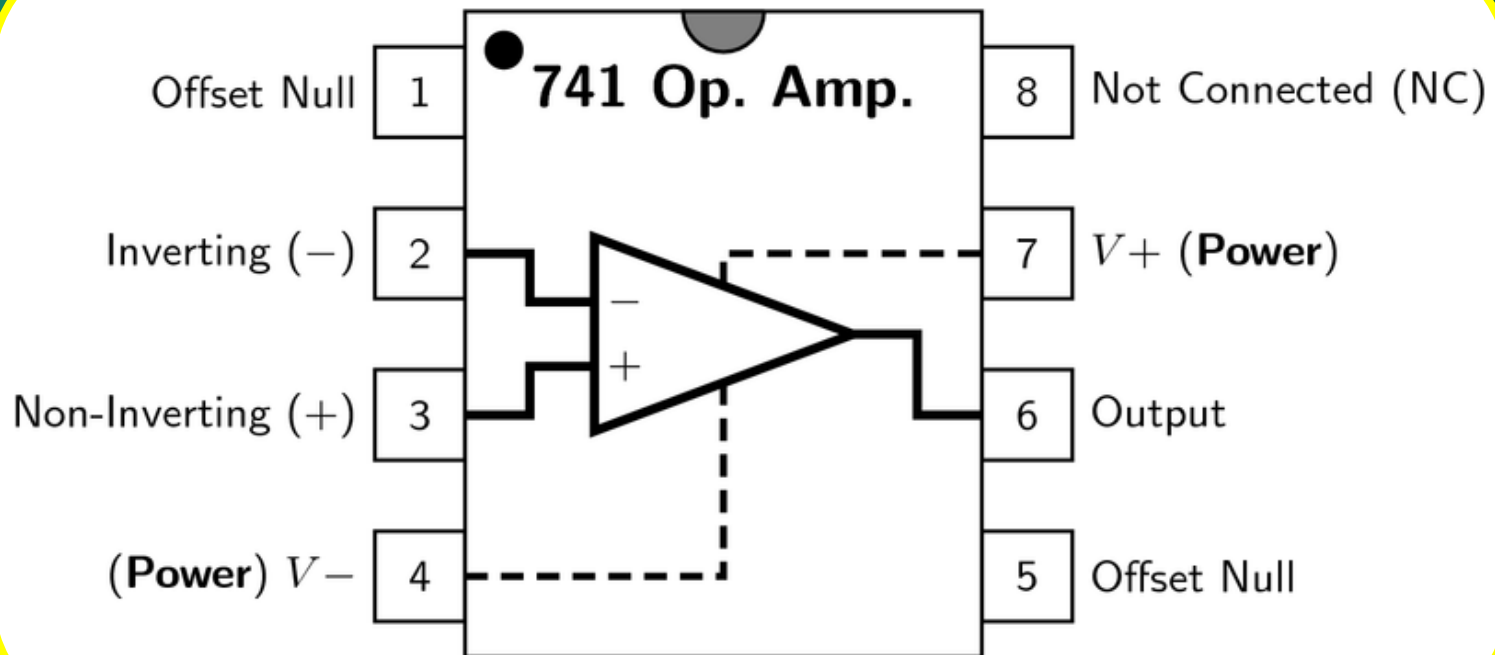


Power Supply (Fixed)


Power Supply

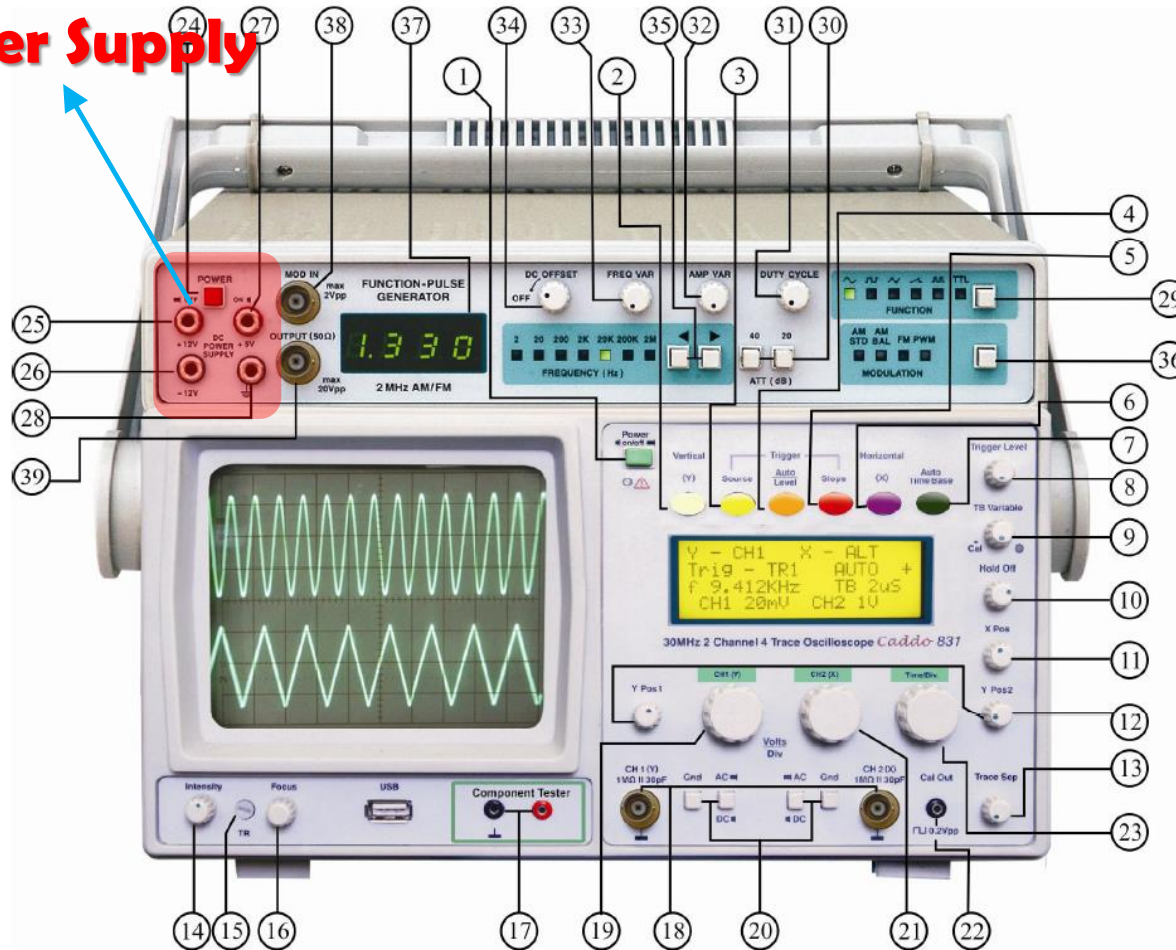

Signal Source

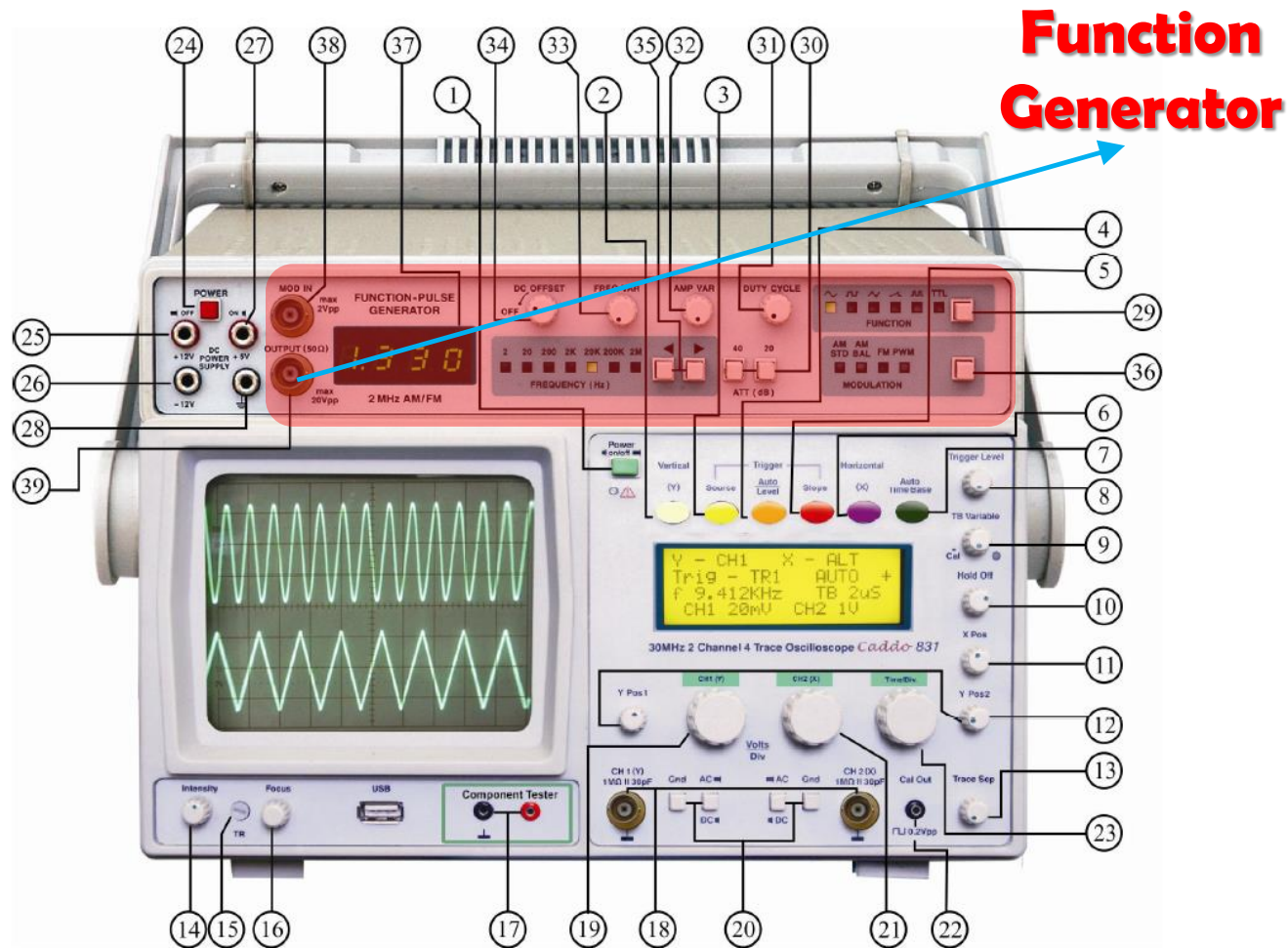


Oscilloscope

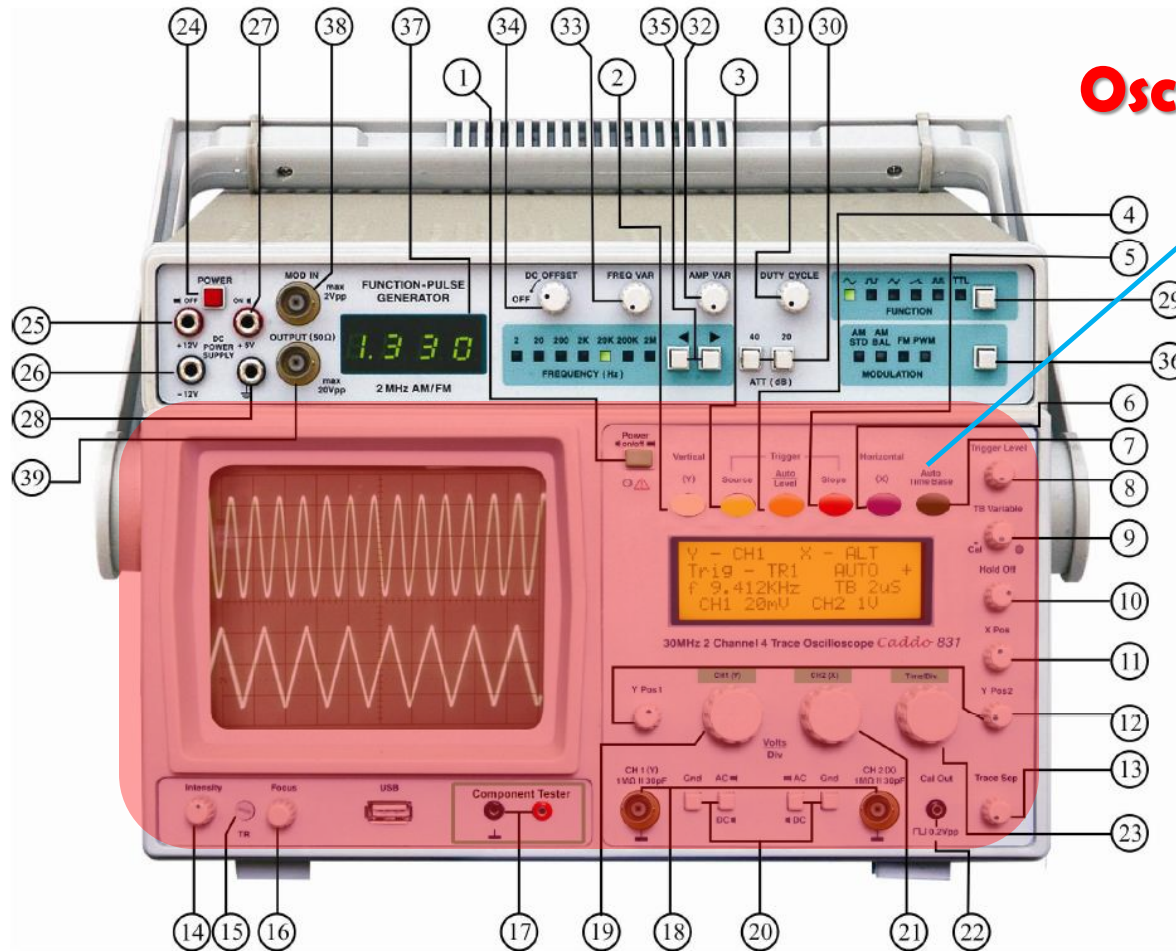

Oscilloscope

Summing Amplifier

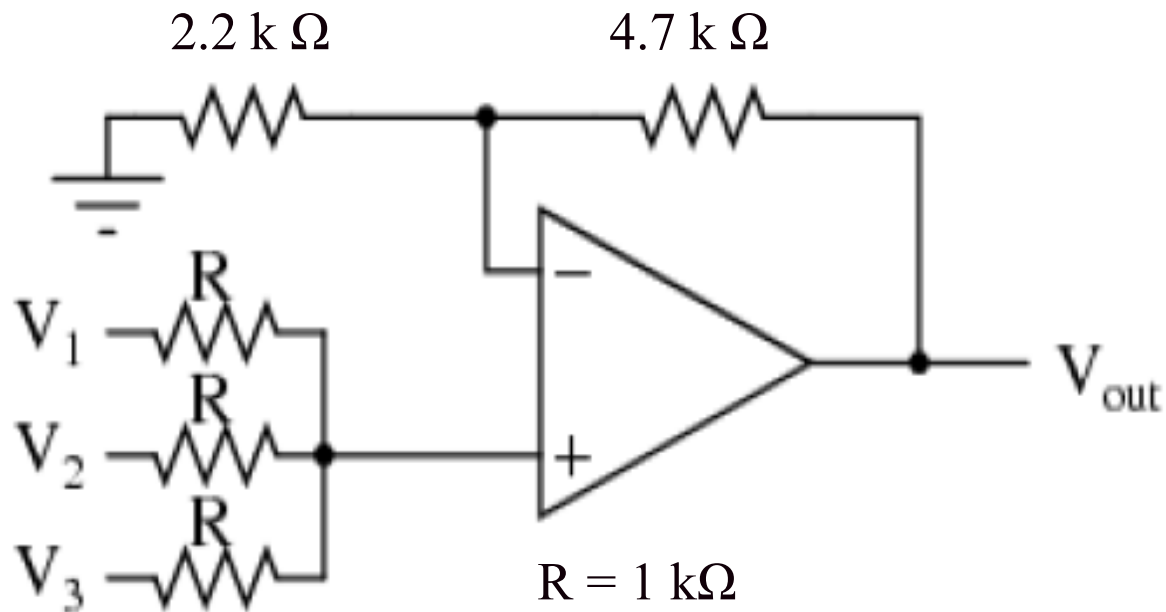

Summing Amplifier

Output voltage due to source V_1 acting alone.

Summing Amplifier

Output voltage due to source V_1 acting alone.

$$V_{\text{out1}} = \left(1 + \frac{4.7}{2.2}\right) \left(\frac{0.5k}{1k + 0.5k}\right) V_1 \approx V_1$$

Summing Amplifier

Output voltage due to source V_1 acting alone.

$$V_{\text{out1}} = \left(1 + \frac{4.7}{2.2}\right) \left(\frac{0.5k}{1k + 0.5k}\right) V_1 \approx V_1$$

Output voltage due to source V_2 acting alone.

$$V_{\text{out2}} = \left(1 + \frac{4.7}{2.2}\right) \left(\frac{0.5k}{1k + 0.5k}\right) V_2 \approx V_2$$

Summing Amplifier

Output voltage due to source V_1 acting alone.

$$V_{\text{out1}} = \left(1 + \frac{4.7}{2.2}\right) \left(\frac{0.5k}{1k + 0.5k}\right) V_1 \approx V_1$$

Output voltage due to source V_2 acting alone.

$$V_{\text{out2}} = \left(1 + \frac{4.7}{2.2}\right) \left(\frac{0.5k}{1k + 0.5k}\right) V_2 \approx V_2$$

Output voltage due to source V_3 acting alone.

$$V_{\text{out3}} = \left(1 + \frac{4.7}{2.2}\right) \left(\frac{0.5k}{1k + 0.5k}\right) V_3 \approx V_3$$

Summing Amplifier


Output voltage due to all the sources (applying superposition principle)

$$V_{\text{out}} = V_1 + V_2 + V_3$$


Observations

S. No	V_1	V_2	V_3	V_{out}
1	0	0	0	
2	1 V (peak)	0	0	
3	0	1 V (peak)	0	
4	0	0	1 V (peak)	
5	1 V (peak)	1 V (peak)	0	
6	1 V (peak)	0	1 V (peak)	
7	0	1 V (peak)	1 V (peak)	
8	1 V (peak)	1 V (peak)	1 V (peak)	

Averaging Amplifier

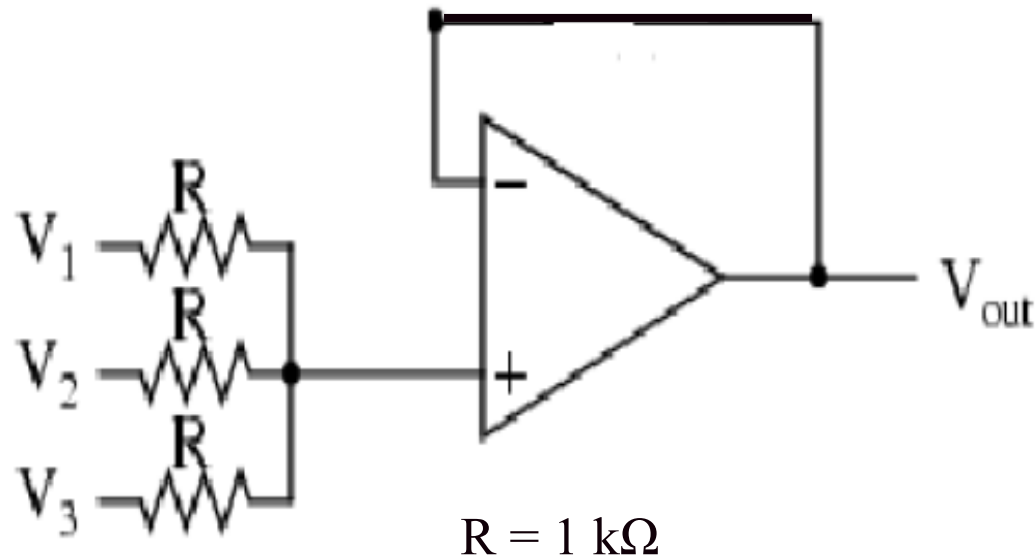

Averaging Amplifier

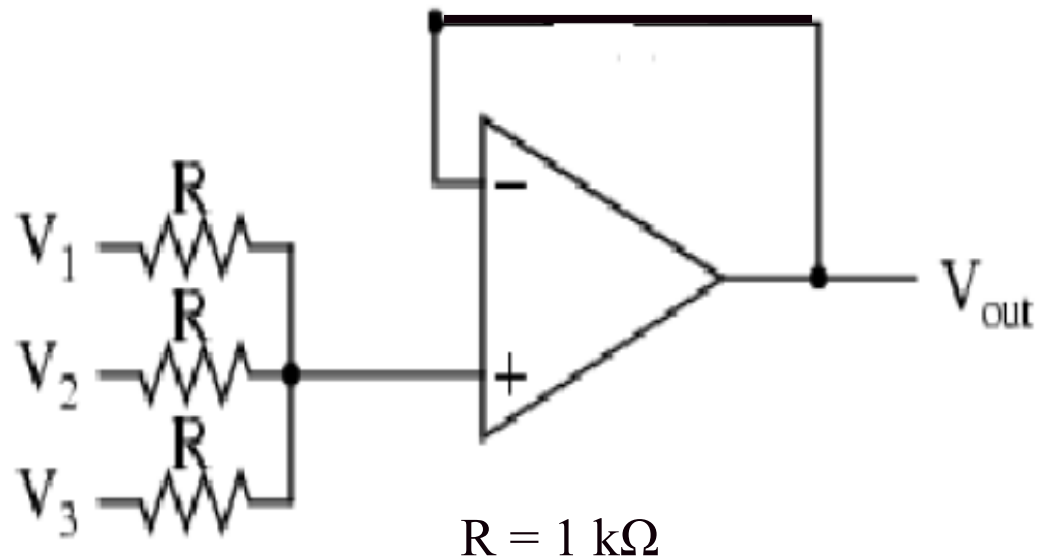


$$V_{out} = \frac{V_1 + V_2 + V_3}{3}$$


Observations

S. No	V_1	V_2	V_3	V_{out}
1	0	0	0	
2	1 V (peak)	0	0	
3	0	1 V (peak)	0	
4	0	0	1 V (peak)	
5	1 V (peak)	1 V (peak)	0	
6	1 V (peak)	0	1 V (peak)	
7	0	1 V (peak)	1 V (peak)	
8	1 V (peak)	1 V (peak)	1 V (peak)	

Difference Amplifier

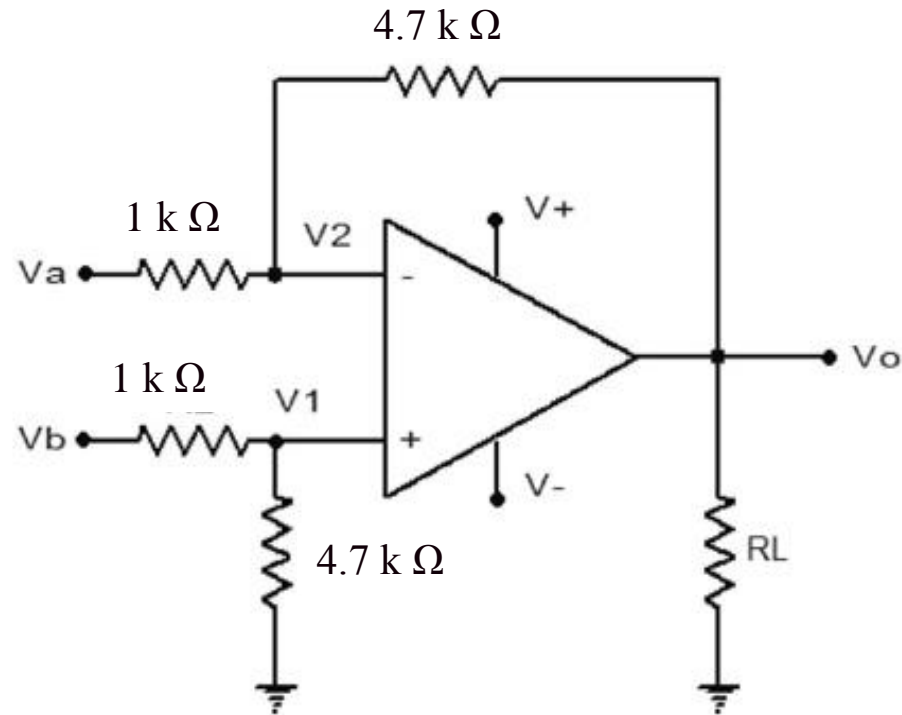

Difference Amplifier

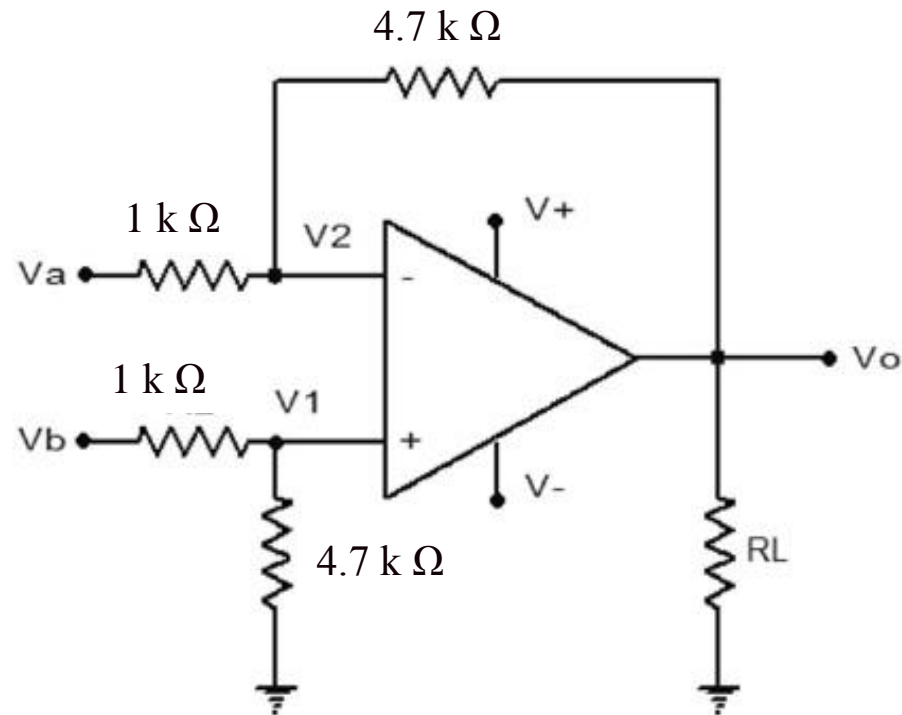

$$V_o = 4.7(V_b - V_a)$$

Observations

S. No	V_a	V_b	V_o
1	0	0	
2	1 V (peak)	0	
3	0	1 V (peak)	
4	1 V (peak)	1 V (peak)	